

POLYPHASE CIRCUITS

- ❖ Nearly all electrical power generated and distributed in three phase at the operating frequency of 50 Hz (India) or 60 Hz (US).
- ❖ If one phase or two phases are required, then they are taken from the three-phase system directly rather than generating independently.
- ❖ The instantaneous power in the three-phase system is constant and not pulsating in nature like single phase system.
- ❖ As a result, the power transmission is uniform, and the vibration is less in the rotating electrical machines.
- ❖ For the same amount of power with same transmission efficiency, three phase system is more economical than single phase system.
- ❖ For the aforementioned conditions, the volume of copper used in three phase system is less than the same of single-phase system.
- ❖ Circuit diagram of single-phase system and the three phase system.

POLYPHASE VOLTAGES


- ❖ We begin our discussion with three phase balanced voltage.
- ❖ Three phase voltages are usually generated with three phase generator.
- ❖ A typical three-phase system consists of three voltage sources connected to loads by three or four wires.
- ❖ A three-phase system is equivalent to three single-phase circuits.
- ❖ A three-phase system can be star connected or delta connected.
- ❖ In case of three-phase voltages, the voltage magnitudes are same for each of the three phases; however, the three phases are electrically 120° apart from each other.

$$V_{An} = V_m \angle 0^\circ$$

$$V_{Bn} = V_m \angle -120^\circ$$


$$V_{Cn} = V_m \angle -240^\circ = V_m \angle +120^\circ$$

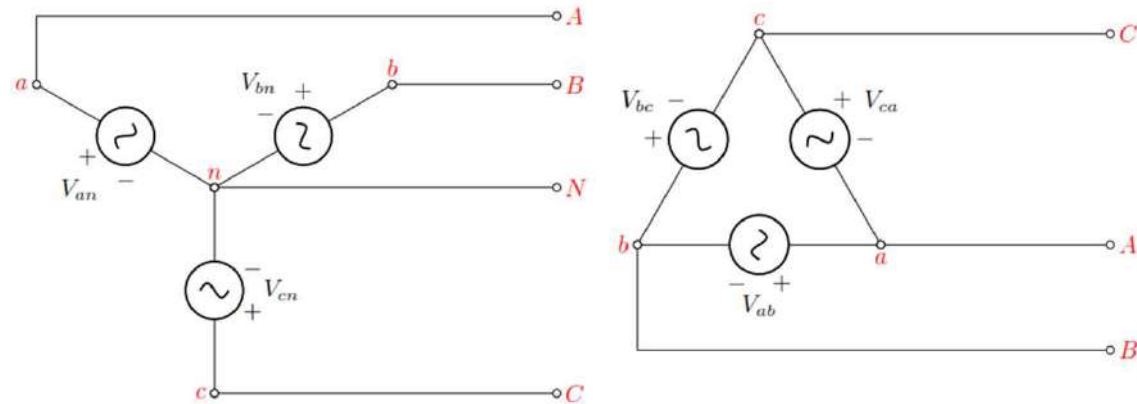Phase sequence is **A-B-C**, or **B-C-A**, or **C-A-B**




POLYPHASE LOADS

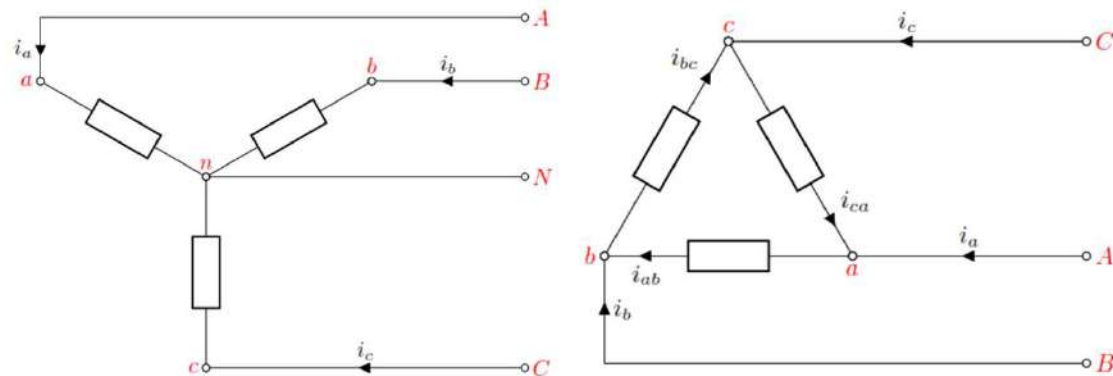- ❖ General Concept of load. Electrically, load is represented by current.
- ❖ Three phase load also either star or delta connected like the three-phase voltage source.
- ❖ Balanced load is one for which the phase impedances are equal in magnitude and phase. From the concept of load, electrically a balanced three-phase current should flow through the balanced three phase load.
- ❖



Y - Y System :-

Three Phase System

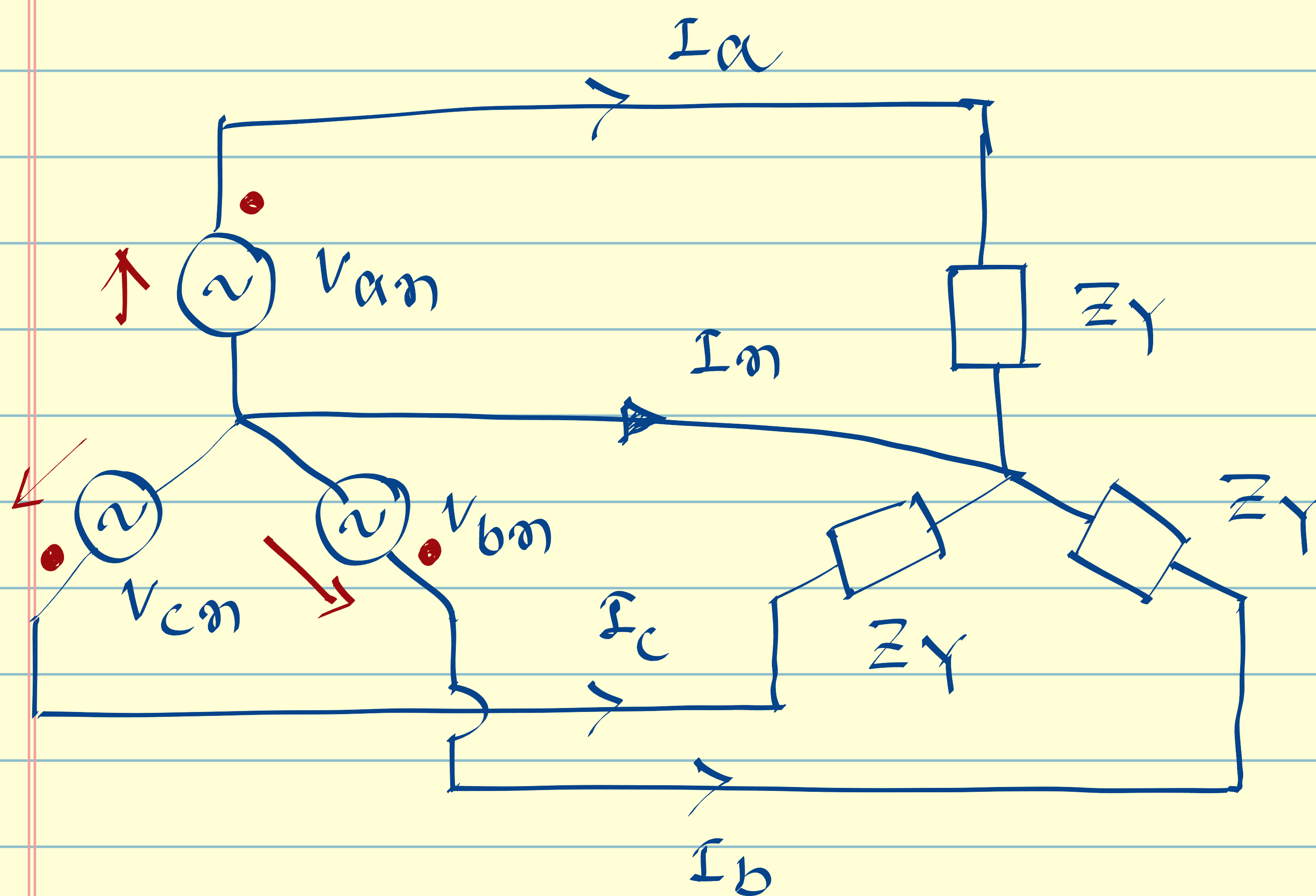

Phase voltages are

$$|I_a| = |I_b| = |I_c| \\ = I_p$$

$$V_{an} = V_p \angle 0$$

$$V_{bn} = V_p \angle -120$$

$$V_{cn} = V_p \angle +120 = V_p \angle -240$$

For balanced system $I_n = 0$. Therefore, for balanced system one can skip 4th wire.


Voltage appears across any two lines

Apply KVL

$$V_{an} - I_a Z_Y + I_b Z_Y - V_{bn} = 0$$

$$V_{an} - V_{bn} = (I_a - I_b) Z_Y$$

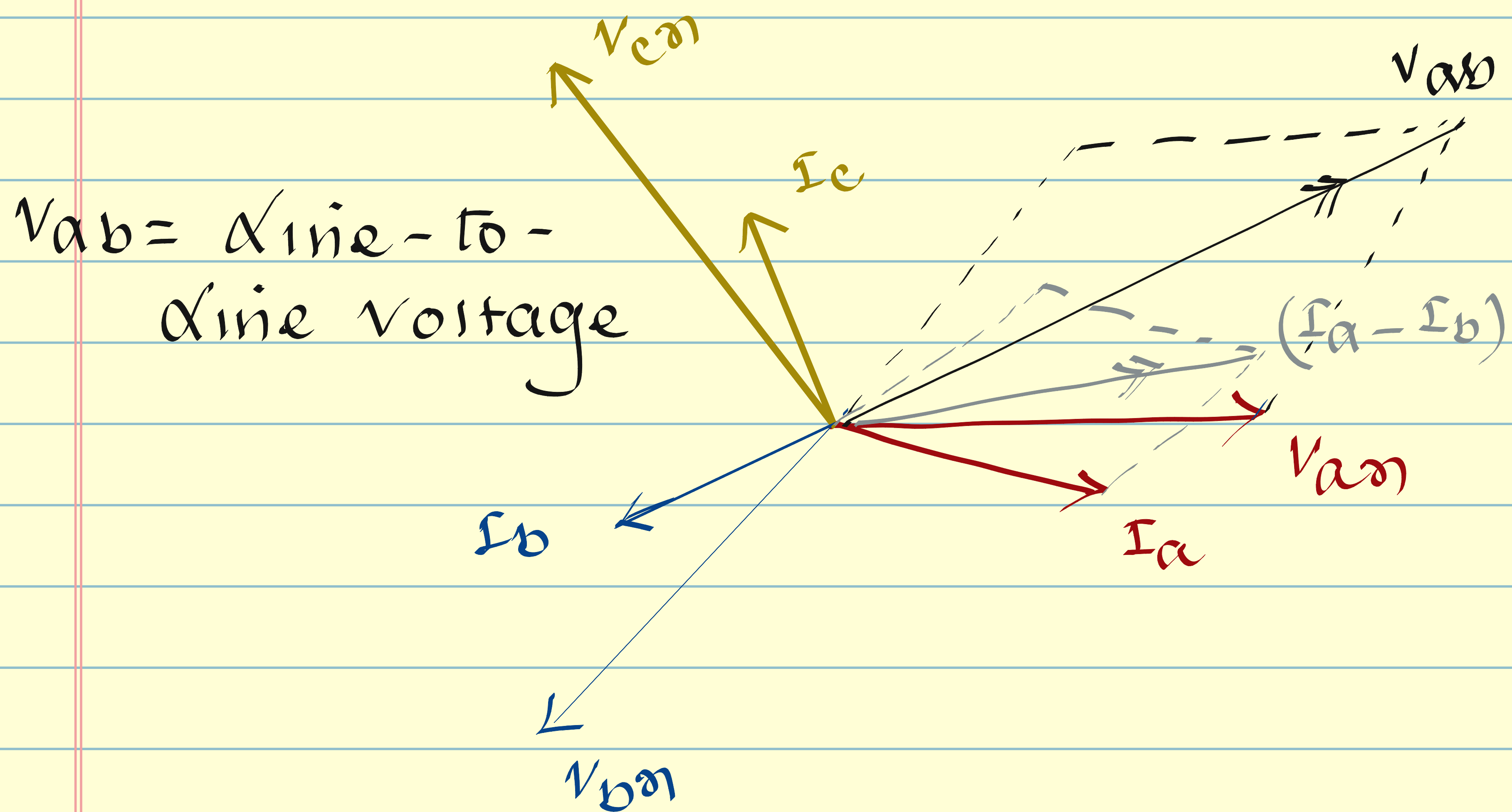Now, assume the Z_Y is resistive inductive



$$I_a - I_b = \frac{V_{ab}}{Z_Y} = \frac{\sqrt{3} V_p \angle 30^\circ}{Z_Y}$$

$$I_a - I_b = \sqrt{3} I_p \angle 30^\circ$$


$$I_p = \frac{V_p}{Z_Y}$$

$$I_a = I_p \angle 0 = \frac{V_p \angle 0}{Z_Y} = \frac{V_{an}}{Z_Y}$$


$$I_b = \frac{V_p \angle -120}{Z_Y} = \frac{V_{bn}}{Z_Y}$$

$$I_c = \frac{V_{cn}}{Z_Y}$$

Single phase equivalent

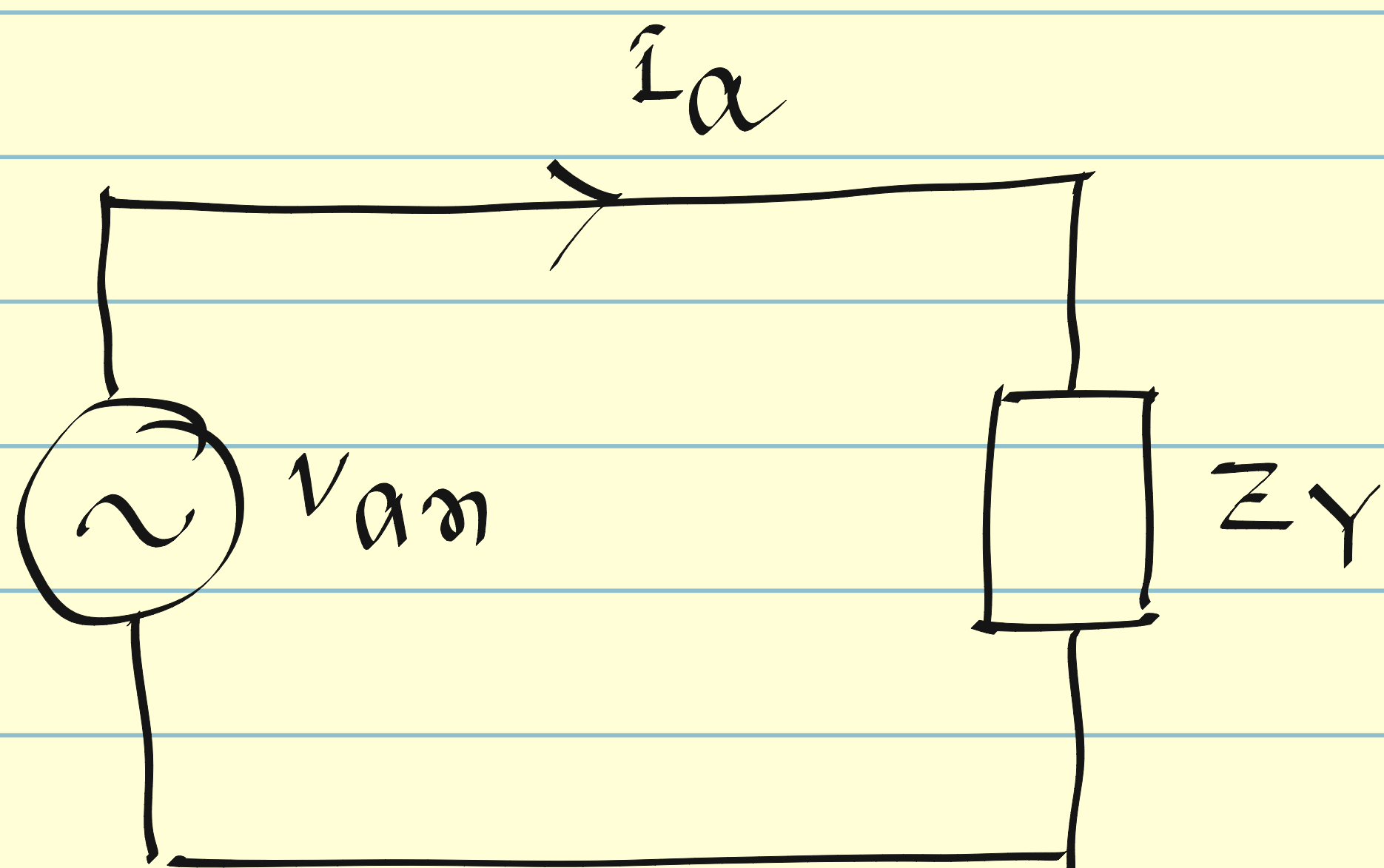

Y-Δ System:-

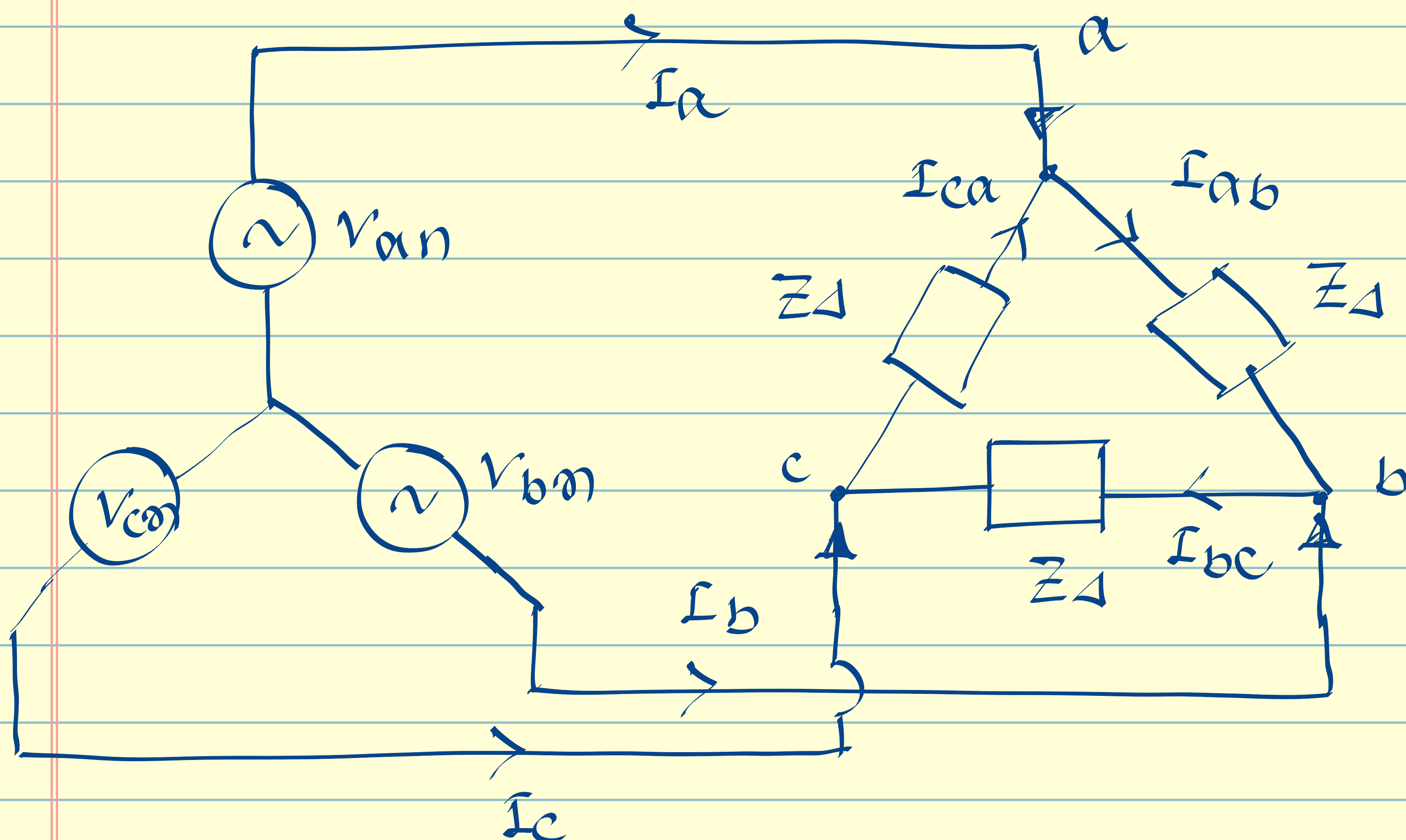

Apply KVL

$$V_{an} - I_{ab} Z_{\Delta} - V_{bn} = 0$$

$$\Rightarrow I_{ab} = \frac{V_{an} - V_{bn}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}}$$

$$I_a = I_{ab} - I_{ca}$$

$$I_{ab} + I_{bc} + I_{ca} = 0$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

$$\begin{aligned} I_a - I_b &= I_{ab} - I_{ca} - I_{bc} + I_{ab} \\ &= 3 I_{ab} \end{aligned}$$

$$I_{ab} = \frac{I_a - I_b}{3}$$

$$I_a - I_b = \frac{3 V_{ab}}{Z_{\Delta}} = \frac{V_{ab}}{(Z_{\Delta}/3)}$$

$$I_a - I_b = \sqrt{3} I_p \angle 30^\circ$$

$$V_{ab} = \sqrt{3} V_p \angle 30^\circ$$

$$I_p = \frac{V_p}{(Z_{\Delta}/3)}$$


$$I_a = \frac{V_{an}}{(Z_{\Delta}/3)} \quad I_b = \frac{V_{bn}}{(Z_{\Delta}/3)}$$

$$I_c = \frac{V_{cn}}{(Z_{\Delta}/3)}$$


$$\begin{aligned} I_{ab} &= (I_a - I_b)/3 \\ &= \frac{\sqrt{3} I_p \angle 30^\circ}{3} = \frac{I_p}{\sqrt{3}} \angle 30^\circ \end{aligned}$$

$$\begin{aligned} |I_{ab}| &= \text{Phase current} \\ &= \frac{\text{Line current}}{\sqrt{3}} \end{aligned}$$

Single phase equivalent ckt

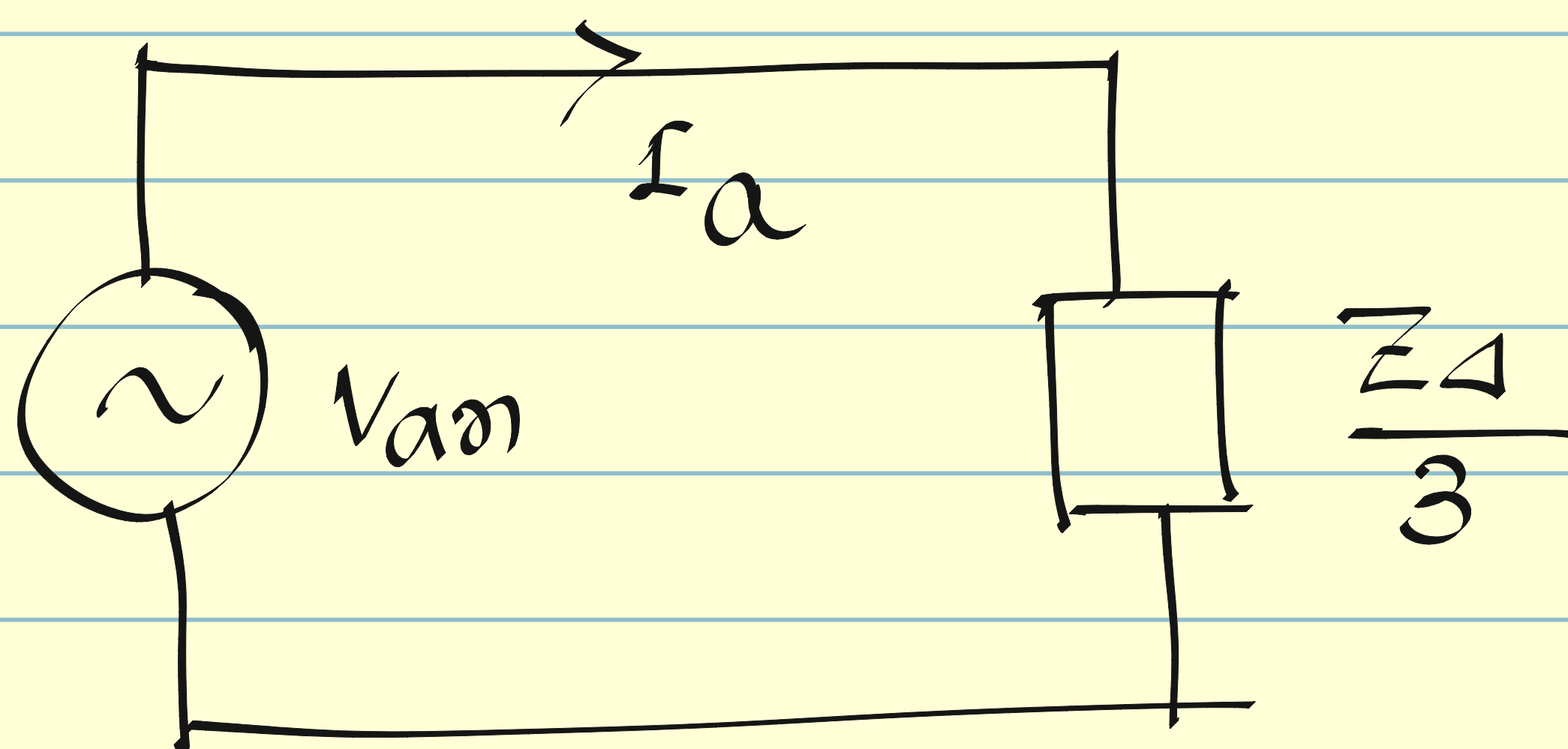

Δ-Υ System :-

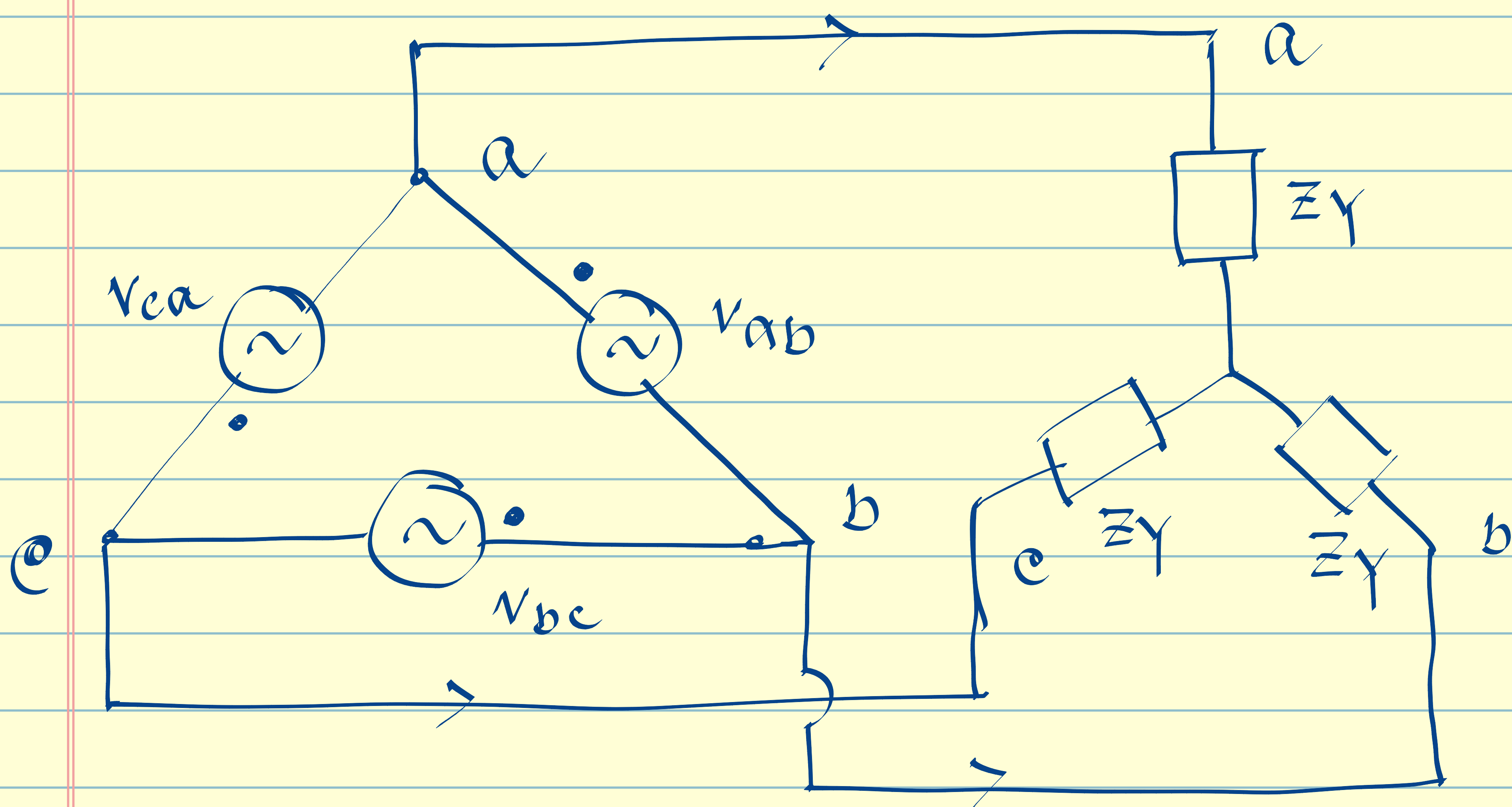

Apply KVL

$$V_{ab} = V_p \angle 0$$

$$V_{bc} = V_p \angle -120$$

$$V_{ca} = V_p \angle +120$$

$$V_{ab} - I_a Z_Y + I_b Z_Y = 0$$


$$\Rightarrow V_{ab} = (I_a - I_b) Z_Y$$

$$\Rightarrow I_a - I_b = \frac{V_{ab}}{Z_Y}$$


$$\Rightarrow \sqrt{3} I_p \angle 30 = \frac{V_{ab}}{Z_Y}$$

$$I_p = \left(\frac{V_p}{\sqrt{3}} \angle -30 \right) \frac{1}{Z_Y}$$

Single phase equivalent ckt

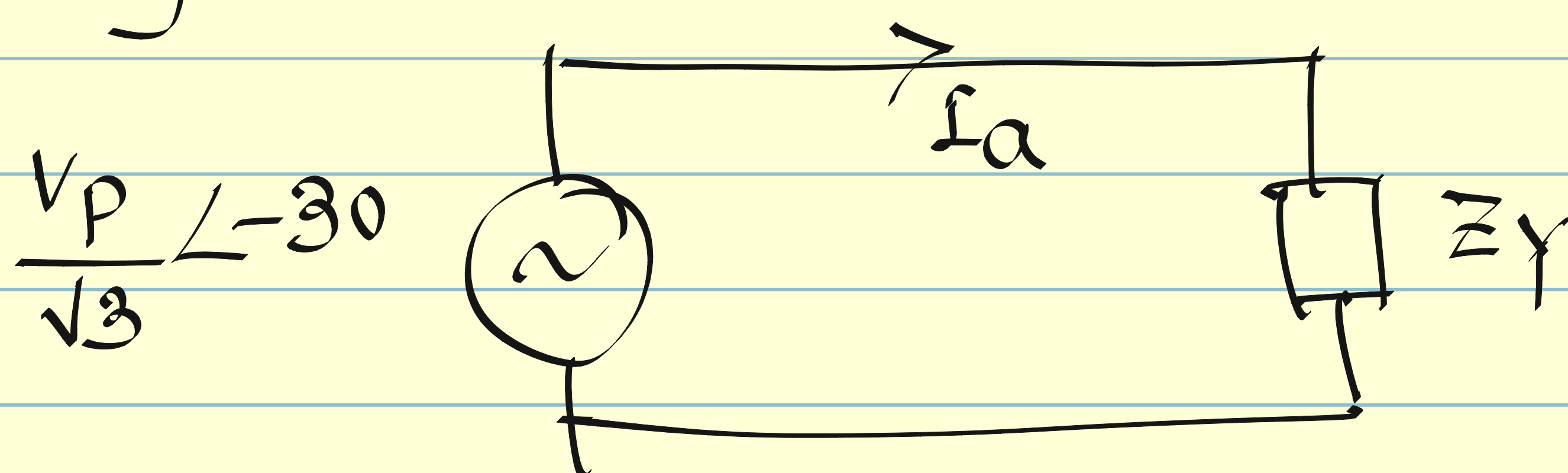

Δ-Δ System:-

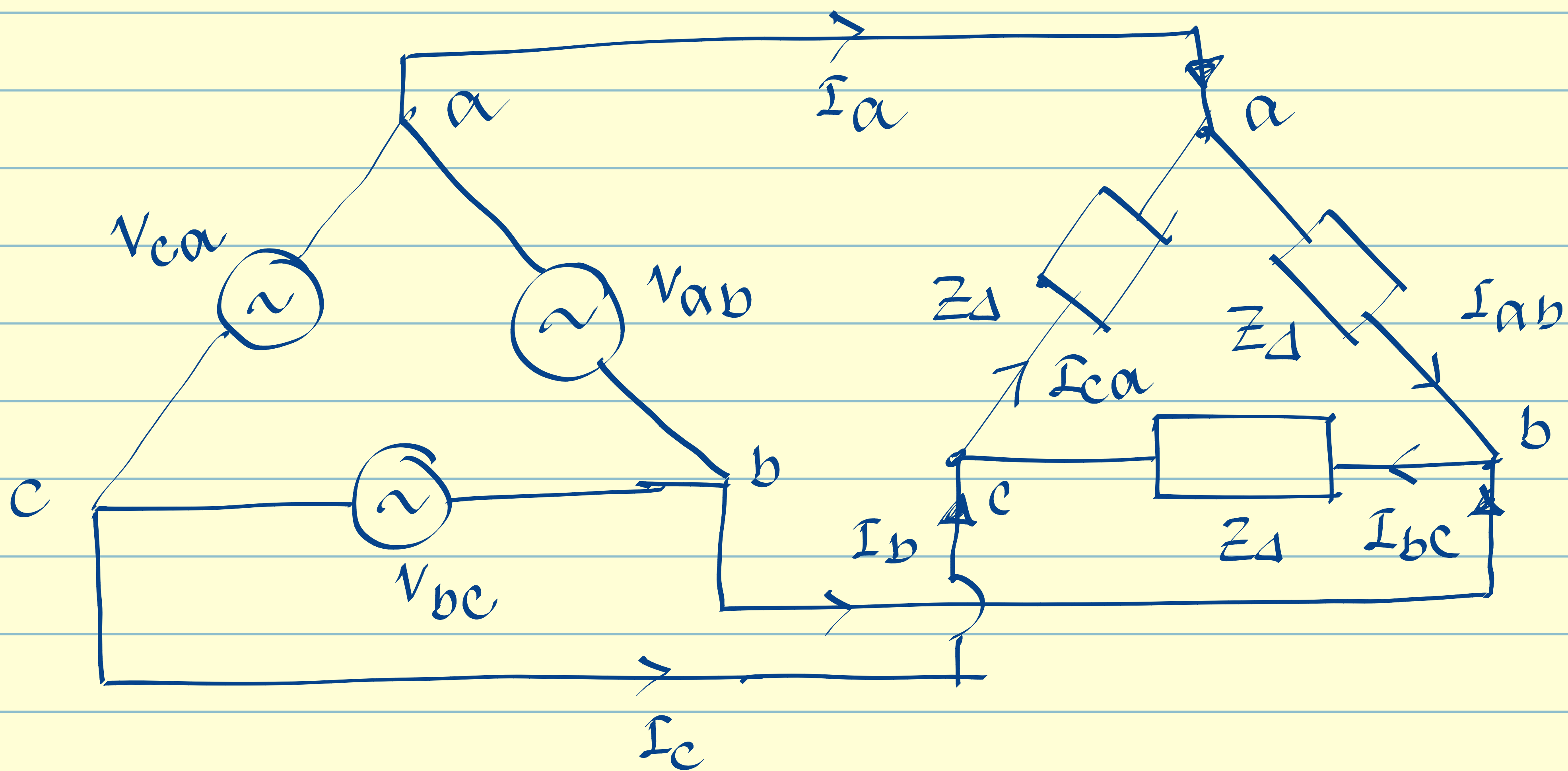

$$V_{ab} = V_p \angle 0^\circ$$

$$V_{bc} = V_p \angle -120^\circ$$

$$V_{ca} = V_p \angle +120^\circ$$

Apply KVL


$$\tilde{V}_{ab} = \tilde{I}_{ab} \tilde{Z}_\Delta$$

$$\Rightarrow I_{ab} = \frac{V_{ab}}{Z_\Delta} = \frac{V_p \angle 0^\circ}{Z_\Delta}$$

$$\Rightarrow \frac{1}{3} (I_a - I_b) = \frac{V_p \angle 0^\circ}{Z_\Delta}$$

$$\Rightarrow \sqrt{3} I_p \angle 30^\circ = \frac{V_p \angle 0^\circ}{Z_\Delta/3}$$
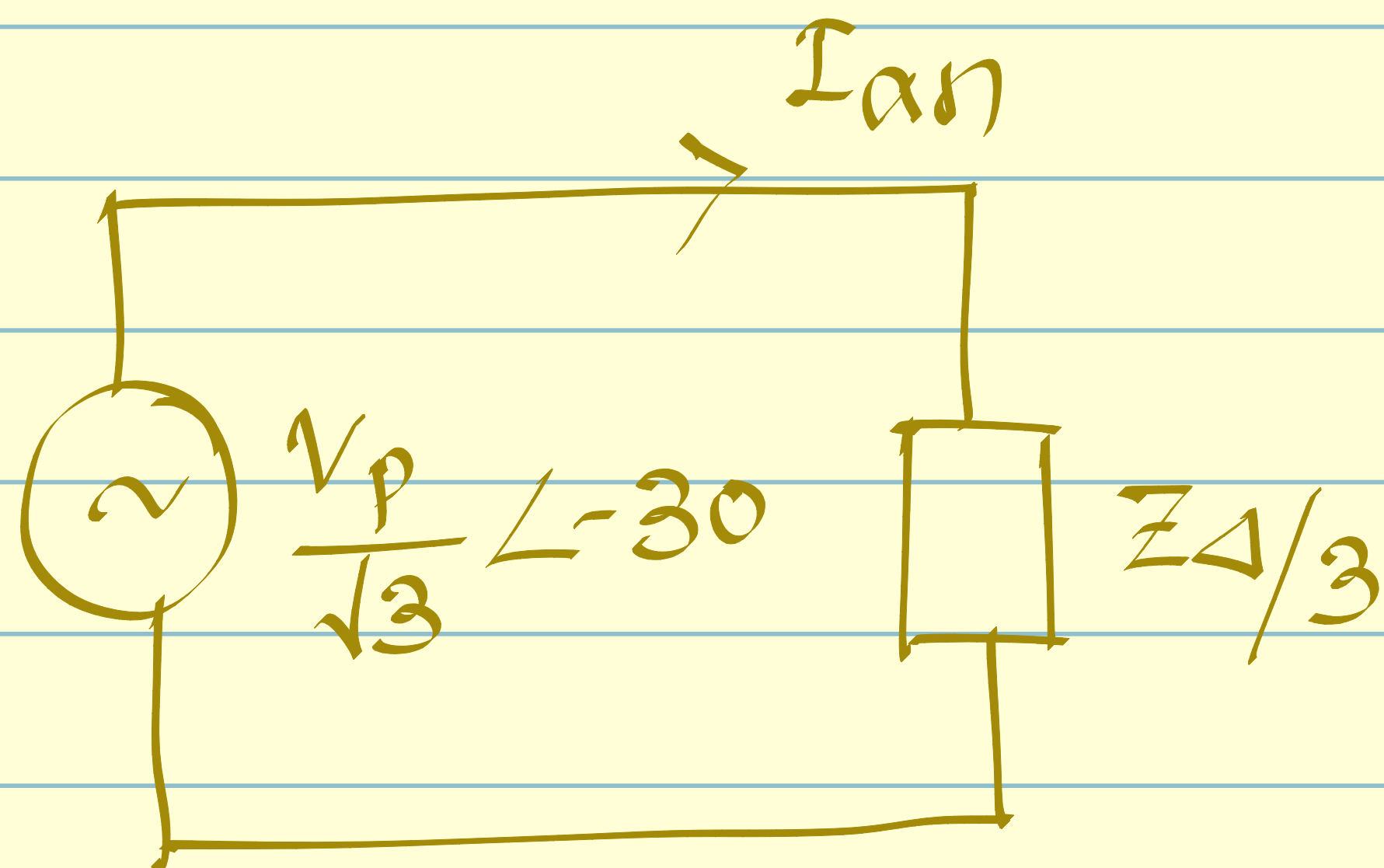
$$I_p = \left(\frac{V_p}{\sqrt{3}} \angle -30^\circ \right) \cdot \frac{1}{Z_\Delta/3}$$



Power in 3- ϕ balanced System:-

Let us consider a balanced γ Connected load for which, the per phase impedance is Z_Y

$$\text{where } Z_Y = |Z_Y| \angle \theta$$

$$V_{an} = V_m \cos \omega t$$

$$V_{bn} = V_m \cos (\omega t - 120^\circ)$$

$$V_{cn} = V_m \cos (\omega t + 120^\circ)$$

$$i_a = I_m \cos (\omega t - \theta)$$

$$i_b = I_m \cos (\omega t - \theta - 120^\circ)$$

$$i_c = I_m \cos (\omega t - \theta + 120^\circ)$$

3- ϕ instantaneous power consumed by the γ Connected load is

$$p = V_{an} i_a + V_{bn} i_b + V_{cn} i_c$$

$$= \frac{1}{2} V_m I_m \left[2 \cos \omega t \cos (\omega t - \theta) + \right.$$

$$2 \cos (\omega t - 120^\circ) \cos (\omega t - \theta - 120^\circ) + 2 \cos (\omega t + 120^\circ) \cos (\omega t + 120^\circ - \theta) \left. \right]$$

$$= \frac{1}{2} V_m I_m \left[\cos \theta + \cos (2\omega t - \theta) + \cos \theta + \cos (2\omega t - \theta - 240^\circ) + \cos \theta + \cos (2\omega t - \theta + 240^\circ) \right]$$

$$= \frac{3}{2} V_m I_m \cos \theta$$

$$= 3 V_p I_p \cos \theta$$

V_p, I_p are the per phase rms voltage and current

$$V_p = V_m / \sqrt{2} \quad I_p = I_m / \sqrt{2}$$

* 3- ϕ instantaneous power is constant w.r.t time. This is the general expression of 3 ϕ power valid for both γ and Δ connected load.

* This is one of the reasons, behind the generation & transmission of 3 ϕ power.

Now the per phase average power is

$$P_{1\phi} = V_p I_p \cos \theta$$

$$Q_{1\phi} = V_p I_p \sin \theta$$

$$S_{1\phi} = P_{1\phi} + j Q_{1\phi} = \tilde{V} \tilde{I}^*$$


$$S_{3\phi} = P_{3\phi} + j Q_{3\phi} = 3 \tilde{V} \tilde{I}^*$$

$$P_{3\phi} = 3 V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta$$

$$Q_{3\phi} = \sqrt{3} V_L I_L \sin \theta$$

Transmitted Power Same }
Efficiency Same.

3 ϕ 3 wire System:-

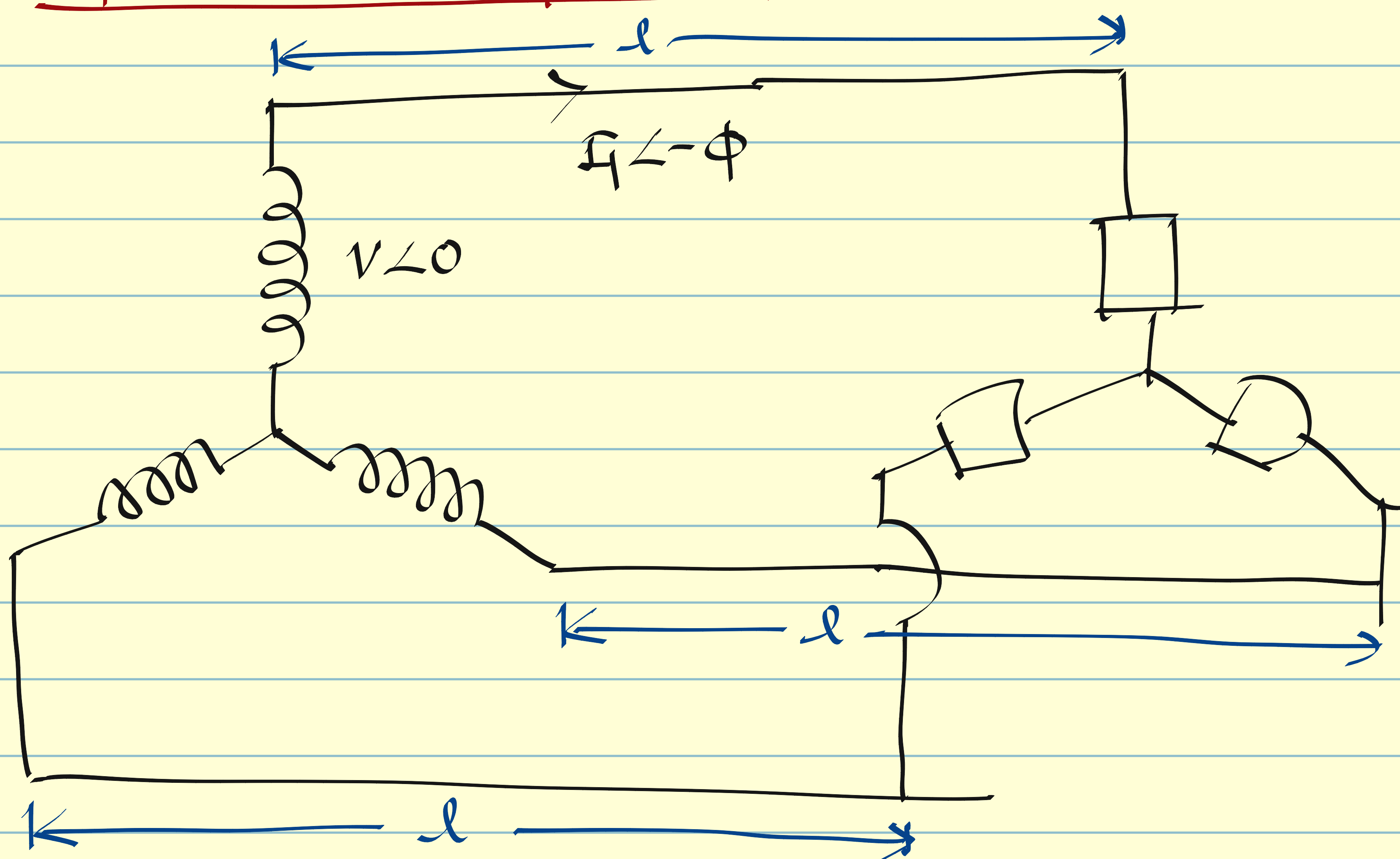

active power $P = 3 V I \cos \phi$

$$I_1 = \frac{P}{3 V \cos \phi}$$

$$R_1 = \int \frac{l}{A_1}$$

Total Power loss

$$W_{3\phi} = 3 I_1^2 R_1$$


$$= 3 \cdot \left(\frac{P}{3 V \cos \phi} \right)^2 \times \int \frac{l}{A_1}$$

$$A_1 = \frac{P^2 \int l}{3 V^2 \cos^2 \phi W_{3\phi}}$$

$$\text{Volume} = 3 l A_1 = \frac{P^2 \int l^2}{V^2 \cos^2 \phi W_{3\phi}}$$

(Vol_{3 ϕ})

1 ϕ 2 wire System :-

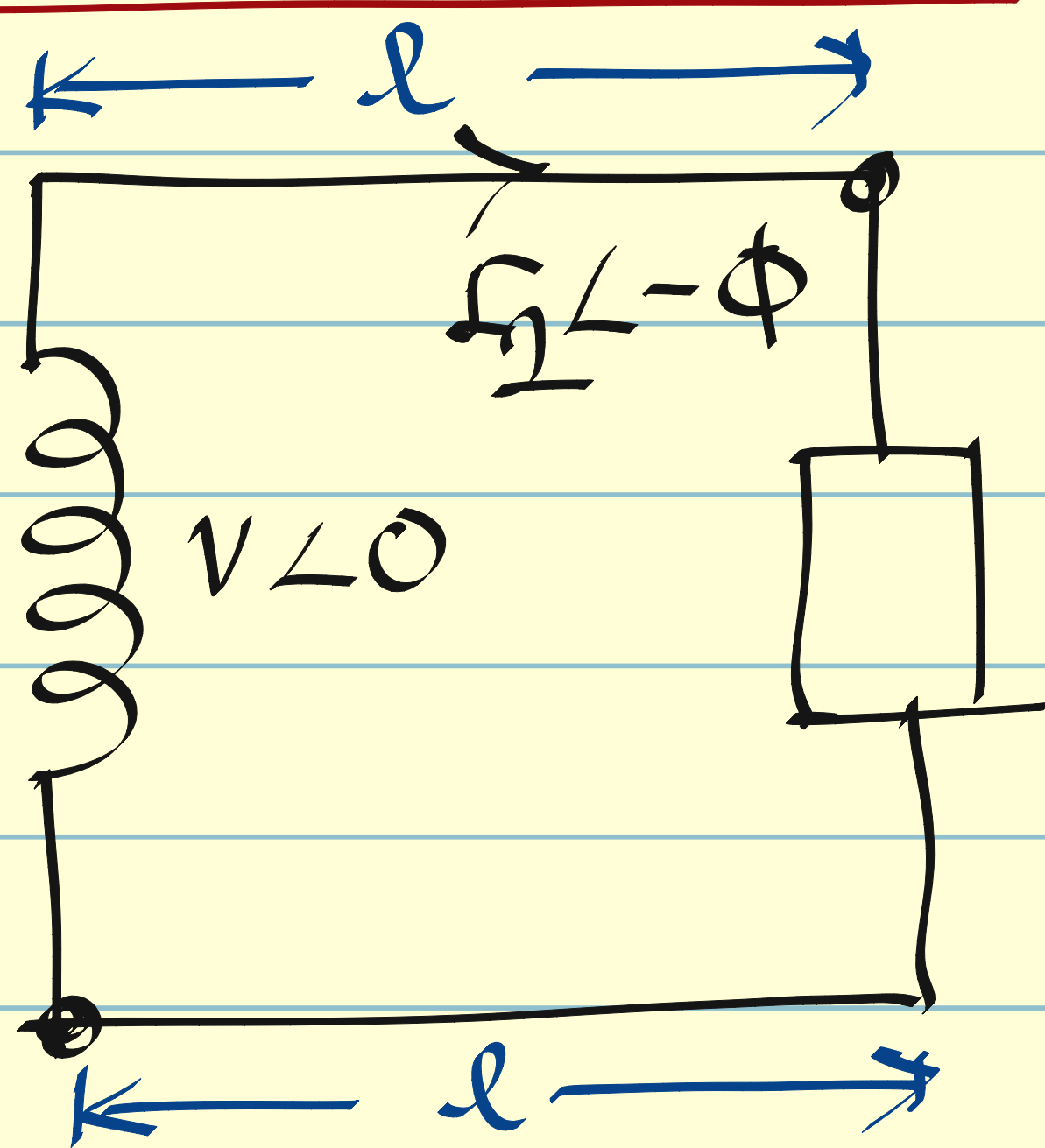

$$P = V I_2 \cos \phi$$

$$I_2 = \frac{P}{V \cos \phi}$$

$$R_2 = \int \frac{l}{A_2}$$

$$W_{1\phi} = 2 I_2^2 \times R_2$$

$$= 2 \frac{P^2}{V^2 \cos^2 \phi} \int \frac{l}{A_2}$$

$$A_2 = \frac{2 P^2 \int l}{V^2 \cos^2 \phi W_{1\phi}}$$

efficiency is
Same for both
of the cases.

$$\text{Volume} = 2 l A_2$$

$$(\text{Vol } 1\phi) = 2 l \cdot \frac{2 P^2 \int l}{V^2 \cos^2 \phi W_{1\phi}}$$

$$= \frac{4 P^2 \int l^2}{V^2 \cos^2 \phi W_{1\phi}}$$

$$\frac{\text{Vol } 1\phi}{4} = \text{Vol } 3\phi$$

$$\boxed{\text{Vol } 1\phi > \text{Vol } 3\phi}$$

More cu is required
for 1 ϕ compared to
3 phase.