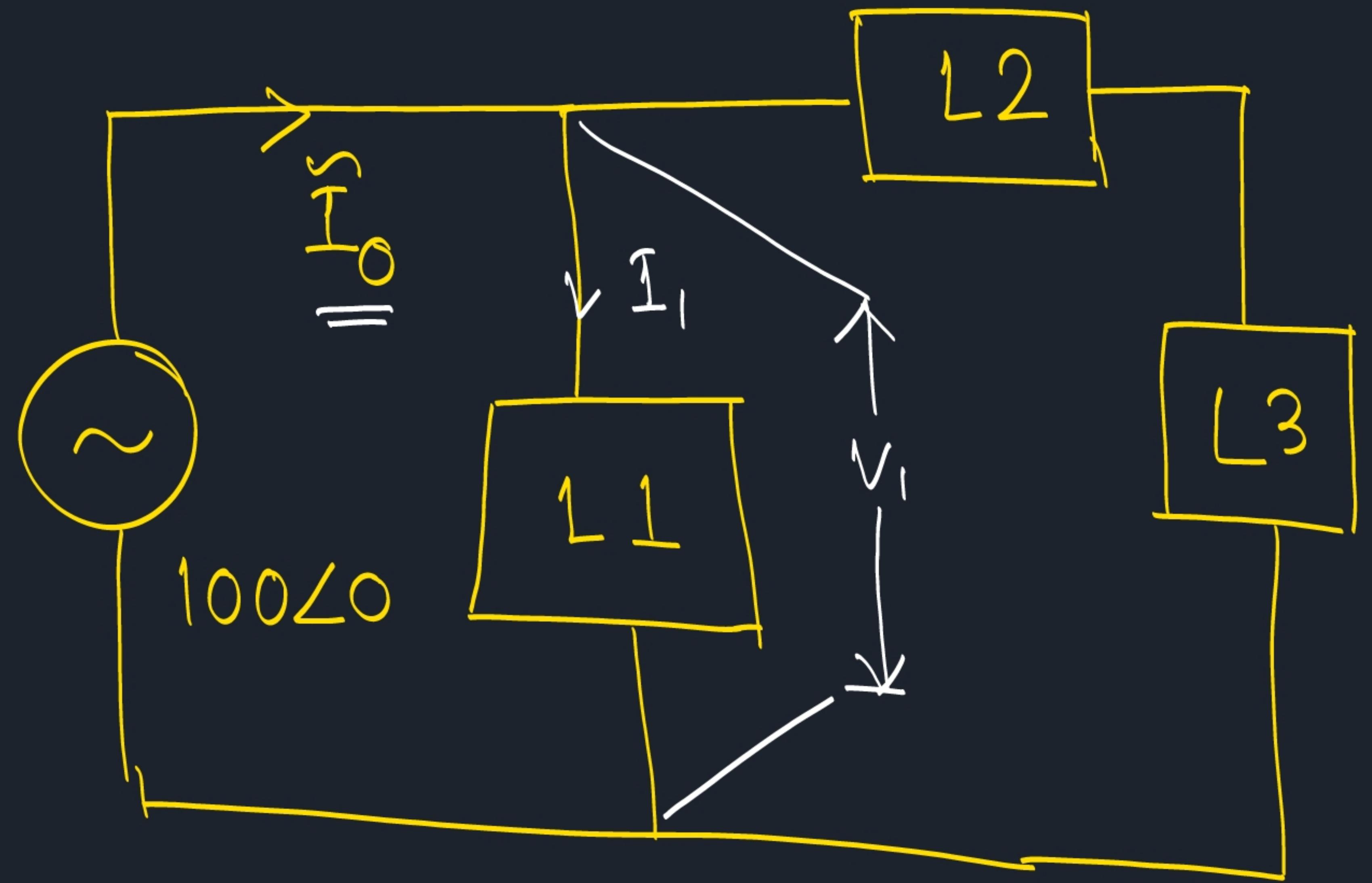


111

Problem :-

$$\frac{Q}{P} = \tan \theta$$



L₁: 2 KVA, 0.707 pf (lead)

L₂: 1.2 kW, 0.8 KVAR (Cap)

L₃: 4 kW, 0.9 pf (lag)

$$P + jQ = \tilde{V} \tilde{I}^*$$

$$P - jQ = \tilde{V}^* \tilde{I}$$

L₁ :- $S_1 = P_1 - jQ_1$

$$P_1 = S_1 \cos \theta_1 = (2 \times 0.707) \text{ kW}$$

$$Q_1 = S_1 \sin \theta_1 = 2 \times \sin \theta_1 \cos^{-1}(0.707) \text{ KVAR}$$

L₂ :- $S_2 = P_2 - jQ_2$

$$P_2 = 1.2 \text{ kW}$$

$$Q_2 = +0.8 \text{ KVAR}$$

$$S = S_1 + S_2 + S_3$$

$$= \sqrt{6.614 - j0.241} \text{ KVA}$$

$$= \sqrt{I_0^*}$$

$$I_0 = 66.29 \angle 2.4^\circ \text{ Amps}$$

L₃ :- $S_3 = P_3 + jQ_3$


$$P_3 = 4 \text{ kW}$$

$$Q_3 = 4 \times \tan \theta_3 \cos^{-1}(0.9)$$

$$Q_3 = 4 \text{ KVAR}$$





POLYPHASE CKT :-

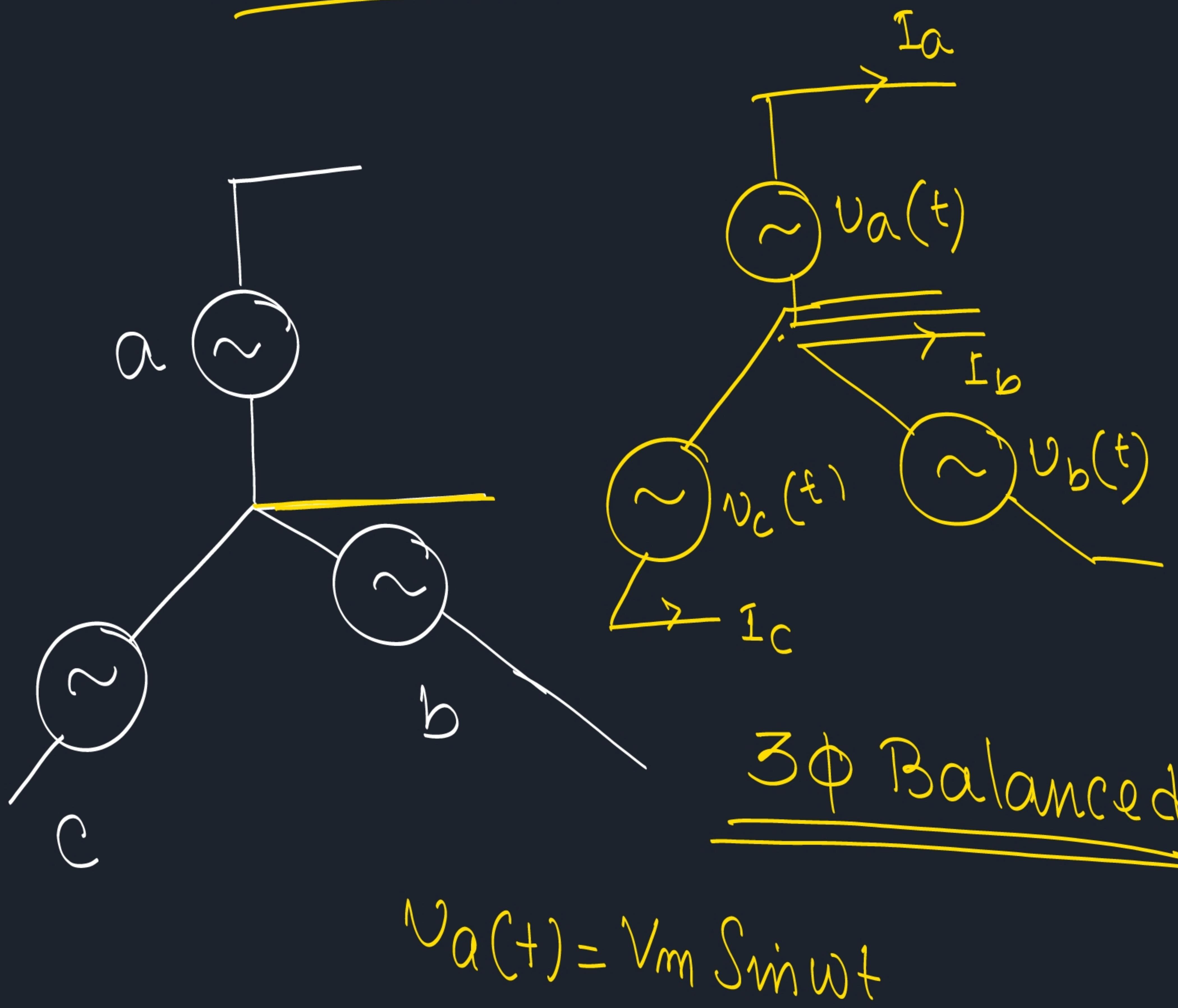

$$V_a(t) + V_b(t) + V_c(t) = 0 \quad \text{at } t$$

$$|V_a| = |V_b| = |V_c| = k.$$

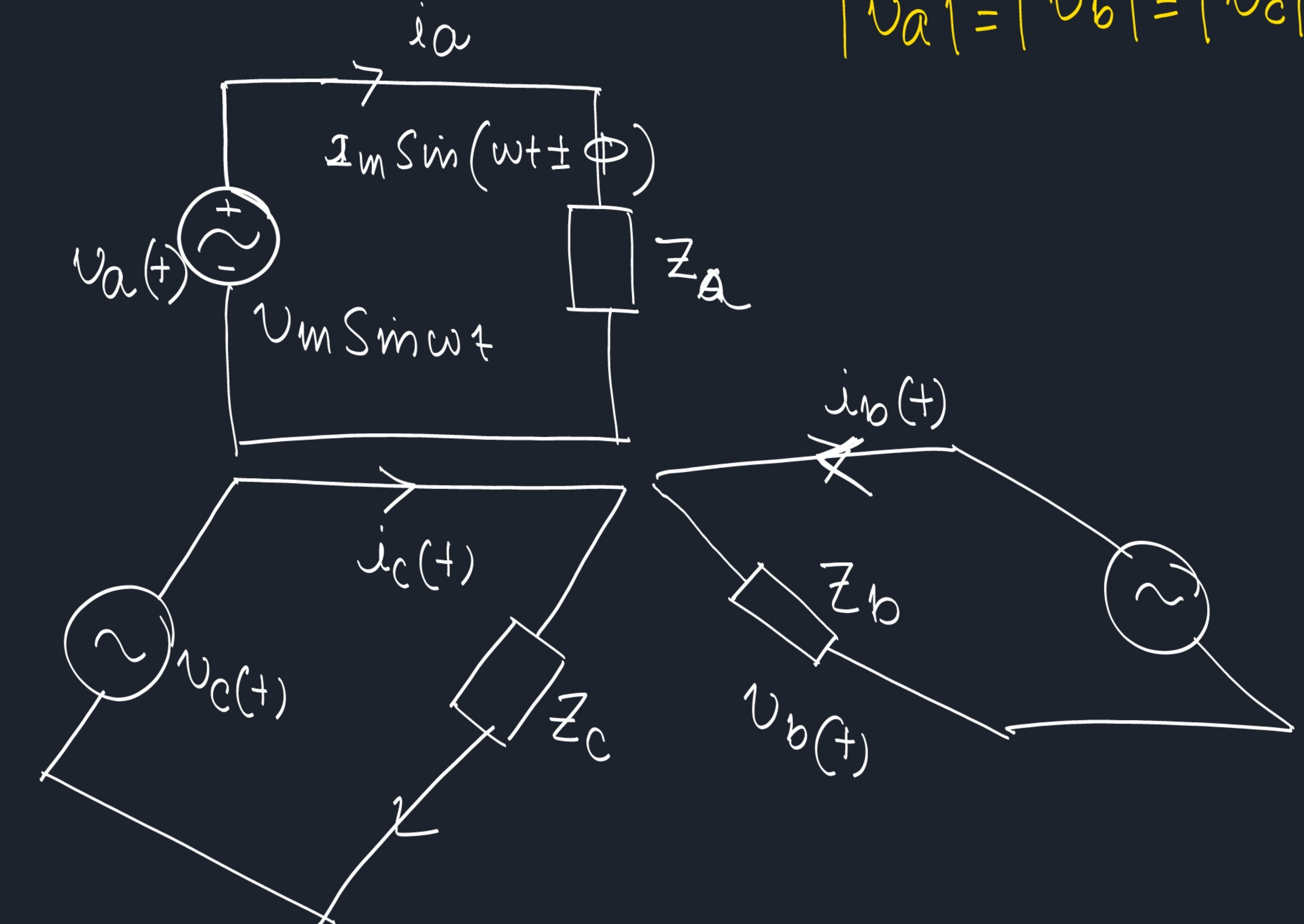

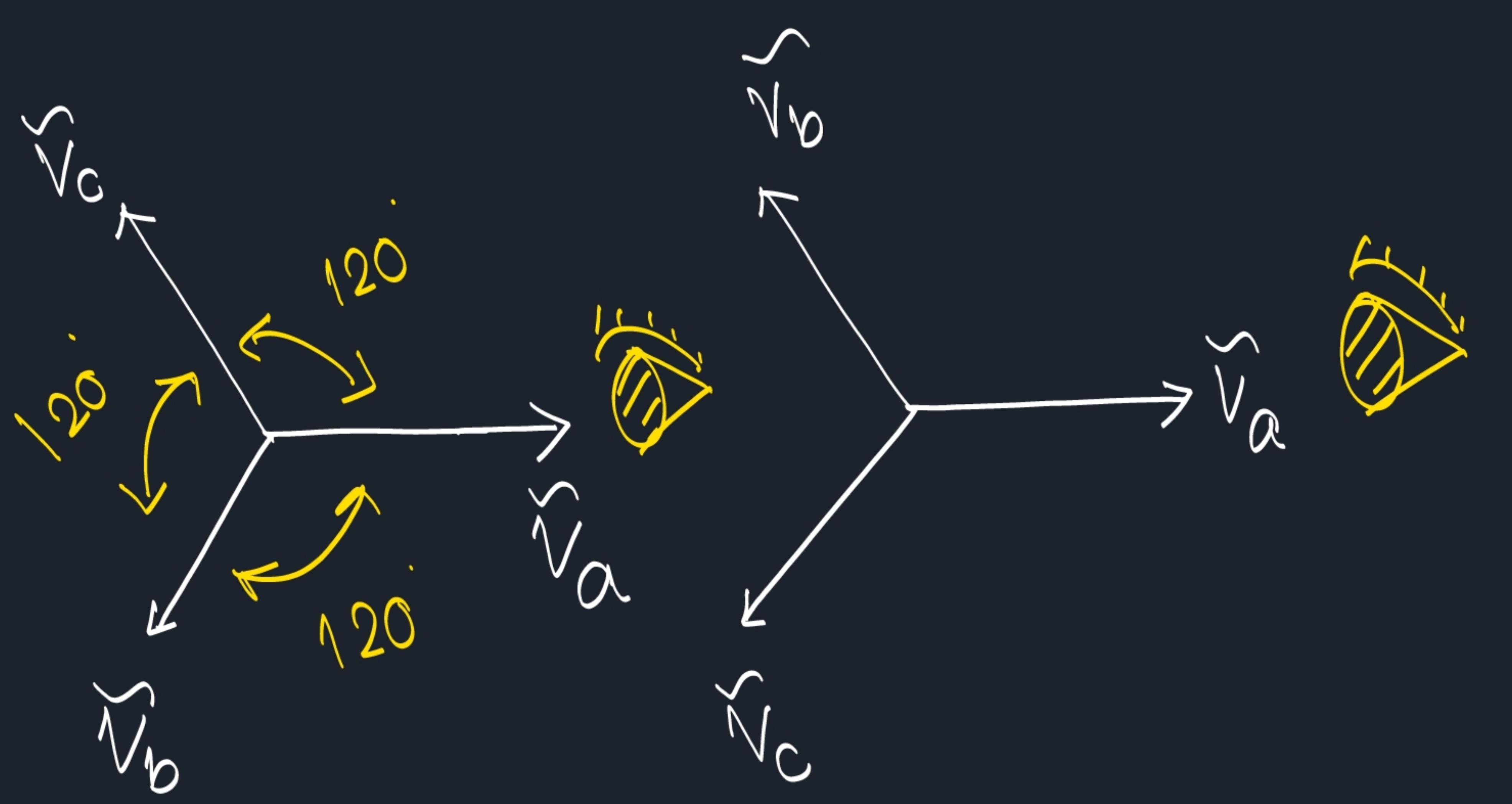

a - b - c - a - b - c
 $(+V_e)$ Seq

a - c - b - a - c - b
 $(-V_e)$ Seq.

$$\frac{a-b-c}{\tilde{V}_a = V_m \angle 0^\circ} \quad \left. \begin{array}{l} \tilde{V}_a = V_m \angle 0^\circ \\ \tilde{V}_b = V_m \angle -120^\circ \\ \tilde{V}_c = V_m \angle +120^\circ \end{array} \right\} \begin{array}{l} v_a(+) = V_m \sin(\omega t) \\ v_b(+) = V_m \sin(\omega t - 120^\circ) \\ v_c(+) = V_m \sin(\omega t + 120^\circ) \end{array}$$


$$\frac{a-c-b-a-c-b}{\tilde{V}_a = V_m \angle 0^\circ} \quad \left. \begin{array}{l} \tilde{V}_a = V_m \angle 0^\circ \\ \tilde{V}_b = V_m \angle 120^\circ \\ \tilde{V}_c = V_m \angle -120^\circ \end{array} \right\} \begin{array}{l} v_a(+) = V_m \sin \omega t \\ v_b(+) = V_m \sin(\omega t + 120^\circ) \\ v_c(+) = V_m \sin(\omega t - 120^\circ) \end{array}$$

$$V_a(+) + V_b(+) + V_c(+) = 0$$

$$\tilde{V}_a + \tilde{V}_b + \tilde{V}_c = 0$$



$$|V_a| = |V_b| = |V_c| = 100\text{V}$$

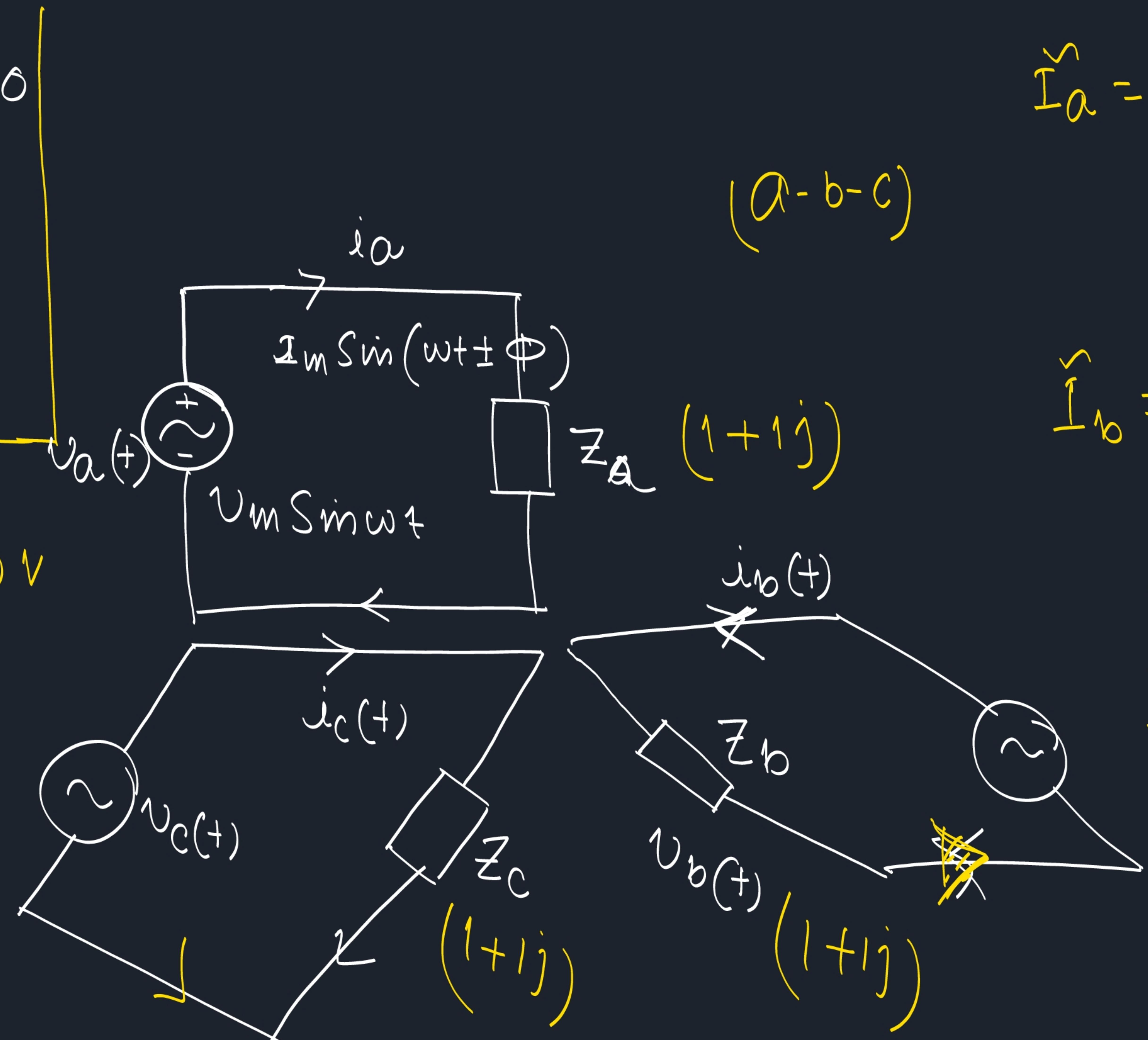

$$\tilde{I}_a = \frac{\tilde{V}_a}{z_a} = \frac{100 \angle 0}{1+j}$$


$$= 70.7 \angle -45^\circ$$

$$\tilde{I}_b = \frac{100 \angle -120^\circ}{1+j}$$

$$= 70.7 \angle -120-45^\circ$$

$$\tilde{I}_c = \frac{\tilde{V}_c}{z_c} = \frac{100 \angle 120^\circ}{1+j}$$

$$= 70.7 \angle 120-45^\circ$$

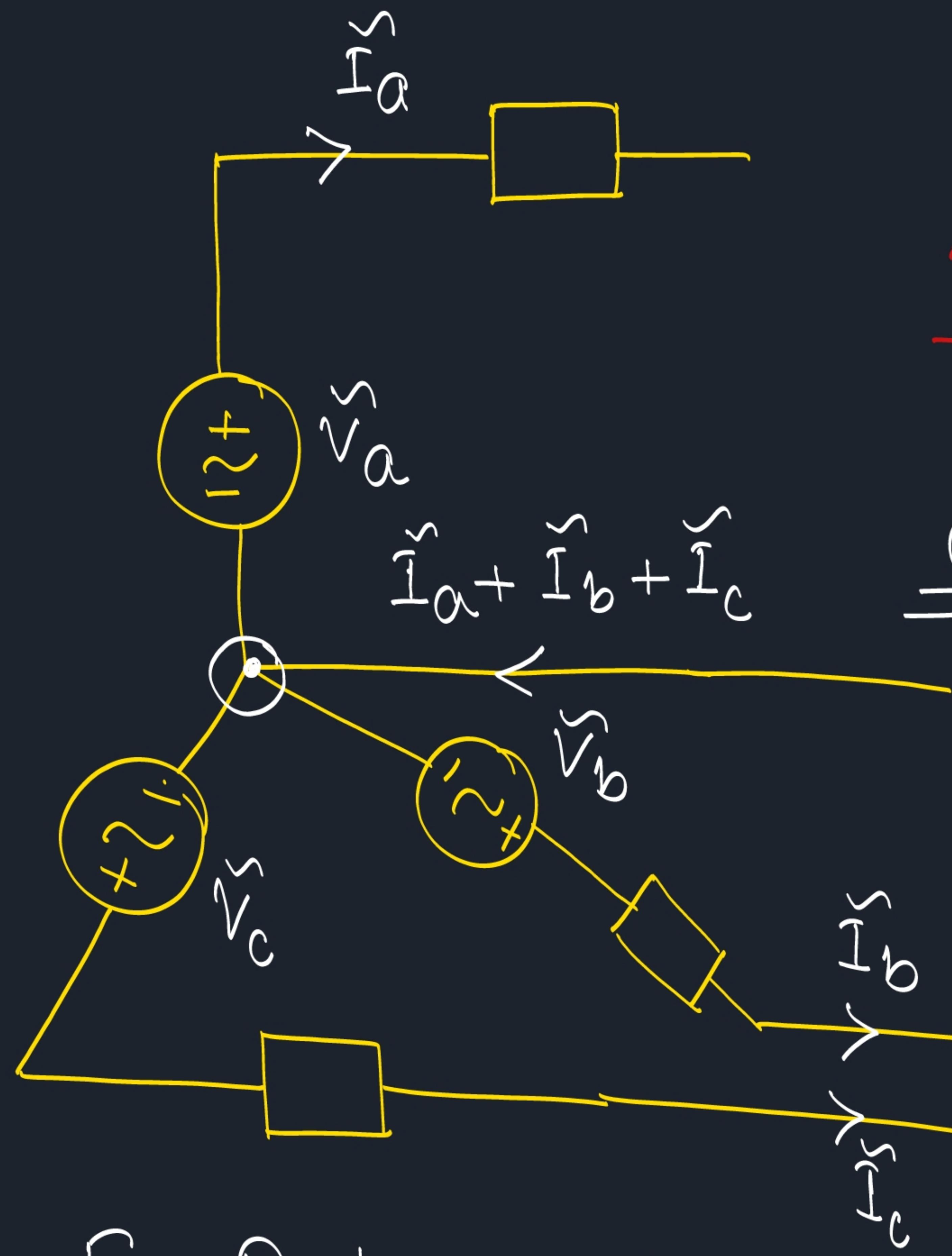




R - Y - B

a - b - c

For Balanced System
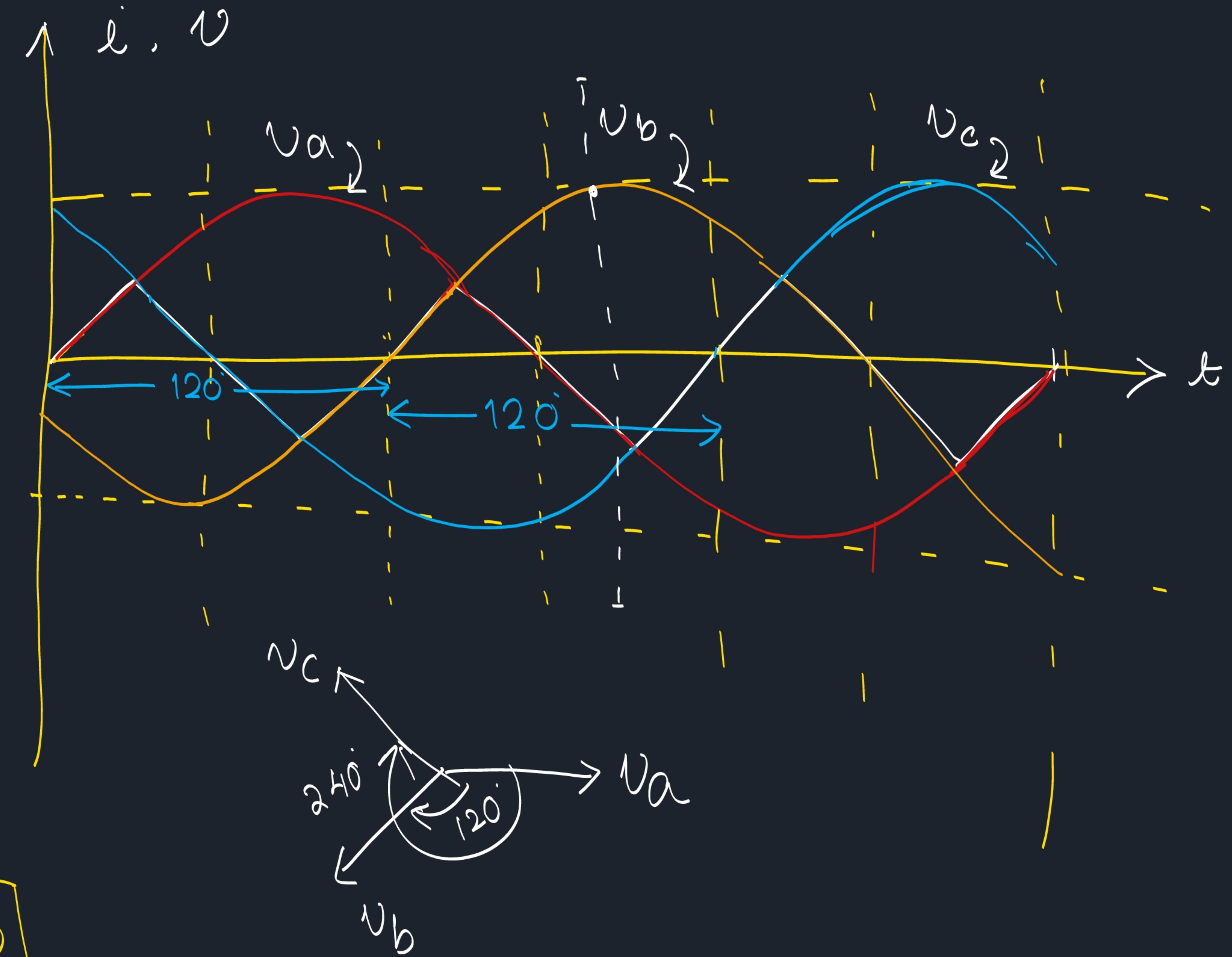
$$\boxed{\text{I}_{a+} + \text{I}_{b-} + \text{I}_{c-} = 0}$$



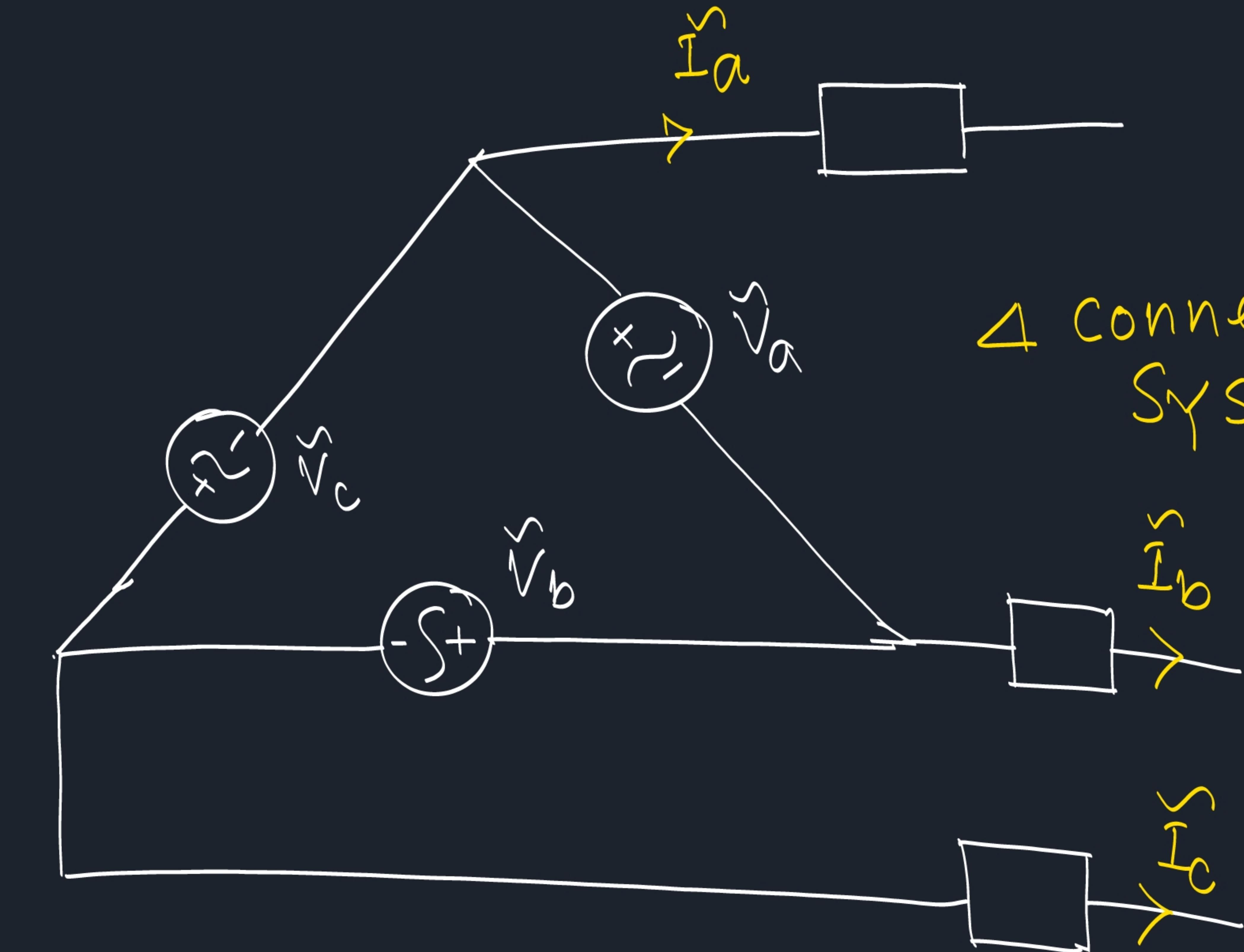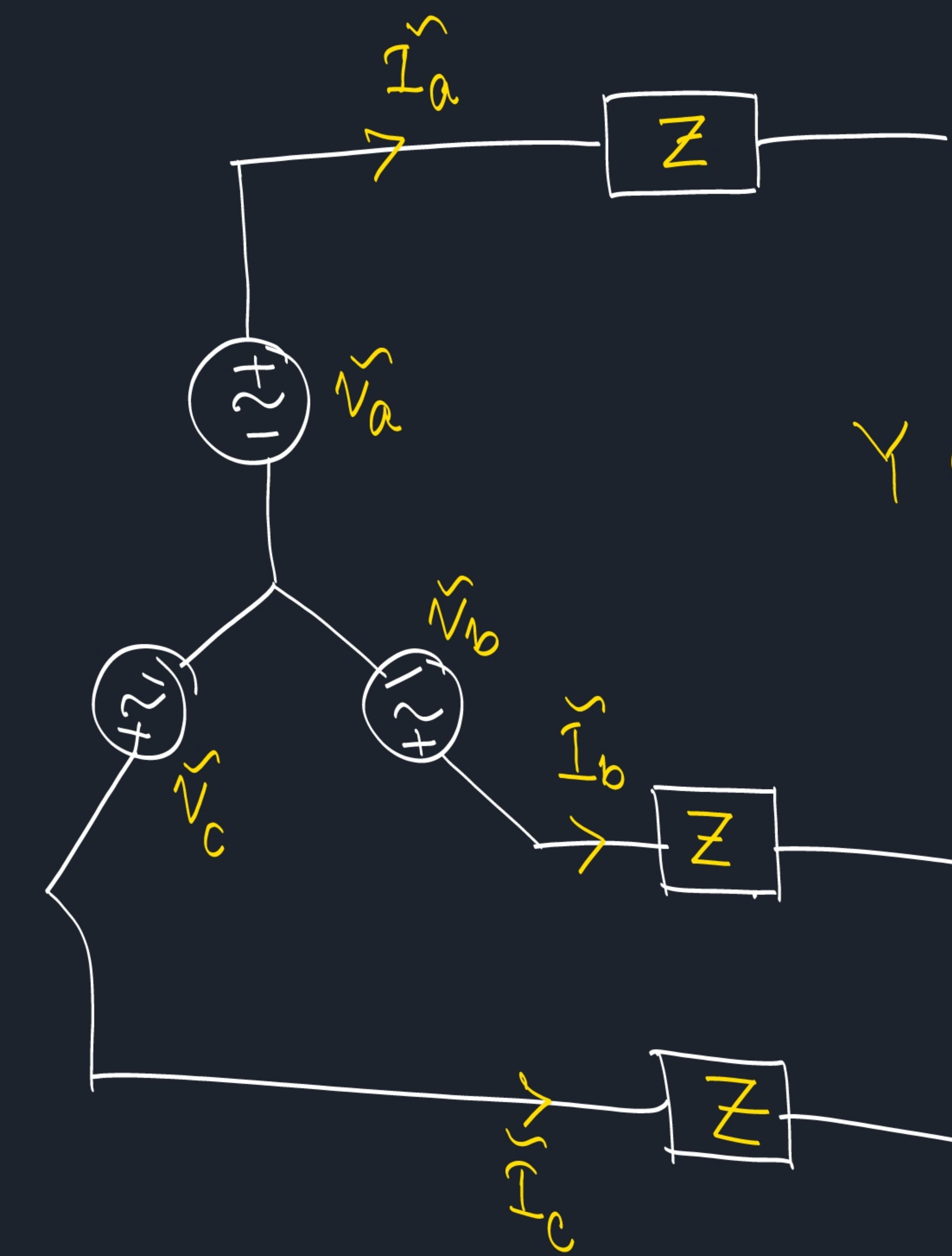

Source

1.



2.



3.




4.



Load



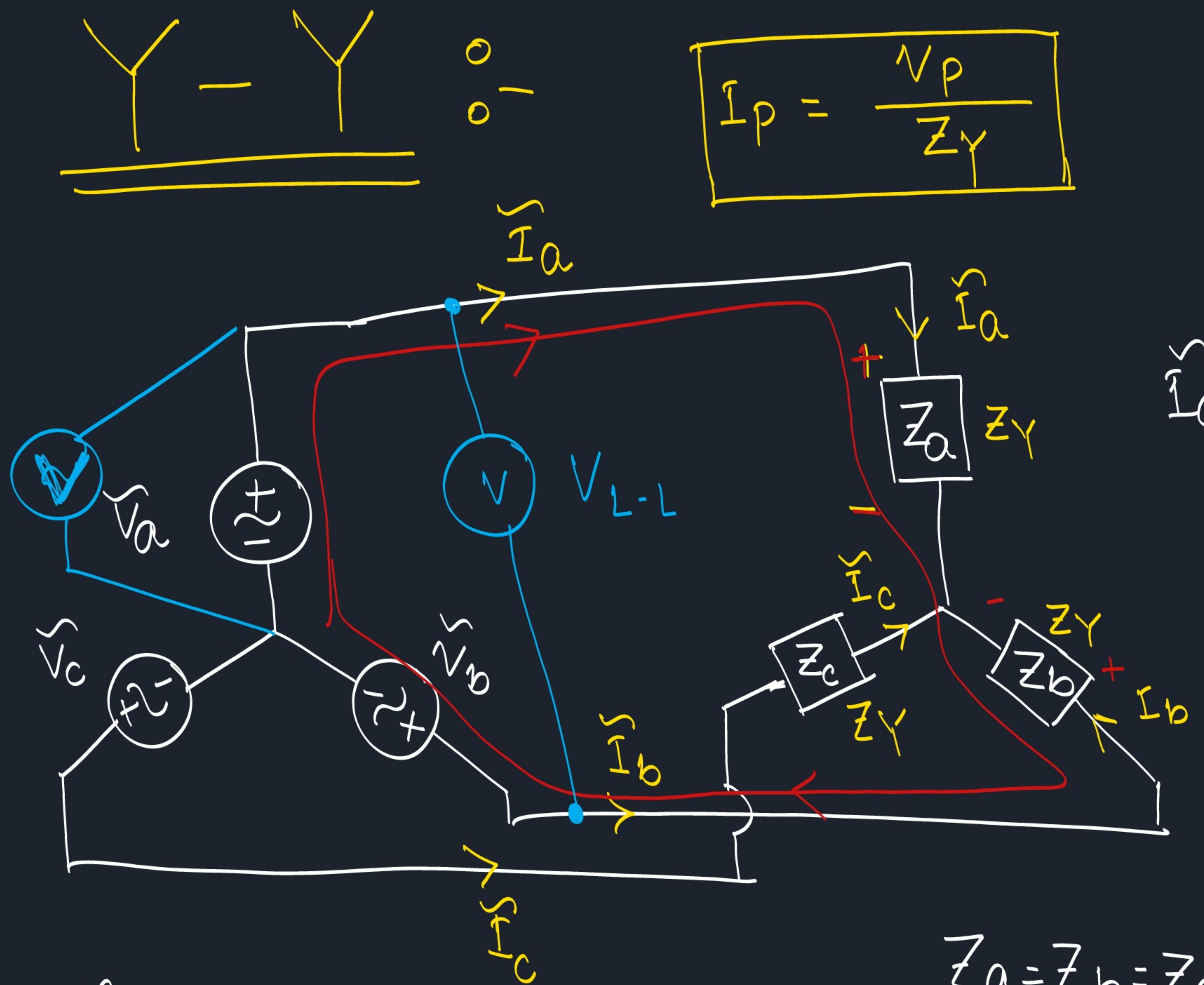


$$\tilde{V}_a + \tilde{V}_b + \tilde{V}_c = 0$$

$$|\tilde{V}_a| = |\tilde{V}_b| = |\tilde{V}_c|$$

$$Z_a = Z_b = Z_c = Z_Y$$

$$I_P = \frac{V_p}{Z_Y}$$

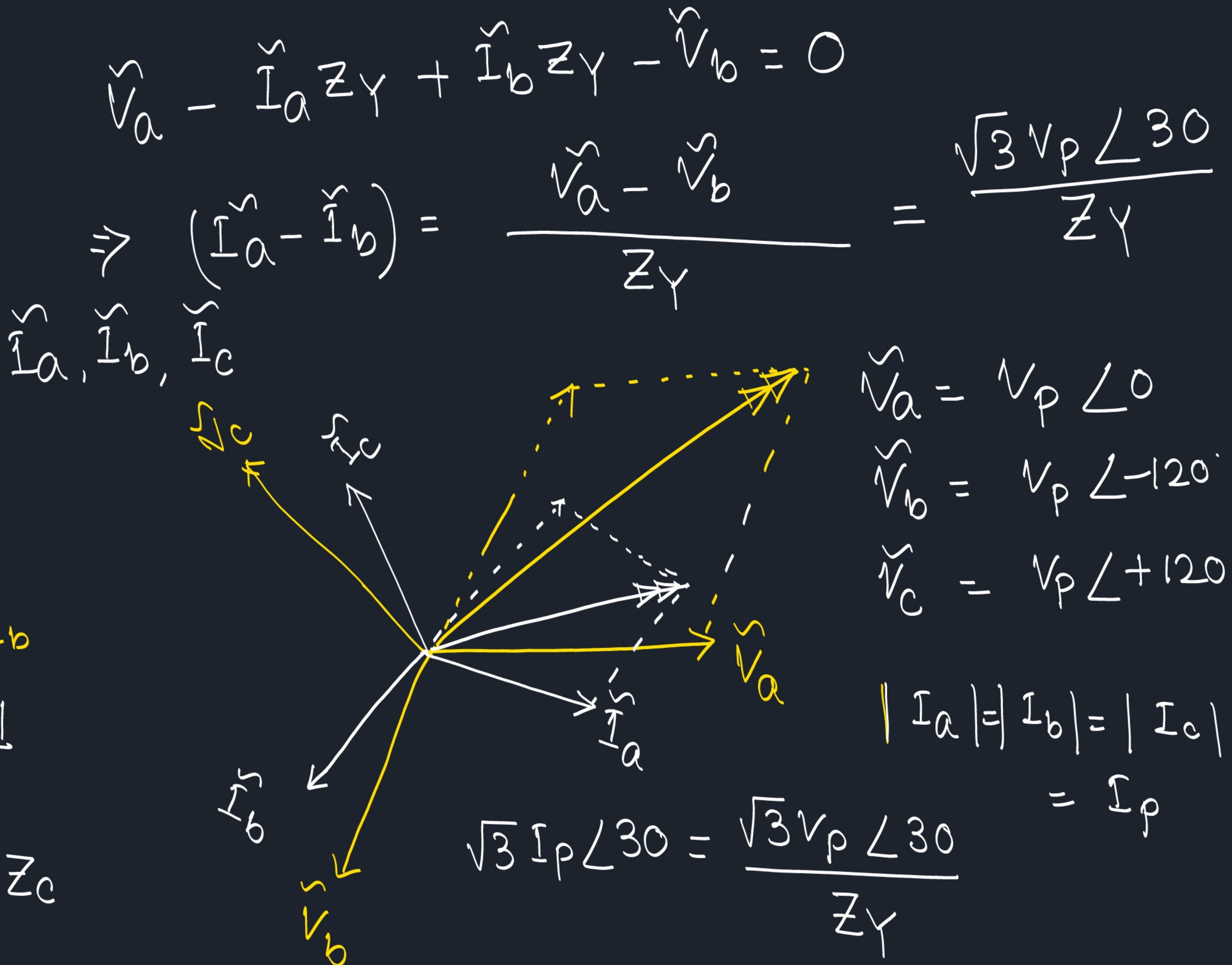

$$\tilde{I}_a = I_p \angle 0$$

$$= \frac{V_p}{Z_Y} \angle 0 = \frac{V_p}{|Z_Y|} \angle -\theta$$


$$Z_Y = |Z_Y| \angle \theta$$

$$\downarrow \\ 1 + 1j$$


$$\tilde{I}_b = \frac{V_p}{|Z_Y|} \angle -\theta - 120^\circ$$

$$\tilde{I}_c = -\frac{V_p}{|Z_Y|} \angle -\theta + 120^\circ$$

$$Y \quad \left\{ \begin{array}{l} |V_{L-L}| = \sqrt{3} |V_{ph}| \\ |\tilde{I}_L| = |\tilde{I}_{ph}| \end{array} \right.$$

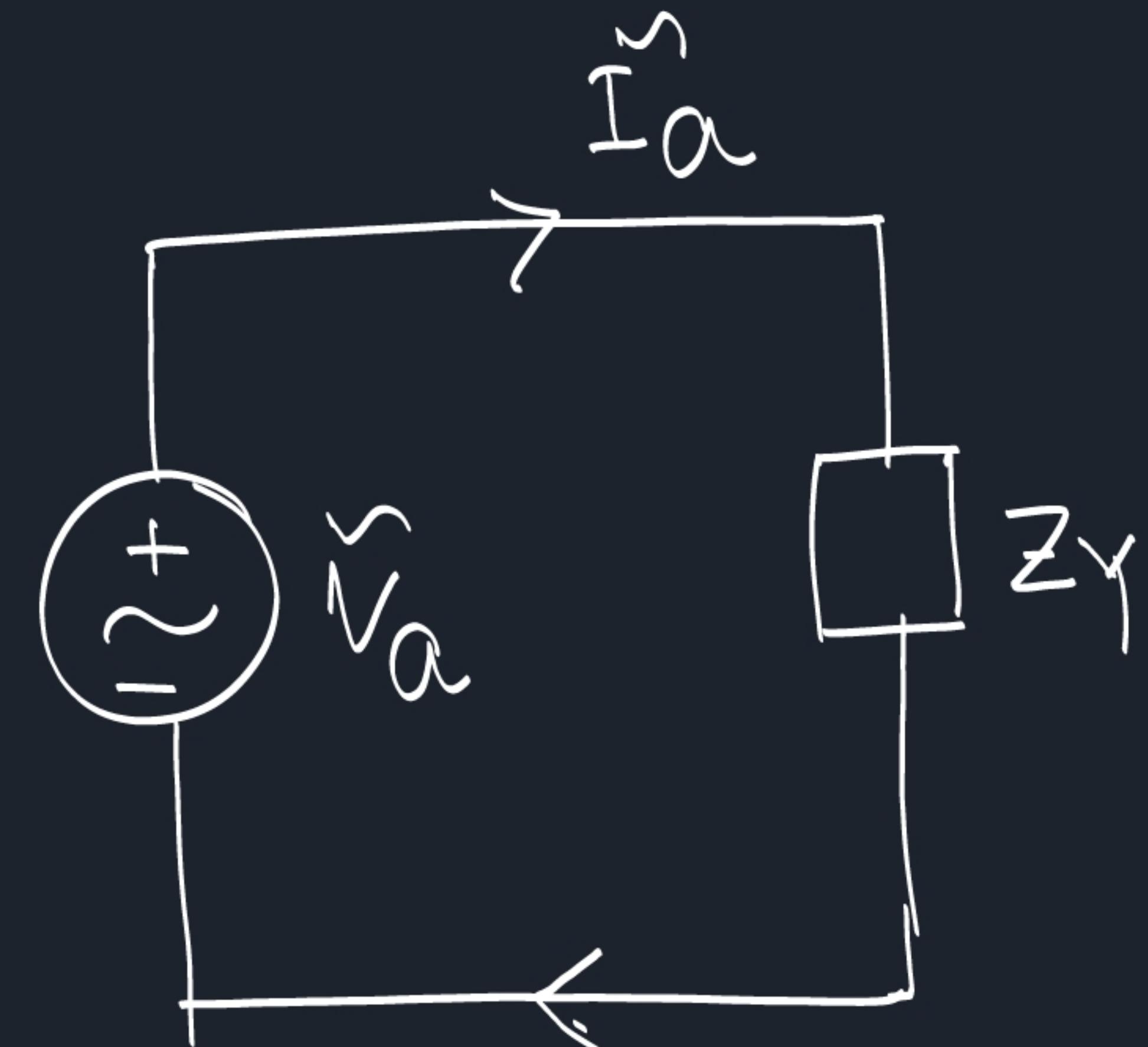

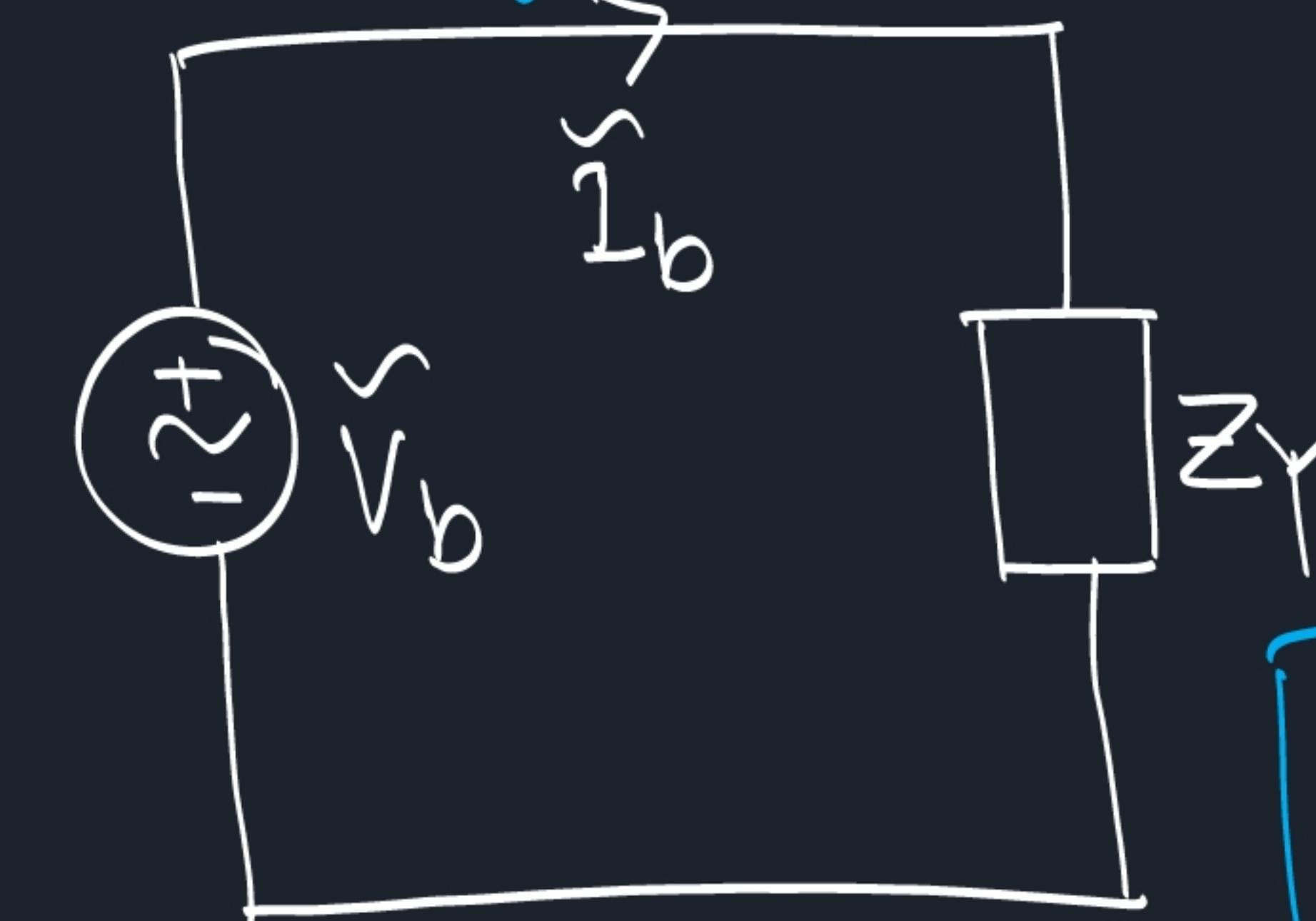
$$\begin{aligned} \tilde{V}_a - \tilde{V}_b &= \sqrt{3} V_p \angle 30^\circ \\ &= (\underbrace{V_p \angle 0}_{\tilde{V}_a}) \cdot \sqrt{3} \angle 30^\circ \end{aligned}$$




$$\boxed{\tilde{V}_a - \tilde{V}_b = \tilde{V}_a (\sqrt{3} \angle 30^\circ)}$$

$$\begin{aligned} \tilde{V}_a &= V_p \angle 0 \\ V_{L-L} &= \tilde{V}_a - \tilde{V}_b \\ &= \tilde{V}_{ab} \end{aligned}$$

$$V_{ph} = \tilde{V}_a$$

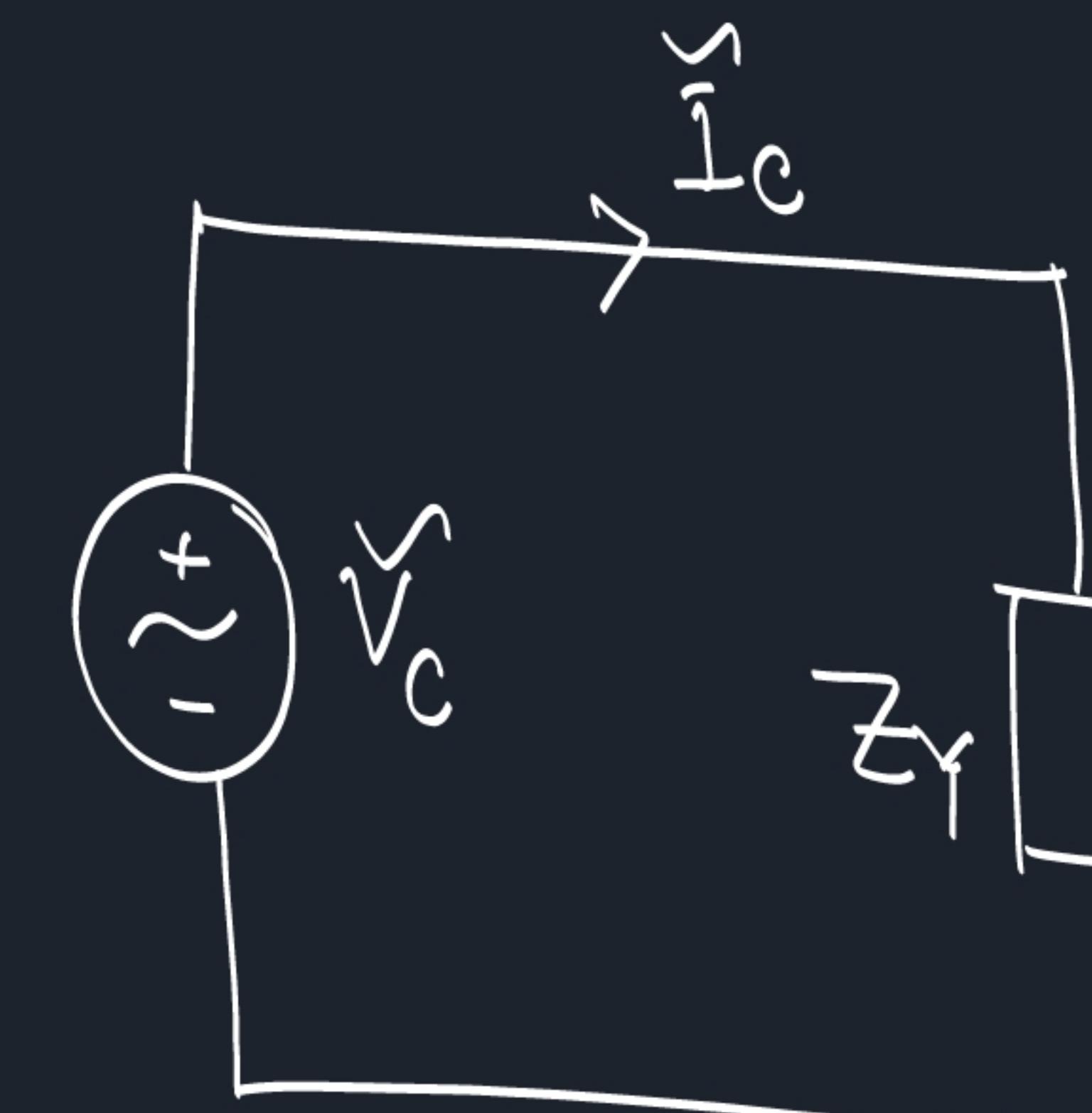

$\text{Y} - \Delta \quad 0^\circ$

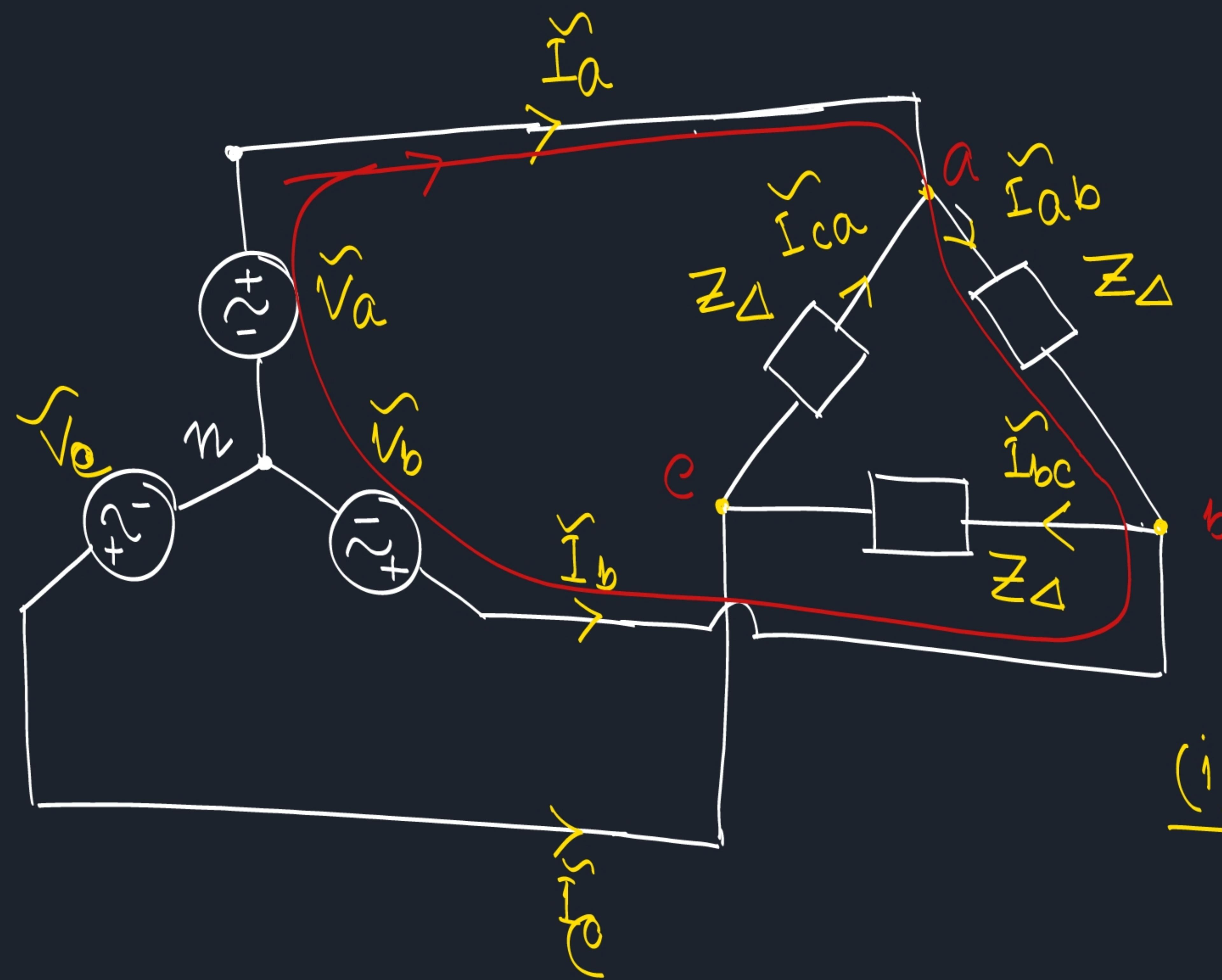

KVL

$$\tilde{V}_a - \tilde{I}_{ab} Z_\Delta - \tilde{V}_b = 0$$

$$\Rightarrow \tilde{I}_{ab} = \frac{\tilde{V}_a - \tilde{V}_b}{Z_\Delta}$$

$$\tilde{V}_a - \tilde{V}_b = V_p \sqrt{3} \angle +30^\circ$$

$$\tilde{I}_a = \tilde{I}_{ab} - \tilde{I}_{ca} \dots (i)$$

$$\tilde{I}_b = \tilde{I}_{bc} - \tilde{I}_{ab} \dots (ii)$$

$$\tilde{I}_c = \tilde{I}_{ca} - \tilde{I}_{bc} \dots (iii)$$

$$\tilde{I}_{ab} + \tilde{I}_{bc} + \tilde{I}_{ca} = 0$$

as the S/S is balanced.

(i)-(ii)

$$\tilde{I}_a - \tilde{I}_b = 2 \tilde{I}_{ab} - (\tilde{I}_{bc} + \tilde{I}_{ca})$$

$$\boxed{\tilde{I}_{ab} = \frac{\tilde{I}_a - \tilde{I}_b}{3}}$$

1850.

$$\left. \begin{aligned} \tilde{I}_{ab} &= \frac{\tilde{V}_a - \tilde{V}_b}{Z_\Delta} \\ \tilde{I}_{ab} &= \frac{\tilde{I}_a - \tilde{I}_b}{3} \end{aligned} \right\}$$

$$\tilde{V}_a - \tilde{V}_b = \sqrt{3} V_p \angle 30^\circ$$


$$\tilde{I}_a - \tilde{I}_b = \sqrt{3} I_p \angle 30^\circ$$

$$I_p = \frac{V_p}{\left(\frac{Z_\Delta}{3}\right)}$$

$$|I_p| = \frac{|V_p|}{\left|\frac{Z_\Delta}{3}\right|}$$

$$\tilde{I}_a = I_p \angle \theta$$


$$= \left| \frac{V_p}{\frac{Z_\Delta}{3}} \right| \angle \theta$$

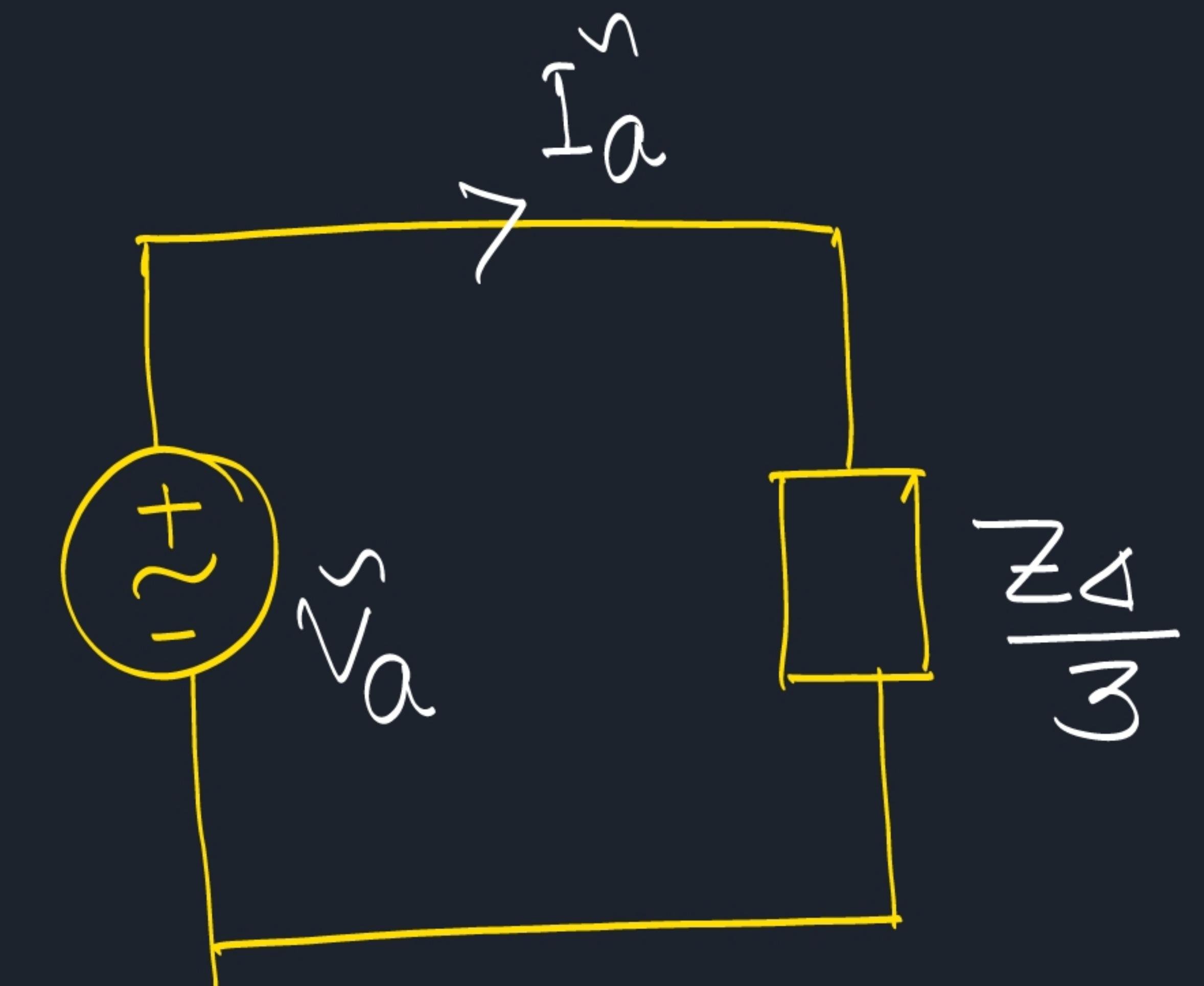

$$\tilde{I}_{ab} = \frac{\tilde{I}_a - \tilde{I}_b}{3}$$

$$I_{L-L} = \sqrt{3} I_p$$

Single phase equivalent eqy.

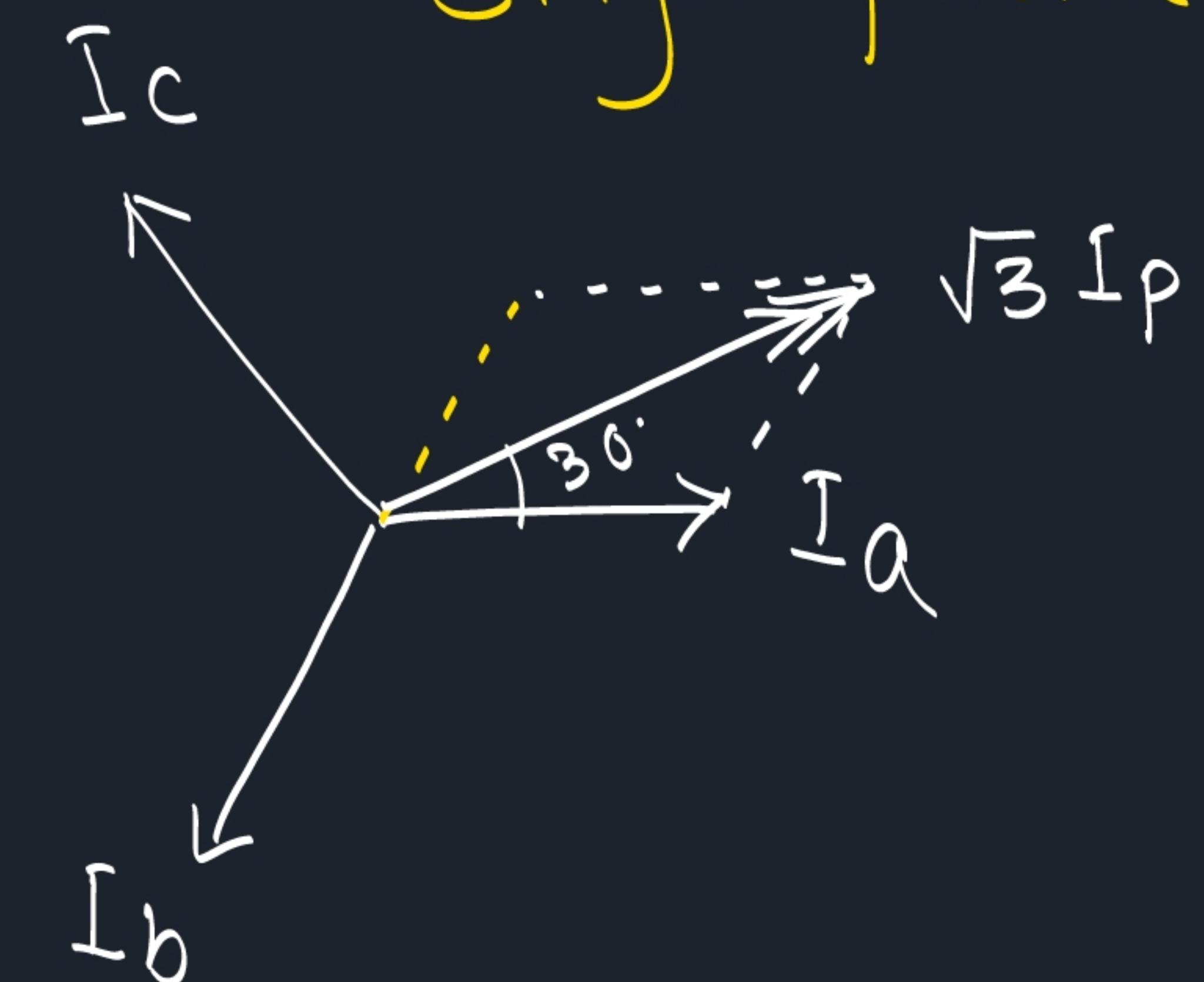

$$|\tilde{I}_{ab}| = \frac{I_p}{\sqrt{3}}$$



Voltage

Line voltage
= Phase voltage

$$= \sqrt{3} \times \text{Phase Voltage}$$

$$\boxed{V_{L-L} = \sqrt{3} V_{ph}}$$

Current

$$\boxed{I_L = I_{ph}}$$

Current

$$\boxed{I_L = \sqrt{3} I_{ph}}$$





Voltage


Line voltage

= Phase voltage

$$\boxed{V_{L-L} = V_{ph}}$$

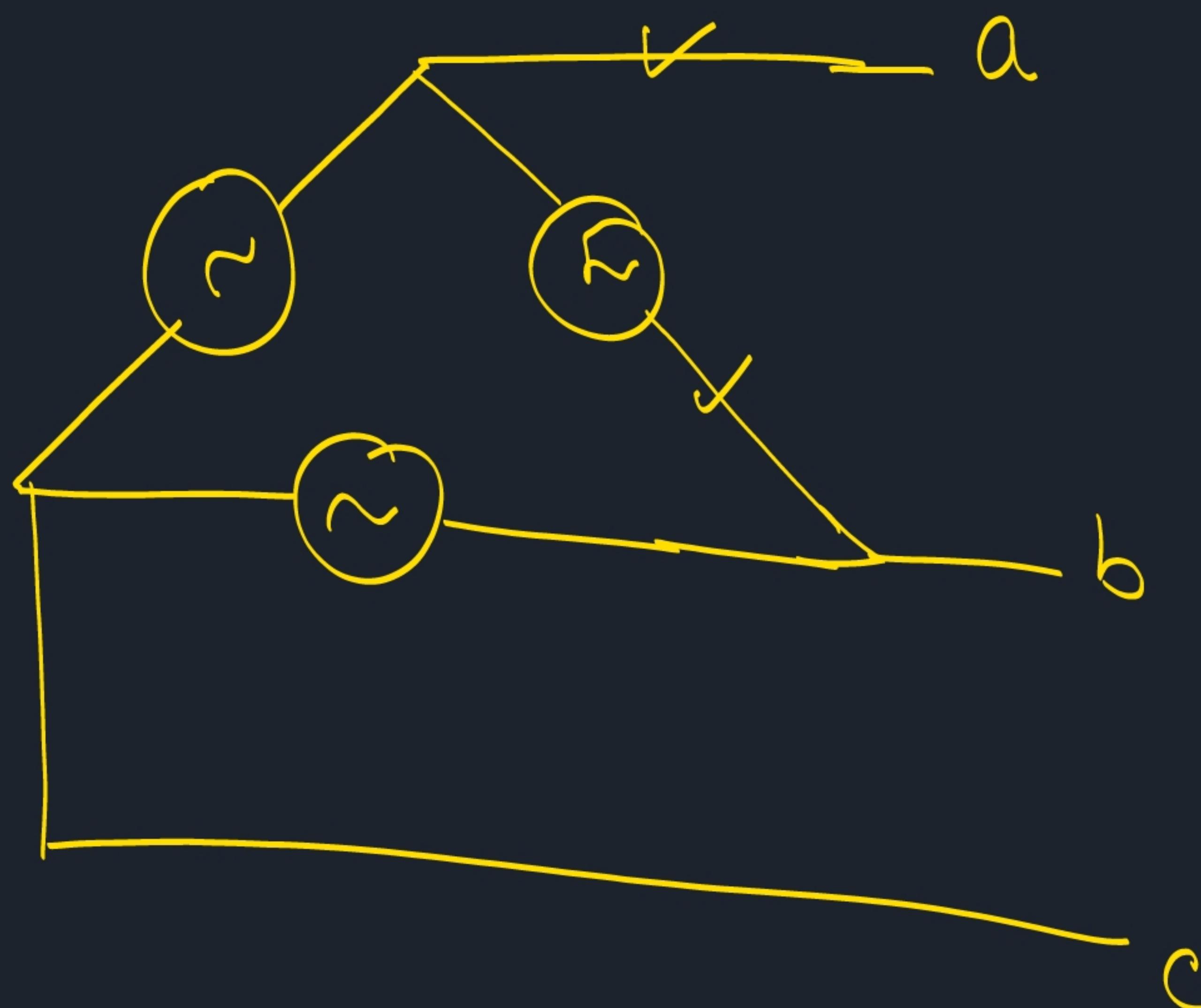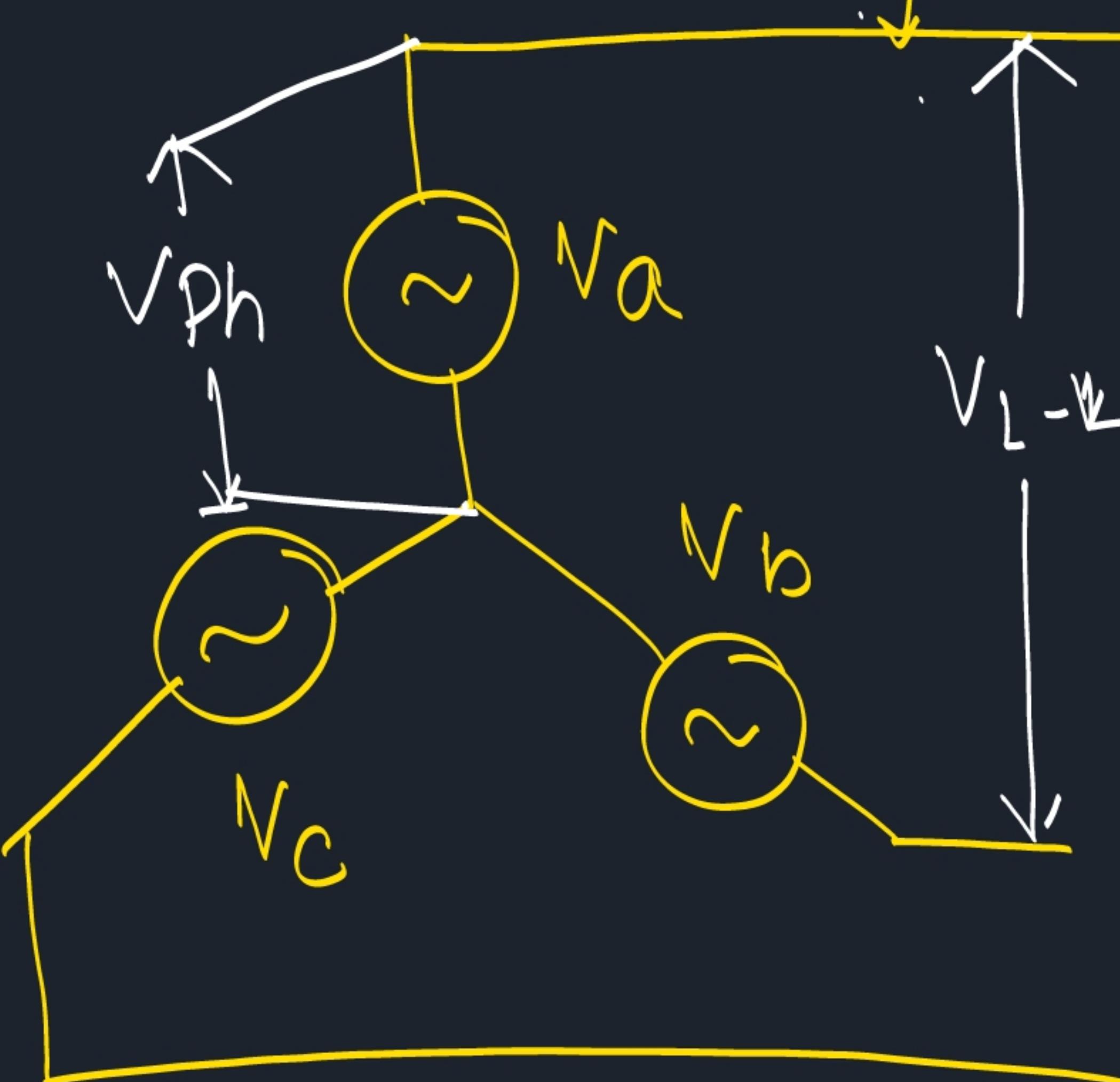

$$\Delta - Y$$

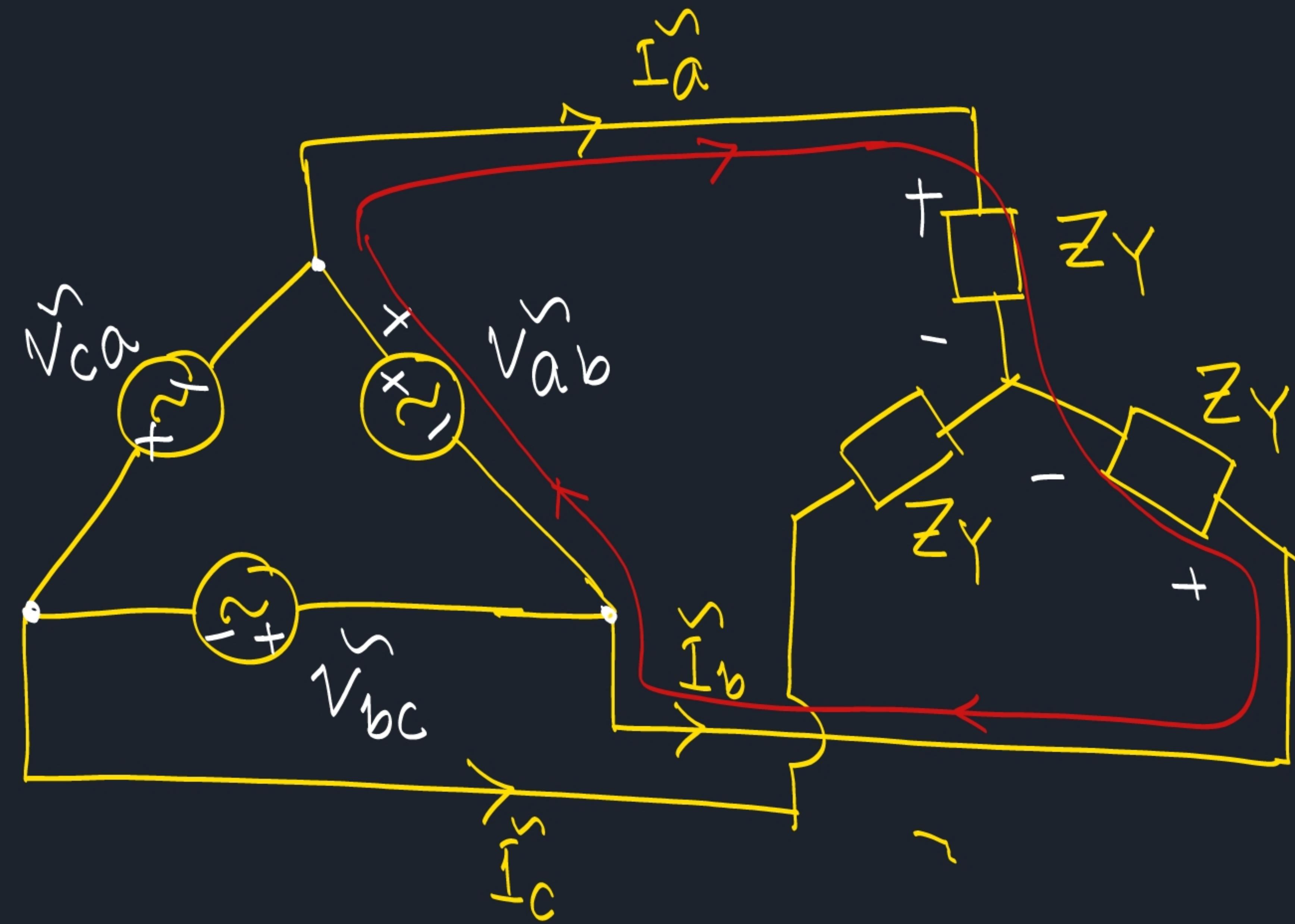


$$\tilde{V}_{ab} - \tilde{I}_a Z_Y + \tilde{I}_b Z_Y = 0$$

$$\Rightarrow \tilde{I}_a - \tilde{I}_b = \frac{\tilde{V}_{ab}}{Z_Y}$$

$$\Rightarrow \sqrt{3} I_p \angle 30^\circ = \frac{V_p \angle 0}{Z_Y}$$
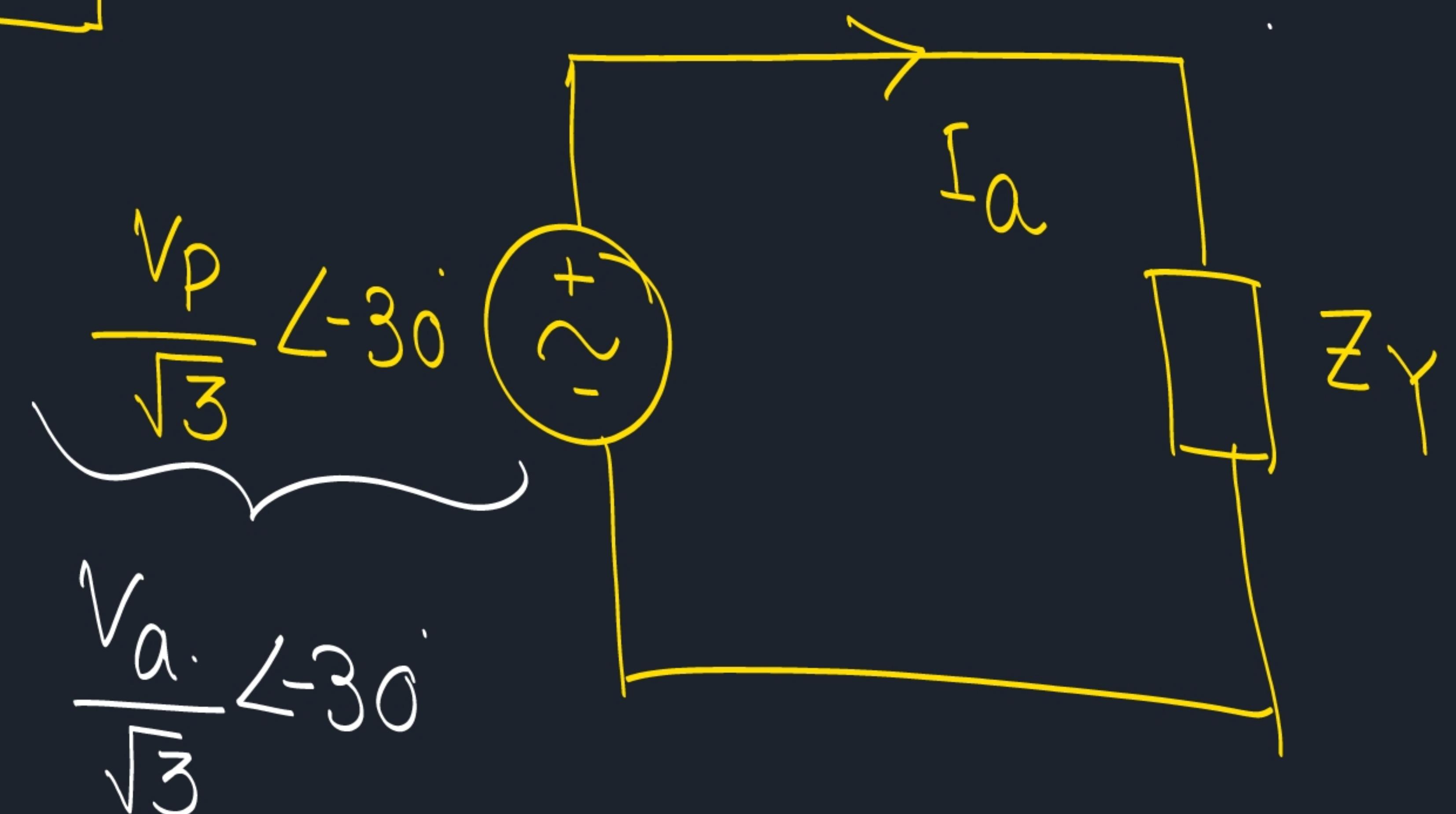
$$\Rightarrow I_p = \left(\frac{V_p}{\sqrt{3}} \angle -30^\circ \right) \cdot \frac{1}{Z_Y}$$





$$\tilde{V}_{ab} = V_p \angle 0$$

$$\tilde{V}_{bc} = V_p \angle -120^\circ$$


$$\tilde{V}_{ca} = V_p \angle +120^\circ$$

Δ - Δ

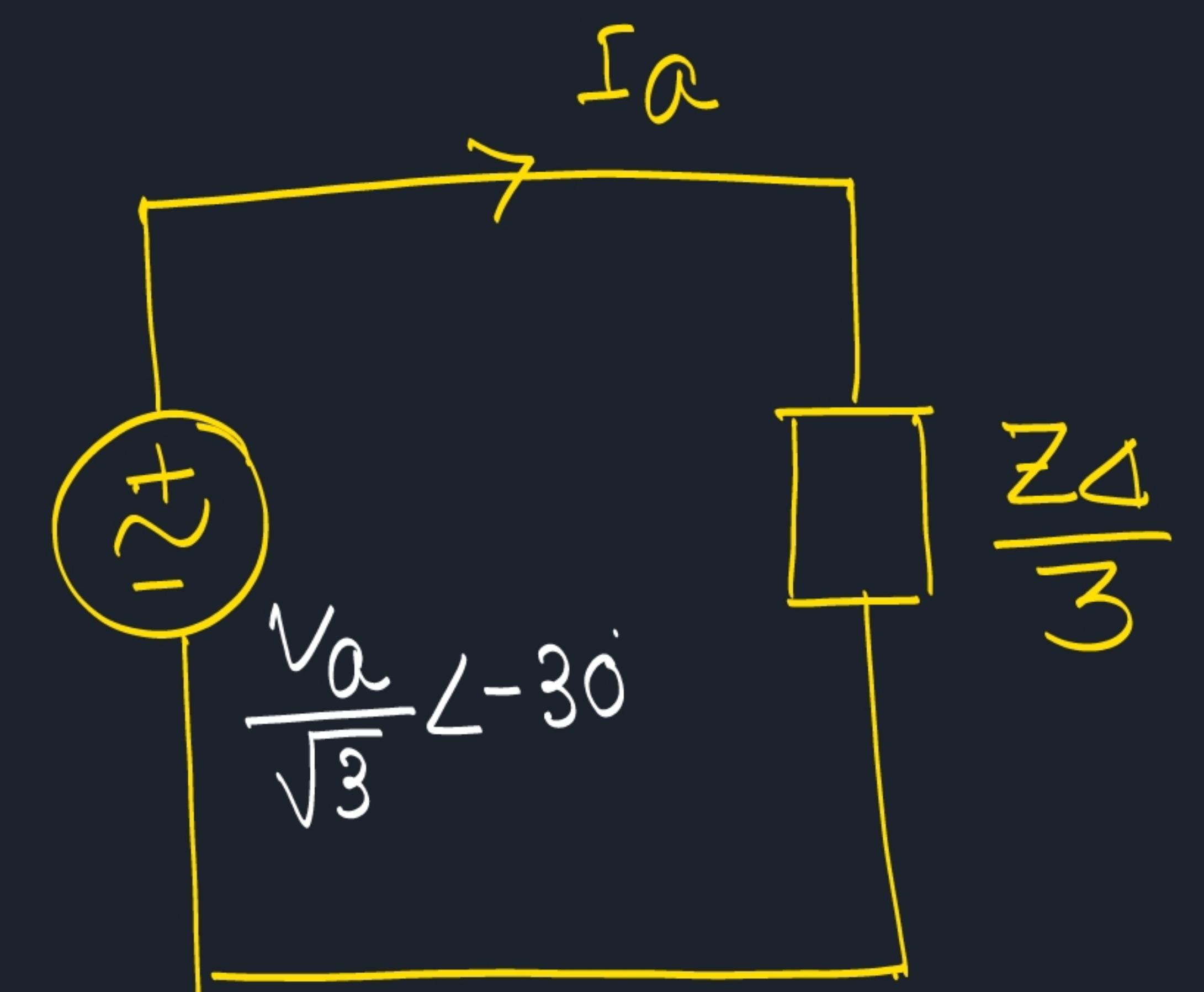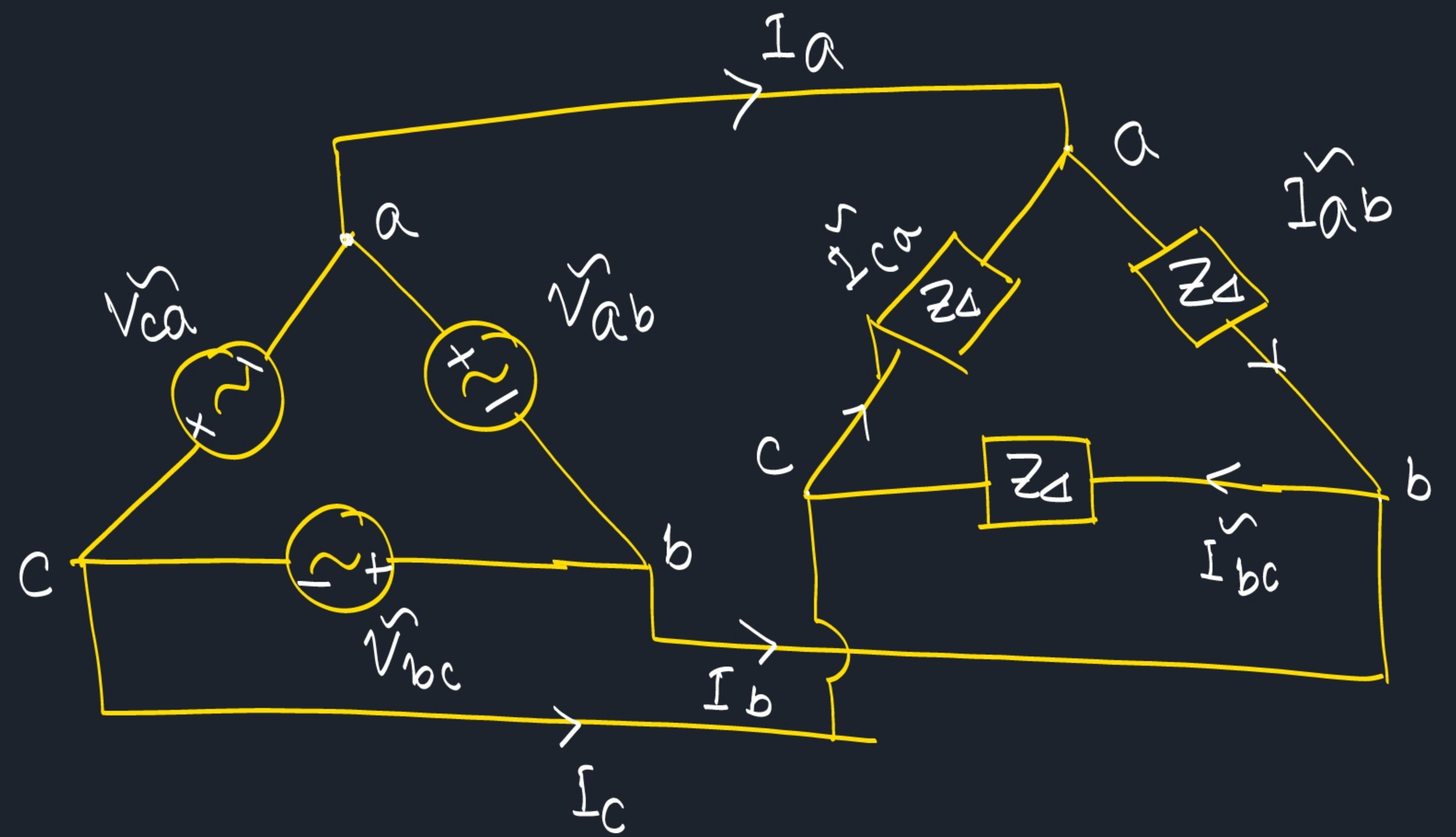


 Problem:-

$$Z_\Delta = 8 + j4$$

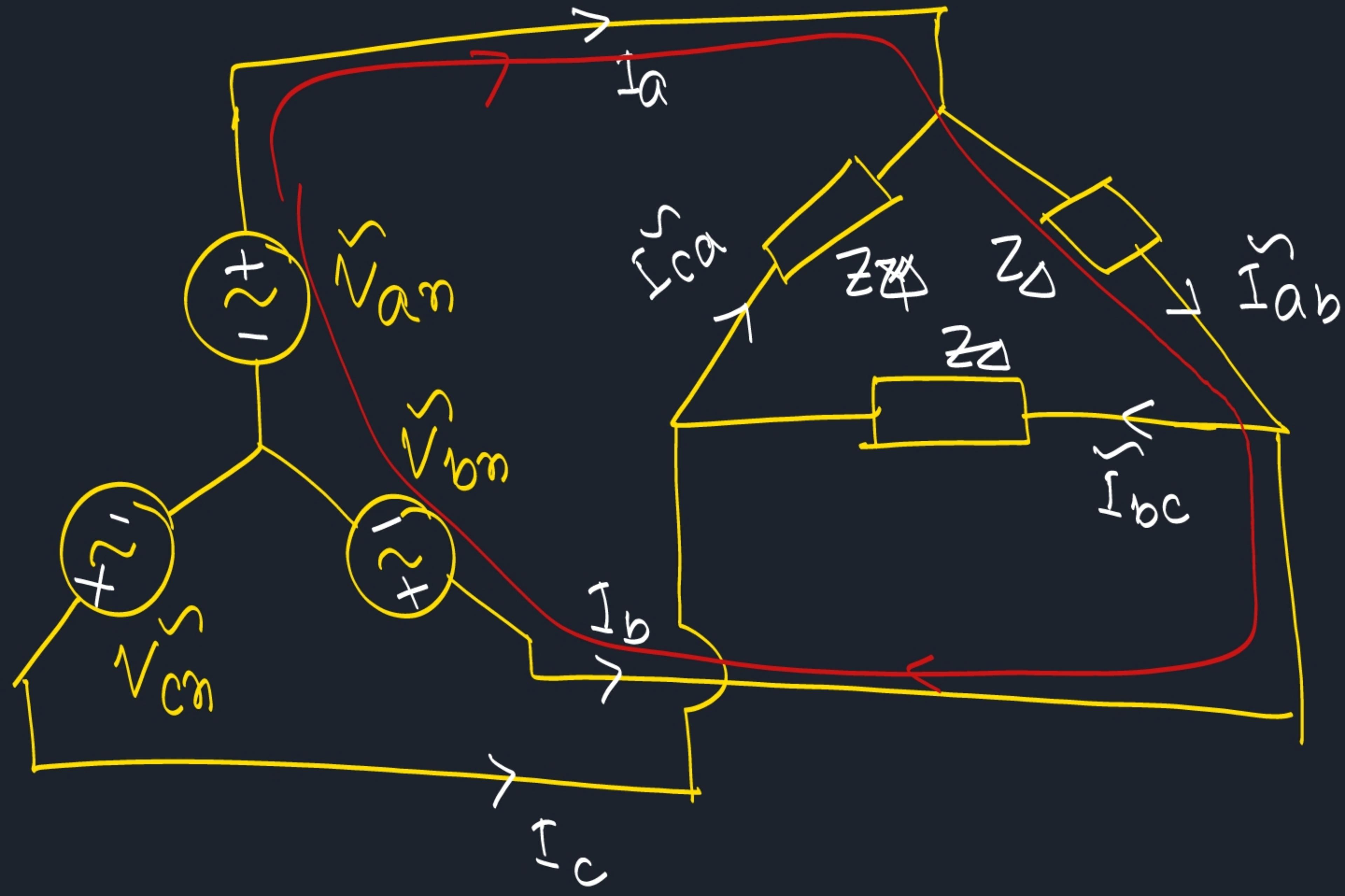

$$\begin{aligned} V_{an} - I_{ab} Z_\Delta - V_{bn} &= 0 \\ I_{ab} &= \frac{V_{an} - V_{bn}}{Z_\Delta} \\ &= \frac{100 \angle 0 - 100 \angle -120}{8 + j4} \\ &= 19.365 \angle 3.4349 \end{aligned}$$

 Problem:-

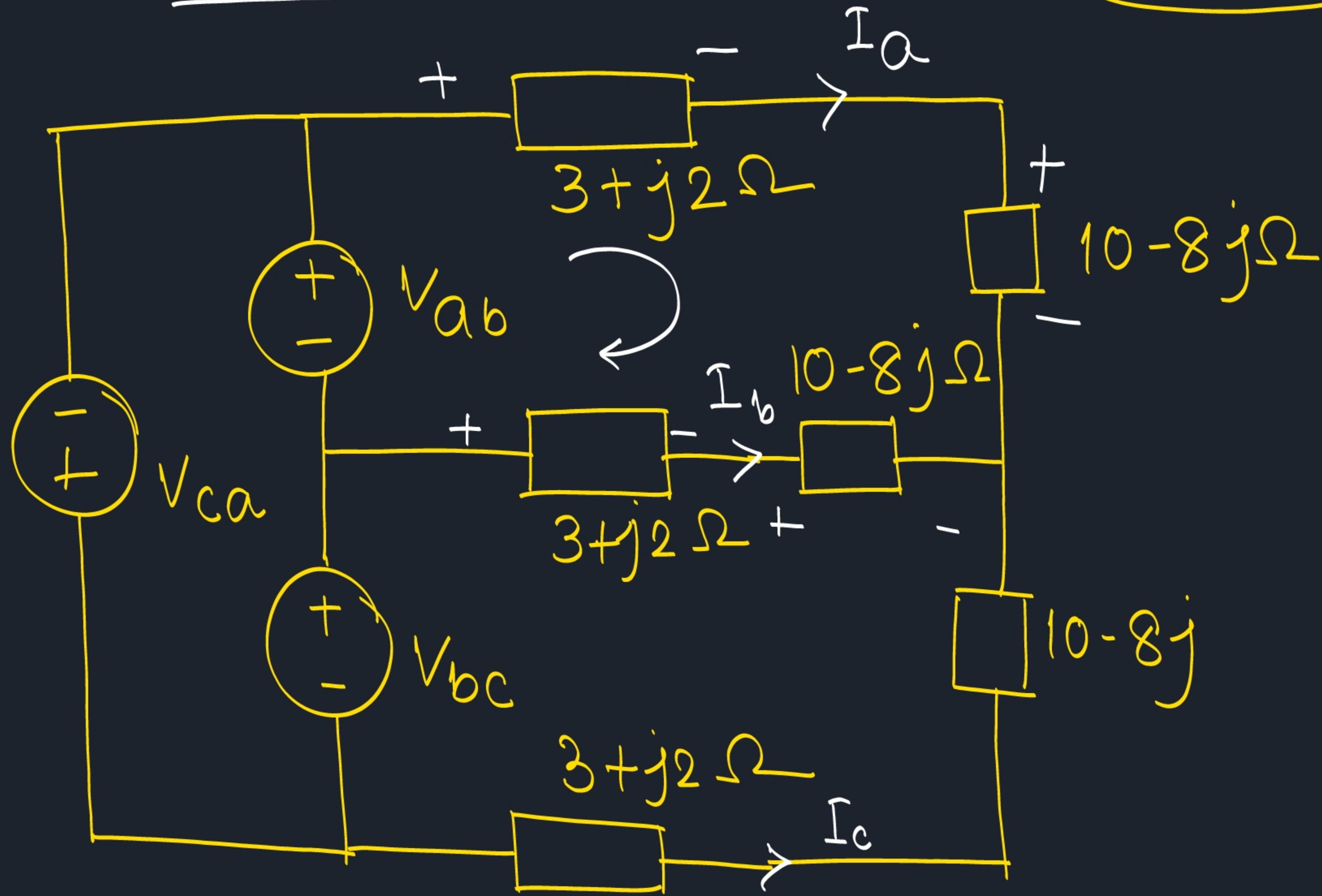

$$V_{ab} = 440 \angle 10^\circ$$

Draw phasor Diagram.

7867

$$V_{ab} = (3 + j2 + 10 - 8j)(I_a - I_b)$$


$$\frac{I_a - I_b}{I_{ab}} = \frac{440 \angle 10^\circ}{13 - j6.0} \quad V_{ab}$$

$$\Rightarrow \sqrt{3} I_p \angle 30^\circ = \frac{440 \angle 10^\circ}{13 - j6}$$

$$\Rightarrow I_p = \frac{440 \angle 10^\circ}{(13 - j6) \times \sqrt{3} \angle 30^\circ} = (17.7425 \angle 4.7751^\circ)$$

$$I_a = (17.7425 \angle 4.7751^\circ) \text{ Amp.}$$

Amp.

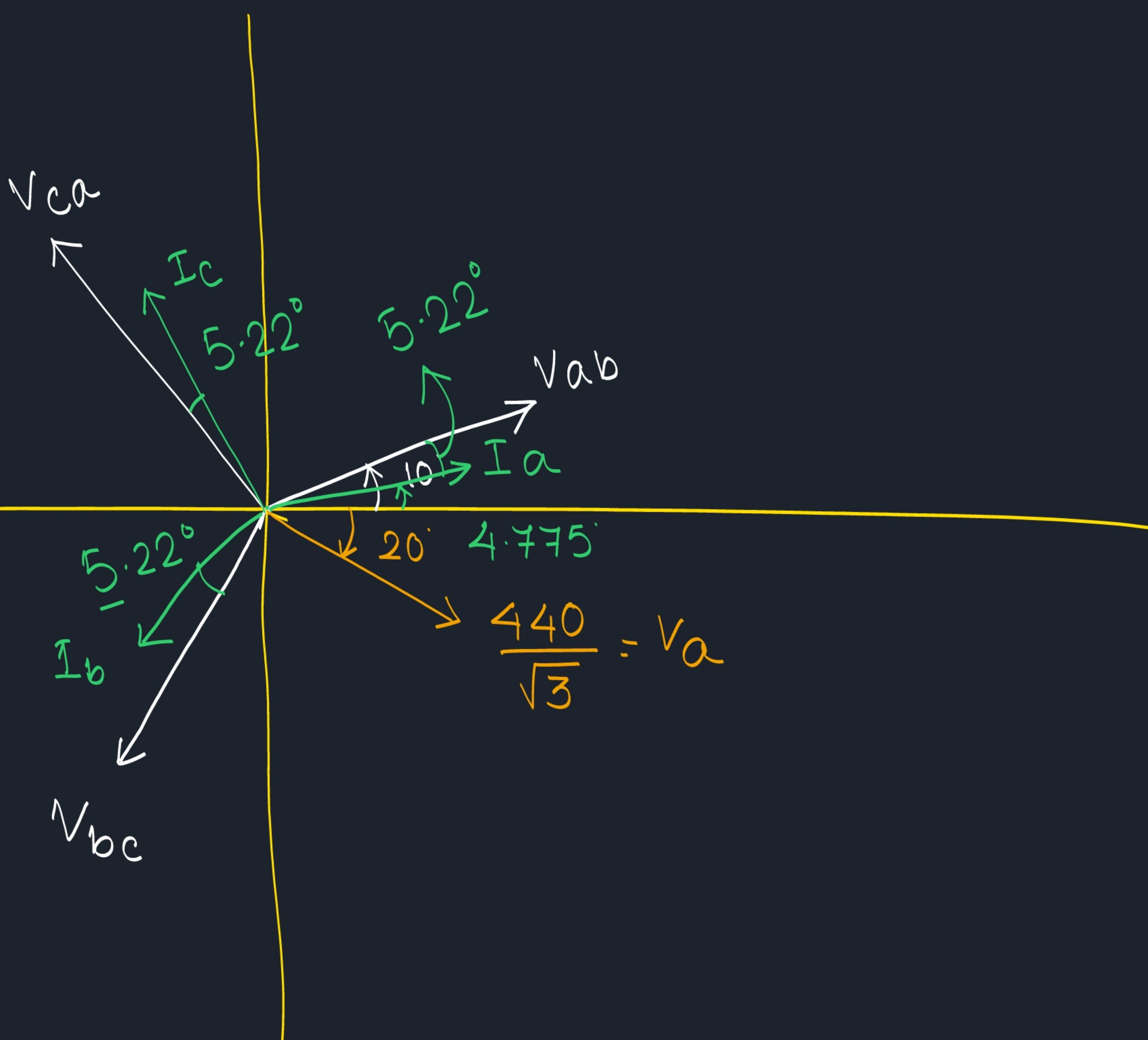

$$\tilde{V}_{ab} = \tilde{V}_a - \tilde{V}_b$$

$$= \sqrt{3} V_p \angle 30^\circ$$


$$I_a = \frac{V_a}{13 - j6} = \frac{V_a}{|Z| \angle \theta}$$

$$\frac{440}{\sqrt{3} \times |Z|} = ?$$

$$= \frac{V_a}{|Z|} \angle 24.775^\circ$$

$$\theta = -24.775$$

Unbalanced 3Φ System:-

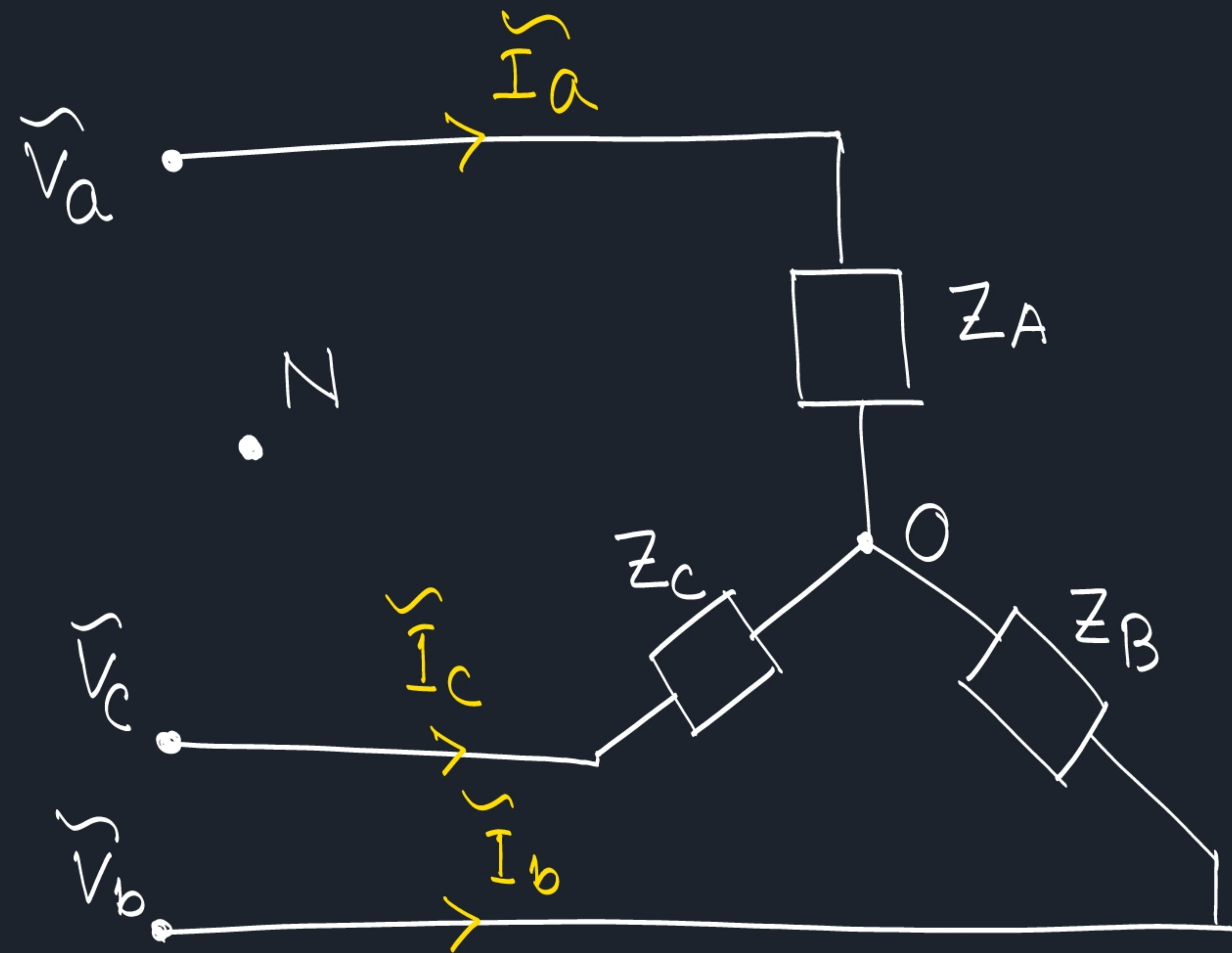

$$\tilde{I}_a + \tilde{I}_b + \tilde{I}_c = 0$$

$$\tilde{I}_a = \frac{\tilde{V}_{AO}}{Z_A}$$

$$\tilde{I}_b = \frac{\tilde{V}_{BO}}{Z_B}$$

$$\tilde{I}_c = \frac{\tilde{V}_{CO}}{Z_C}$$

$$\tilde{V}_{AN} + \tilde{V}_{BN} + \tilde{V}_{CN} = 0$$

$$\tilde{V}_{AO} = \tilde{V}_{AN} - \tilde{V}_{ON} ; \quad \tilde{V}_{BO} = \tilde{V}_{BN} - \tilde{V}_{ON}$$



$$\tilde{V}_{CO} = \tilde{V}_{CN} - \tilde{V}_{ON}$$

$$\frac{\tilde{V}_{AO}}{Z_A} + \frac{\tilde{V}_{BO}}{Z_B} + \frac{\tilde{V}_{CO}}{Z_C} = 0$$

$$\Rightarrow \frac{\tilde{V}_{AN}}{Z_A} + \frac{\tilde{V}_{BN}}{Z_B} + \frac{\tilde{V}_{CN}}{Z_C} = \tilde{V}_{ON} \left(\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C} \right)$$

$$\tilde{V}_{ON} = \frac{\frac{\tilde{V}_{AN}}{Z_A} + \frac{\tilde{V}_{BN}}{Z_B} + \frac{\tilde{V}_{CN}}{Z_C}}{\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C}}$$

 Problem :-

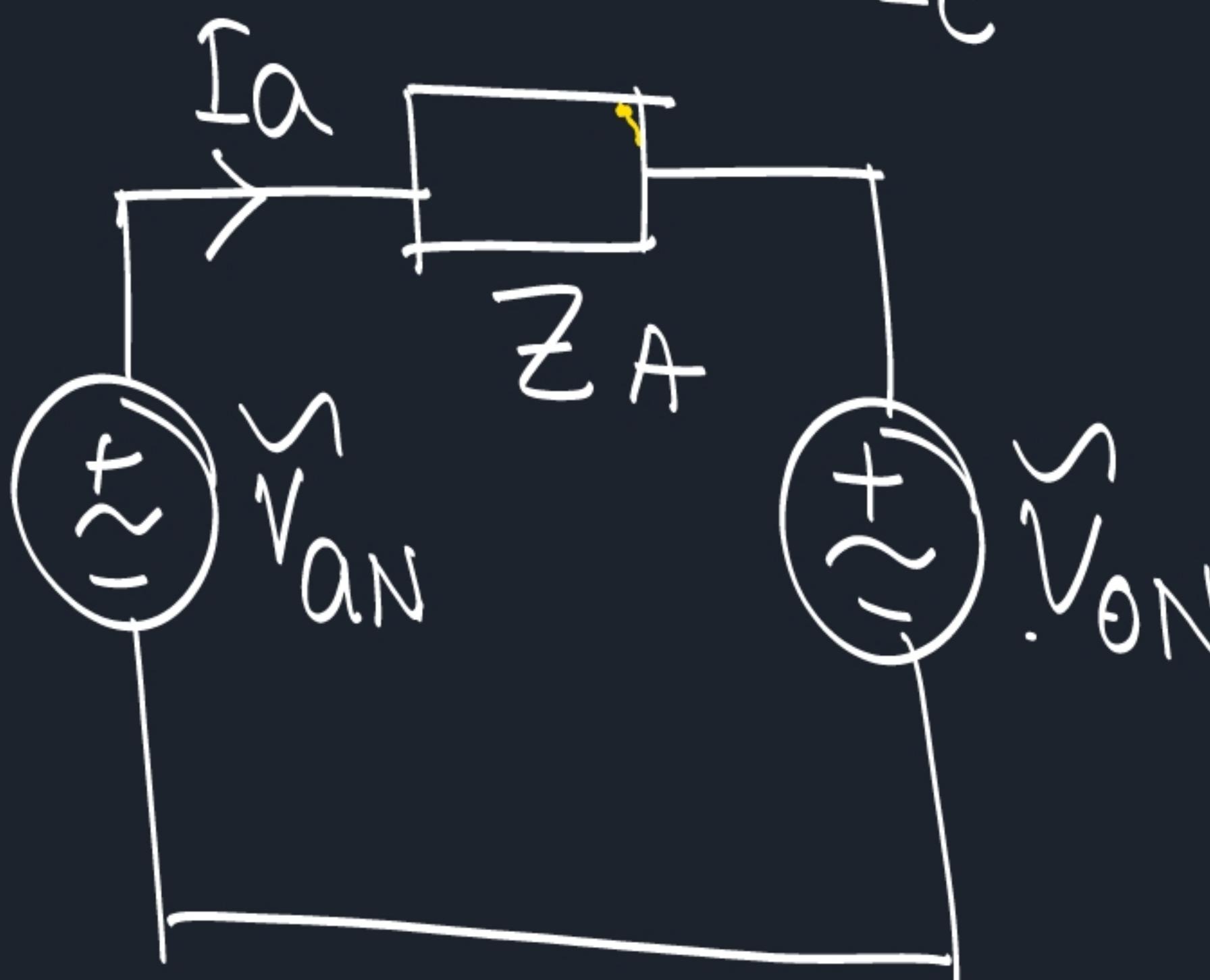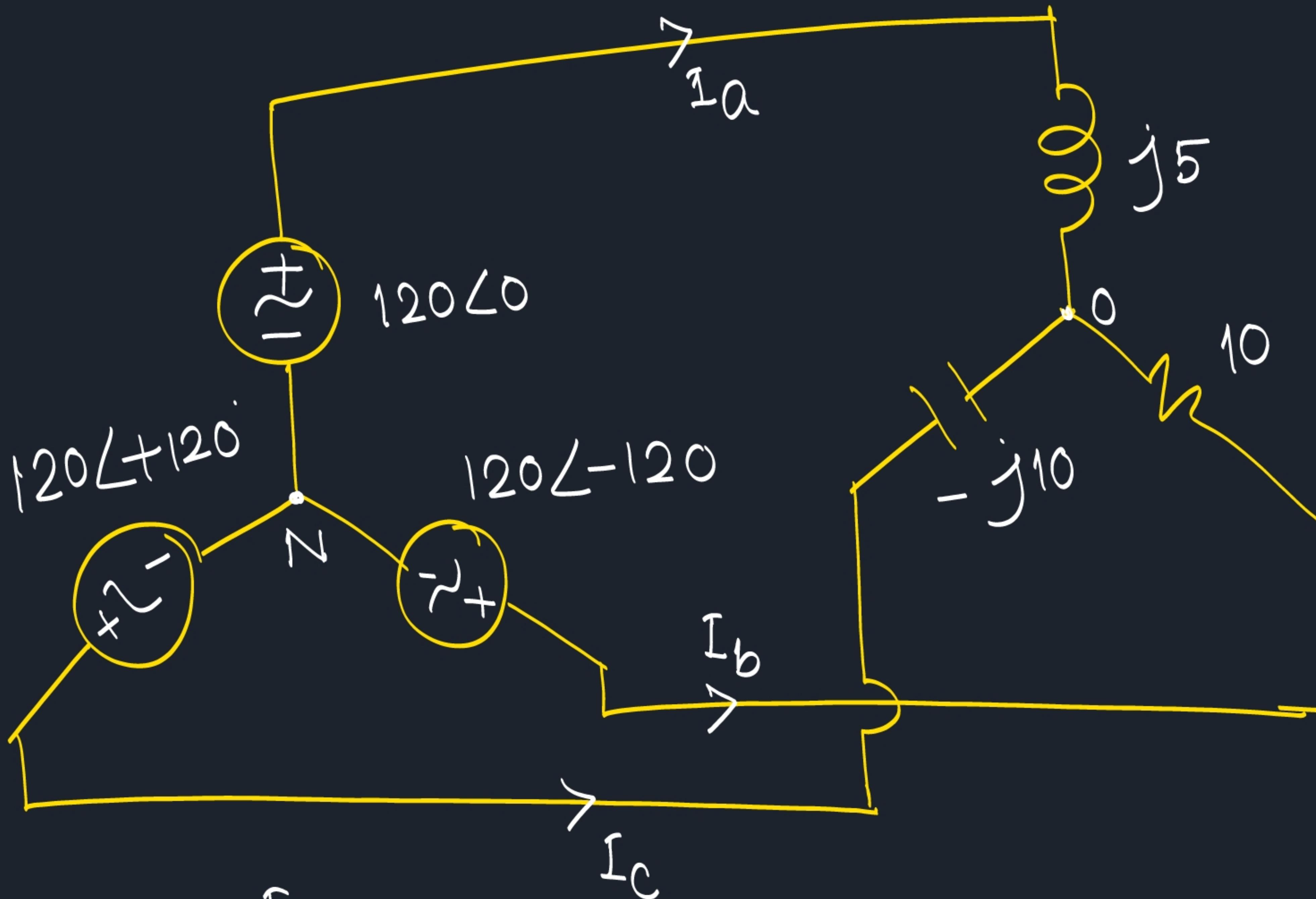

$$\begin{aligned}
 \tilde{V}_{ON} &= \frac{\tilde{V}_{AN} + \frac{\tilde{V}_{BN}}{Z_B} + \frac{\tilde{V}_{CN}}{Z_C}}{\frac{1}{Z_A} + \frac{1}{Z_B} + \frac{1}{Z_C}} \\
 &= 308.2406 \angle -67.088^\circ \text{ V} \\
 I_a &= \frac{\tilde{V}_{AN} - \tilde{V}_{ON}}{Z_A} \\
 &= \frac{120\angle 0 - 308.2406 \angle -67.088}{j5} \\
 &= 56.784 \angle 0.000569^\circ \text{ Amp.}
 \end{aligned}$$

Power in 3φ
Balanced S/S :-

$$v_a(t) = v_{AN}(t) = V_m \cos(\omega t)$$

$$v_b(t) = V_m \cos(\omega t - 120^\circ)$$

$$v_c(t) = V_m \cos(\omega t + 120^\circ)$$

$$i_a(t) = I_m \cos(\omega t - \theta)$$

$$i_b(t) = I_m \cos(\omega t - \theta - 120^\circ)$$

$$i_c(t) = I_m \cos(\omega t - \theta + 120^\circ)$$

$$\begin{aligned} p(t) &= v_{AN}(t) i_a(t) + v_{BN}(t) i_b(t) + v_{CN}(t) i_c(t) \\ &= V_m I_m \cos(\omega t) \cos(\omega t - \theta) + V_m I_m \cos(\omega t - 120^\circ) \\ &\quad \cos(\omega t - \theta - 120^\circ) + V_m I_m \cos(\omega t + 120^\circ) \\ &\quad \cos(\omega t + \theta + 120^\circ) \end{aligned}$$

$$\begin{aligned} &\frac{V_m I_m}{2} \left\{ \cos \omega t \cos(\omega t - \theta) \right\} \\ &= \frac{V_m I_m}{2} \left[\cos \theta + \cos(2\omega t - \theta) \right] \end{aligned}$$


$$p(t) = \frac{3}{2} V_m I_m \cos \theta$$

$$P_{3\phi} = 3 V_{rms} I_{rms} \cos \theta$$

6911

$$Q_{3\phi} = 3 V_{\text{rms}} I_{\text{rms}} \sin \theta$$
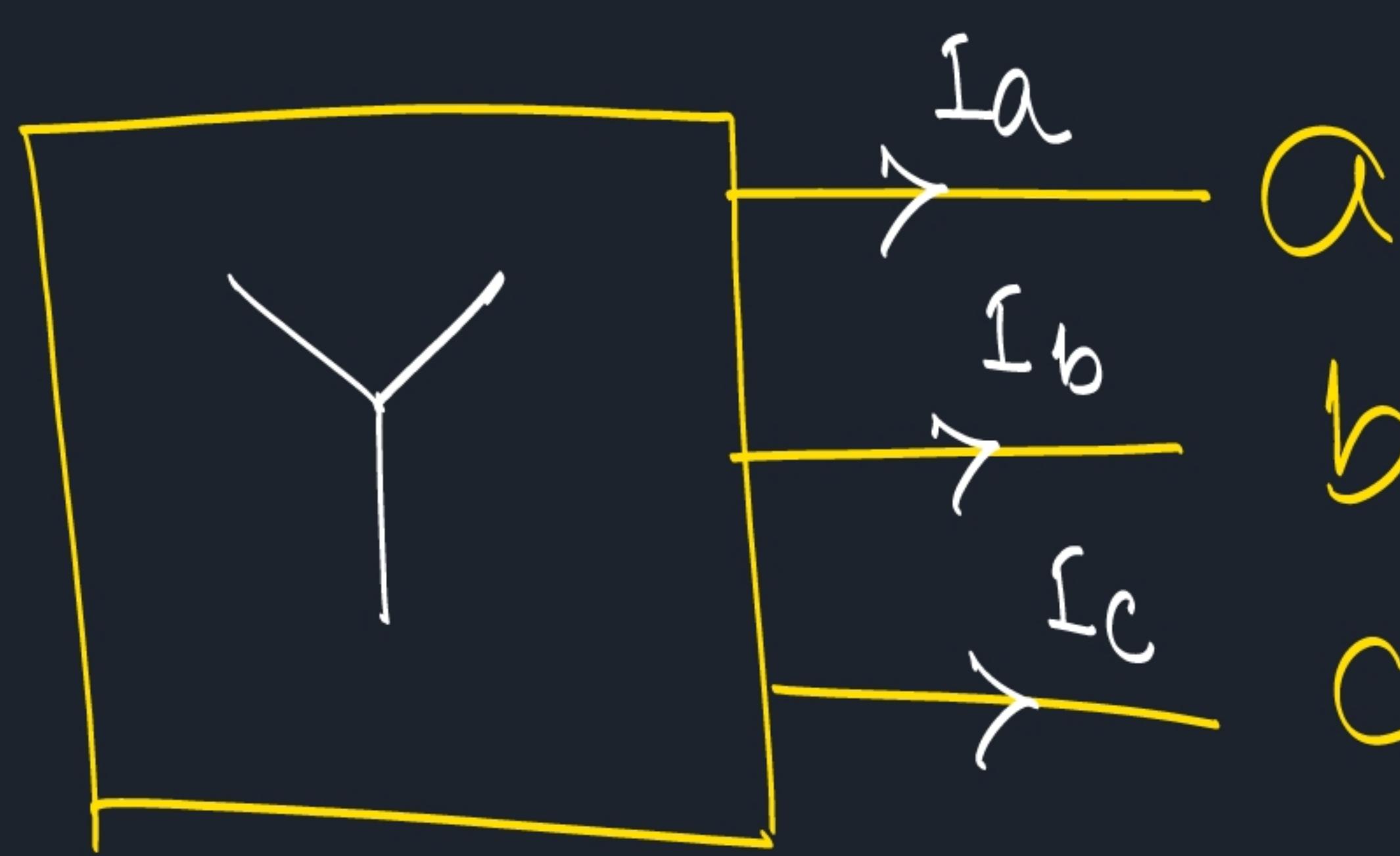
$$P_{3\phi} = 3 V_{\text{rms}}^{\text{Ph}} I_{\text{rms}}^{\text{Ph}} \cos \theta$$



$$V_{\text{rms}}^{\text{L-L}} = \sqrt{3} V_{\text{rms}}^{\text{Ph}}$$

$$I_{\text{rms}}^{\text{L-L}} = I_{\text{rms}}^{\text{Ph}}$$

$$P_{3\phi}^Y = \sqrt{3} V_{\text{rms}}^{\text{L-L}} I_{\text{rms}}^{\text{L-L}} \cos \theta$$

$$P_{3\phi} = \sqrt{3} V_{\text{rms}}^{\text{L-L}} I_{\text{rms}}^{\text{L-L}} \cos \theta$$

$$Q_{3\phi} = \sqrt{3} V_{\text{rms}}^{\text{L-L}} I_{\text{rms}}^{\text{L-L}} \sin \theta$$



$$V_{\text{rms}}^{\text{L-L}} = V_{\text{rms}}^{\text{Ph}}$$

$$I_{\text{rms}}^{\text{L-L}} = \sqrt{3} I_{\text{rms}}^{\text{Ph}}$$

$$\cancel{P_{3\phi}^{\triangle} = \sqrt{3} V_{\text{rms}}^{\text{L-L}} I_{\text{rms}}^{\text{L-L}} \cos \theta}$$

$$S_{3\phi} = P_{3\phi} + j Q_{3\phi}$$


$$= \sqrt{3} V_{rms}^{L-L} I_{rms}^{L-L} (\cos\theta + j \sin\theta).$$

$$S_{1\phi} = \tilde{V} \tilde{I}^*$$

$$S_{3\phi} = 3 \tilde{V}_{ph} \tilde{I}_{ph}^*$$

$$= \sqrt{3} \tilde{V}_{L-L} \tilde{I}_{L-L}^*$$

3φ 3 wire balanced.

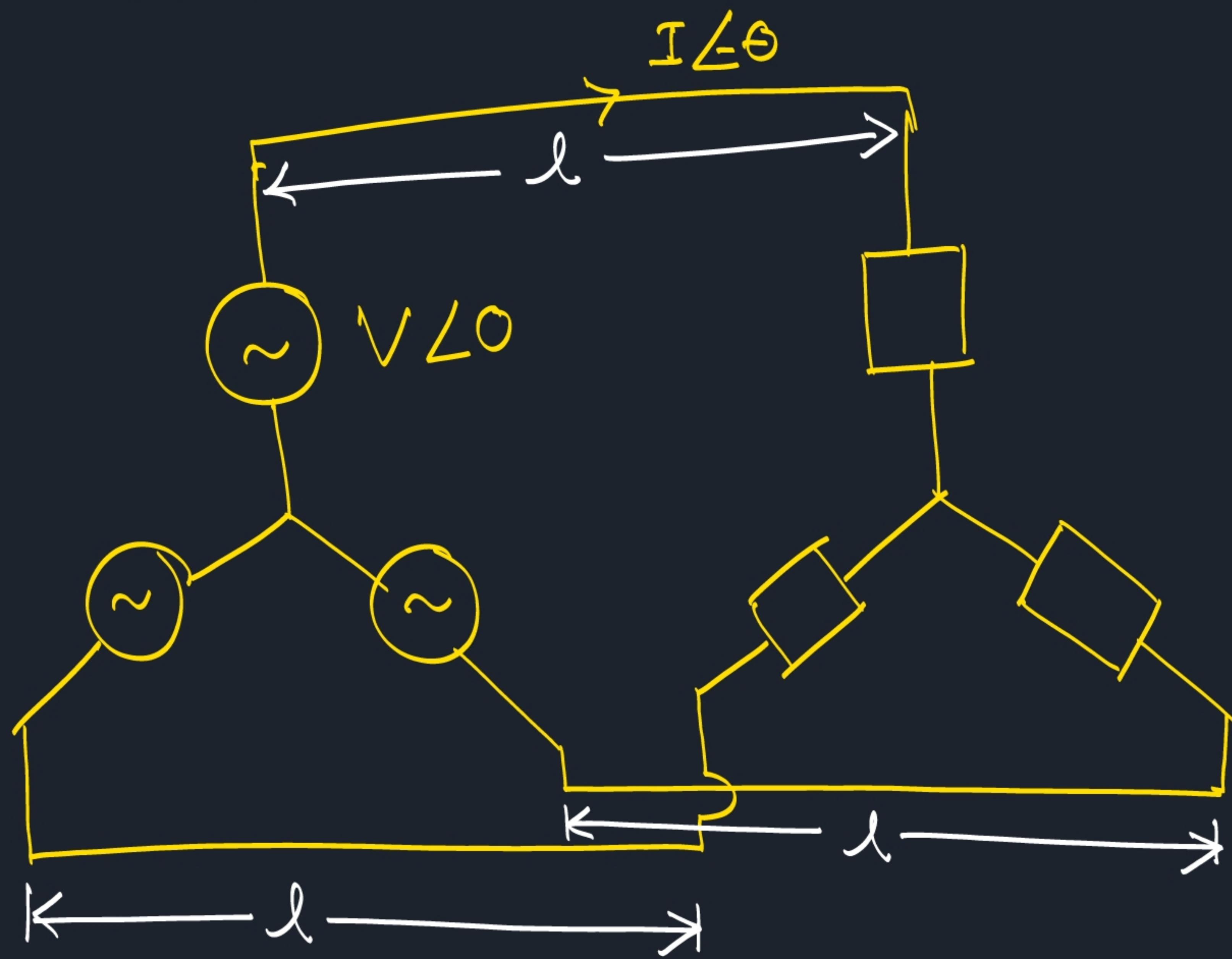

$$P = 3V^2 \cos\theta$$

$$W_{3\phi} = 3I^2 R_I$$

$$R_F = \frac{f l}{A_I}$$

$$I = \frac{P}{3V \cos\theta}$$

$$W_{3\phi} = 3 \cdot \left(\frac{P}{3V \cos\theta} \right)^2 \cdot \frac{f l}{A_I}$$


$$A_I = \frac{P f l}{3V^2 \cos^2\theta W_{3\phi}}$$

$$(Vol)_{3\phi} = 3A_I l$$

$$= 3 \cdot \frac{P^2 f l^2}{3V^2 \cos^2\theta W_{3\phi}}$$

$$\boxed{(Vol)_{3\phi} = \frac{P^2 f l^2}{3V^2 \cos^2\theta W_{3\phi}}}$$

1Φ S/S :-

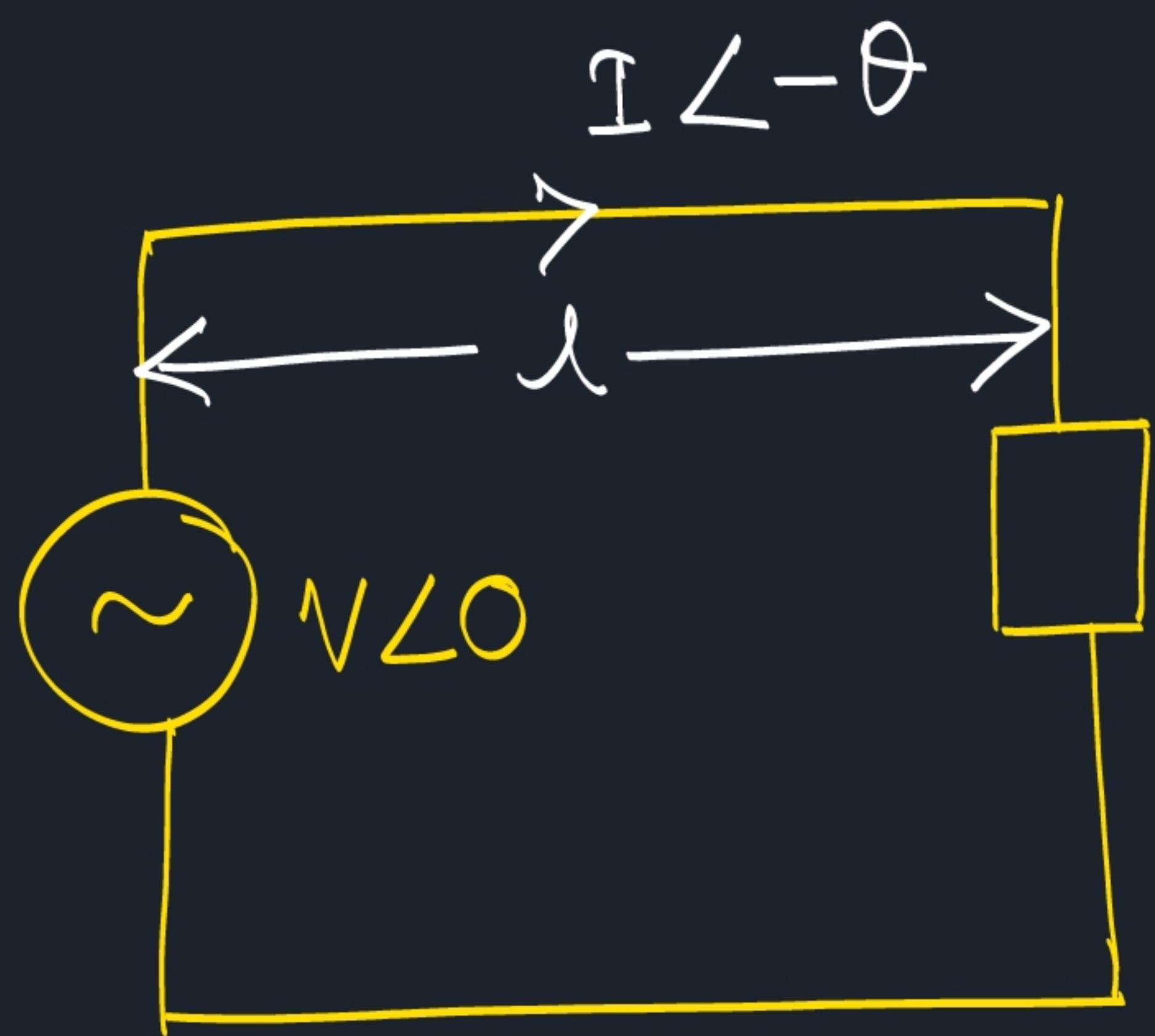

$$P = V I \cos \theta$$

$$I = \frac{P}{V \cos \theta}$$

$$W_{1\phi} = I^2 R_2$$
$$= \frac{P^2}{V^2 \cos^2 \theta} \cdot \frac{f \cdot (2\ell)}{A_2}$$

$$A_2 = \frac{2 P^2 \ell f}{V^2 \cos^2 \theta W_{1\phi}}$$

$$(Vol)_{1\phi} = 2\ell A_2$$
$$= \frac{4 P^2 \ell^2 f}{V^2 \cos^2 \theta W_{1\phi}}$$

$$W_{1\phi} = W_{3\phi}$$

$$\frac{(Vol)_{1\phi}}{4} = (Vol)_{3\phi}$$

$$(Vol)_{1\phi} > (Vol)_{3\phi}$$