

ELECTRICAL DEVICES & CIRCUITS

COURSE CODE: NEEE 101

VENUE: NLHC-G3

TIME: 09.00 AM-09.50 AM

COURSE INSTRUCTOR:

PROF. SOUMYABRATA BARIK

CHAMBER:


131-D; DEPARTMENT OF ELECTRICAL ENGINEERING

EMAIL ID:

soumyabrata@iitism.ac.in

BEHAVIOR OF L IN THE CIRCUIT

- ❖ In an inductor the current can not change instantaneously.
- ❖ Let us consider the following circuits. Here, the initial current flowing through the inductor is I_0 before the switch is on.
- ❖ If $I_0 = 0$, then just after switching i.e., @ $t = 0^+$ the inductor will behave like an open circuit.
- ❖ If $I_0 \neq 0$, then just after switching i.e., @ $t = 0^+$ the inductor will behave like a current source of magnitude I_0 .
- ❖ At @ $t = \infty$, the inductor will behave like a short circuit as $v = L \frac{di}{dt} = 0$.

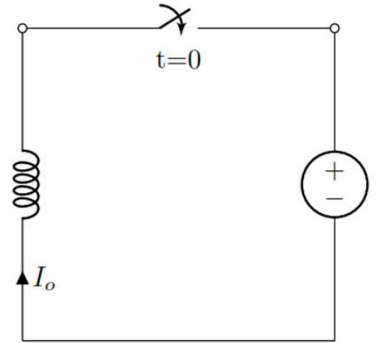

SOURCE FREE RESPONSE (R-L CIRCUIT)



- ❖ If the current flowing through the series path is $i(t)$ and the initial current of the inductor is $i_L(t = 0^+) = I_0$, then the differential equation will be

$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = 0$$

- ❖ The expression of current is


$$i(t) = I_0 e^{-\frac{R}{L}t}$$

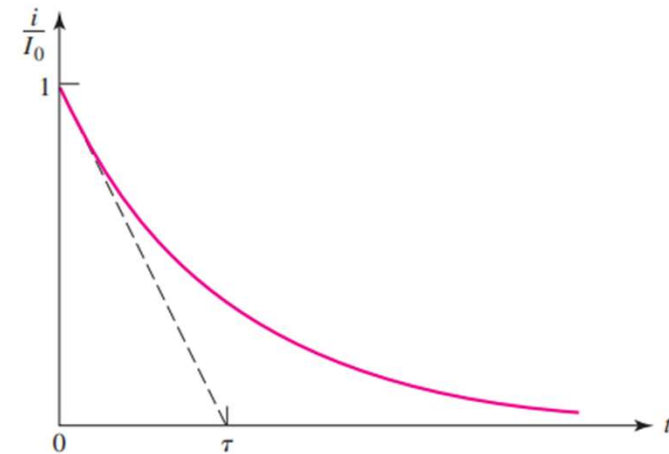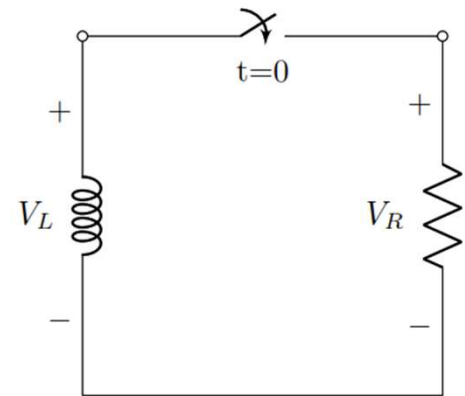- ❖ The ratio $\frac{L}{R}$ is also known as time constant (τ) of the circuit. This is the time required by the circuit for $\frac{i}{I_0}$ drop to zero with a constant decreasing rate of $\frac{R}{L}$.



BEHAVIOR OF C IN THE CIRCUIT

- ❖ In a capacitor the voltage can not change instantaneously.
- ❖ Let us consider the following circuits. Here, the initial voltage of the capacitor is V_0 before the switch is on.
- ❖ If $V_0 = 0$, then just after switching i.e., @ $t = 0^+$ the capacitor will behave like a short circuit.
- ❖ If $V_0 \neq 0$, then just after switching i.e., @ $t = 0^+$ the capacitor will behave like a voltage source of magnitude V_0 .
- ❖ At @ $t = \infty$, the capacitor will behave like an open circuit as $i = C \frac{dv}{dt} = 0$.

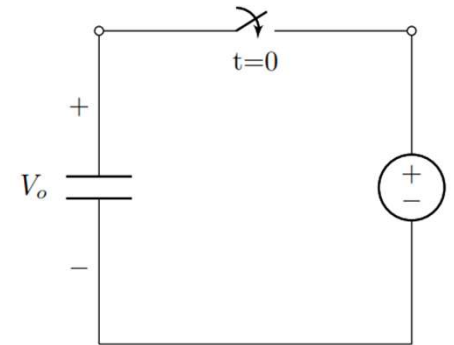

SOURCE FREE RESPONSE (R-C CIRCUIT)



- ❖ If the voltage across the capacitor is $v(t)$ and the initial voltage of the capacitor is $v_c(t = 0^+) = V_0$, then the differential equation will be

$$\frac{dv(t)}{dt} + \frac{1}{RC}v(t) = 0$$

- ❖ The expression of current is

$$v(t) = V_0 e^{-\frac{1}{RC}t}$$

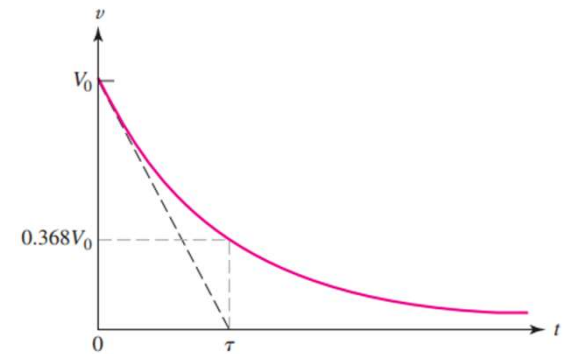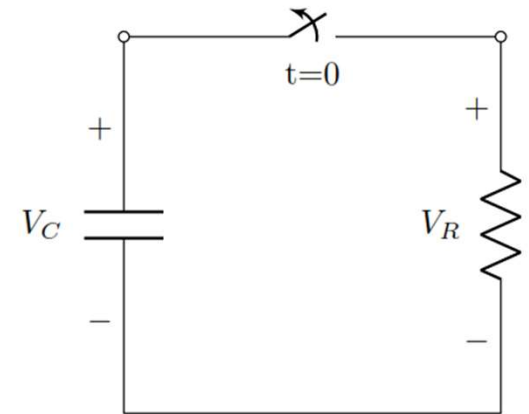- ❖ The product RC is also known as time constant (τ) of the circuit. This is the time required by the circuit for $\frac{v}{V_0}$ drop to zero with a constant decreasing rate of $\frac{1}{RC}$.



FORCED RESPONSE

- ❖ Let us consider a general first order differential equation as below

$$\frac{di}{dt} + Pi = Q$$

- ❖ The integrating factor as $e^{\int P dt} = e^{Pt}$. The solution of that differential equation is

$$i(t) = Ae^{-Pt} + e^{-P} \int Qe^{Pt} dt$$

- ❖ Here the first term is known as the natural response (Complementary Response), whereas the second term is the forced response (Particular Integral).

RESPONSE OF CIRCUITS WITH L, C

- ❖ Analysis of a circuit with inductor or capacitor depends on the solution of integrodifferential equations.
- ❖ Solution of the integrodifferential equation provides the response of the circuit.
- ❖ Source free response is also known as the **natural response/transient response**.
- ❖ An inductor or a capacitor can not store the energy forever.
- ❖ The energy dissipated into heat energy due to the presence of resistance intrinsically associated with the inductor and capacitor.
- ❖ Mathematically, natural response is also known as **complementary function**.
- ❖ When an independent source is applied to a circuit, part of the response will resemble the nature of the particular source.
- ❖ This part of response is known as **forced response/particular solutions**.
- ❖ Total response=Natural response+ Forced Response=Complementary Solution+ Particular Solution

FORCED RESPONSE (R-L CIRCUIT)



- ❖ If the current flowing through the series path is $i(t)$ and the initial current of the inductor is $i_L(t = 0^+) = 0$, then the differential equation will be

$$\frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{V_0}{L}$$

- ❖ The expression of current is

$$i(t) = \frac{V_0}{R} (1 - e^{-\frac{R}{L}t})$$

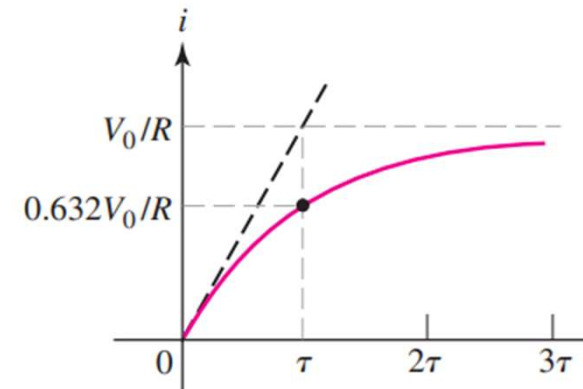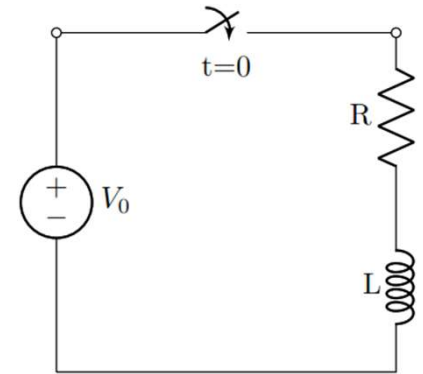- ❖ The ratio $\frac{L}{R}$ is also known as time constant (τ) of the circuit. This is the time required by the circuit for $\frac{i}{I_0}$ drop to zero with a constant decreasing rate of $\frac{R}{L}$.



FORCED RESPONSE (R-C CIRCUIT)


- ❖ If the voltage across the capacitor is $v(t)$ and the initial voltage of the capacitor is $v(t = 0^+) = 0$, then the differential equation will be

$$Ri + \frac{1}{C} \int idt = V_s$$

- ❖ The expression of current is

$$v(t) = V_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

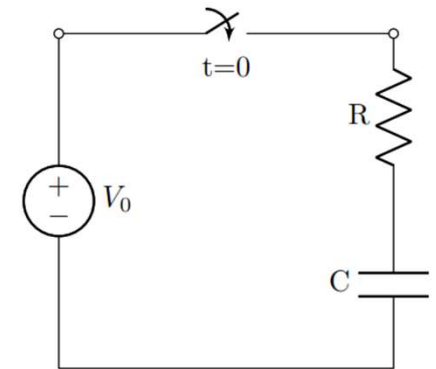- ❖ The product RC is also known as time constant (τ) of the circuit. This is the time required by the circuit for $\frac{v}{V_0}$ drop to zero with a constant decreasing rate of $\frac{1}{RC}$.




SOURCE FREE RESPONSE (R-L CIRCUIT)

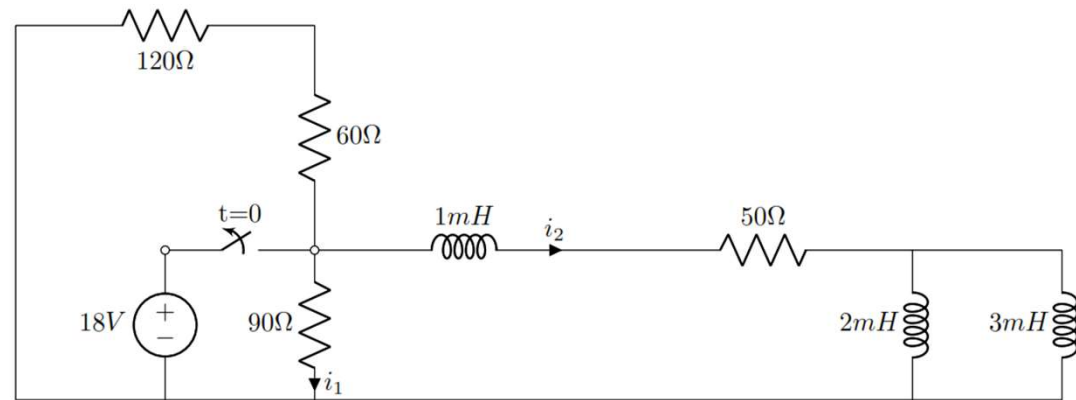Problem-1:

The given circuit was at steady state before the switch is turned off. Determine $i_1(0^-)$, $i_2(0^-)$.

After the switch is off, determine the expression of $i_1(t)$, $i_2(t)$ for $t > 0$.



Ans:


$$i_1(0^-) = 200 \text{ mA}$$

$$i_2(0^-) = 360 \text{ mA}$$

$$i_1(t) = -240e^{-50,000t} \text{ mA}$$

$$i_2(t) = 360e^{-50,000t} \text{ mA}$$

CHARACTERISTICS OF SINUSOIDS

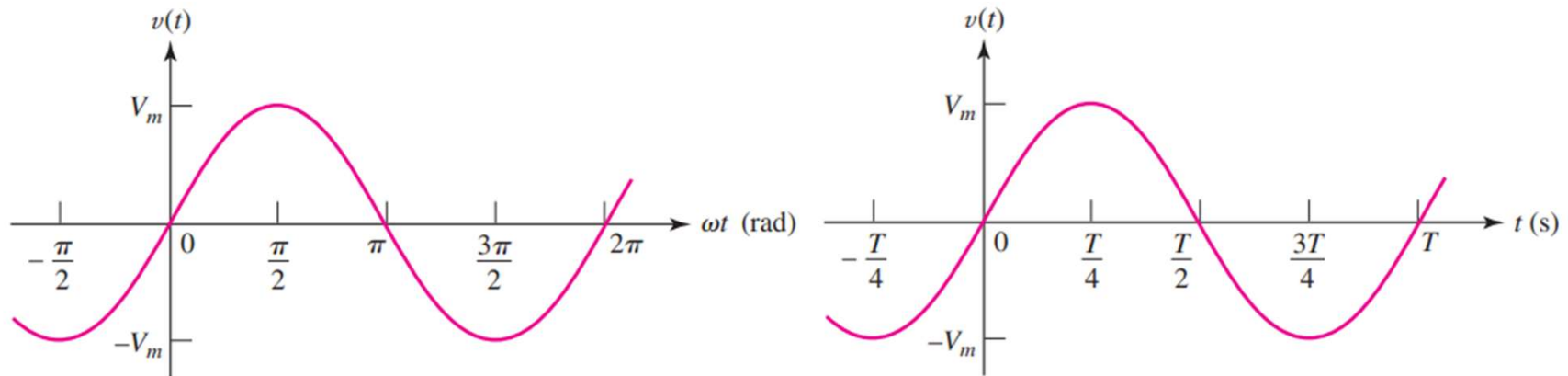

- ❖ A sinusoidally varying voltage function can be represented by $v(t) = V_m \sin(\omega t)$
- ❖ The function repeats itself in every 2π radians. Therefore, period is 2π radians.
- ❖ Frequency $f = 1/T$
- ❖ We know $\omega T = 2\pi$

CONCEPTS OF LAGGING & LEADING

- ❖ More general form of sinusoids is $v(t) = V_m \sin(\omega t + \theta)$
- ❖ Here θ is the phase angle measured in radian. However, for representation purpose sometimes we use to express θ in degree.
- ❖ At $t = 0$, $v(t = 0) = V_m \sin \theta$
- ❖ Therefore, $V_m \sin(\omega t + \theta)$ sinusoid leads $V_m \sin(\omega t)$ sinusoid.

