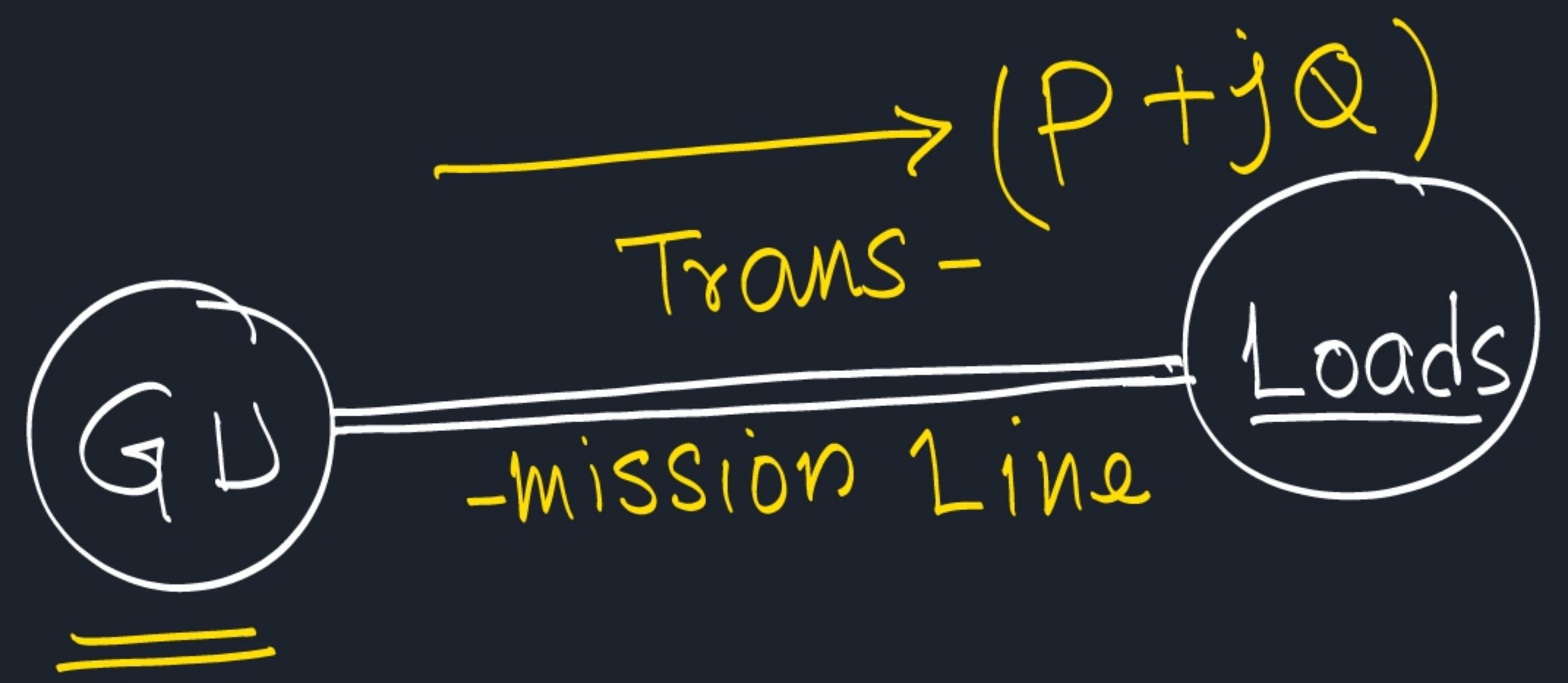


Transformer :-




$$P_{3\phi} = 3 V_{ph} I_{ph} \cos \theta$$


$$I_{ph} = \frac{P_{3\phi}}{3 V_{ph} \cos \theta}$$

$$\begin{aligned} P_{loss} &= 3 (I_{ph})^2 \cdot R_{ph} \\ &= 3 \cdot \frac{P_{3\phi}^2}{9 V_{ph}^2 \cos^2 \theta} \cdot R_{ph} \end{aligned}$$

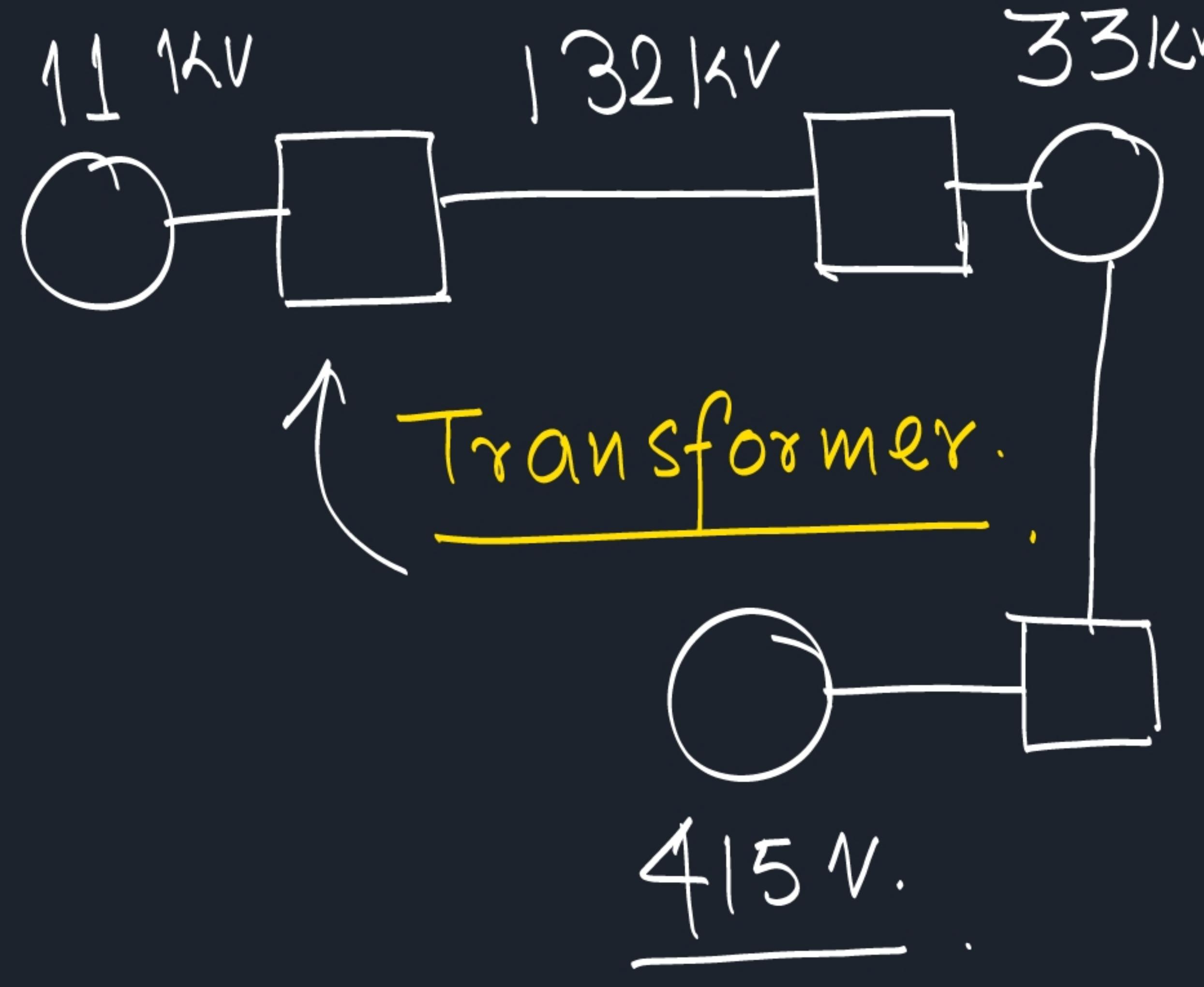$P_{loss} \propto \frac{1}{V_{ph}^2}$ (if $P_{3\phi}, \cos \theta$ Constant)




1. Step Up ↗
2. Step Down ↘

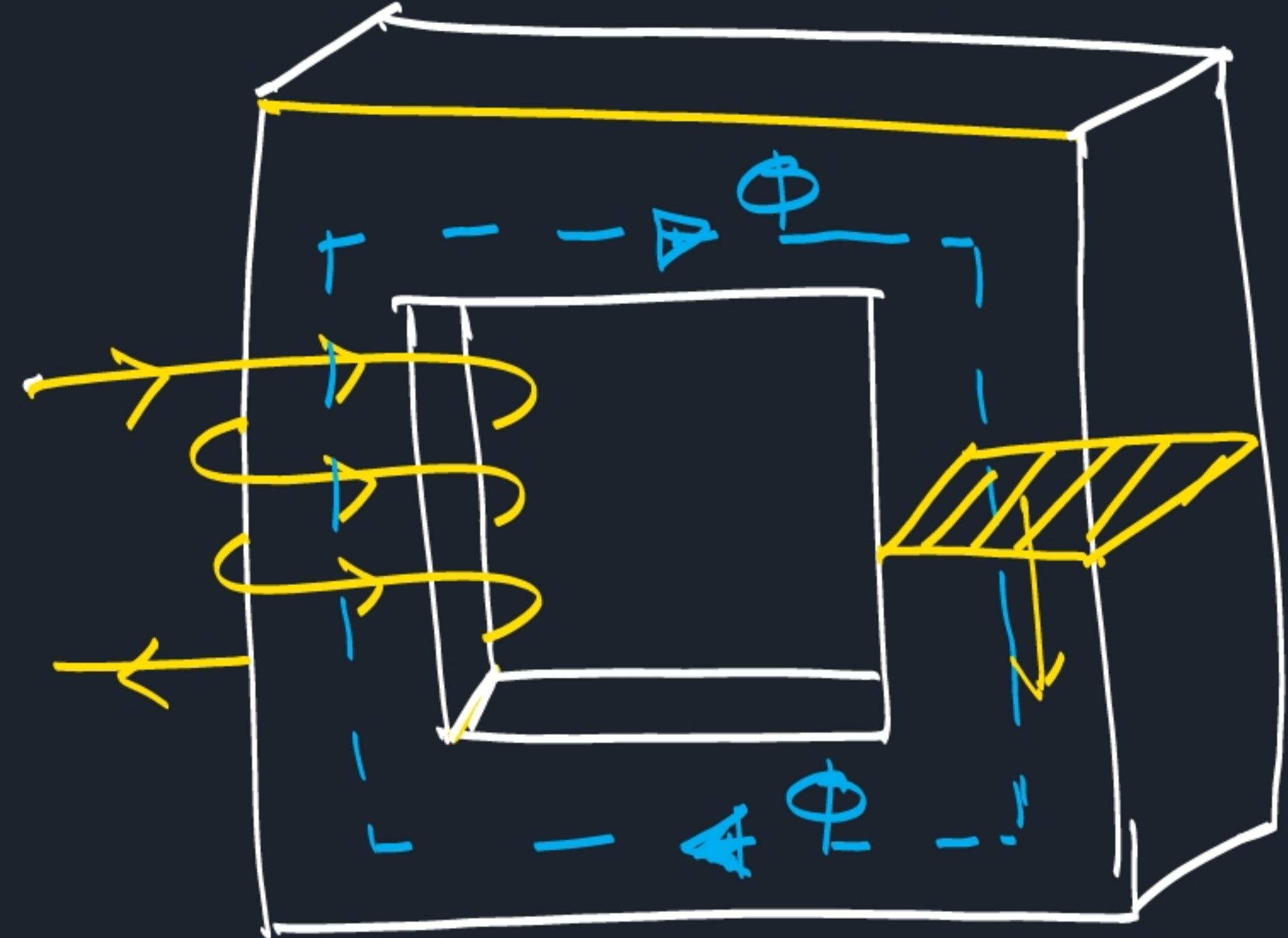

$$\Phi = \vec{B} \cdot \vec{A} = BA \cos \theta$$

$$\boxed{\Phi = BA} \quad \boxed{B = \mu H}$$
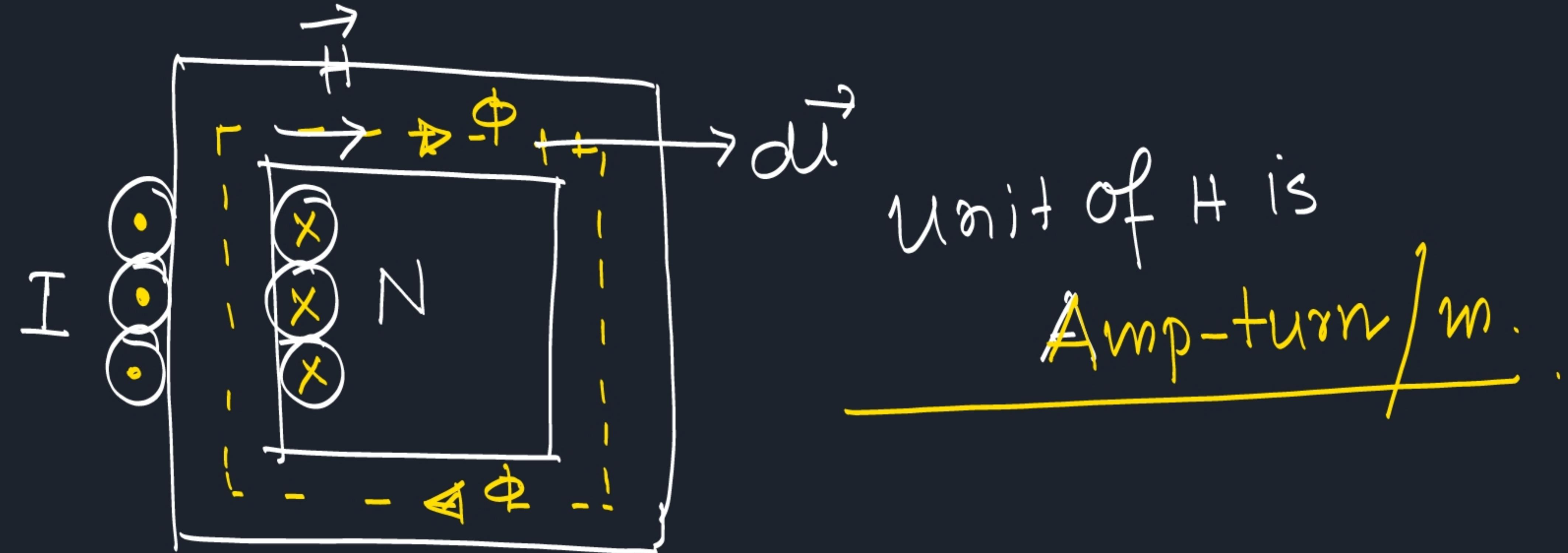
$$\boxed{\mu = \mu_0 \mu_r} \quad 4\pi \times 10^{-7}$$



Ampere's Circuital Law.

$$\oint \vec{H} \cdot d\vec{\mu} = NI$$


$$H \cdot l = NI$$

$$\Rightarrow H = \frac{NI}{l}$$

$$\Rightarrow B = \frac{NI}{l/\mu}$$

$$\boxed{\Phi = \frac{NI}{R}}$$

$$\boxed{i = \frac{V}{R}}$$

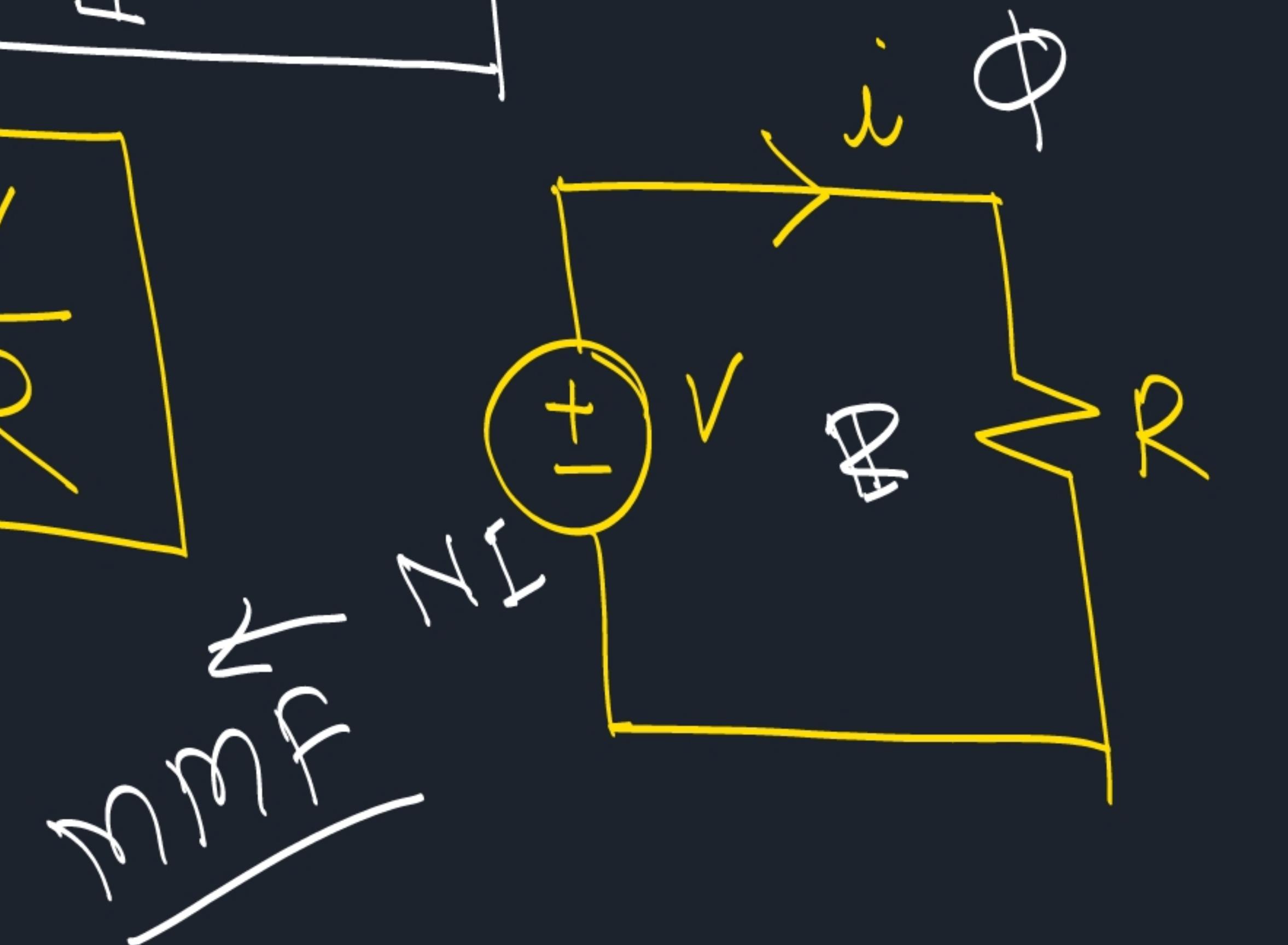

$$\boxed{R = \frac{l}{A \mu_0 \mu_r}}$$


$$\Phi = BA = \frac{NI}{R}$$

$$\frac{\lambda}{\mu A}$$

Reluctance

R

Φ

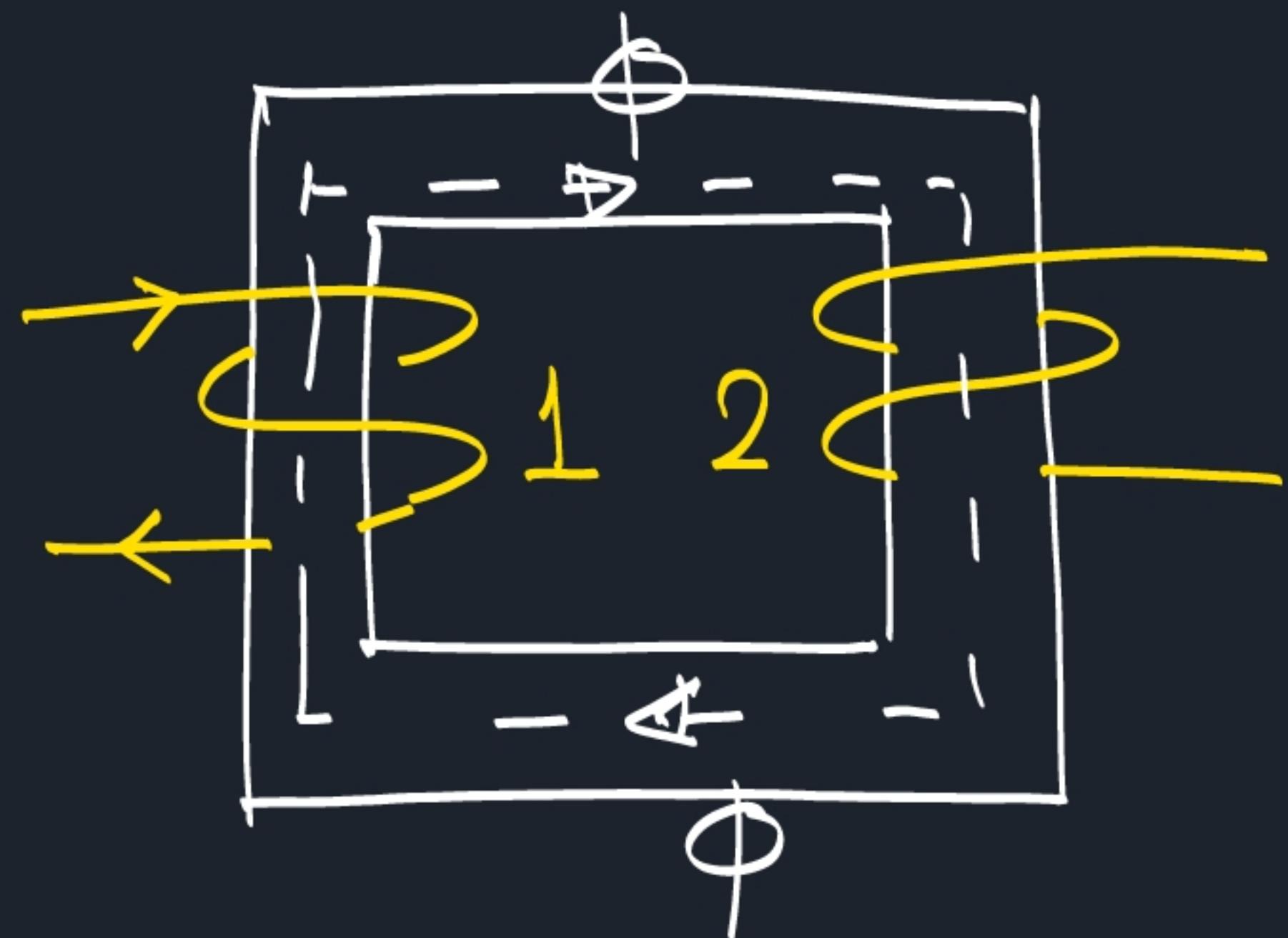

$$\ell_1(t) = -N_1 \frac{d\phi}{dt}$$

$$\frac{\ell_1}{N_1} = - \frac{d\phi}{dt}$$

$$\frac{\ell_1}{N_1} = \frac{\ell_2}{N_2}$$

$$\boxed{\frac{\ell_1}{\ell_2} = \frac{N_1}{N_2}}$$

$$\ell_2(t) = -N_2 \frac{d\phi}{dt}$$


$$\frac{\ell_2}{N_2} = - \frac{d\phi}{dt}$$

$$N_1 < N_2$$

$\ell_1 < \ell_2 \Rightarrow$ Step up T/F.

$$N_1 > N_2$$

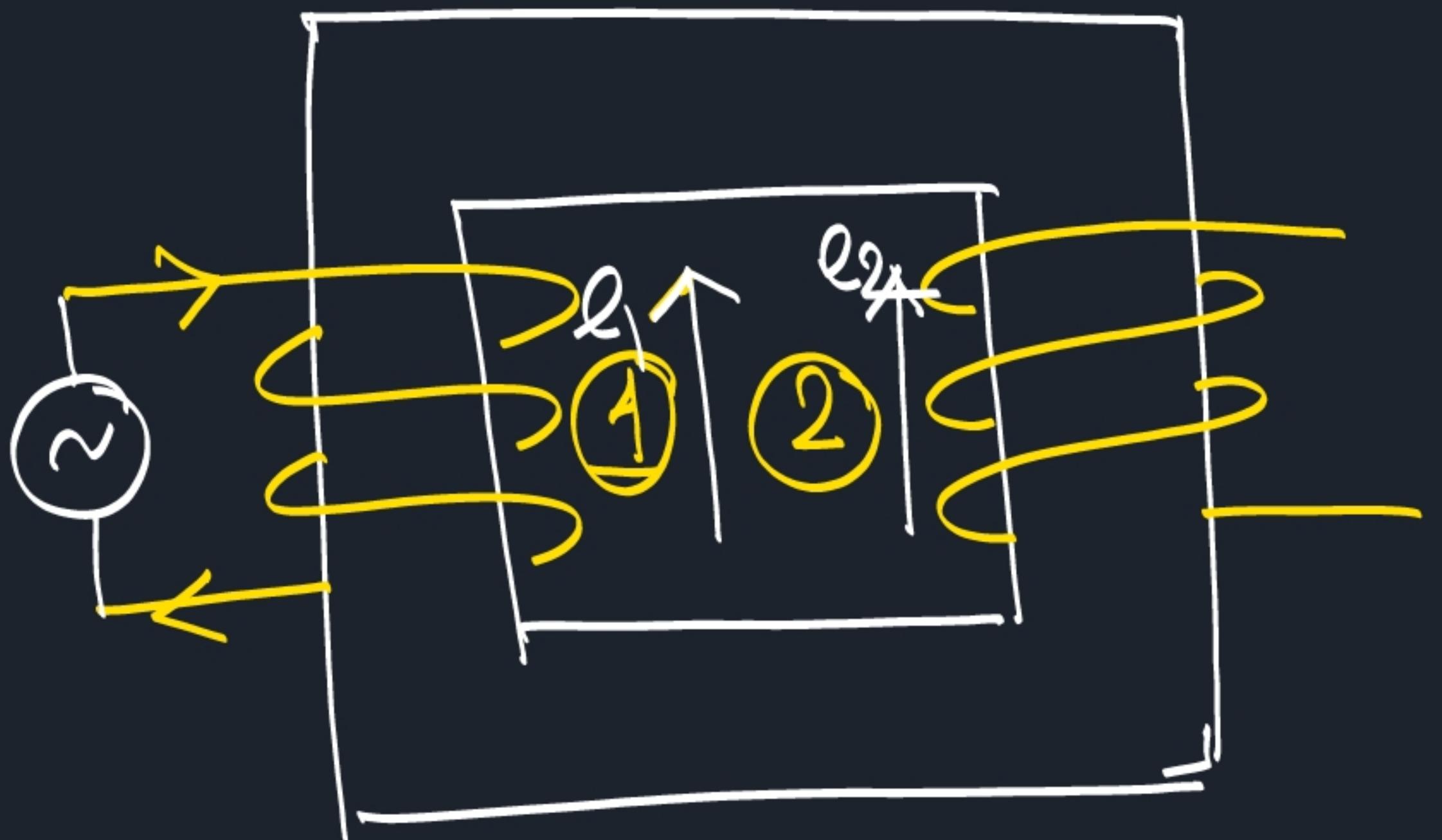$\ell_1 > \ell_2 \Rightarrow$ Step down T/F.



$$e_1 = ? \quad e_2 = ?$$

$$e_1(t) = -N_1 \frac{d\phi(t)}{dt}$$

$$\underline{\phi = BA}$$

$$= B_m \sin \omega t \cdot A$$

$$= \Phi_m \sin \omega t$$

① → Primary

② → Secondary

$$e_1(t) = N_1 \frac{d\phi(t)}{dt}$$

$$e_1(t) = N_1 \Phi_m \omega \cos \omega t \\ = N_1 \Phi_m \omega \sin(\omega t + \pi/2)$$

$$E_1 = \frac{N_1 \Phi_m \omega}{\sqrt{2}}$$

$$= \frac{N_1 \Phi_m 2\pi f}{\sqrt{2}} \cdot$$

$$= \frac{2\pi}{\sqrt{2}} \Phi_m f N_1$$

$$E_1 = 4.44 f \Phi_m N_1$$

$$E_2 = 4.44 f \Phi_m N_2$$


$$f = 50 \text{ Hz}$$

Peak Flux.

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$\Phi_m \propto E_1$$

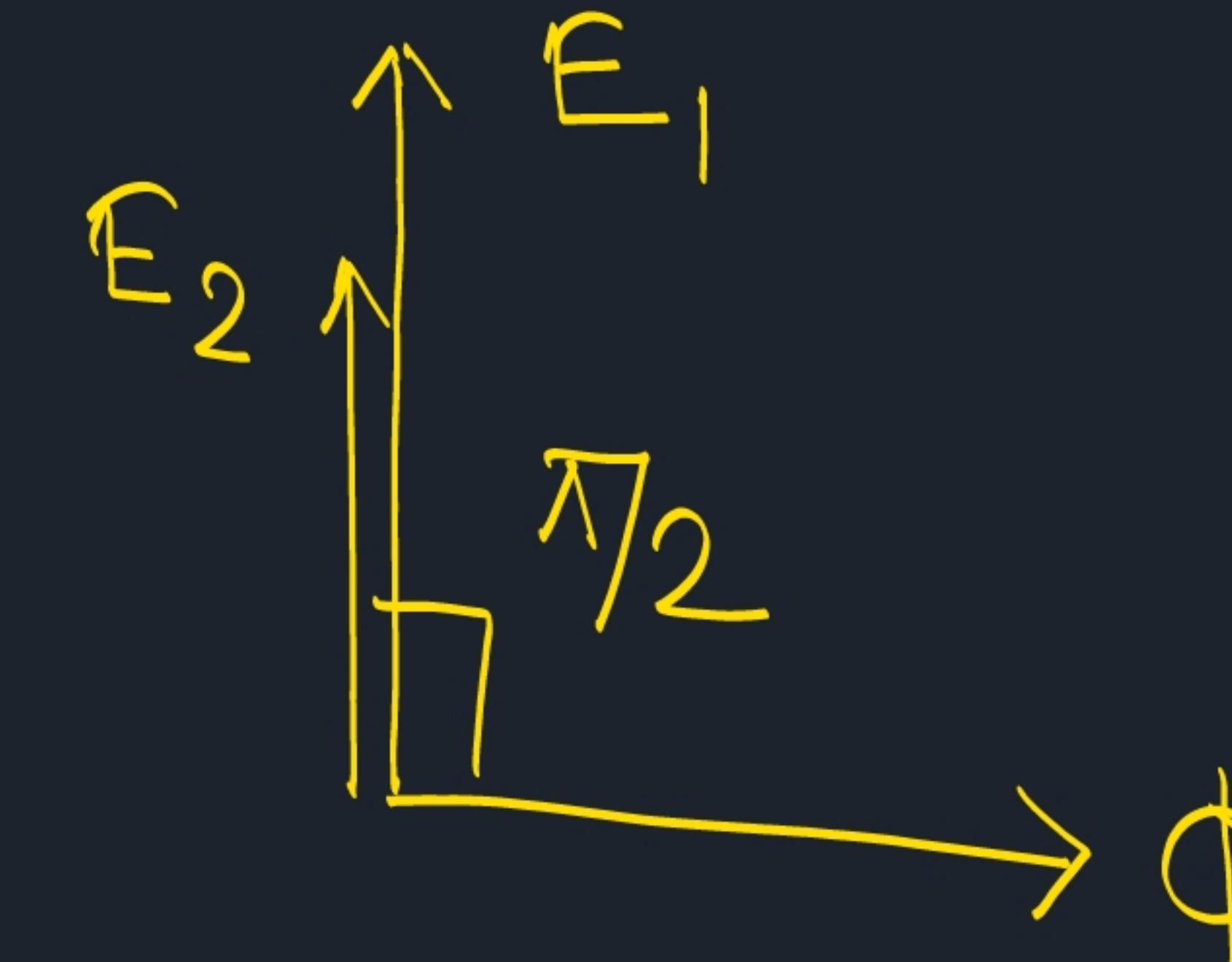T/F \rightarrow constant flux \propto m/c.



$$\Phi = \frac{NI}{R}$$





$$R = \frac{l}{A \mu_0 \mu_s}$$

$$\frac{V_1}{N_1} = \frac{V_2}{N_2} \dots (i)$$

$$I_1 N_1 = I_2 N_2 \dots (ii)$$

3003

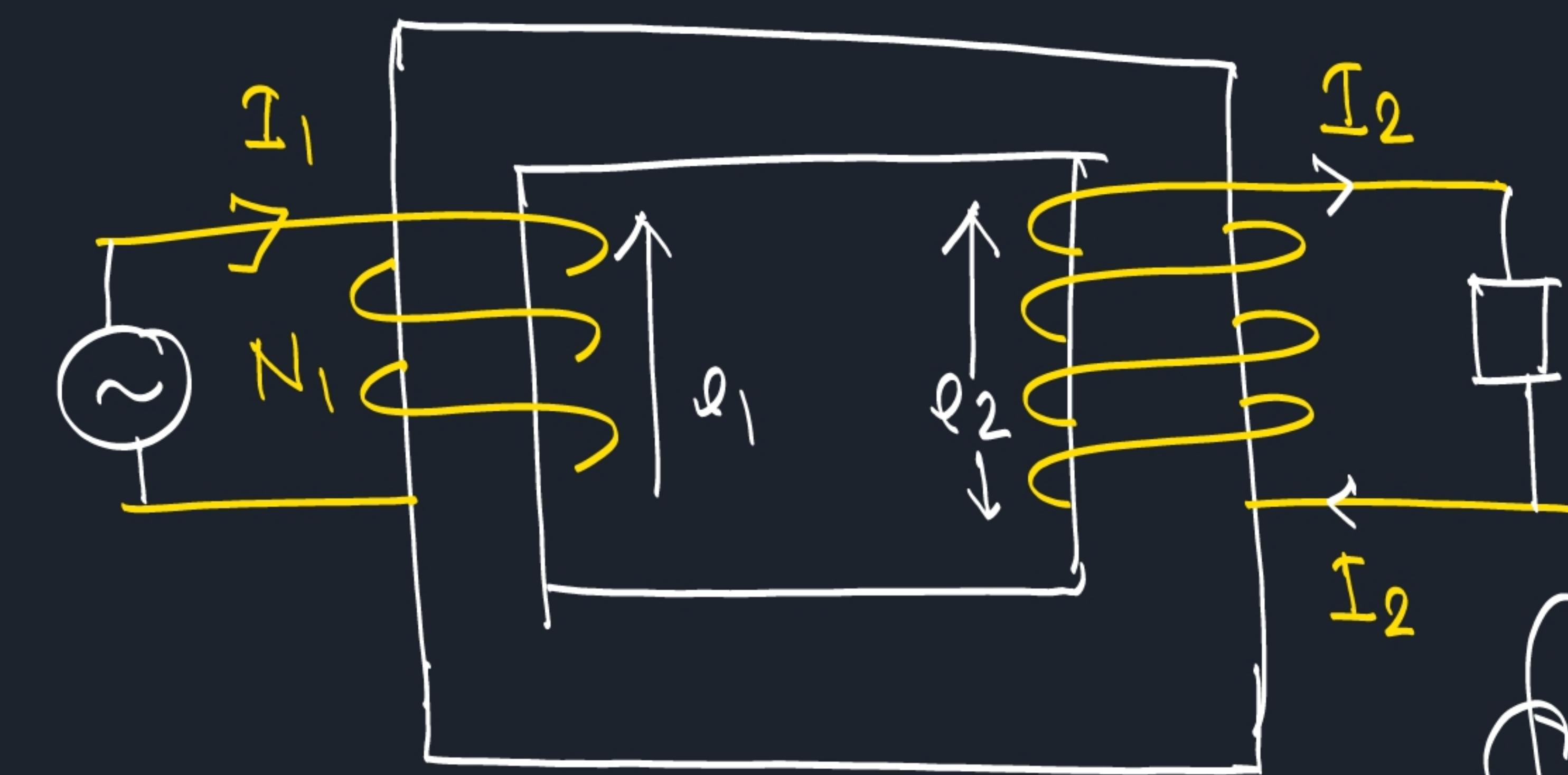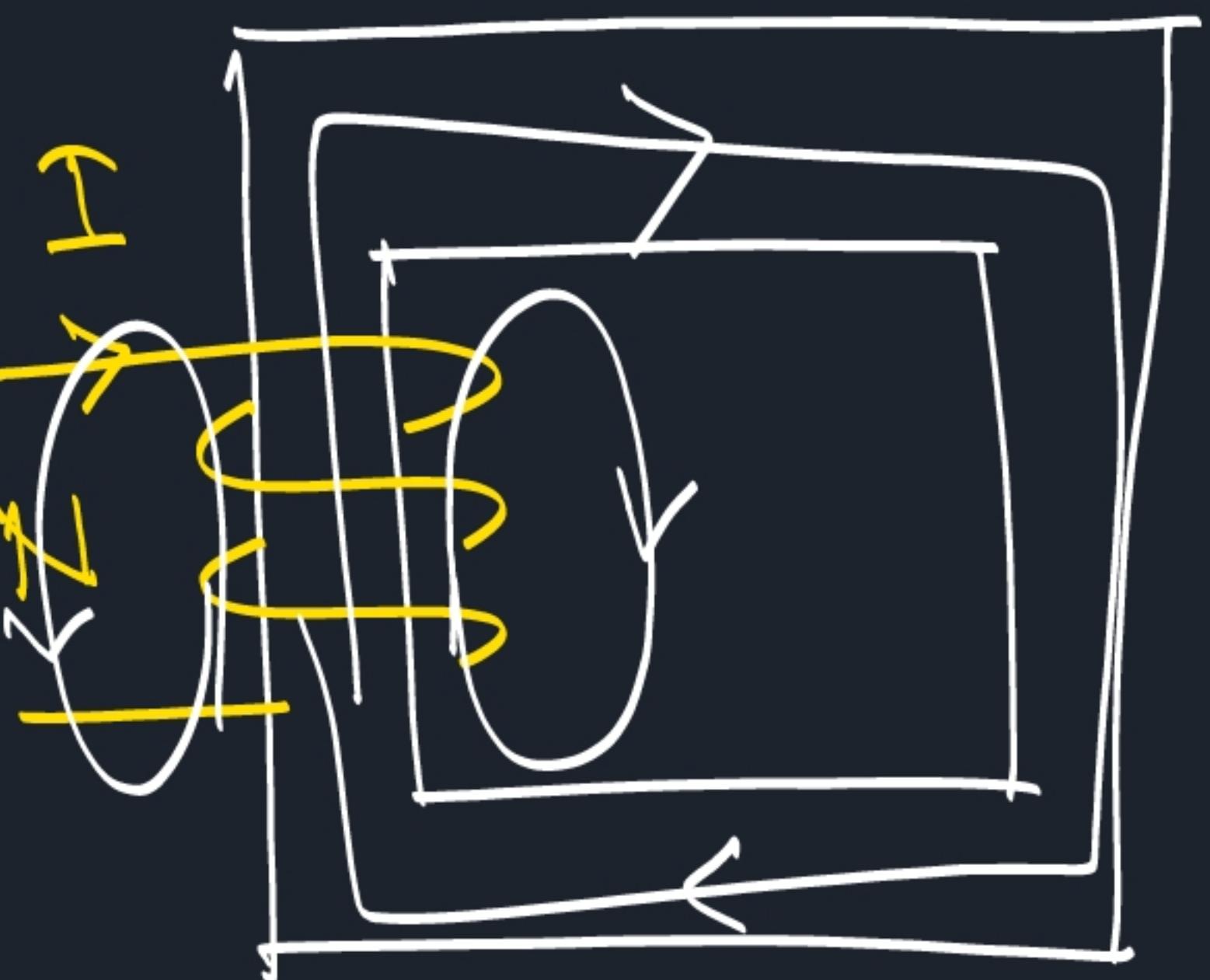

$$I_2 = \frac{E_2}{Z}$$



Ideal Case


$$R \rightarrow 0$$

$$\mu_s \rightarrow \infty$$

$$H = \frac{NI}{l}$$

$$\eta_{T/F} \rightarrow 100\%$$

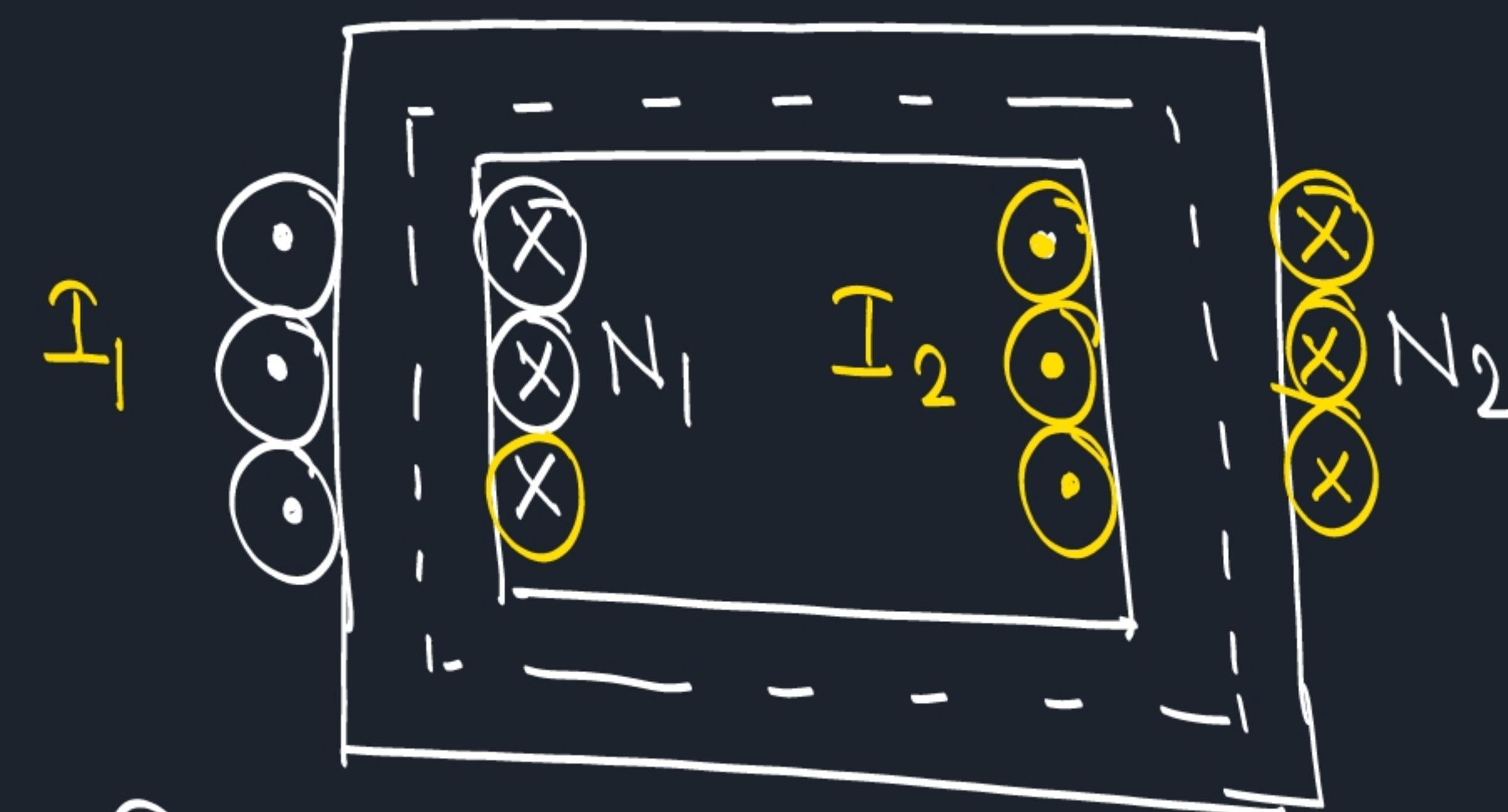
$$V_1 I_1 = V_2 I_2 \Rightarrow \text{VA Rating}$$



$$\oint \vec{H} \cdot d\vec{u} = N_1 I_1 - N_2 I_2 = 0$$

$$N_1 I_1 = N_2 I_2$$

mmf Balance.

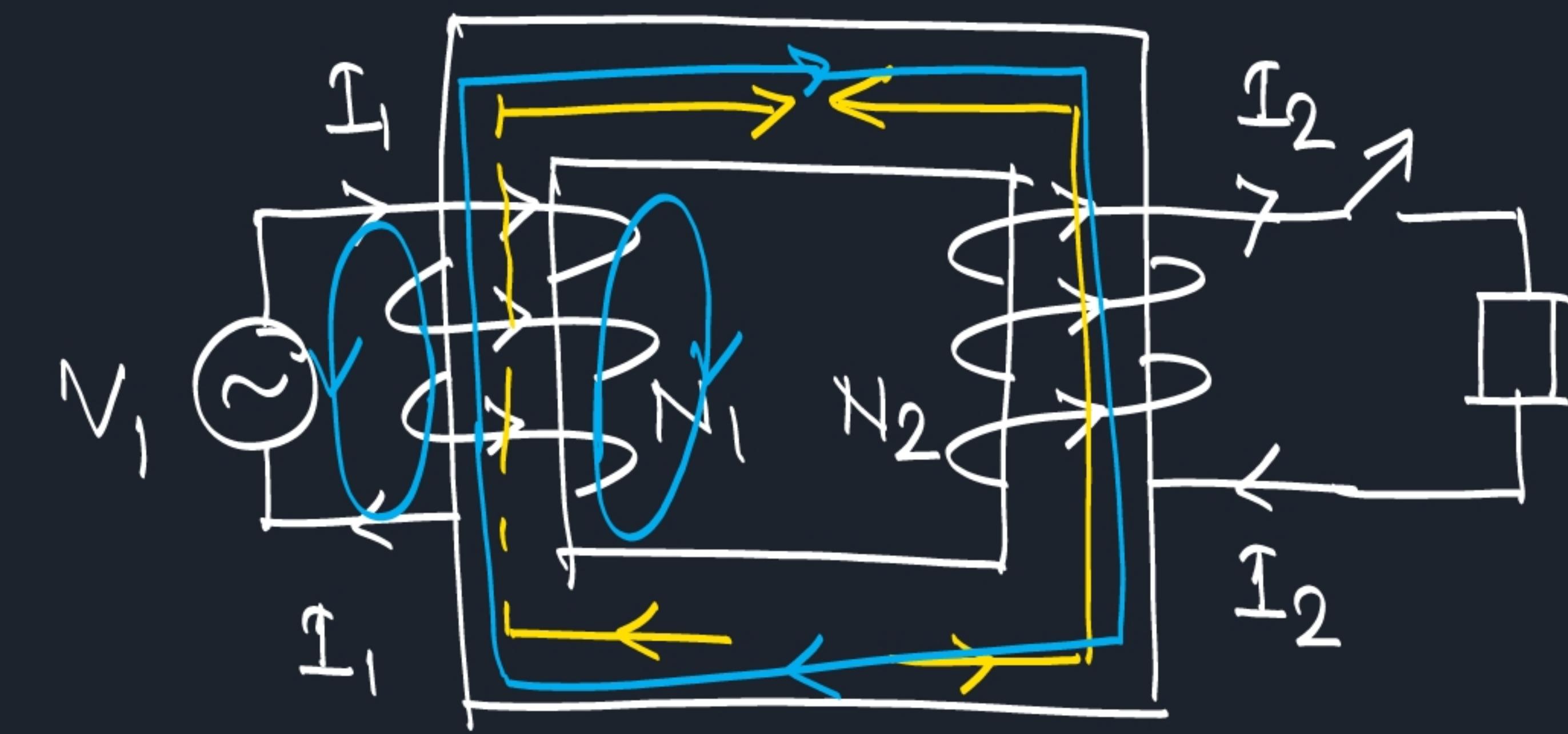

$$\Phi_{\text{total}} = \Phi_m + \Phi_{e1}$$

$$\Phi_m = \frac{N_1 I_m - N_2 I_2 + N_1 I_1'}{R}$$

$$\begin{aligned} E_1^{\text{total}} &= 4.44 f \Phi_{\text{total}} N_1 \\ &= 4.44 f (\Phi_m + \Phi_{e1}) N_1 \\ E_1^{\text{total}} &= \underbrace{4.44 f \Phi_m N_1}_{\text{Magnetic Energy}} + \underbrace{4.44 f \Phi_{e1} N_1}_{\text{Electromagnetic Energy}} \end{aligned}$$

$$\Phi_m = \frac{N_1 I_m}{R}$$

$$\Phi_m' = \frac{N_1 I_m - I_2 N_2}{R}$$


$$N_1 I_1' = N_2 I_2$$



$$I_1 = I_m + I_1'$$

$$V_1 = E_1 + I_1 R_1 + j I_1 X_{e1}$$


$$\begin{aligned} V_1 - I_1 R_1 &= E_1 = \underbrace{4.44 f \Phi_m N_1}_{\text{Magnetic Energy}} + E_{e1} \\ &= E_1 + E_{e1} \end{aligned}$$

$$V_1 - E_1 = I_1 R_1 + E_{e1}$$

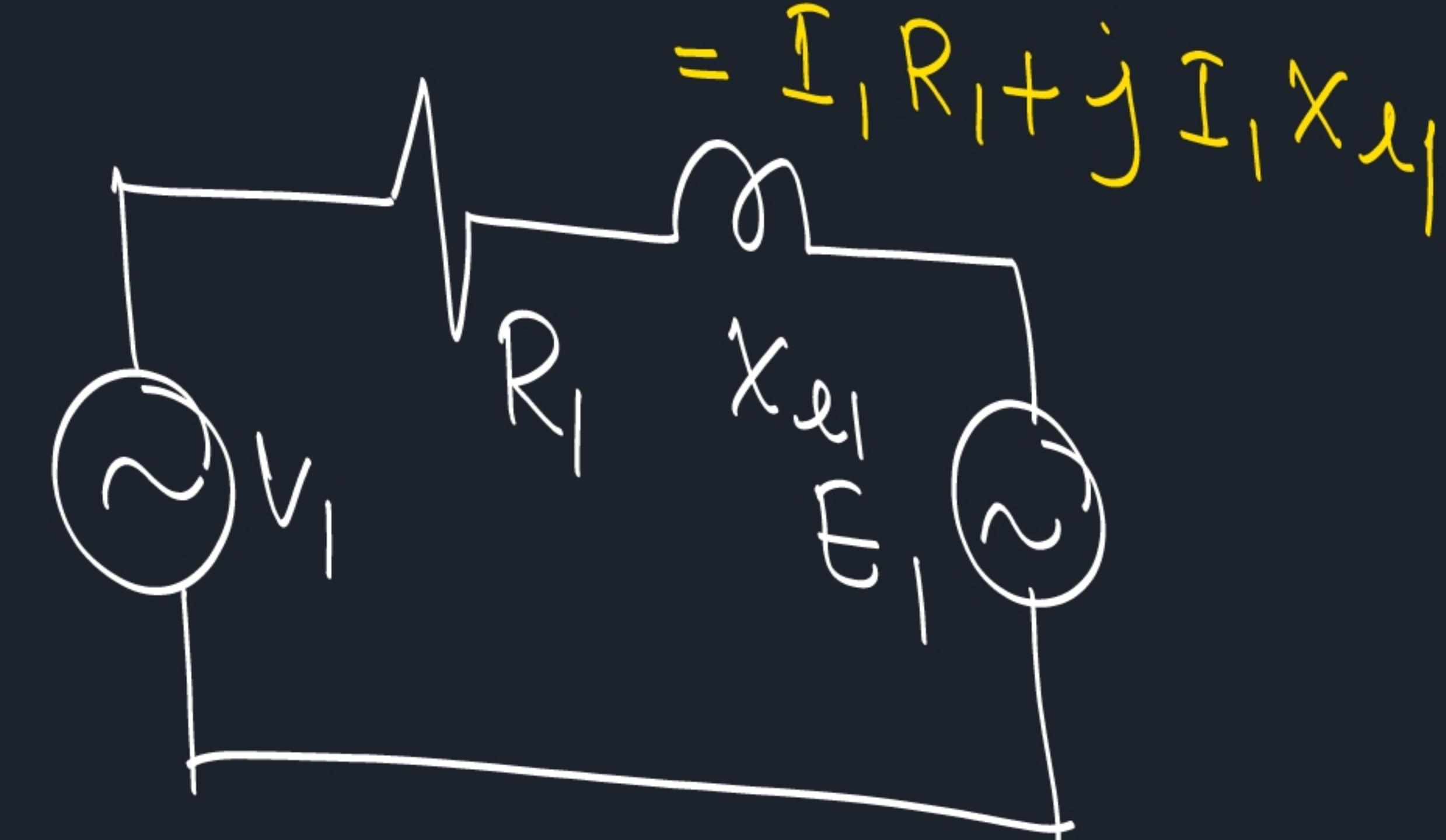

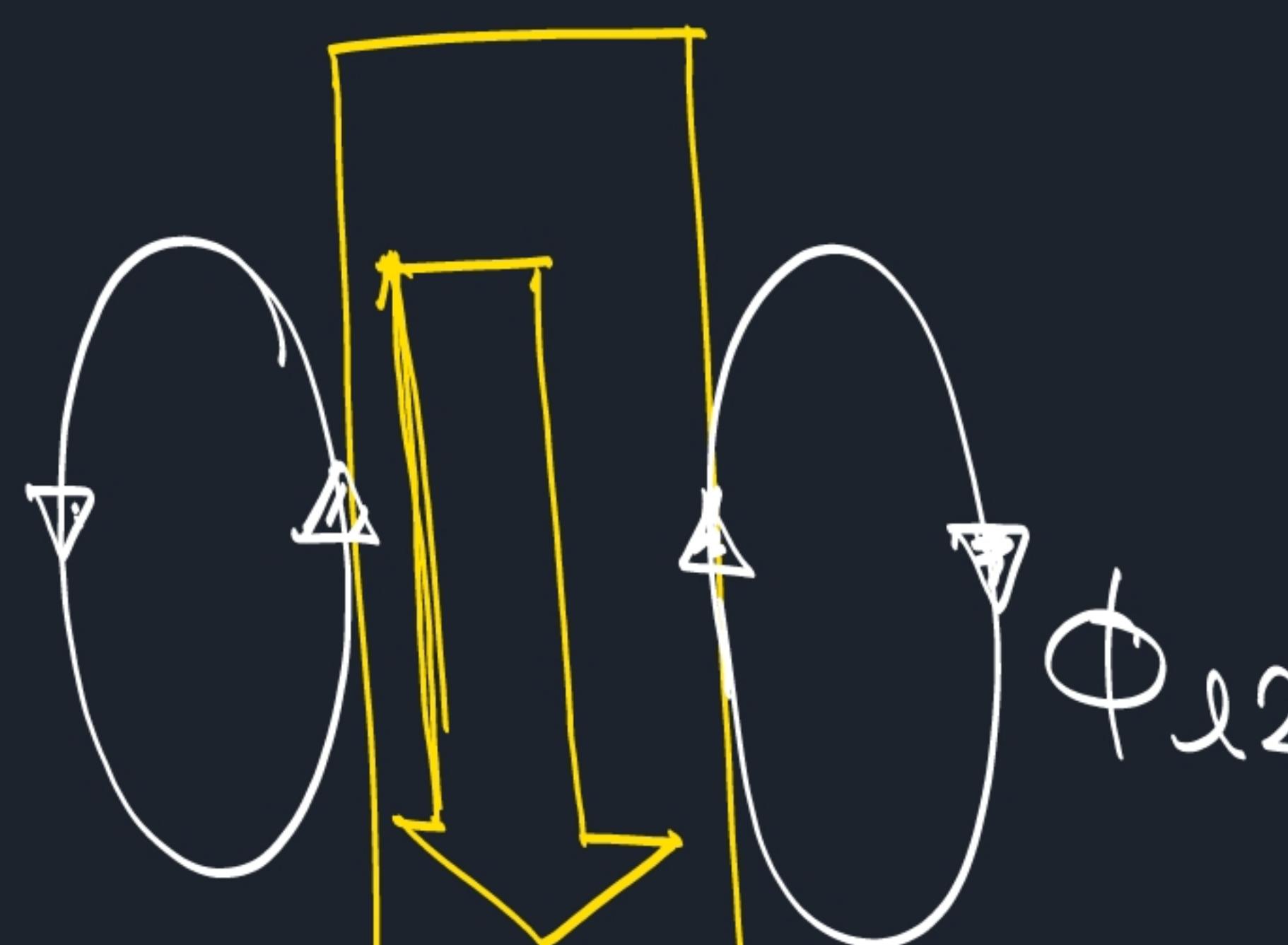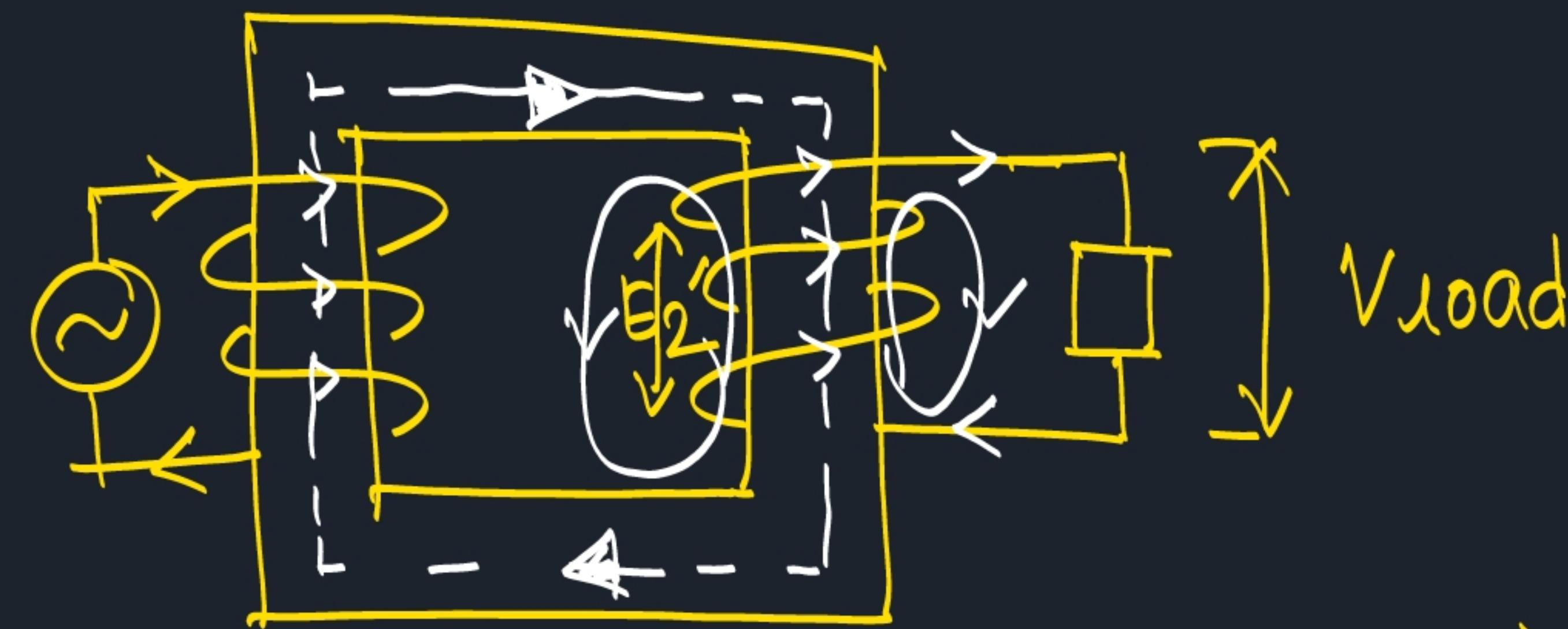


$$\Phi_m \gg \Phi_{12}$$

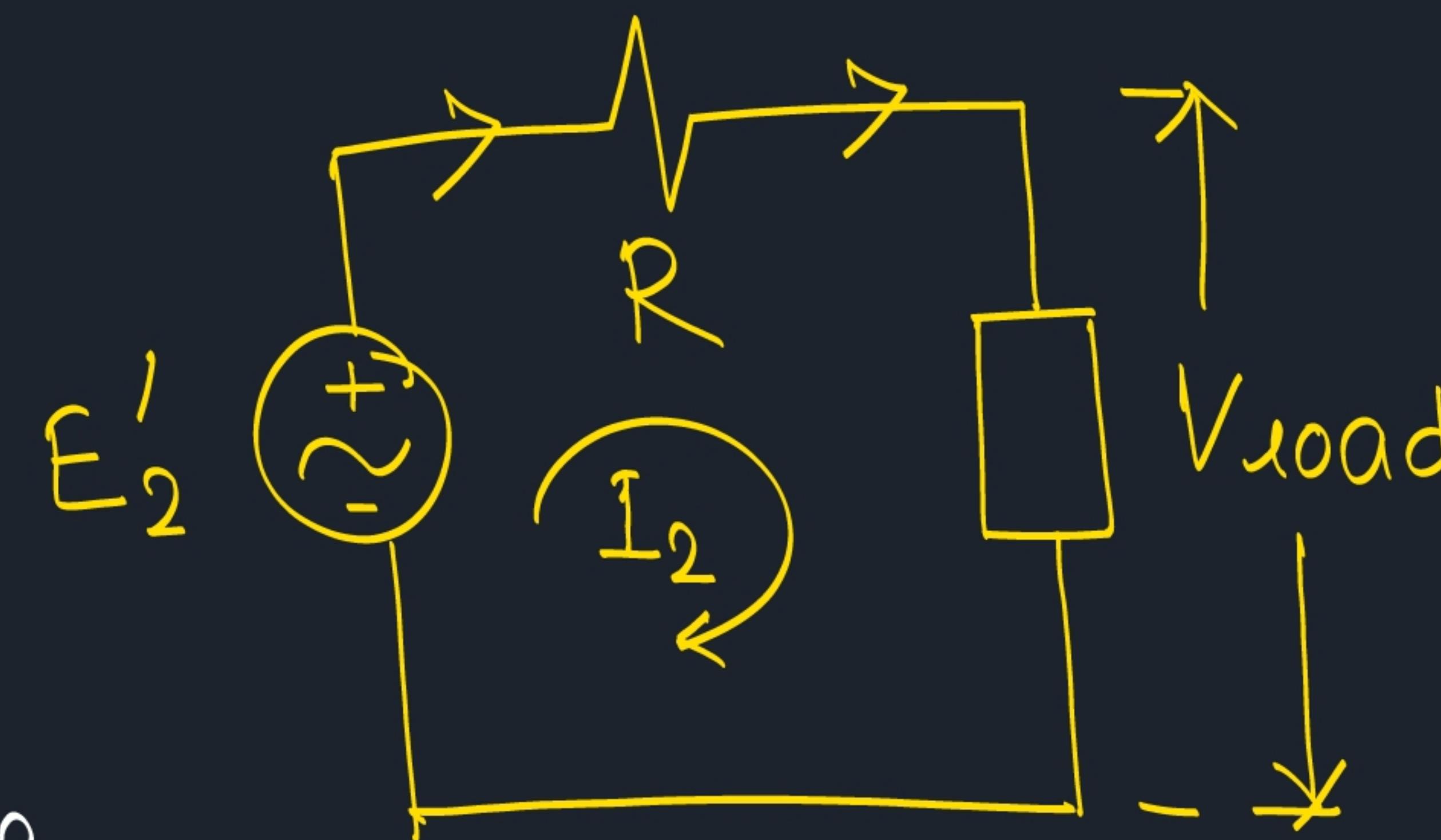


$$\begin{aligned}
 E'_2 &= V_{load} + I_2 R_2 \Rightarrow E_2 - E_{12} = V_{load} + I_2 R_2 \\
 E_2 &= V_{load} + I_2 R_2 + E_{12} \\
 &= V_{load} + I_2 R_2 + (I_2 \times \\
 &\quad j\omega L_2) \\
 E'_2 &= 4.44 f \phi N_2 \\
 &= 4.44 f (\phi_m - \phi_{12}) N_2 \\
 &= \underbrace{4.44 f \phi_m N_2}_{E_2} - \underbrace{4.44 f \phi_{12} N_2}_{E_{12}} \\
 &= E_2 - E_{12}
 \end{aligned}$$

$$E_2 = V_{load} + I_2 R_2 + j I_2 X_{12}$$
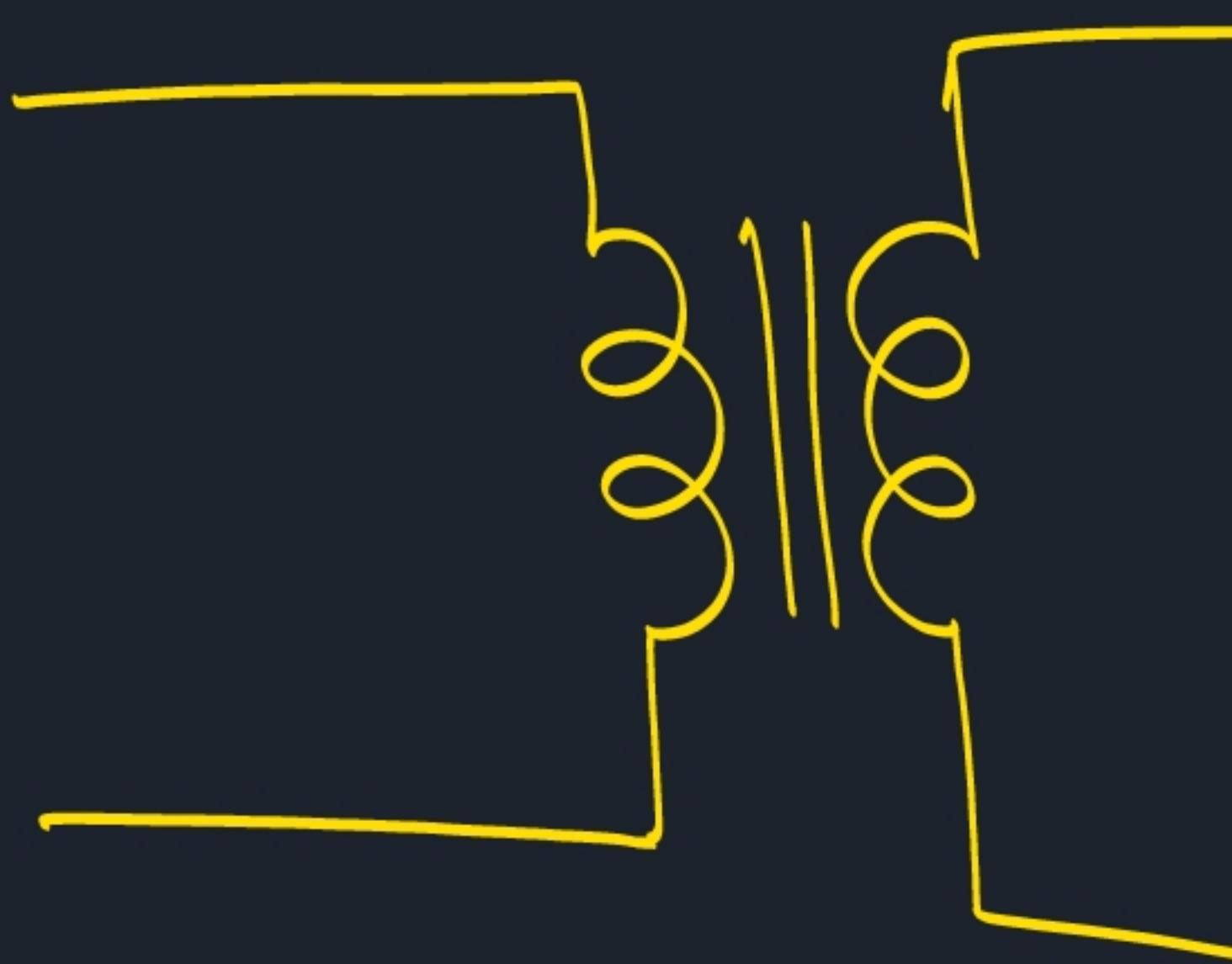
$$\left. \begin{array}{l} V_1 = E_1 + I_1 R_1 + j I_1 X_{L1} \dots \dots \text{(i)} \\ E_2 = V_{\text{load}} + I_2 R_2 + j I_2 X_{L2} \dots \dots \text{(ii)} \\ I_1 = I_m + I'_1 \dots \dots \dots \text{(iii)} \\ I'_1 N_1 = I_2 N_2 \dots \dots \dots \text{(iv)} \end{array} \right\}$$





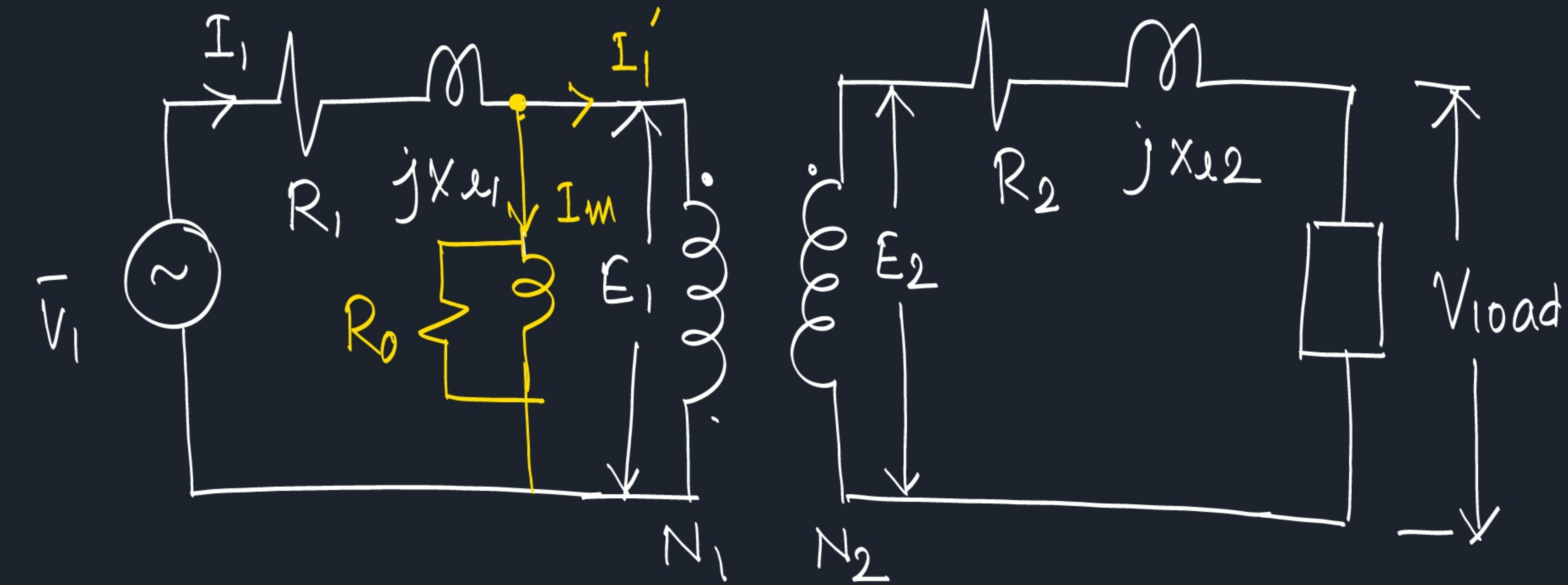I_m creates Φ_m .
i.e. An inductor
Should be associated to Φ_m .



$R_o \Rightarrow$ represents
inter loss of
T/F.
 \rightarrow Hysteresis + Eddy Current.

3874.

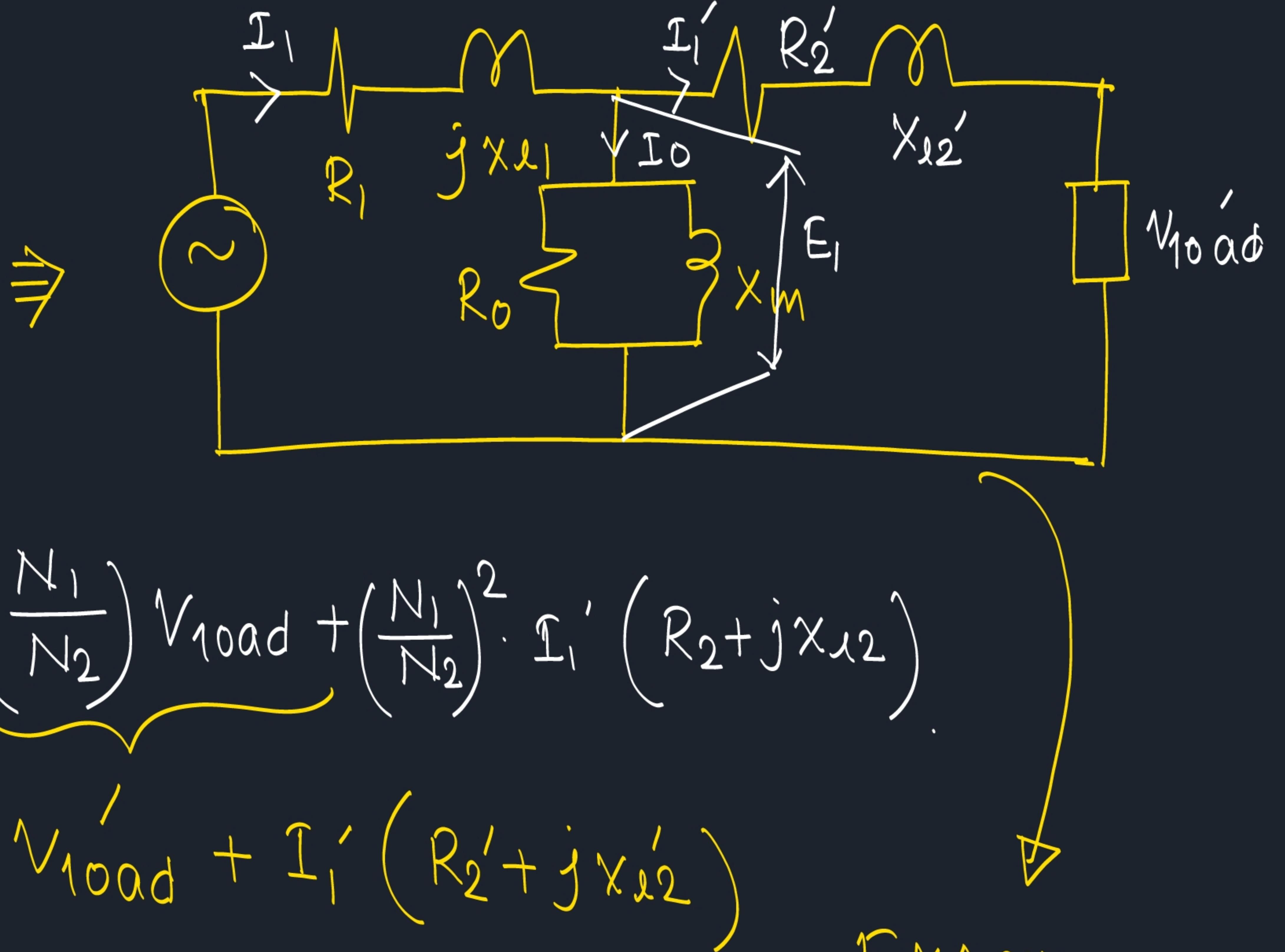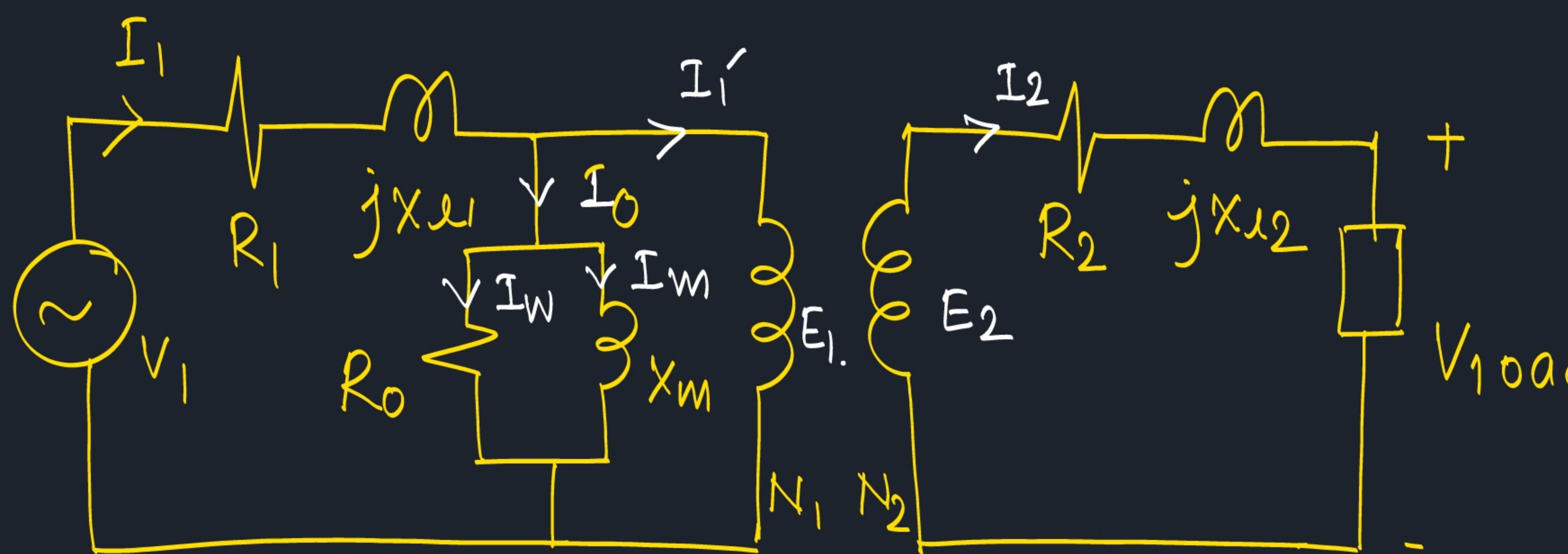

$$E_2 = V_{\text{load}} + I_2 (R_2 + jX_{12})$$

$$\frac{E_1}{E_2} = \frac{N_1}{N_2}$$

$$I_1' N_1 = I_2 N_2$$

$$I_2 = I_1' \left(\frac{N_1}{N_2} \right)$$

$$\Rightarrow E_1 \cdot \frac{N_2}{N_1} = V_{\text{load}} + I_2 (R_2 + jX_{12})$$



$$\Rightarrow E_1 = \left(\frac{N_1}{N_2} \right) \cdot V_{\text{load}} + \left(\frac{N_1}{N_2} \right) I_2 (R_2 + jX_{12})$$

$$\begin{aligned} E_1 &= \underbrace{\left(\frac{N_1}{N_2} \right)}_{= V_1'} V_{\text{load}} + \left(\frac{N_1}{N_2} \right)^2 \cdot I_1' (R_2 + jX_{12}) \\ &= V_1' + I_1' (R_2' + jX_{12}') \end{aligned}$$

$$R_2' = \left(\frac{N_1}{N_2} \right)^2 R_2 \Rightarrow \text{Secondary}$$

$$X_{12}' = \left(\frac{N_1}{N_2} \right)^2 X_{12} \quad \begin{matrix} \text{Referred to} \\ \text{. The Primary} \end{matrix}$$

EXACT
Equivalent Ckt
Of 1st/F.

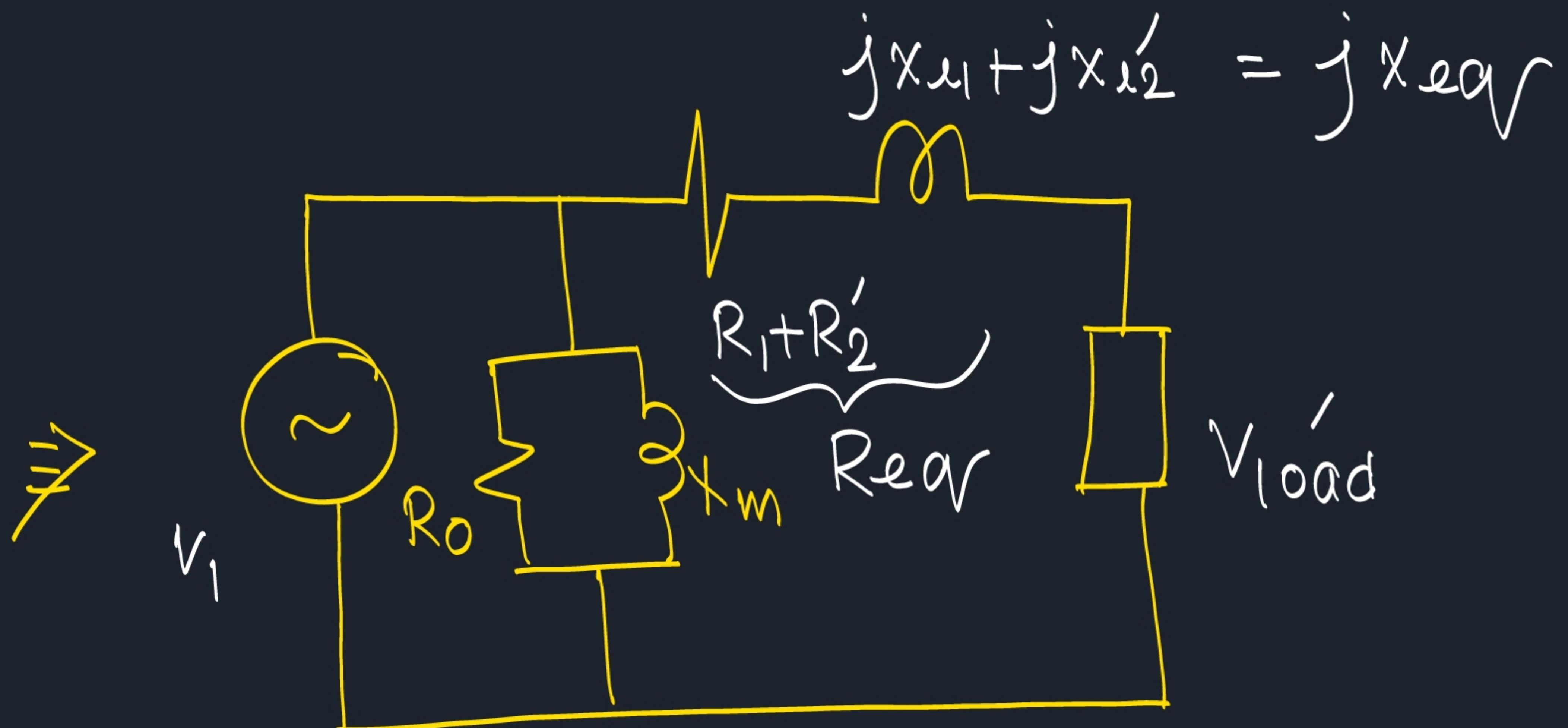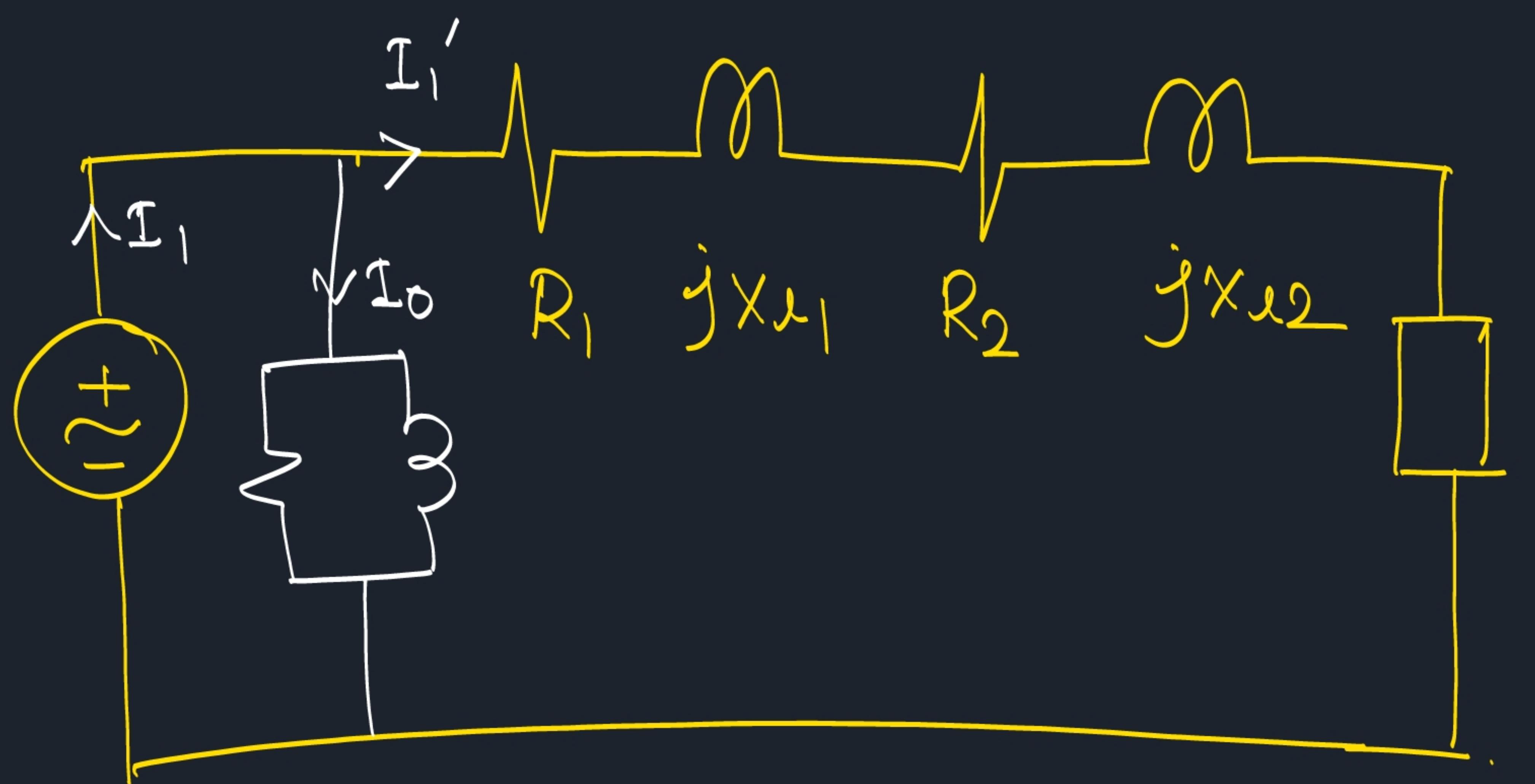

$$\frac{\tilde{I}_0 \ll \tilde{I}_1 \text{ & } \tilde{I}_1'}{\underline{\text{approx. (2-5%)}}}$$

$R_0, X_m \Rightarrow$ Shunt Branch parameters
 $R_{eq}, X_{eq} \Rightarrow$ Series Branch Parameters.

Approximated Equivalent circuit of the T/F.

Approximated

Two tests.



To find out the
parameters of T/F.

i) Open Circuit Test
(OCTest)

ii) Short Circuit Test
(SC Test)


i) Voltmeter
ii) Ammeter
iii) Wattmeter.


$\uparrow V_0, I_0, W_0 \uparrow$

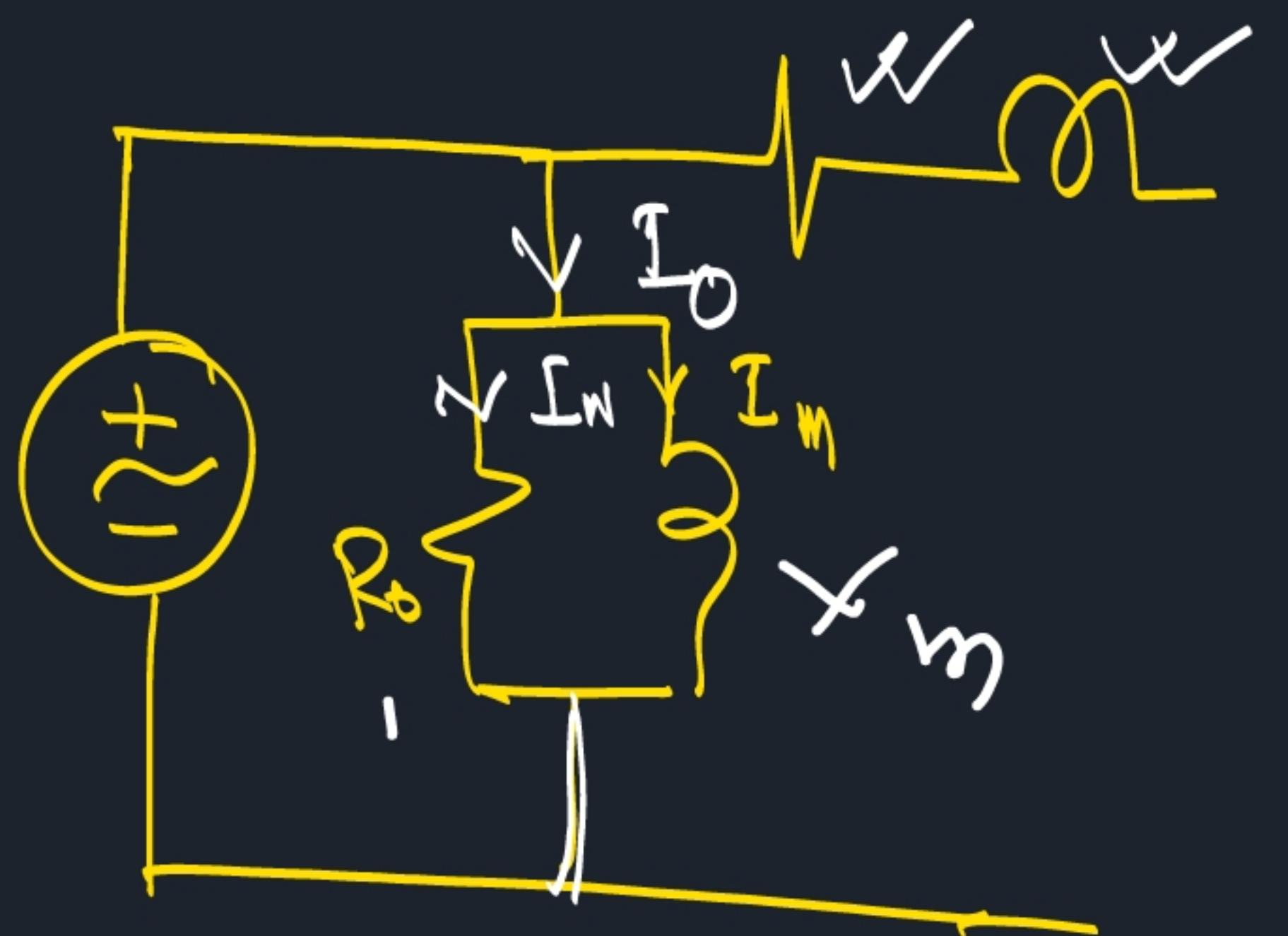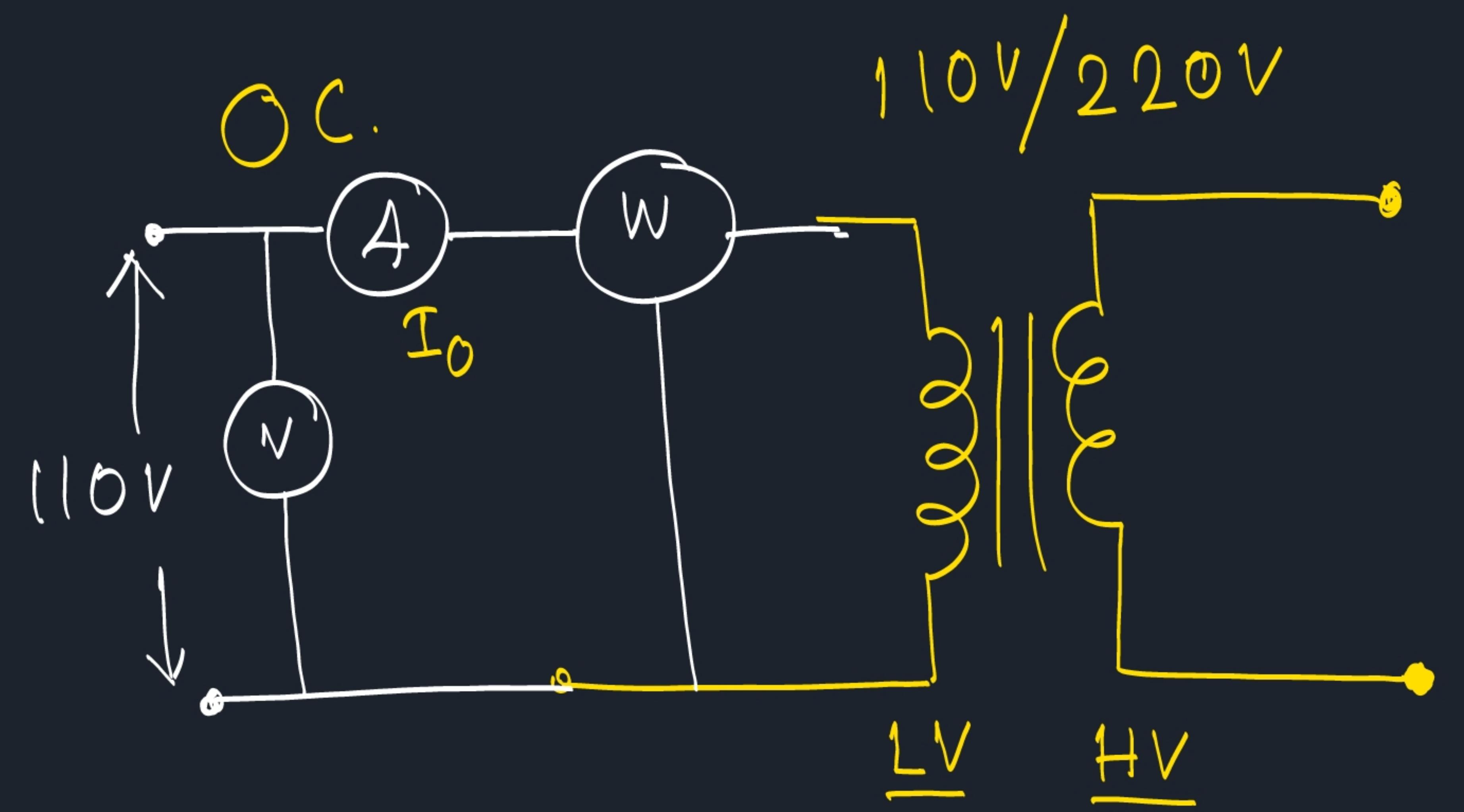

$$W = (I_w^2 \times R_o)$$

V = Rated
Voltage.

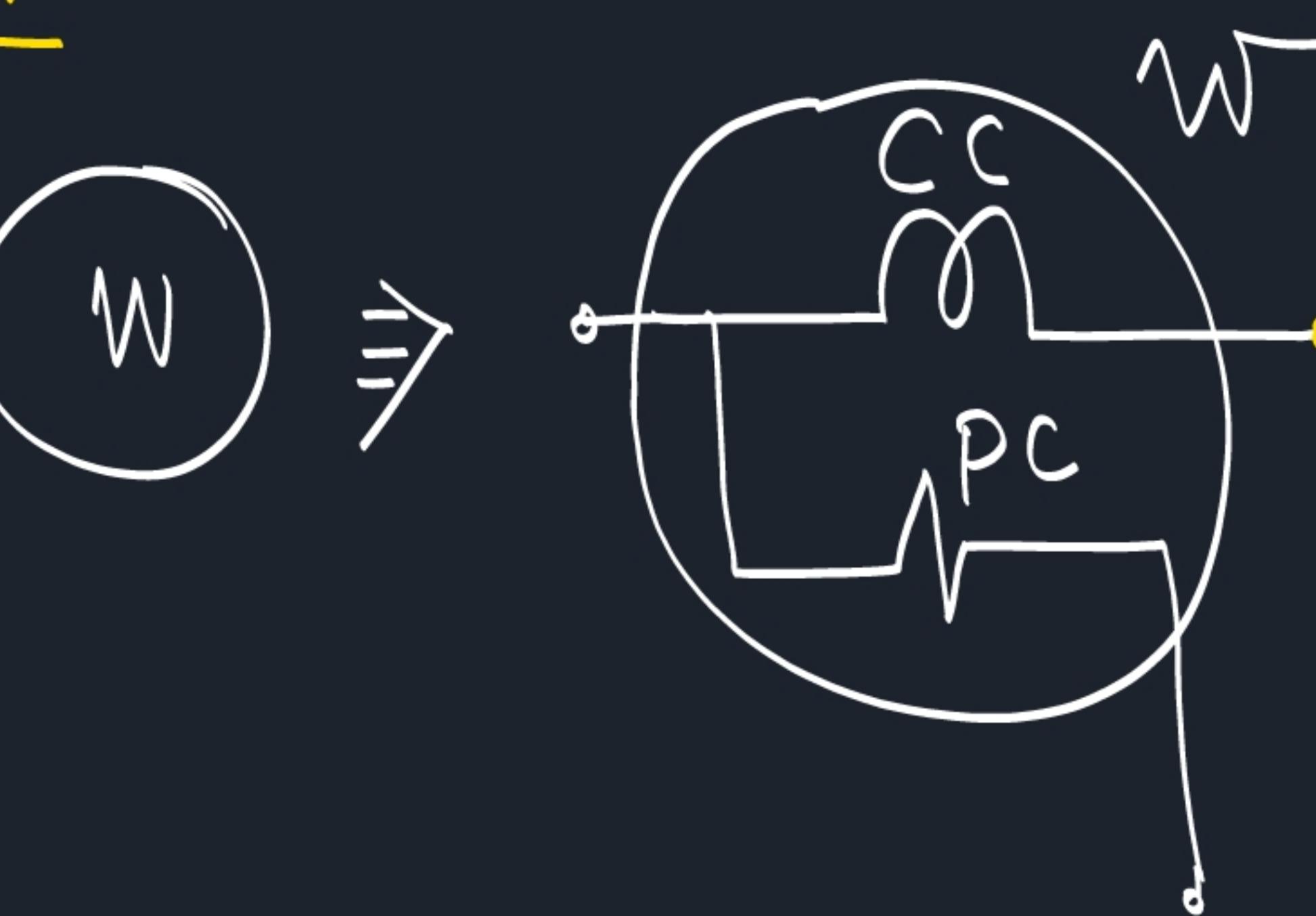

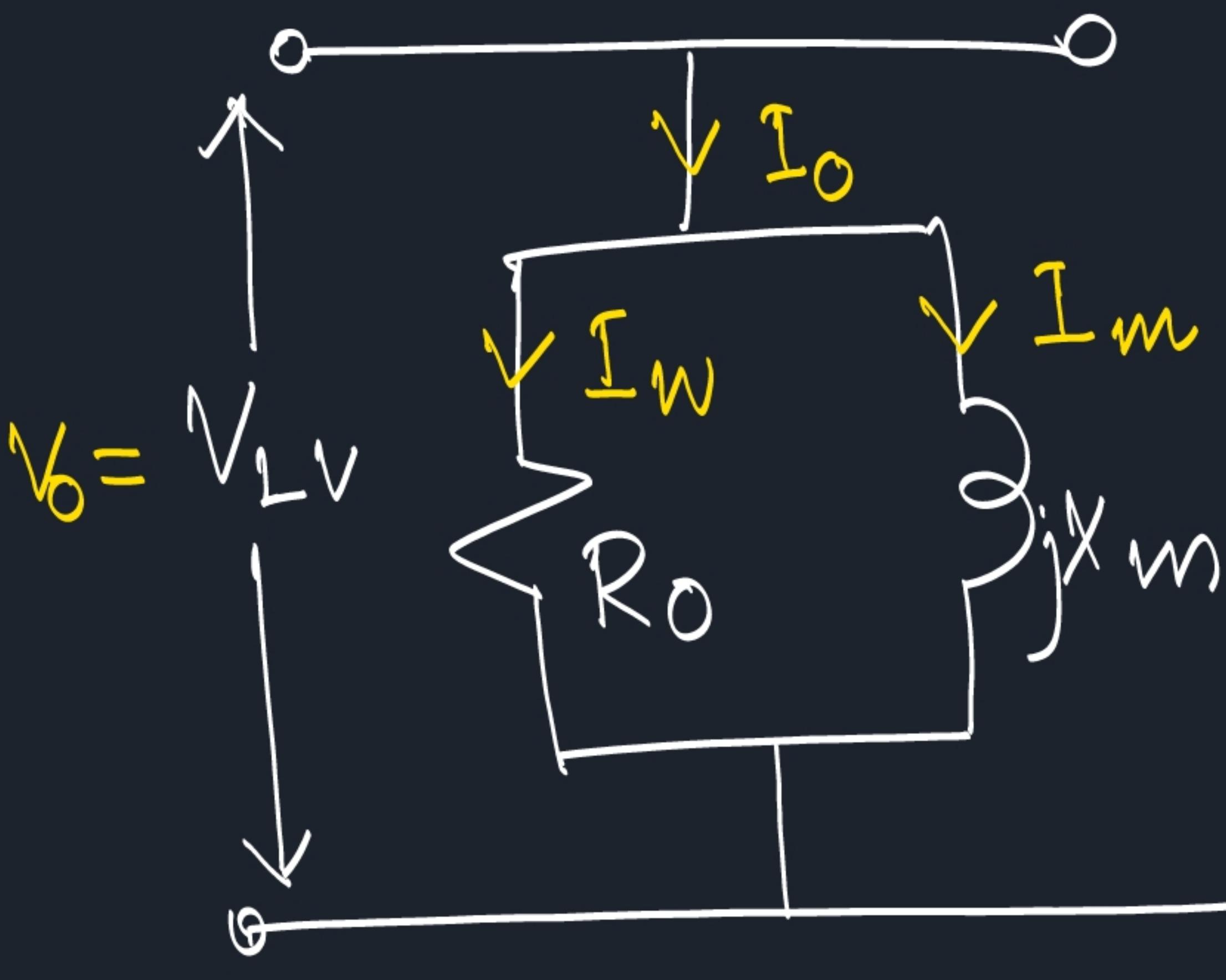

$$\left. \begin{aligned} R_0 &= \frac{V_o}{I_w} \\ jX_m &= \frac{V_o}{I_m} \\ W_o &= I_w^2 R_0 \end{aligned} \right\}$$

$$W_o = V I_w = V_o I_o \cos \theta_o$$

$$\theta_o = \cos^{-1} \left(\frac{W_o}{V_o I_o} \right)$$

$$I_w = |I_o| \cos \theta_o$$

$$V_o, W_o, I_o$$

$$\tilde{I}_o = |I_o| \angle \theta_o$$

Measured
By Ammeter.

$$I_m = |I_o| \sin \theta_o$$

$$R_o = \frac{V_o}{|I_o| \cos \theta_o}$$

$$X_m = \frac{V_o}{|I_o| \sin \theta_o}$$

SC Test :-

1φ T/F




$$\left. \begin{array}{l} V_{LV} I_{LV} = 1000 \\ V_{HV} I_{HV} = 1000 \end{array} \right\}$$

1 KVA Rating

$$V_1 I_1 = V_2 I_2 = 1000$$


$$\left. \begin{array}{l} |I_{LV}| = \frac{1000}{110} \text{ Amp} \\ |I_{HV}| = \frac{1000}{220} \text{ Amp.} \end{array} \right\}$$

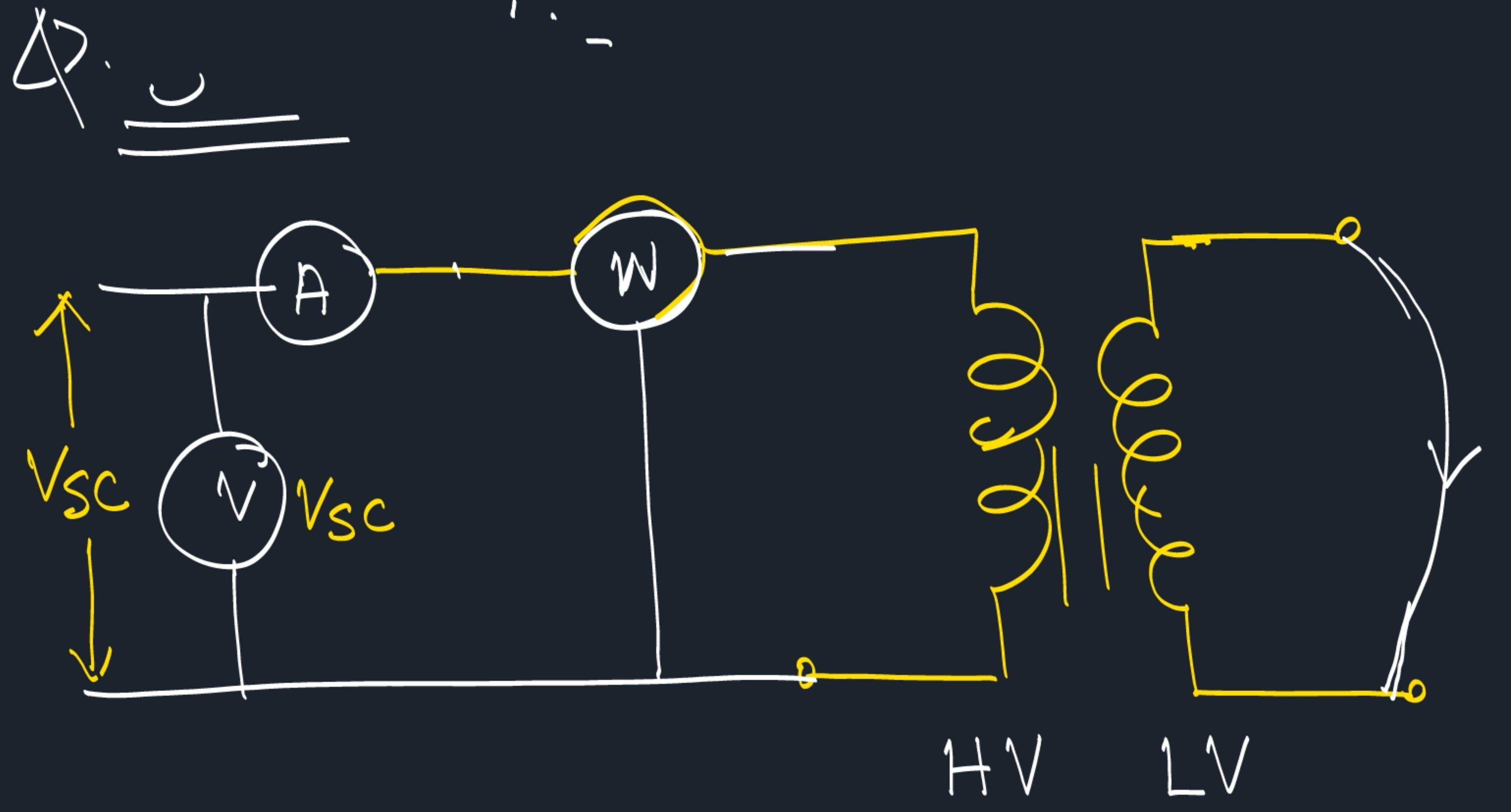

$$\frac{1000}{220} \text{ Amps.}$$

$\underline{\underline{V_{sc}, I_{sc}, W_{sc}}}$

$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}}$$

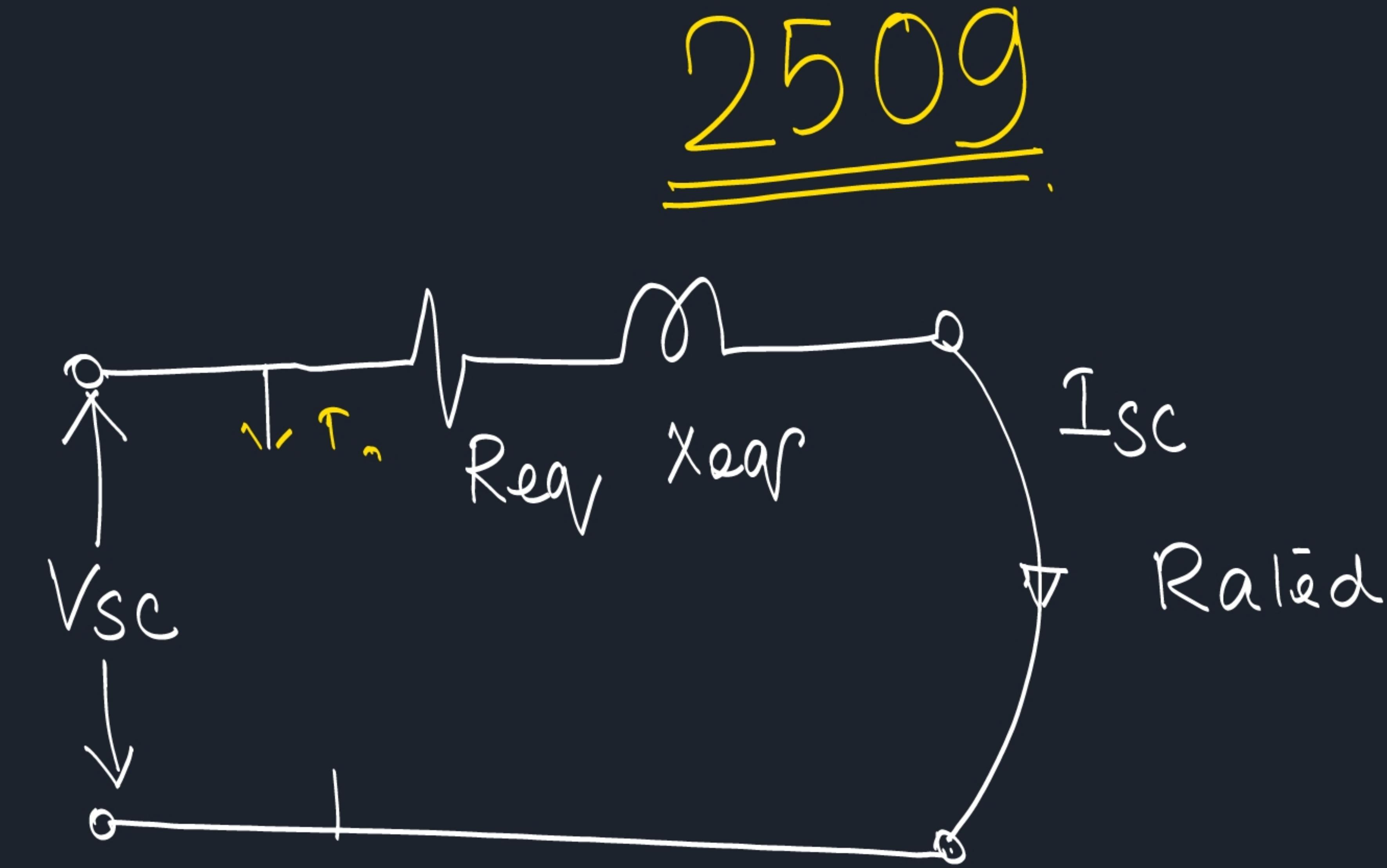

$I_0 \lll I_{sc}$

$$W_{sc} = I_{sc}^2 Req$$

$$Req = \frac{W_{sc}}{I_{sc}^2}$$

$$X_{eq} = \sqrt{Z_{eq}^2 - Req^2}$$

2509

Problem:-

1 Φ T/F

$N_1 = 250$ (pri)

$N_2 = 500$ (Sec)

$A_{core} = 60 \text{ cm}^2$

$f = 50 \text{ Hz}$

$V = 230 \text{ V}$ (Primary)

Peak flux density B_m

$$V_1 = E_1 = 4.44 f \Phi_m N_1$$

$$\Phi_m = \frac{230}{4.44 \times 50 \times 250} \text{ Wb.} = ?$$

$$B_m = \frac{\Phi_m}{A} = \frac{\Phi_m}{60 \times 10^{-4}} \text{ Wb/m}^2 = ?$$

Problem :-

T/F : 5 kVA
200/1000 V

$$(i) \quad \left. \begin{array}{l} V_{LV} = 200 \text{ V} \\ V_{HV} = 1000 \text{ V} \end{array} \right\} \quad V_{HV} I_{HV} = V_{LV} I_{LV} = 5000$$

$$I_{HV} = 5 \text{ Amps.} \quad I_{LV} = \frac{5000}{200} = 25 \text{ Amps}$$

OC. Test : 200 V, 1.2 A, 90 W

(ii) LV Side is chosen for OC Test

$$V_0 = 200 \text{ V}, \quad I_0 = 1.2 \text{ A}, \quad W_0 = 90 \text{ W}$$

Estimate The transformer parameters.

(iii) HV Side is chosen for SC Test

$$V_{SC} = 50 \text{ V}, \quad I_{SC} = 5 \text{ A}, \quad W_{SC} = 110 \text{ W}$$

OC Test :-

Step-1

$$\cos \theta_0 = \frac{w_0}{V_0 I_0}$$

$$= \frac{90}{200 \times 1.2}$$

$$\theta_0 = ? \quad 67.9756^\circ$$

Step-2

$$R_0^{\text{LV}} = \frac{V_0}{I_0 \cos \theta_0} = 444.44 \Omega$$

Step-3

$$X_w^{\text{LV}} = \frac{V_0}{I_0 \sin \theta_0}$$

$$= 179.7866 \Omega$$

SC Test :-

Step-1

$$R_{eq}^{\text{HV}} = \frac{w_{sc}}{I_{sc}^2}$$

$$= \frac{110}{(5)^2} = 4.4 \Omega$$

Step-2

$$|Z_{eq}|^{\text{HV}} = \frac{V_{sc}}{I_{sc}}$$



$$= \frac{50}{5} = 10 \Omega$$

Step-3

$$X_{eq}^{\text{HV}} = \sqrt{|Z_{eq}|^2 - R_{eq}^2}$$

$$= \sqrt{10^2 - (4.4)^2}$$

$$= 8.97 \Omega$$

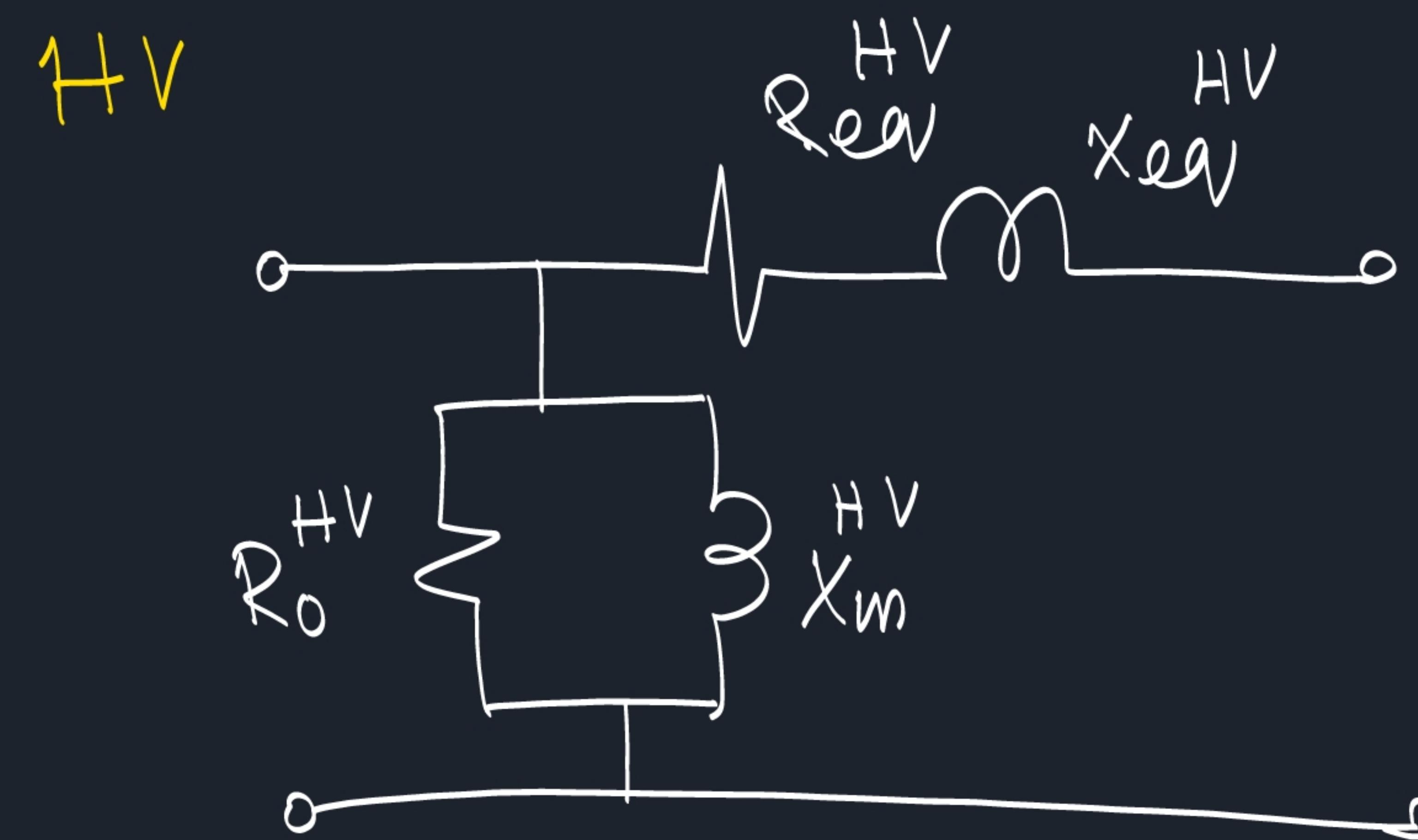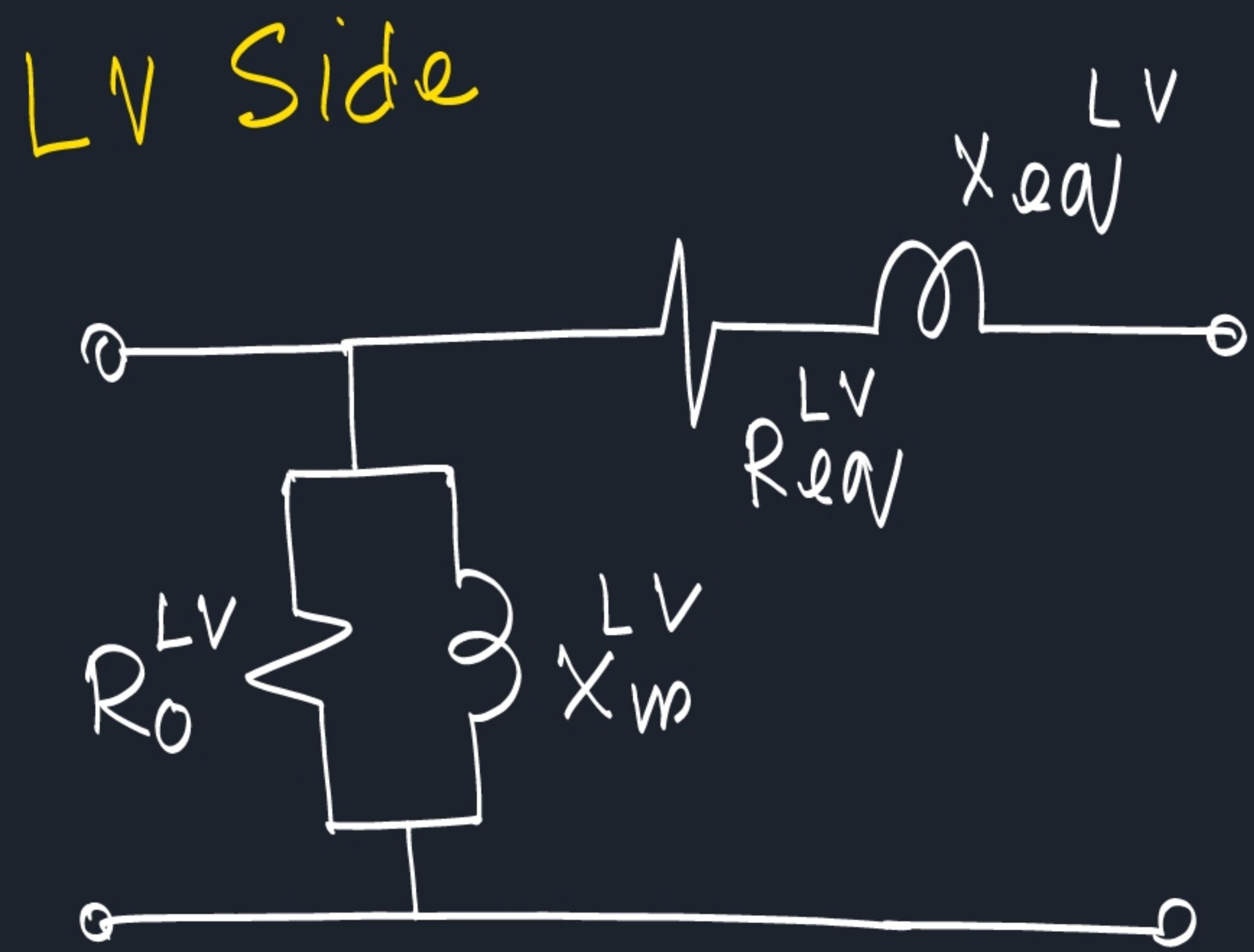

$$\frac{R_{eqV}^{LV}}{R_{eqV}^{HV}} = \left(\frac{N_{LV}}{N_{HV}} \right)^2 = \left(\frac{V_{LV}}{V_{HV}} \right)^2 = \left(\frac{200}{1000} \right)^2$$

$$\frac{X_{eqV}^{LV}}{X_{eqV}^{HV}} = \left(\frac{V_{LV}}{V_{HV}} \right)^2$$