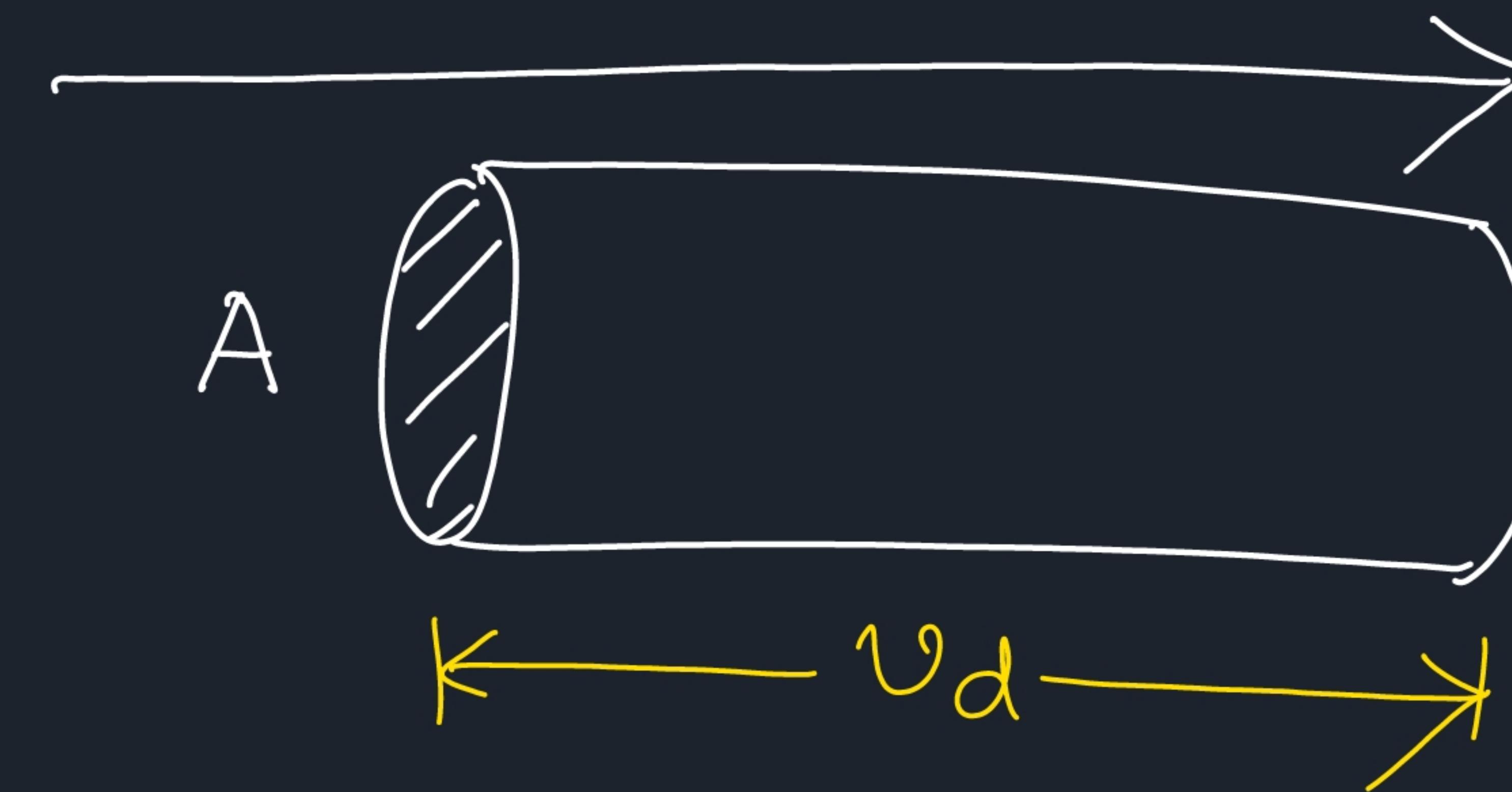




$$v_d = \frac{eE}{m_e} \tau$$

Relaxation Time



Random Motion + Organized Motion.

N_e

$\vec{J} = 6 \vec{E}$

\Rightarrow OHM'S law.

$$E = -\frac{dV}{dx}$$

$$\frac{I}{A} = 6 \frac{V}{l}$$

$$I = \frac{A}{l} \int V$$

$$|E| = \left| \frac{V}{l} \right|$$

$$e N_e A v_d = Q = I$$

$$I = e N_e A \frac{e E}{m_e} \tau$$

$$\frac{I}{A} = \left\{ \frac{e^2 N_e \tau}{m_e} \right\} E = J$$

-

$$V = \frac{\int I}{A} \quad I = R V$$

$$V = R I$$

 Problem:-

Cu wire

$$A = 4 \text{ mm}^2$$

$$\lambda = 4 \text{ m}$$

$$I = 10 \text{ A}$$

$$N_e = 8 \times 10^{28} \text{ m}^{-3}$$

$$V_d = ?$$

$$I = N_e e A V_d$$


$$V_d = \frac{I}{N_e e A}$$

$$0.000195 \text{ V}$$

$$= \frac{10}{8 \times 10^{28} \times 1.602 \times 10^{-19} \times 4 \times 10^{-6}} \text{ m/sec.}$$
$$= 1.95 \times 10^{-4} \text{ m/sec.}$$




Problem:-

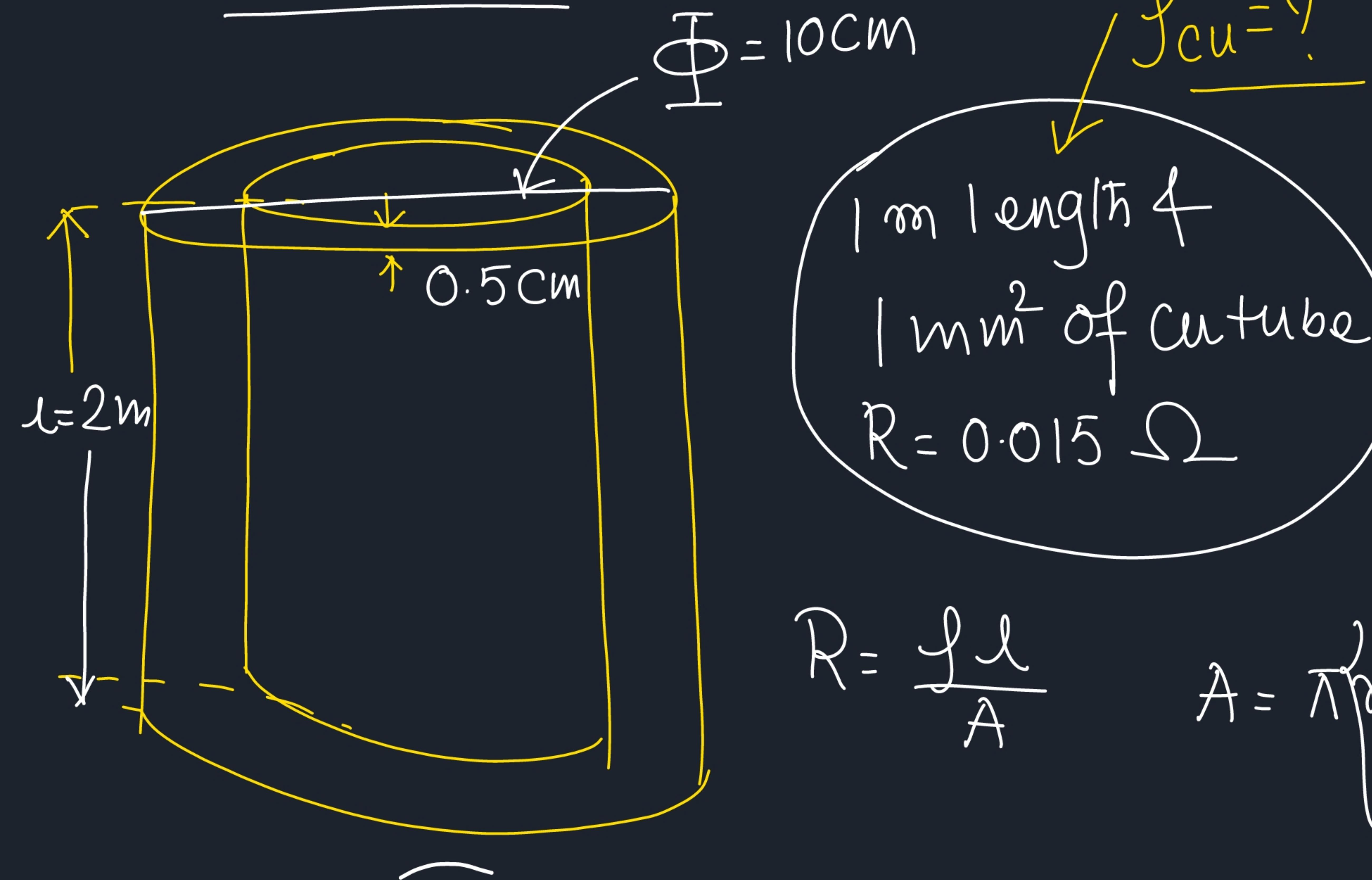

$$R = \frac{\rho l}{A}$$
$$\rho = \frac{RA}{l}$$
$$= \frac{0.015 \times 1 \times 10^{-6}}{1}$$
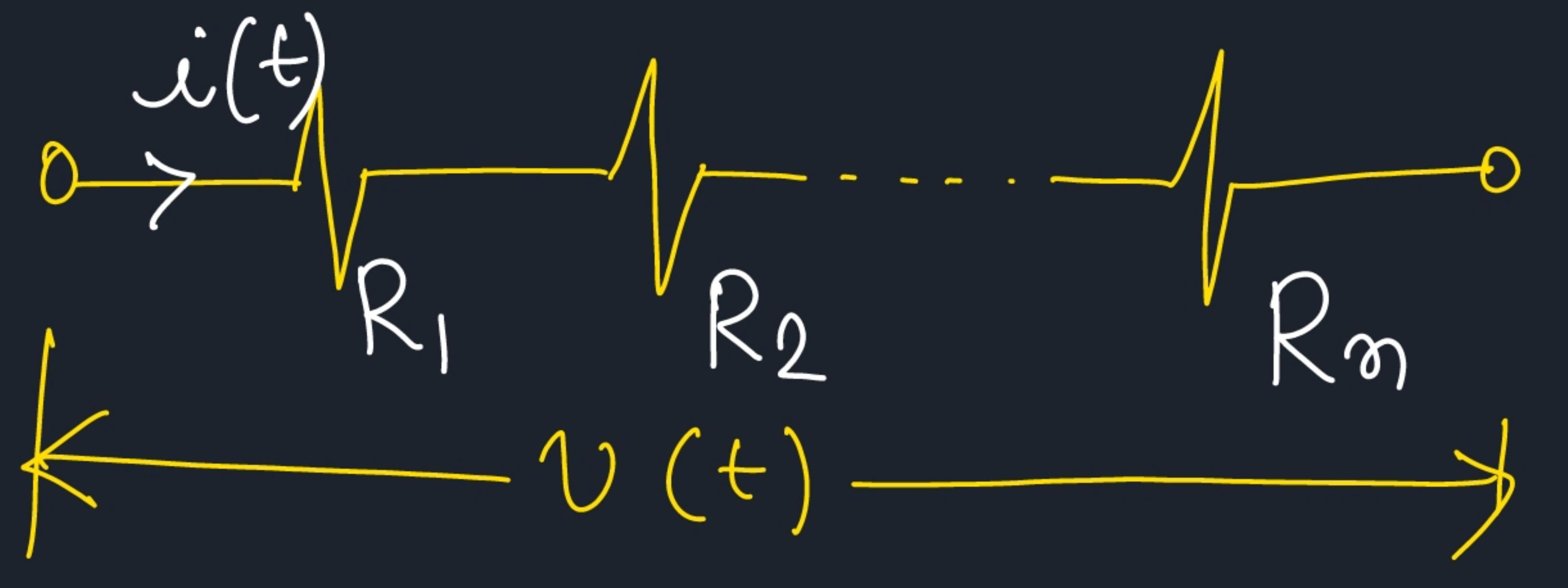
$$R = \frac{\rho l}{A}$$
$$A = \pi \left(R_{ext}^2 - R_{int}^2 \right) = ?$$
$$= 20.1038 \times 10^{-6} \Omega$$



$$\begin{aligned}
 V(t) &= V_1(t) + V_2(t) + \dots + V_n(t) \\
 &= i(t) R_1 + i(t) R_2 + \dots + i(t) R_n \\
 &= \left(\sum_{j=1}^n R_j \right) i(t)
 \end{aligned}$$


$\Rightarrow R_{\text{Req}}$

$$\begin{aligned}
 V_1(t) : V_2(t) : \dots : V_n(t) \\
 = R_1 : R_2 : \dots : R_n
 \end{aligned}$$

$$V_m(t) = \frac{R_m}{\sum_{j=1}^n R_j} V(t) \quad \checkmark$$

$$\begin{aligned}
 P_1(t) : P_2(t) : \dots : P_n(t) \\
 = R_1 : R_2 : \dots : R_n
 \end{aligned}$$
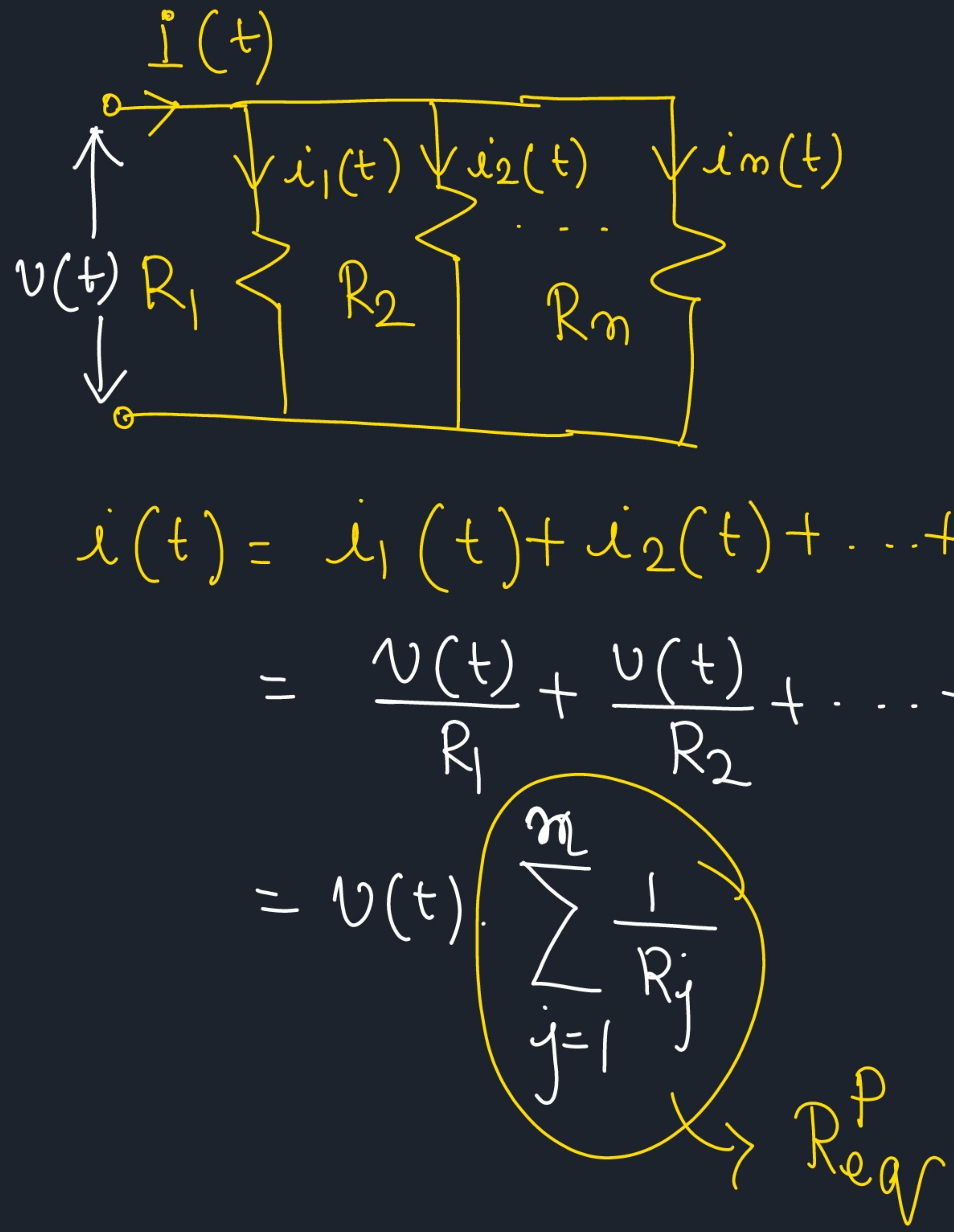
$$P_m(t) = \frac{R_m}{\sum_{j=1}^n R_j} P(t)$$








$$i_1(t) : i_2(t) \dots : i_n(t) = G_1 : G_2 \dots : G_n$$

$$i_m(t) = \frac{G_m}{\sum_{j=1}^n G_j} i(t)$$


$$p_1(t) : p_2(t) \dots : p_n(t) = G_1 : G_2 \dots : G_n$$
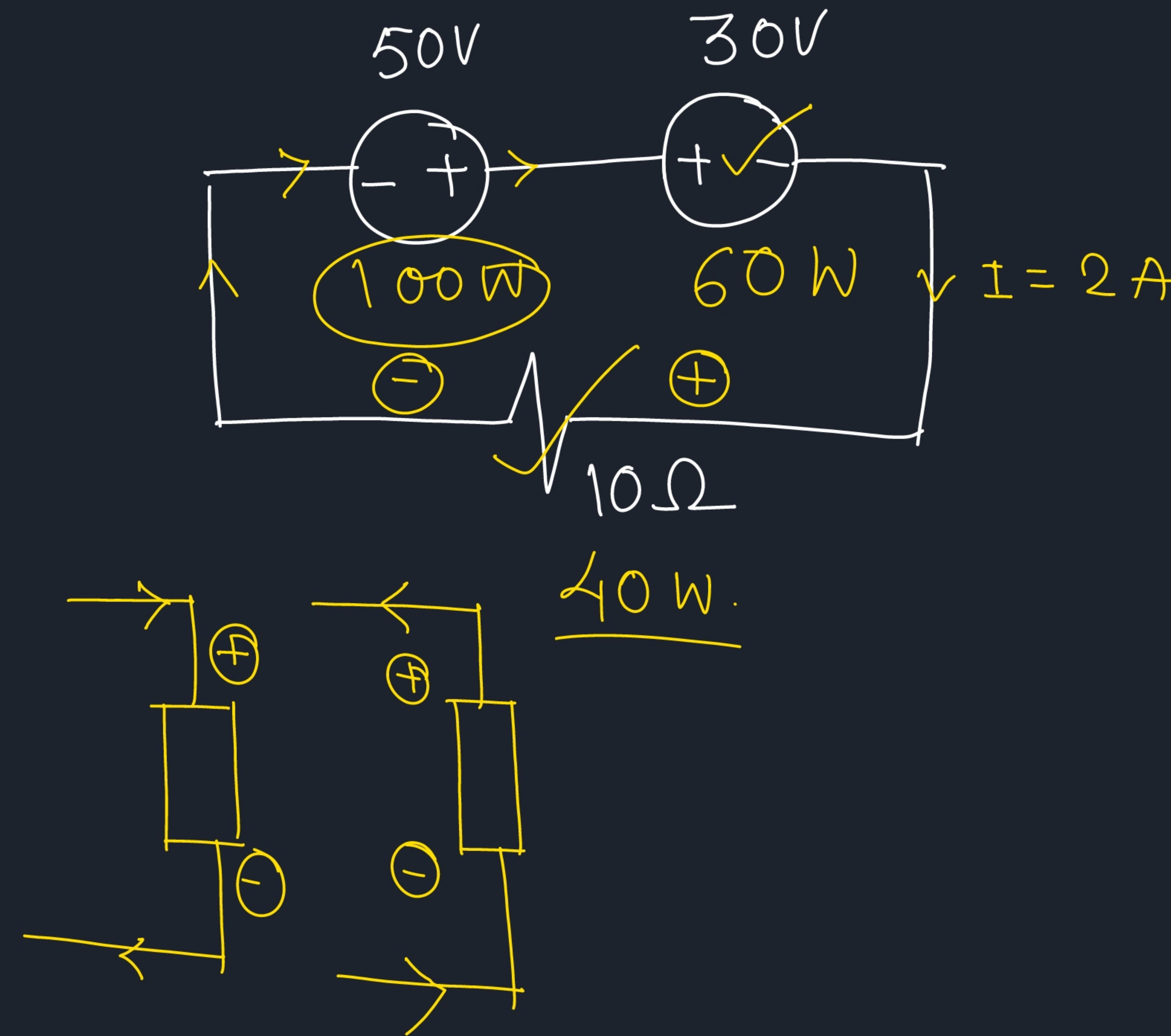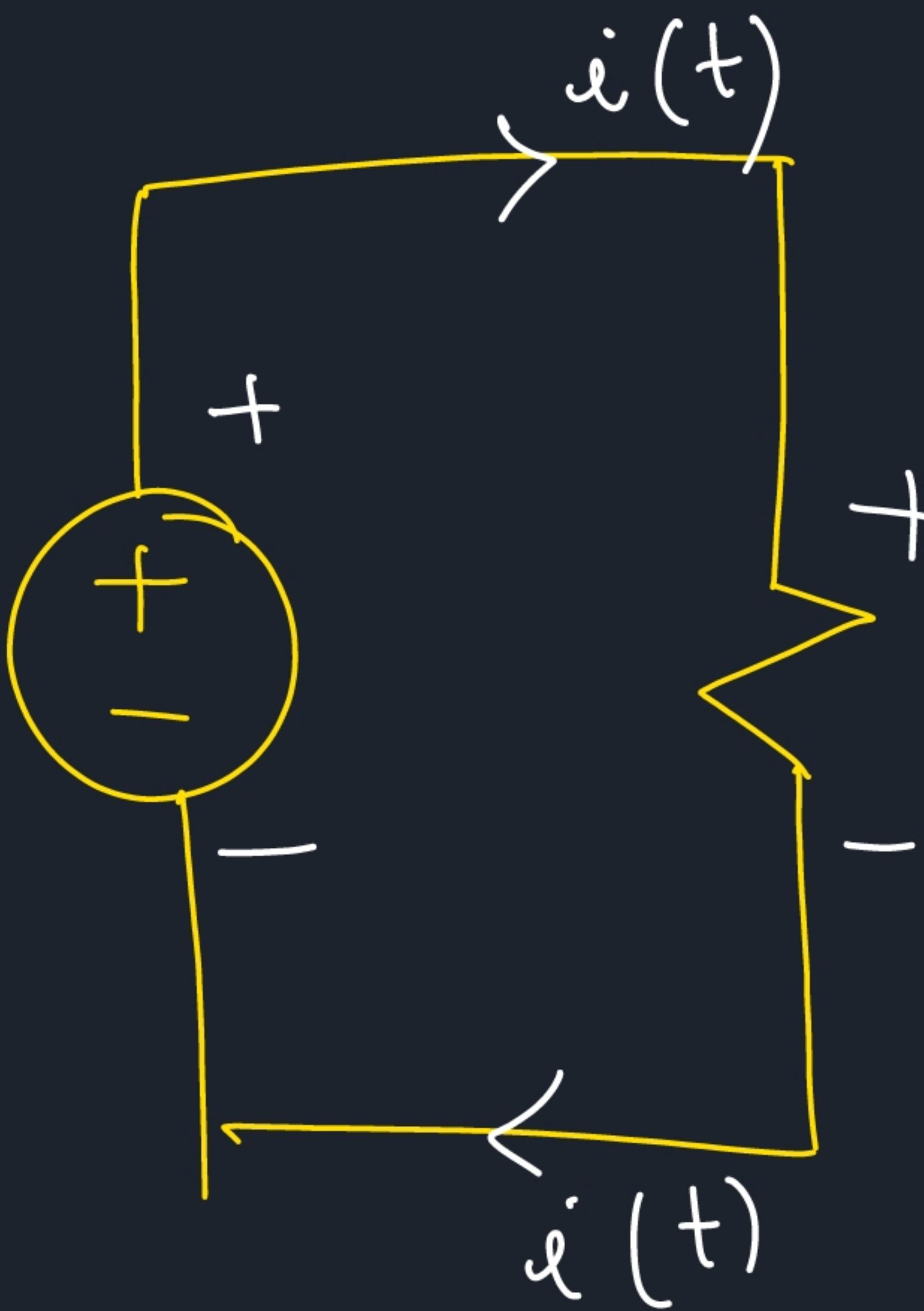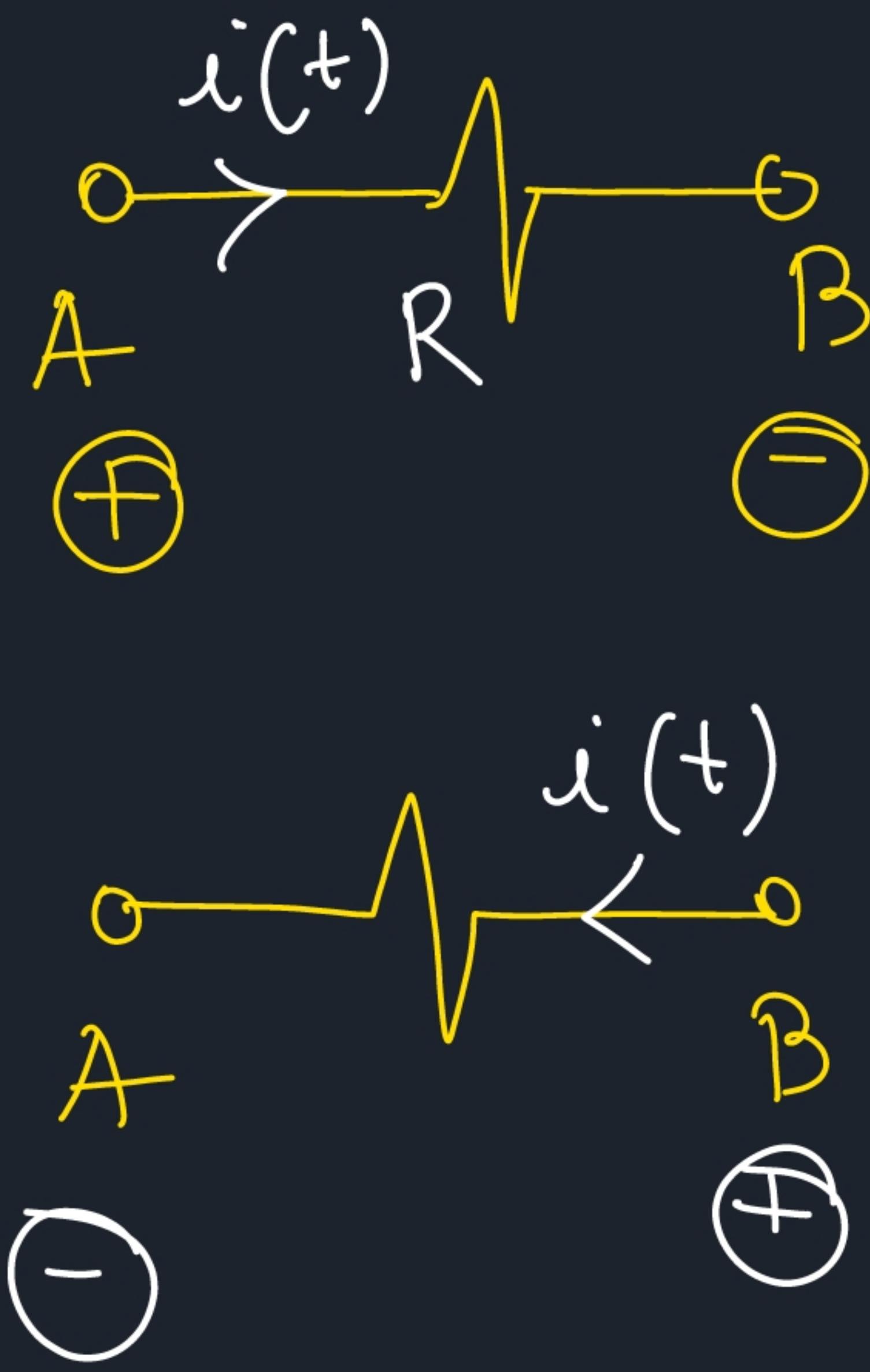
$$p_m(t) = \frac{G_m}{\sum_{j=1}^n G_j} p(t)$$





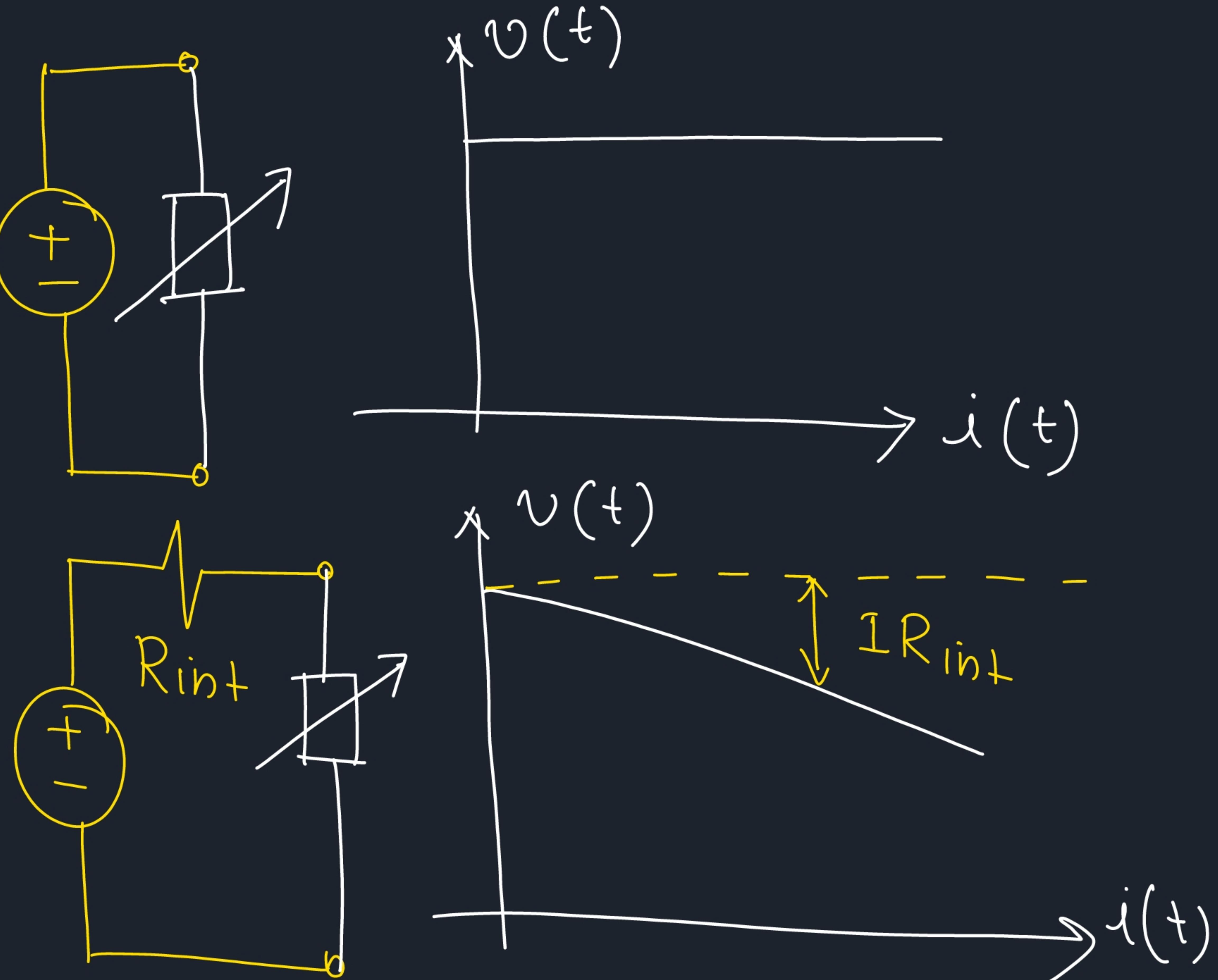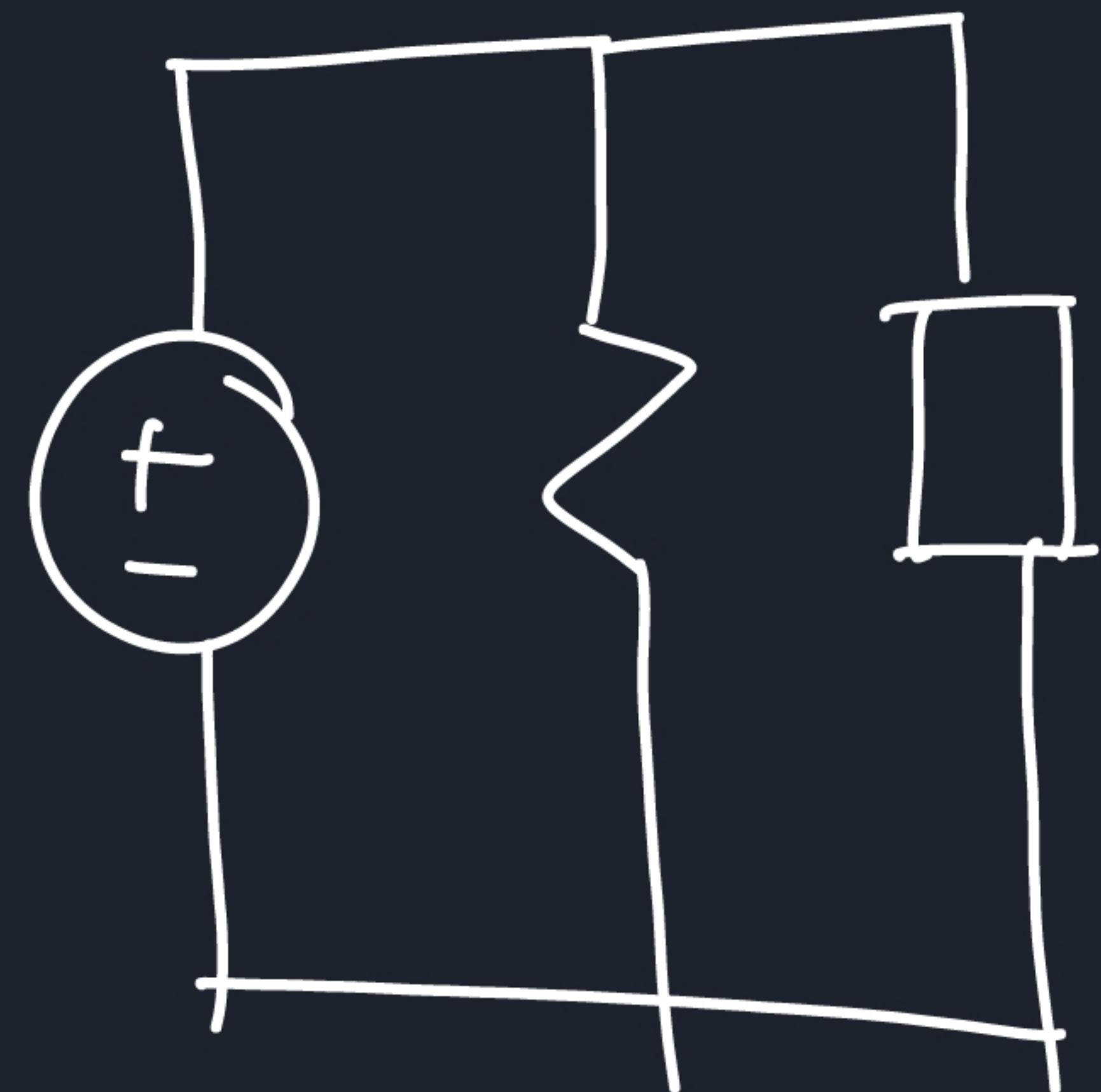


 Current Source:-

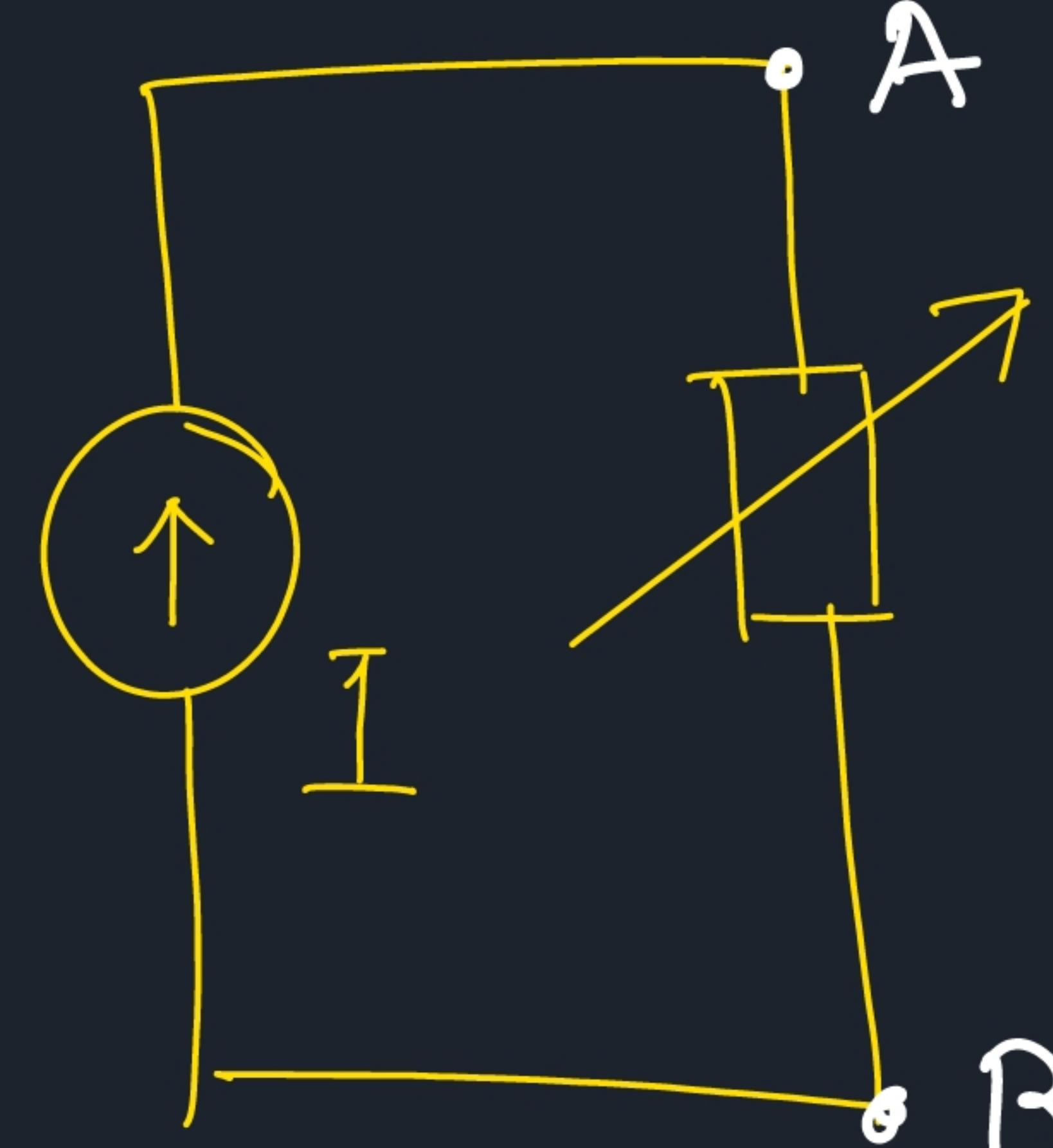


Ideal Current Source.

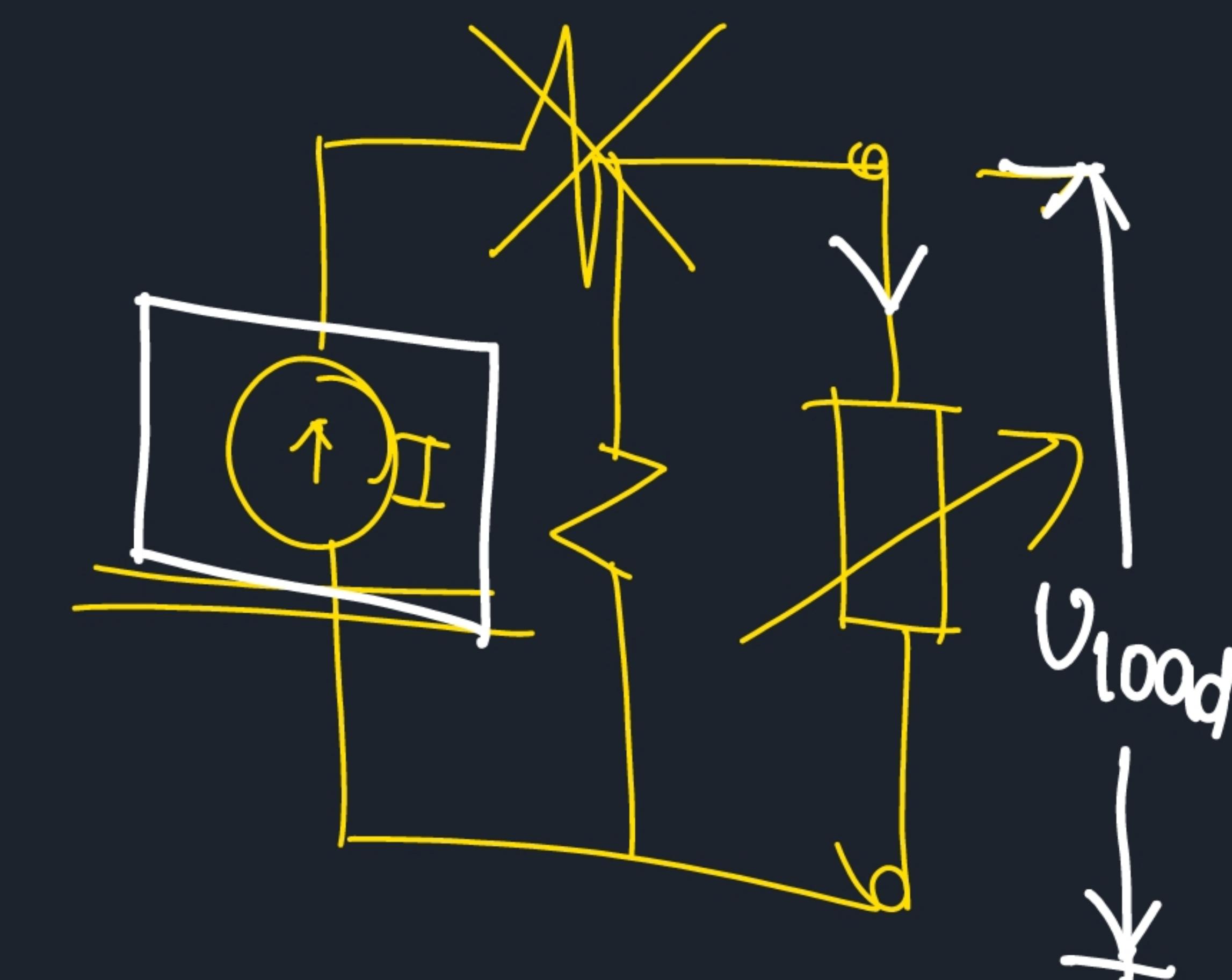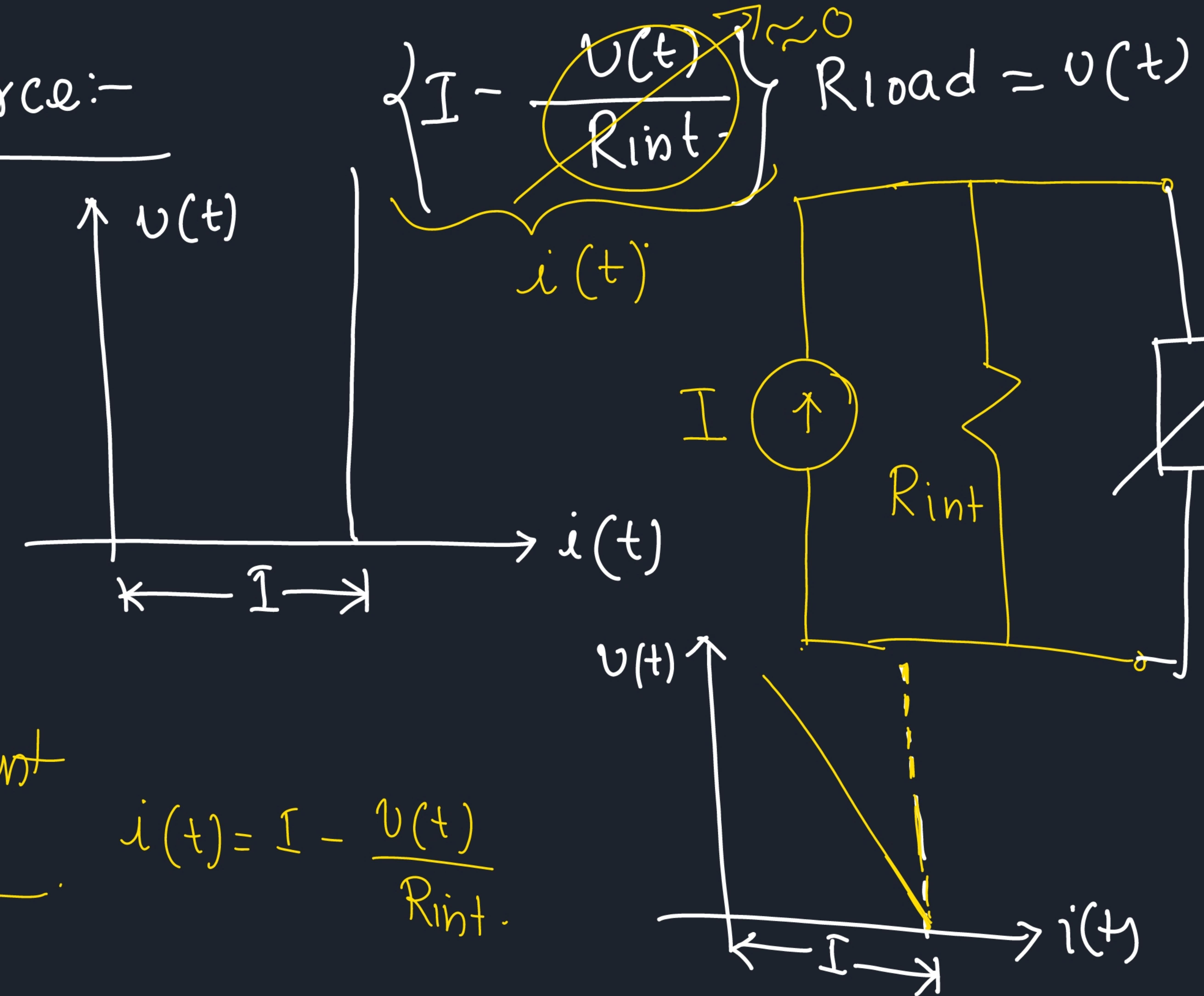

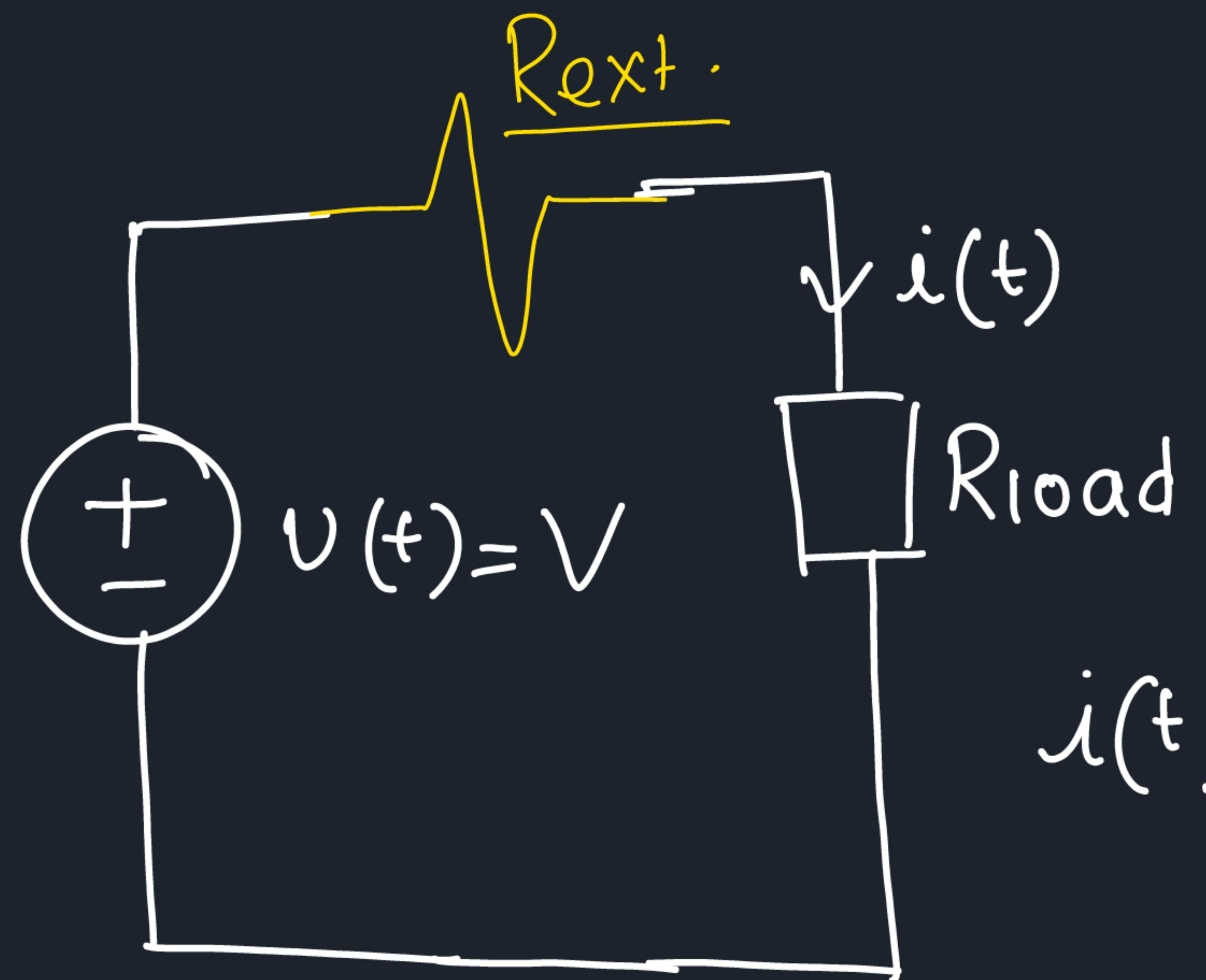


$$i(t) = \frac{V(t)}{R_{load} + R_{ext}}$$

$R_{ext} \gg R_{load}$


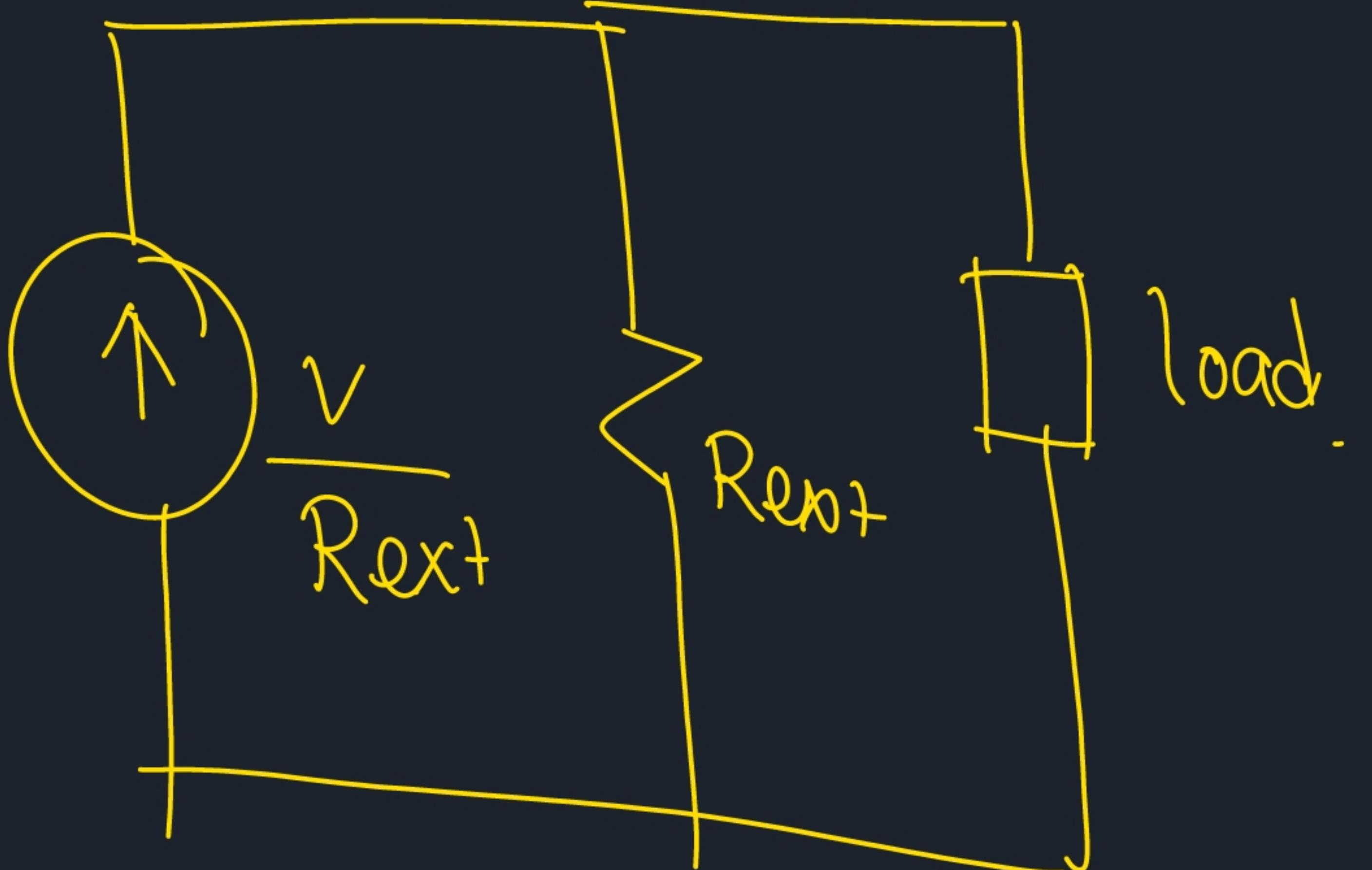


∴


Source Transformation:-

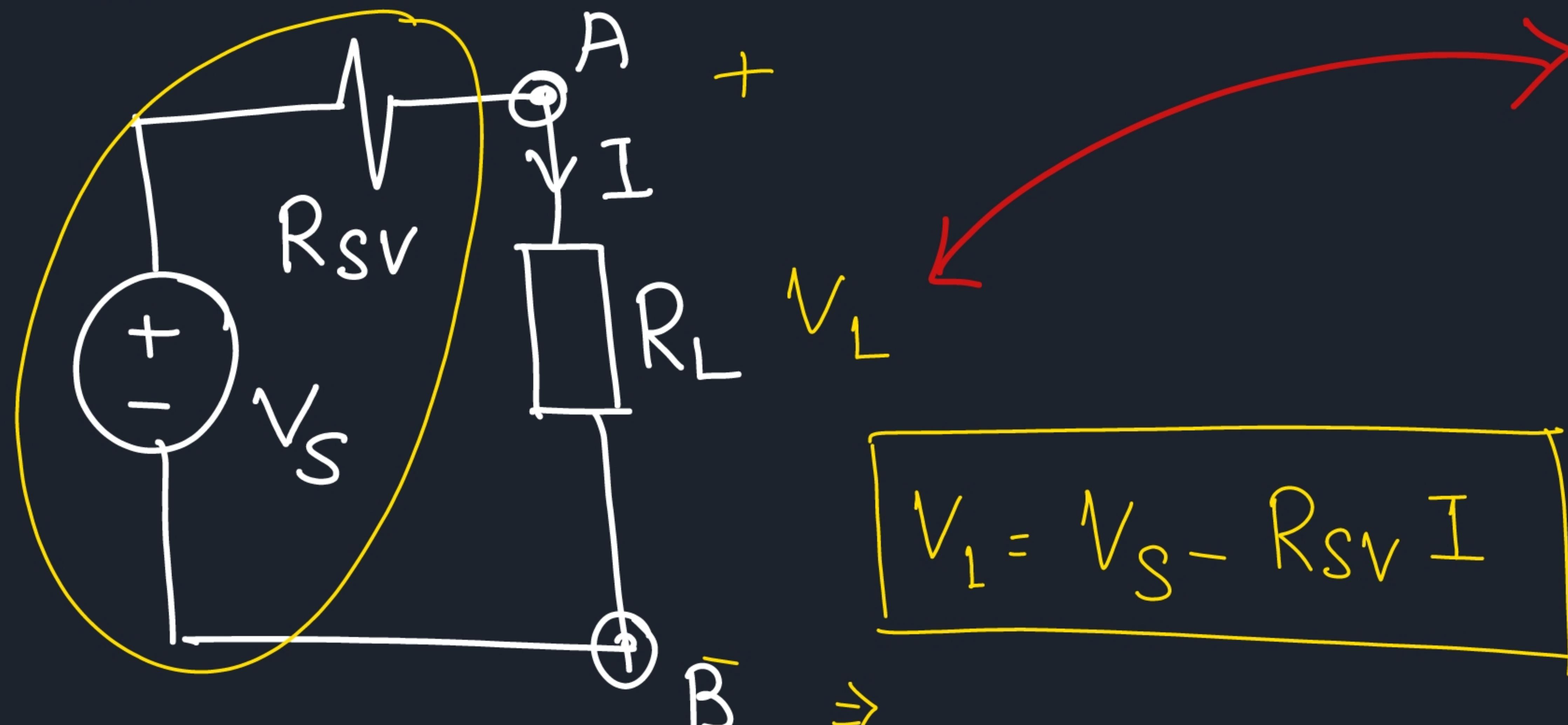


$$V_L = V_s - R_{SV} I$$

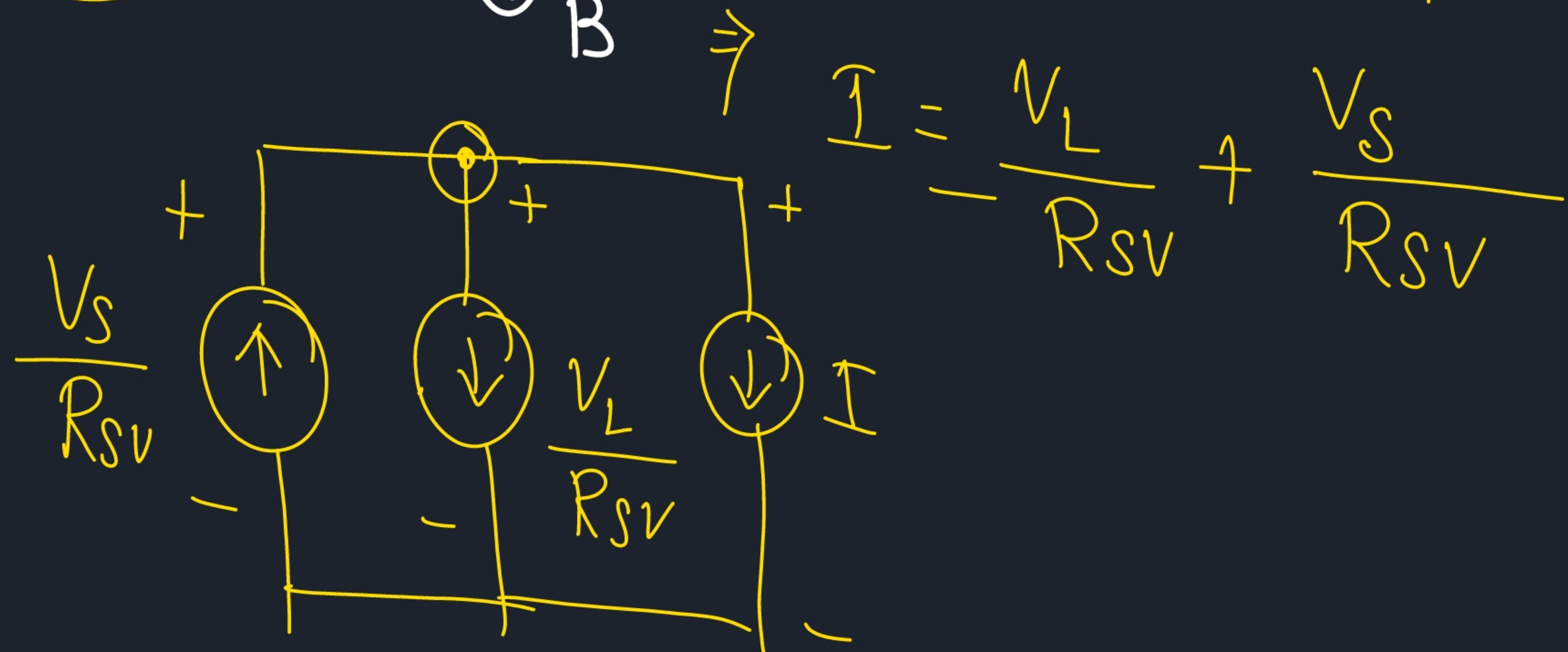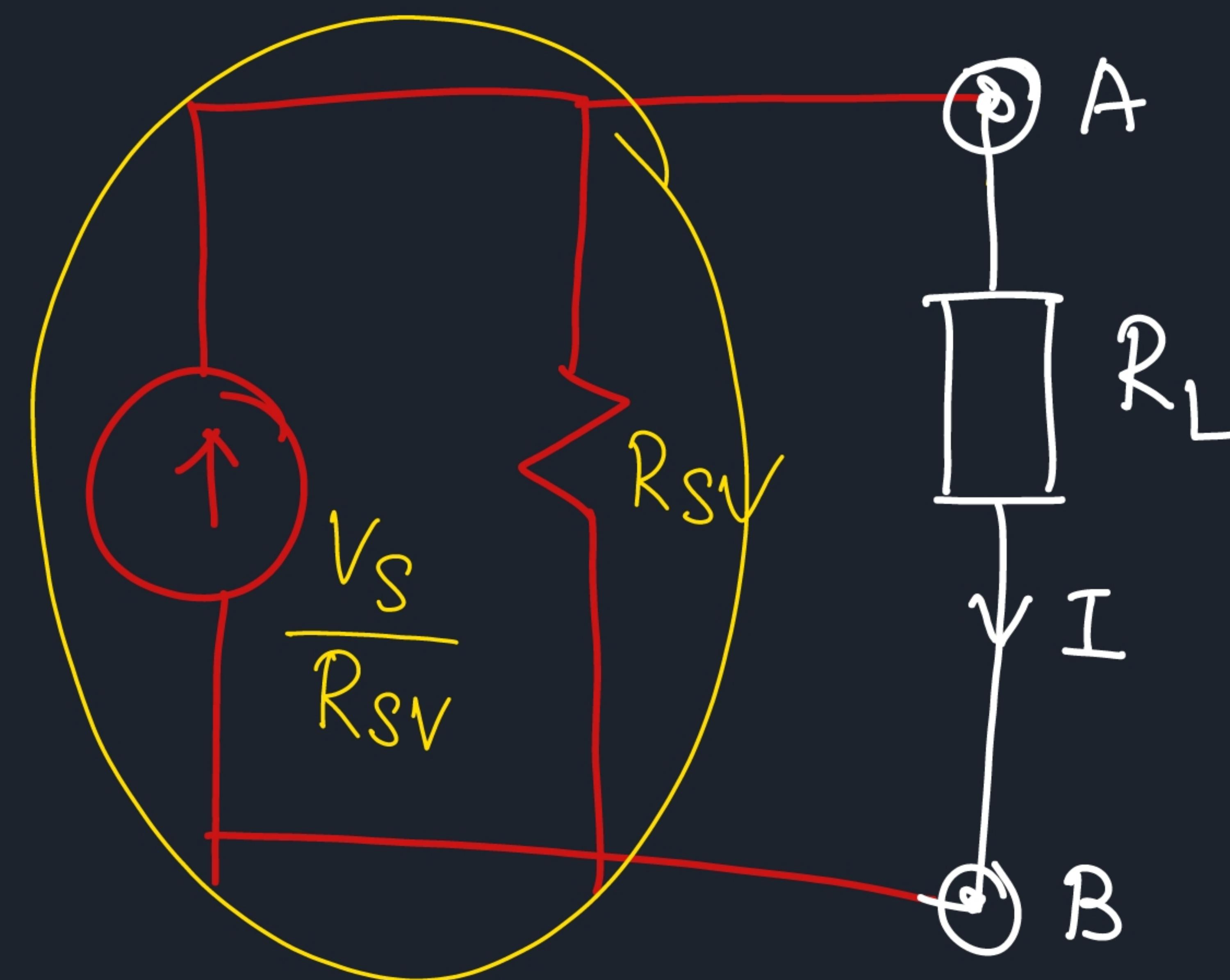


 Problem :-

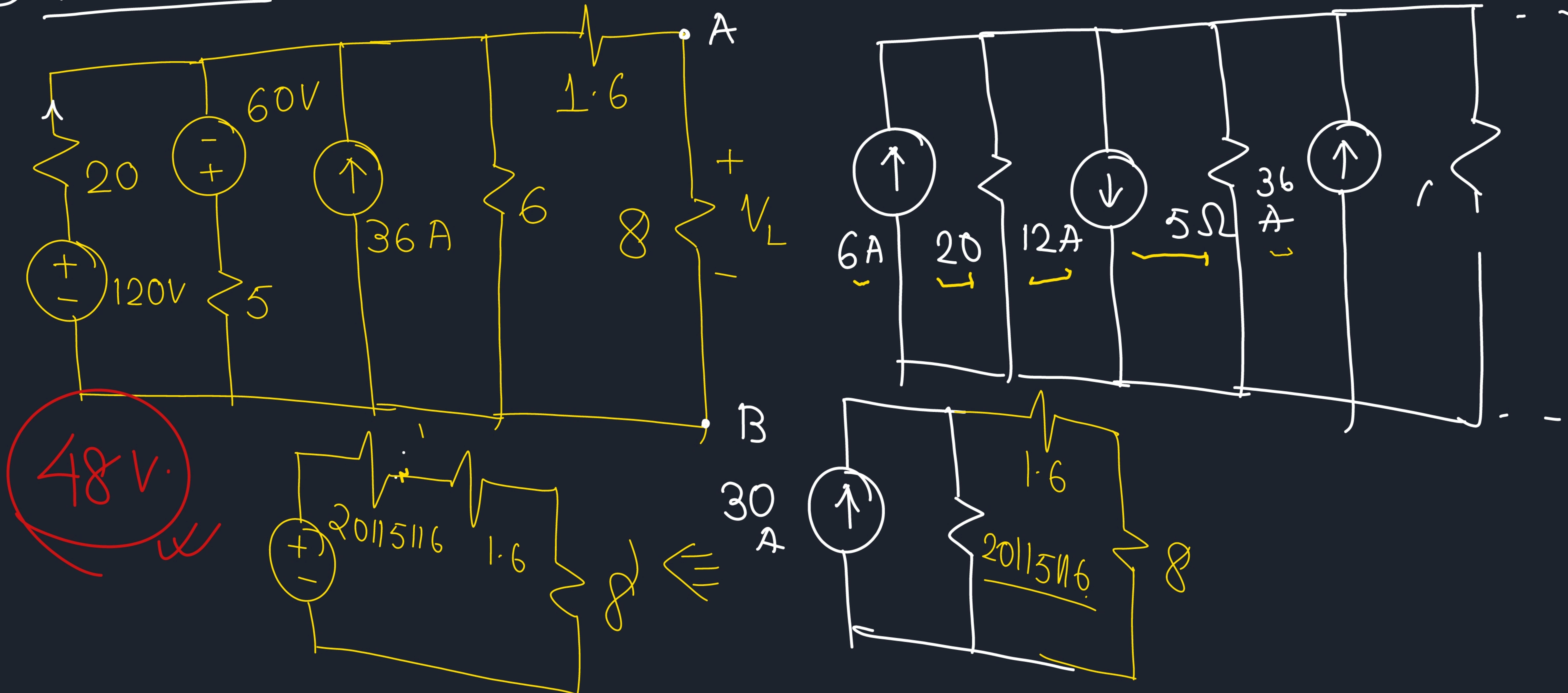


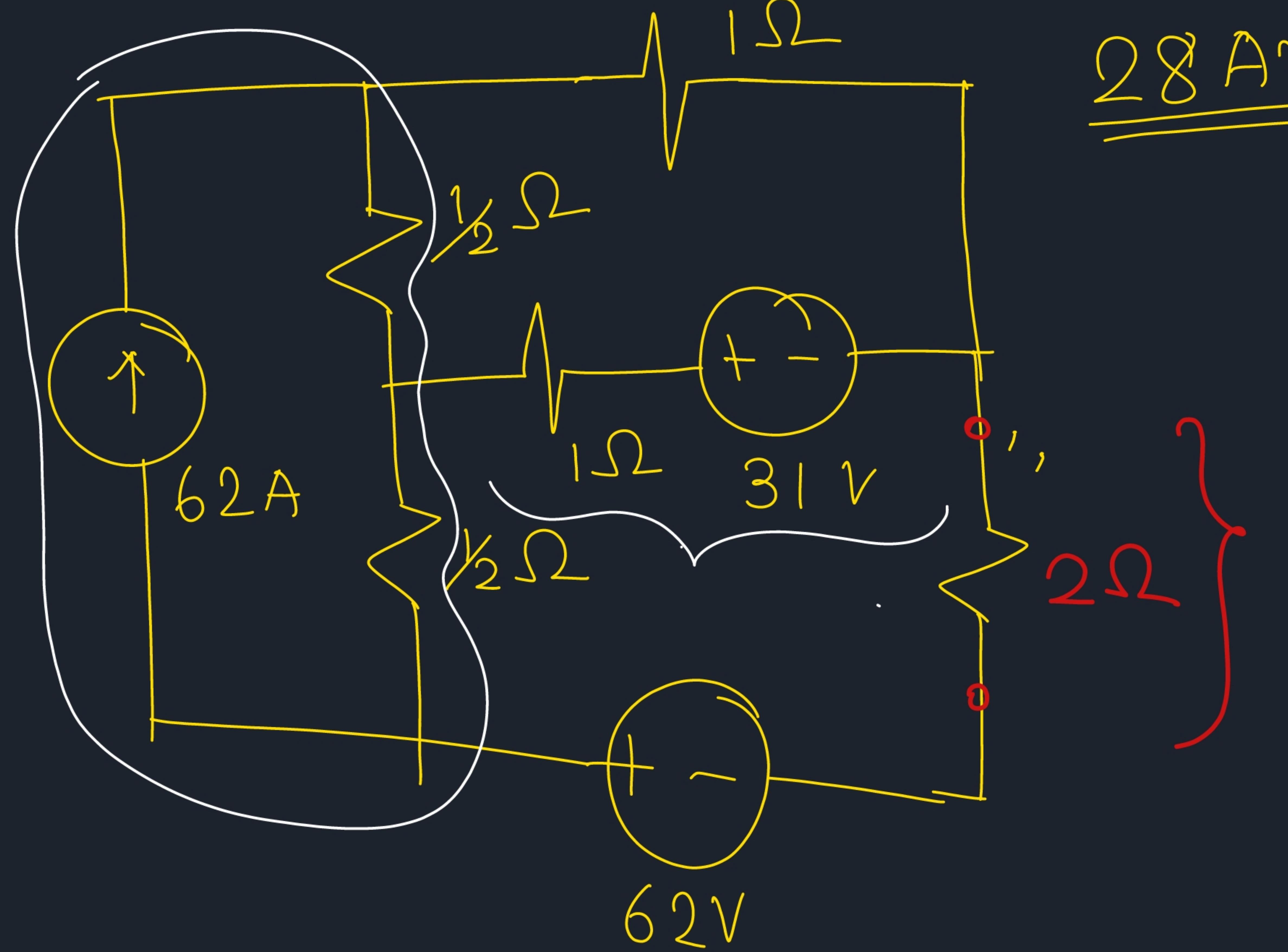


28 Amps.

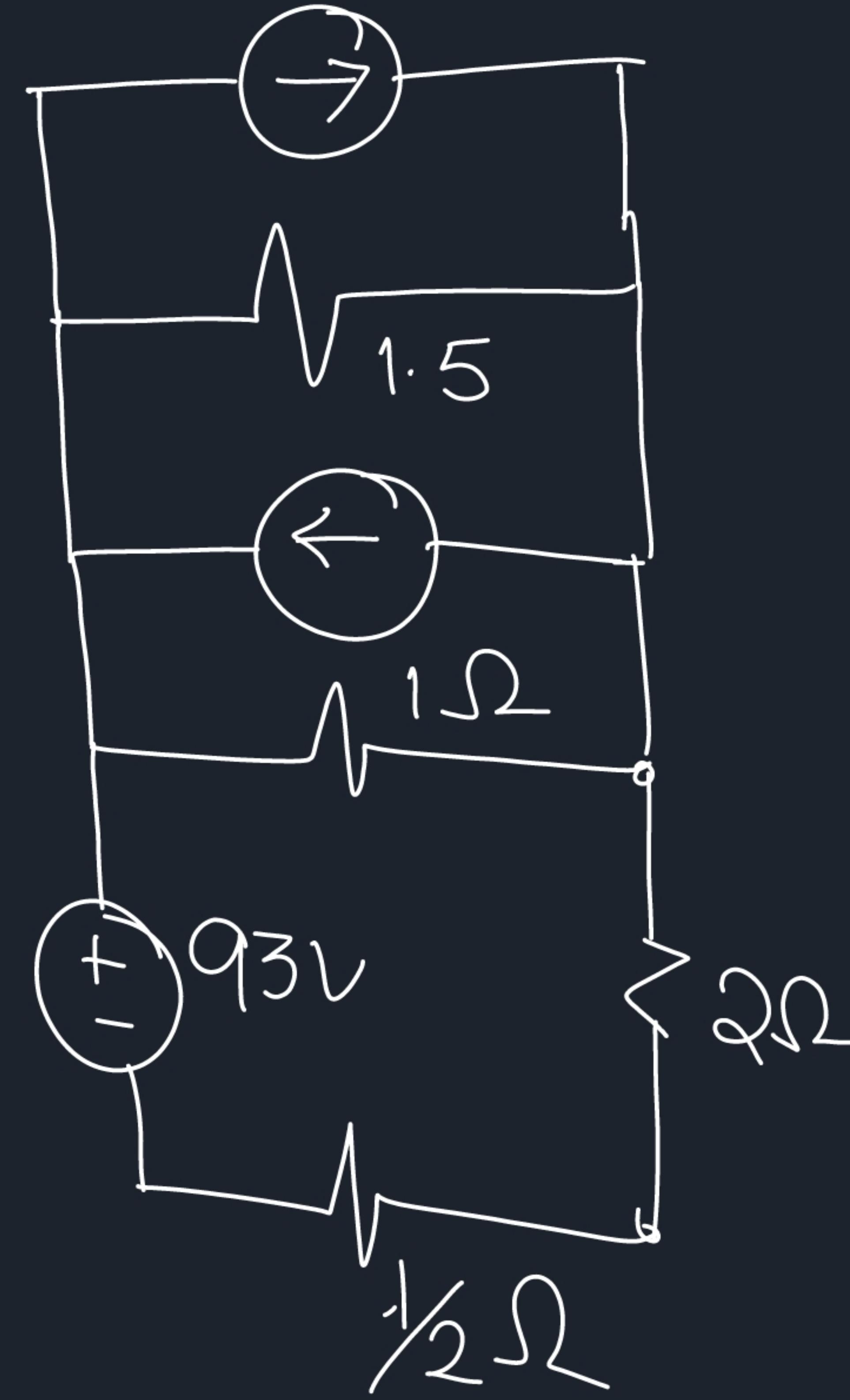

7546

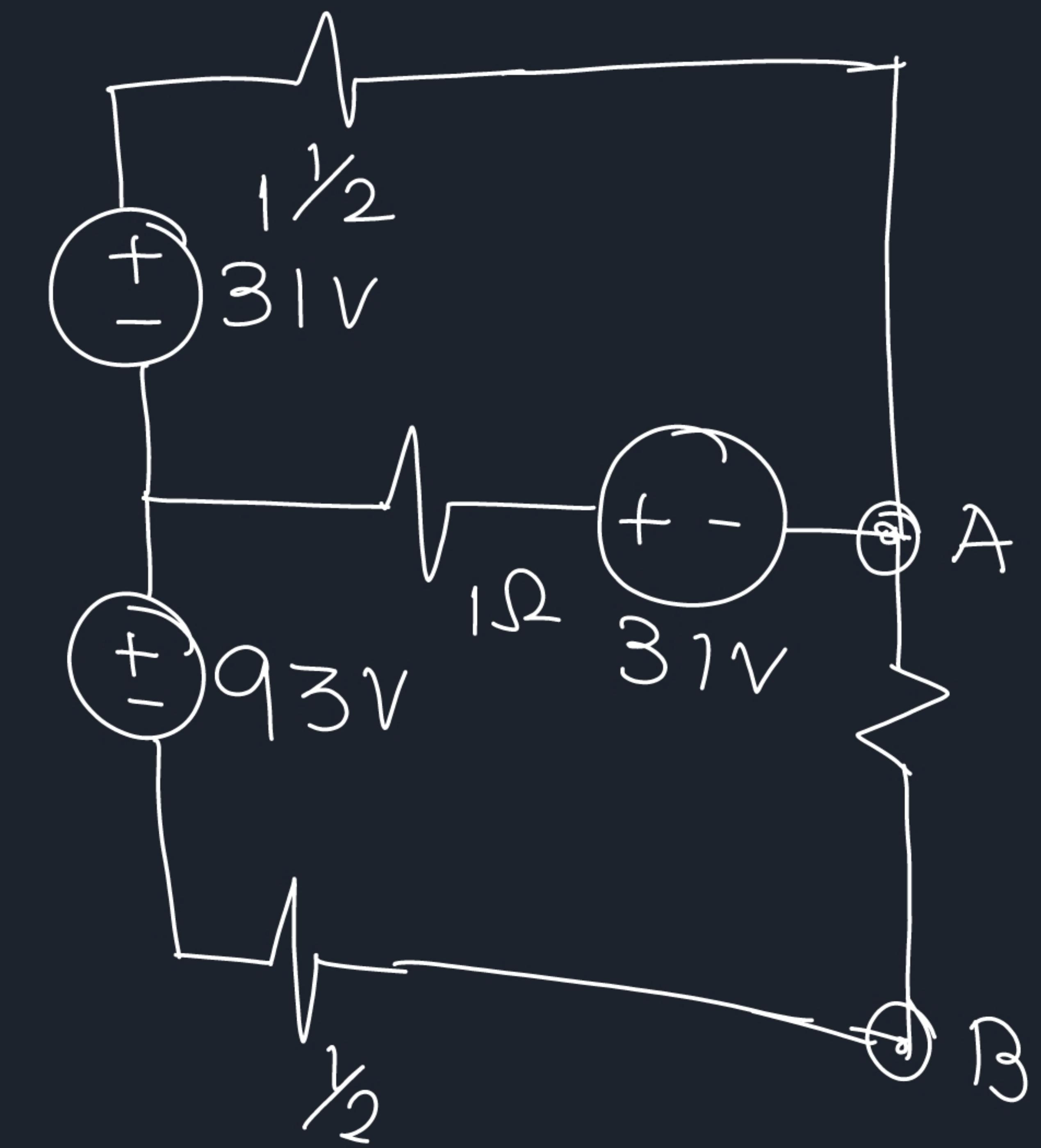

 Inductor :-

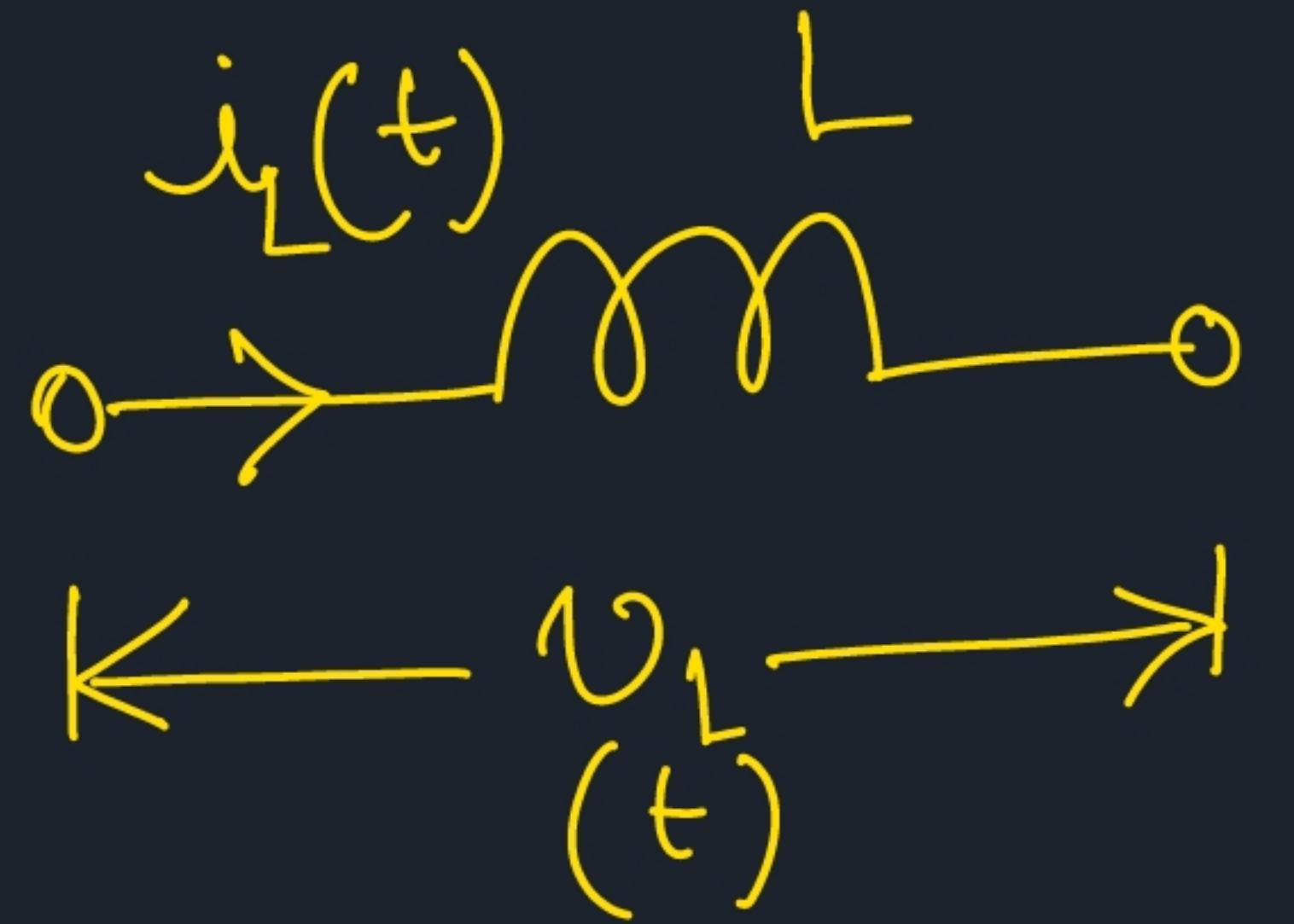

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t) dt = \underbrace{\frac{1}{L} \int_{-\infty}^0 v_L(t) dt}_{I_0} + \frac{1}{L} \int_0^t v_L(t) dt$$


$$i_L(t) = I_0 + \frac{1}{L} \int_0^t v_L(t) dt \xrightarrow{\text{Area of } v_L(t) \text{ plot}} \underline{\underline{\text{Volt-Sec.}}}$$

$$\boxed{N\phi = LI}$$

ψ = flux linkage

$$V = -N \frac{d\phi}{dt}$$

$$= -L \frac{di}{dt}$$

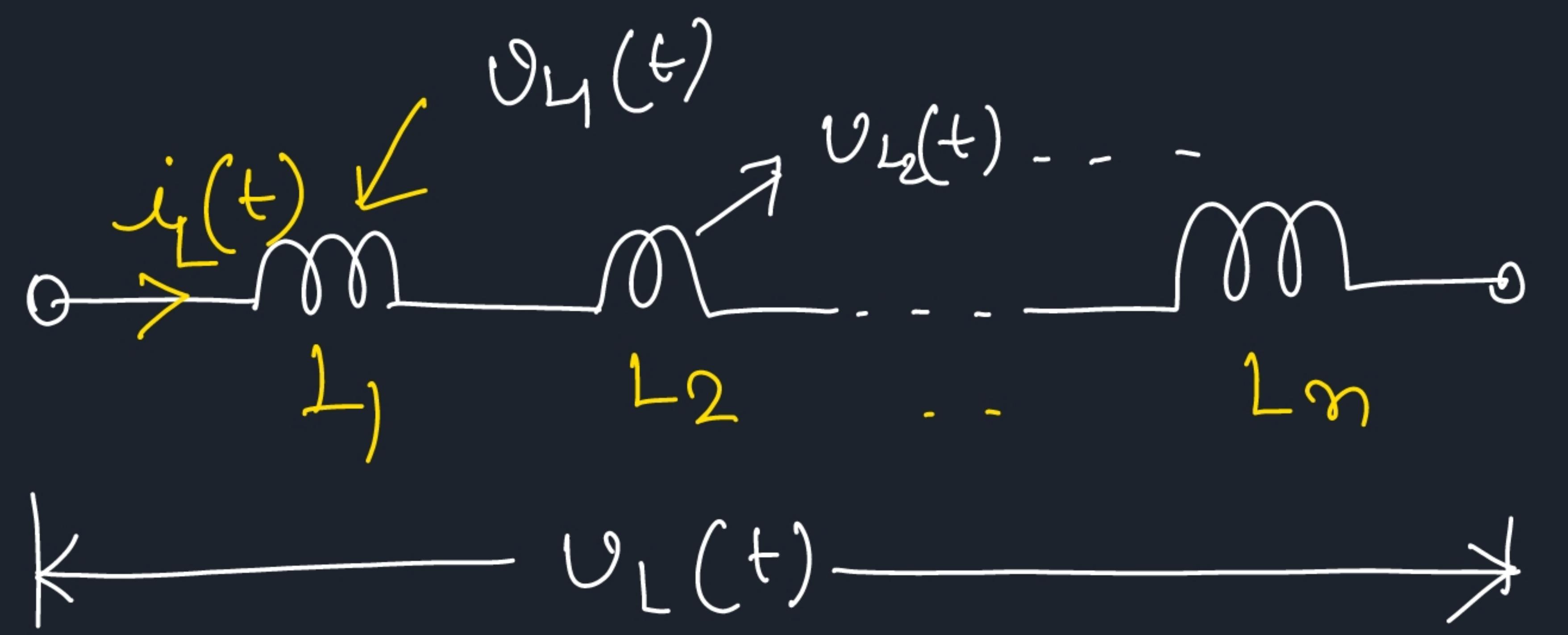

$$V_{L1}(t) : V_{L2}(t) : \dots : V_{Lm}(t) \\ = L_1 : L_2 : \dots : L_m$$

$$V_L(t) = V_{L1}(t) + V_{L2}(t) + \dots + V_{Lm}(t)$$

$$= L_1 \frac{di_L(t)}{dt} + L_2 \frac{di_L(t)}{dt} + \dots + L_m \frac{di_L(t)}{dt}$$

$$= L_{eq} \frac{di_L(t)}{dt}$$

$$V_{Lm} = \frac{L_m}{\sum_{j=1}^n L_j} V_L(t)$$

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}}$$

Capacitor :-



$$V_C(t) = V_C(0) + \frac{1}{C} \int_0^t i_C(t) dt$$

$$i_C(t) = C \frac{dV_C(t)}{dt}$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(t) dt = \frac{1}{C} \int_{-\infty}^0 i_C(t) dt + \frac{1}{C} \int_0^t i_C(t) dt$$

$\underbrace{\qquad\qquad}_{\text{→ Amp-Solc.}}$

$V_C(0)$

$$C_{eq}^S = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

$$C_{eq}^P = C_1 + C_2 + \dots + C_n$$

$$V_R(t) = R i_R(t)$$

$$V_L(t) = L \frac{di_L(t)}{dt}$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(t) dt$$

Linear & Nonlinear Element.

$$y = mx$$

$$\left. \begin{array}{l} i_{R1}(t) \\ \downarrow \\ V_{R1}(t) \end{array} \right\} \quad \left. \begin{array}{l} i_{R2}(t) \\ \downarrow \\ V_{R2}(t) \end{array} \right\} \quad \left. \begin{array}{l} a i_R(t) \\ \downarrow \\ a V_R(t) \end{array} \right\}$$

1. Additivity
2. Homogeneity } \Rightarrow Superposition

$$\begin{aligned} y &= f(x) \\ y_1 &= f(x_1) \\ y_2 &= f(x_2) \end{aligned} \quad \begin{aligned} y_1 + y_2 &= f(x_1 + x_2) \\ ay &= f(ax) \end{aligned}$$

$$y = mx + c.$$

x_1, x_2 Non linear





$$\begin{aligned} & ax_1 \\ & ay_1 \end{aligned} \quad \boxed{v_L(t) = L \frac{di_L(t)}{dt}}$$


$$i_L(t) = \left(I_0 + \int_0^t v_L(t) dt \right)$$

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$i_C(t) = C \frac{dw_C(t)}{dt}$$

Dependent & Independent :- (Sources)

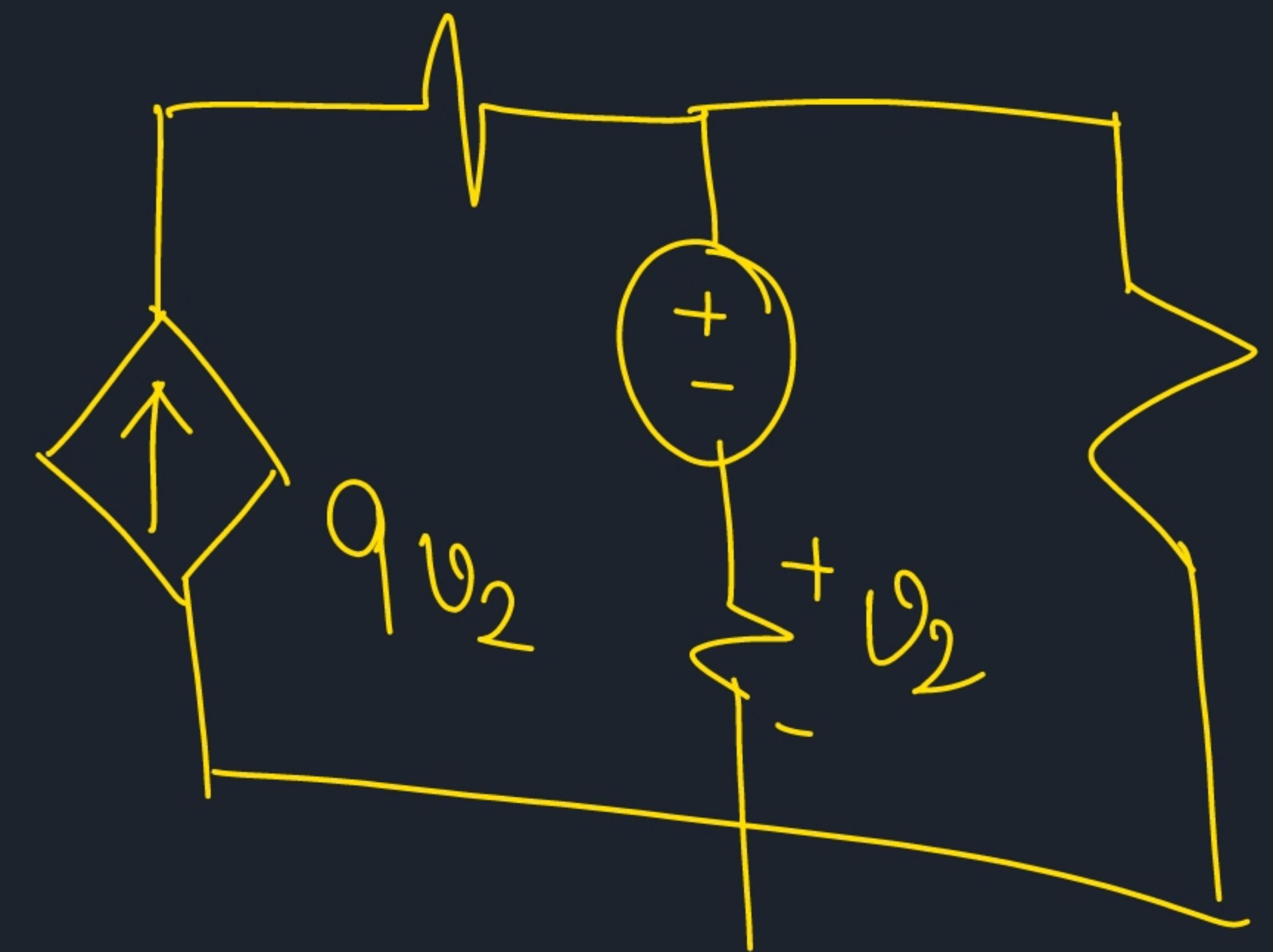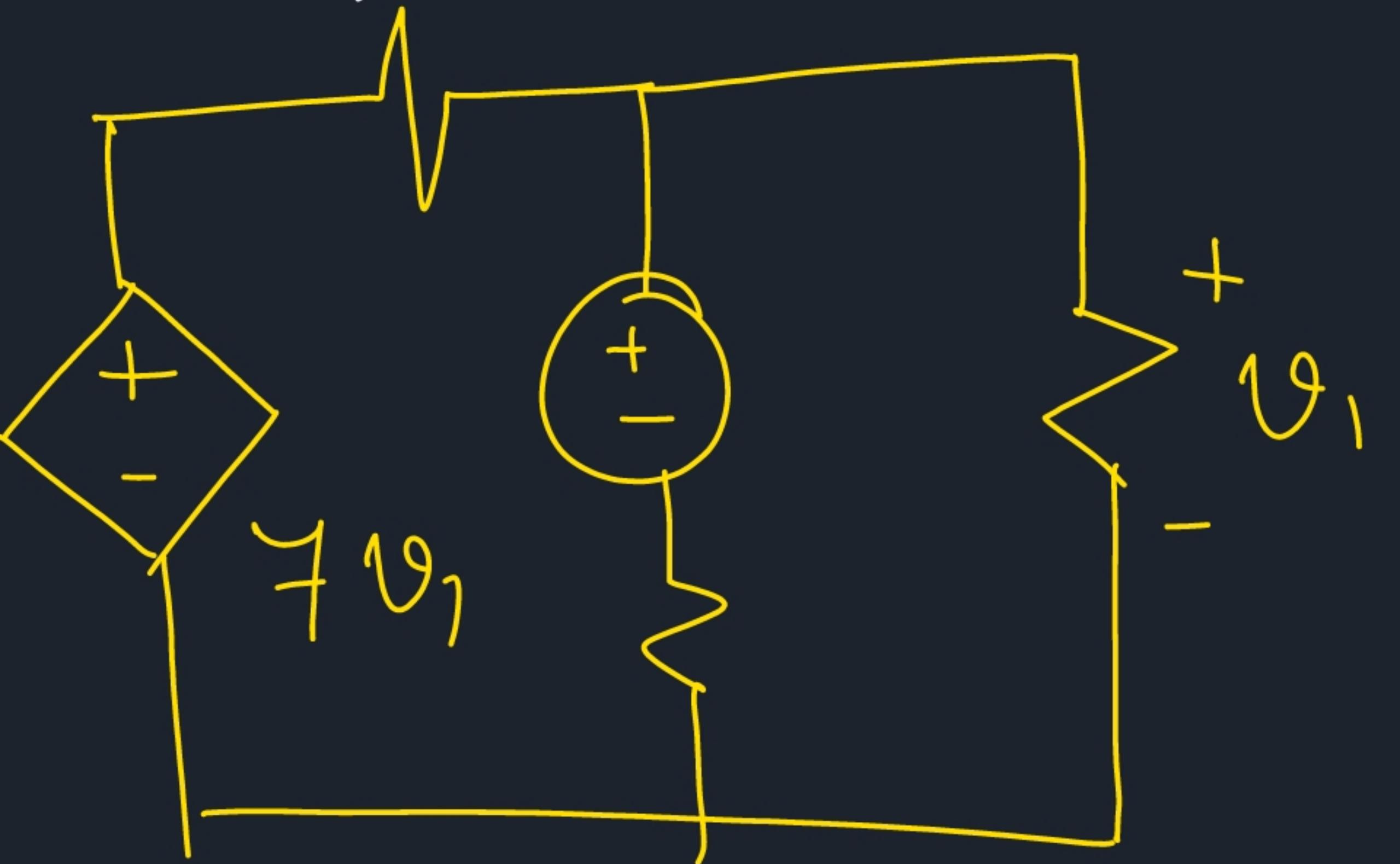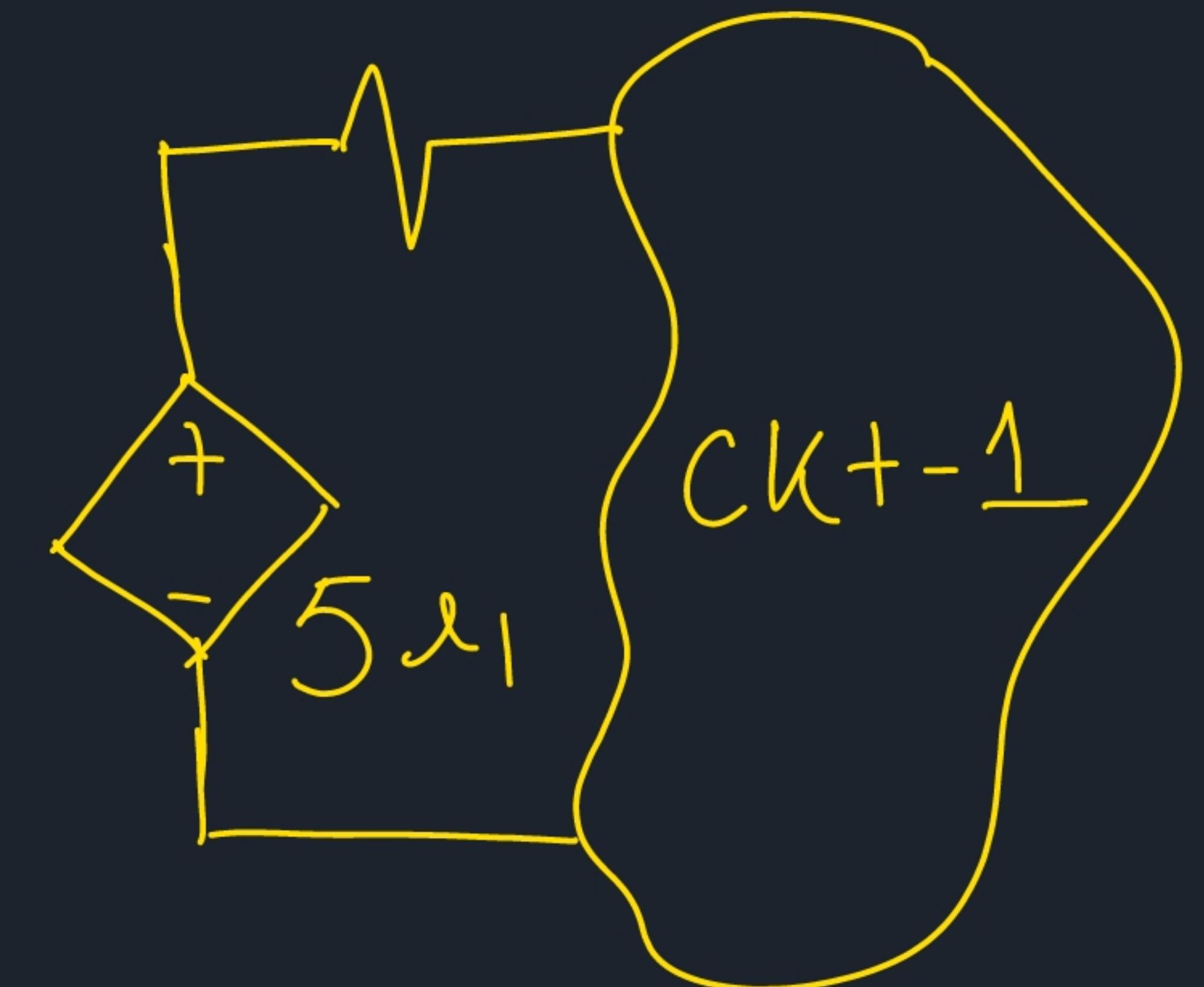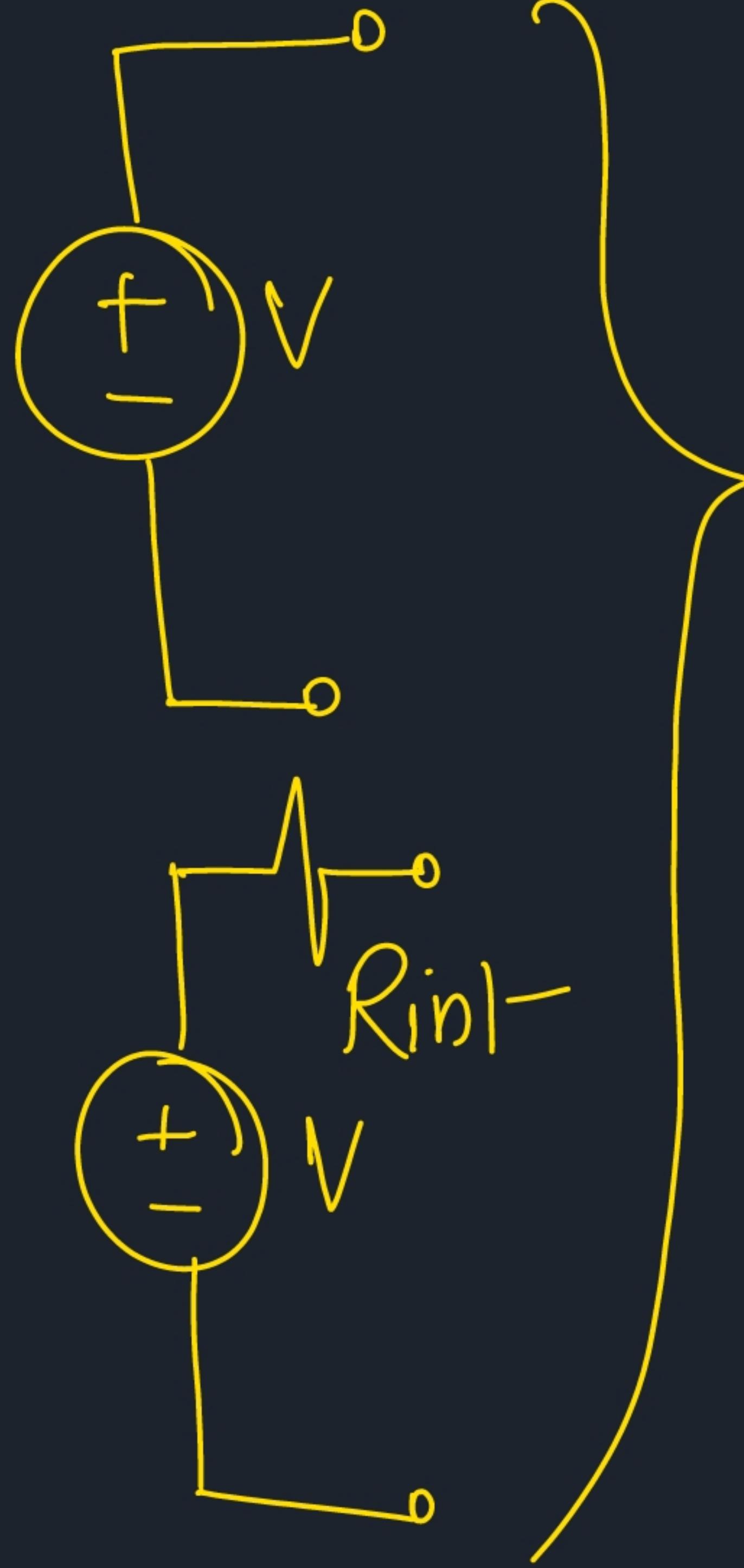

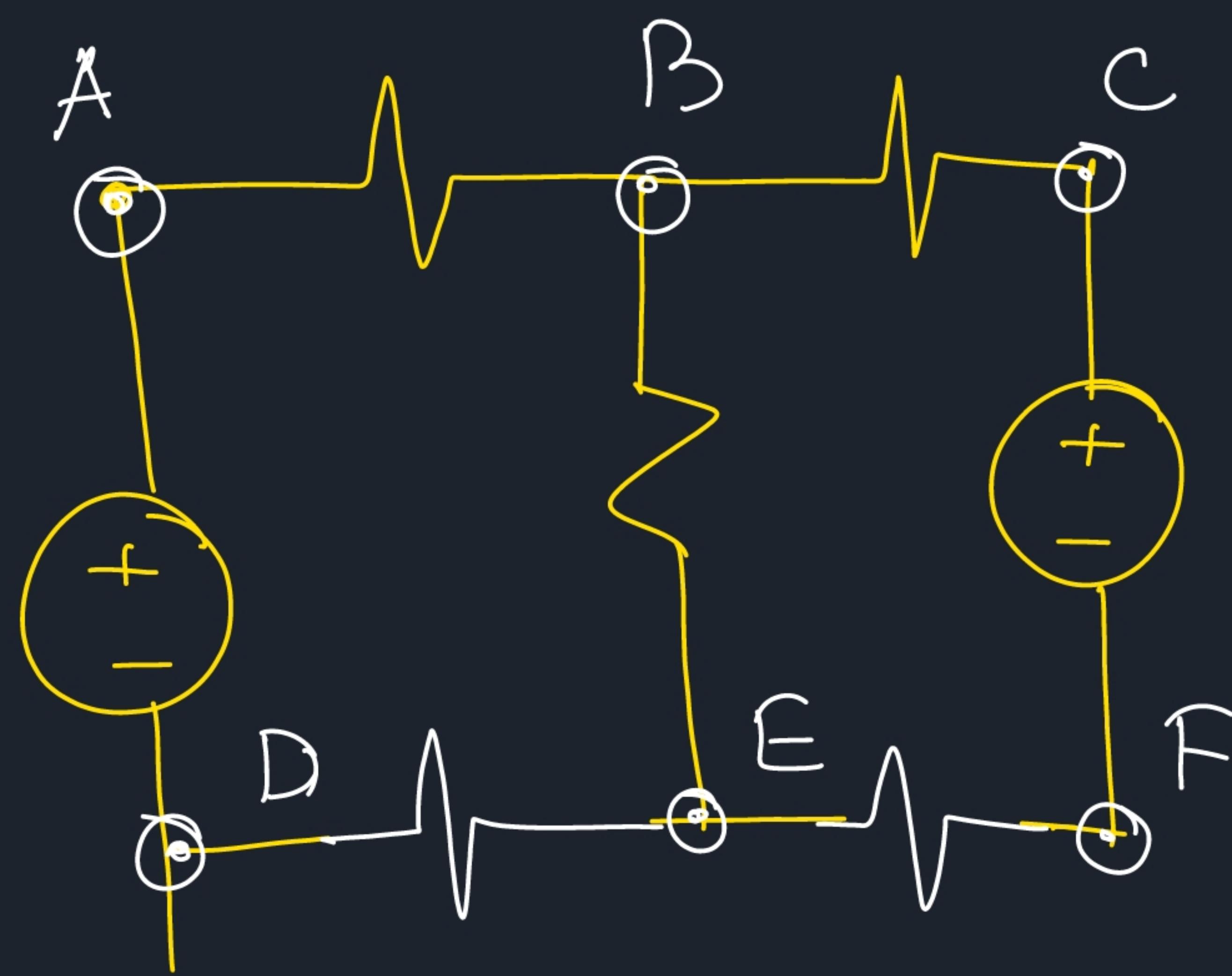

NODE

JUNCTION \Rightarrow B, E

BRANCH \Rightarrow

LOOP \Rightarrow MESH \Rightarrow

NETWORK ANALYSIS.

DIRECT

MESH ANALYSIS

NODAL "

SUPERPOSITION


INDIRECT

THEVENIN'S

NORTON'S

$\text{Y}-\Delta$ Transform.

MESH ANALYSIS:-

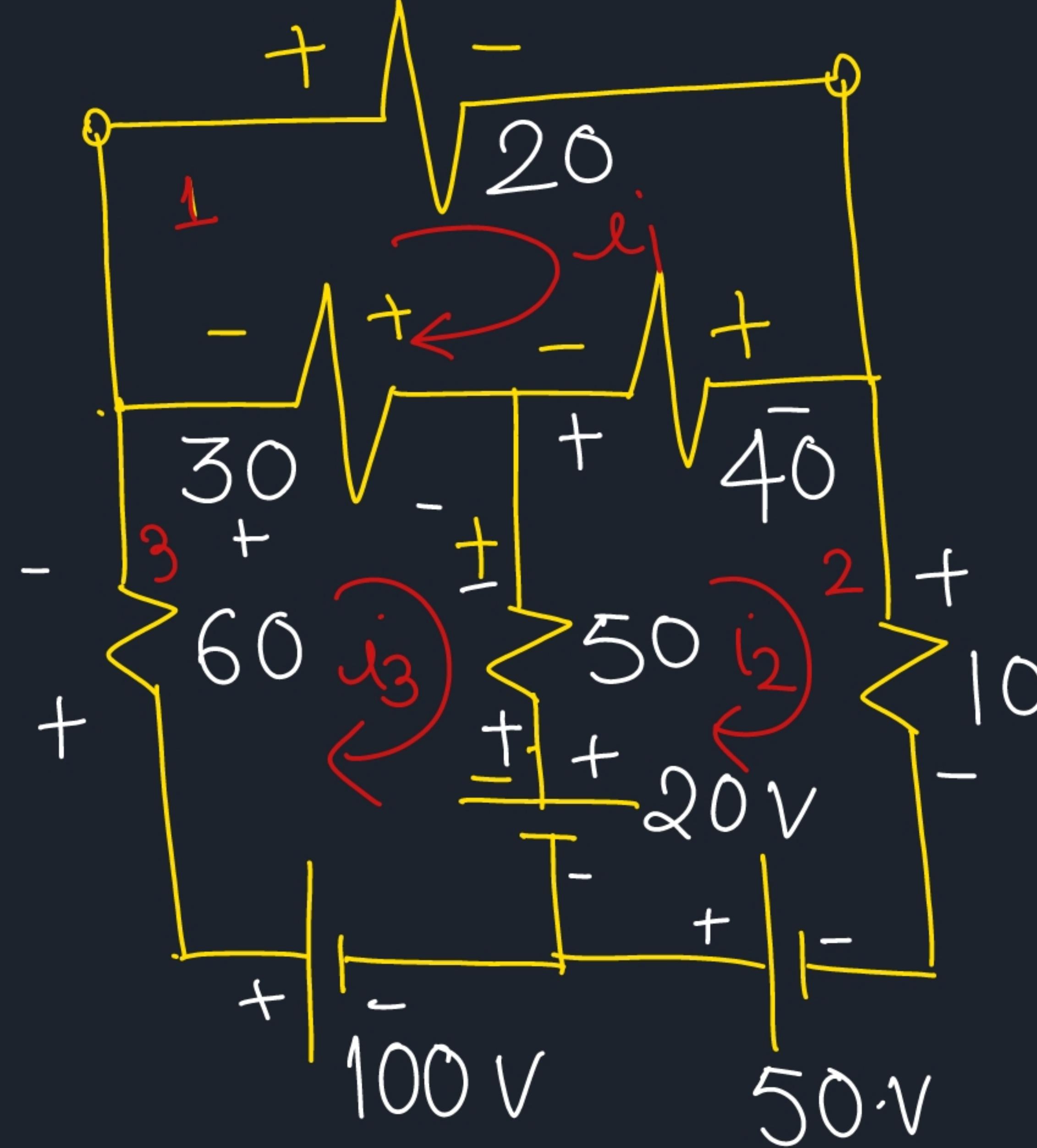

$$I = f(i_1, i_2, i_3)$$

MESH - 1

$$-20i_1 - 40(i_1 - i_2) - 30(i_1 - i_3) = 0$$

MESH - 2 $\Rightarrow i_1(20 + 40 + 30) - i_2(40) - i_3(30) = 0$

$$-40(i_2 - i_1) - 10i_2 + 50 + 20 - 50(i_2 - i_3) = 0 \quad \text{--- (ii)}$$

MESH - 3

$$-60i_3 - 30(i_3 - i_1) - 50(i_3 - i_2) - 20 + 100 = 0 \quad \text{--- (iii)}$$