


NORTON'S THEOREM

❖ Simplify the following circuit to find out the current flowing through 2 Ohm resistance.

❖ The mesh currents are as below

$$i_1 = \frac{3}{13}I_1 - \frac{1}{13}I_2 - \frac{2}{13}V_1$$
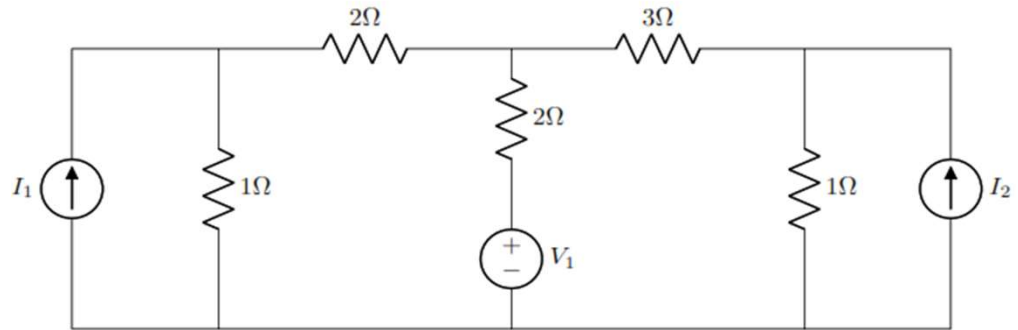
$$i_2 = \frac{1}{13}I_1 - \frac{5}{26}I_2 + \frac{3}{26}V_1$$




$$I_{2\Omega} = i_1 - i_2 = \frac{2}{13}I_1 + \frac{3}{26}I_2 - \frac{7}{26}V_1$$

NORTON'S THEOREM

In this circuit the current can be represented as
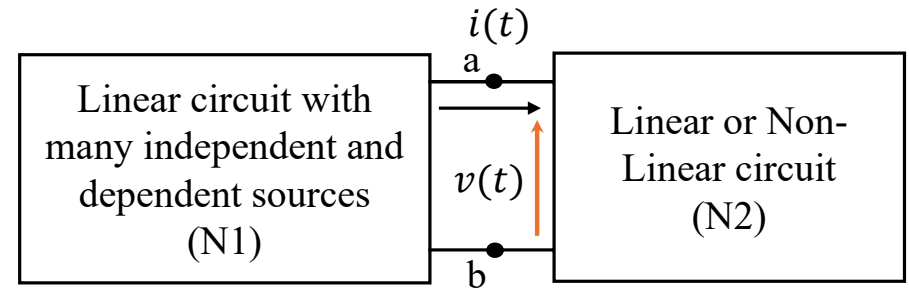
$$i(t) = \sum_{i=1}^n a_i V_i(t) + \sum_{j=1}^m b_j I_j(t) - a_0 v(t)$$



Any linear bilateral network (N1) can be represented by a current source (I_N) in parallel with a resistance (R_N), where

- ❖ The value of the current source is equal to the current that would flow through a-b terminal when a and b terminals are shorted.
- ❖ The parallel resistance of the network N1 is measured between a-b terminal with N2 removed and the source emfs replaced by their internal resistances.

NB:

Ideal voltage sources are replaced by short circuit and the ideal current sources are replaced with open circuit.

NORTON'S THEOREM (INDEPENDENT SOURCES)


Problem-16:

Determine the Norton equivalent circuit of the given network across the load resistance R_L .


Ans:

$$I_N = 2.4 \text{ A}$$

$$R_N = 6.6667 \Omega$$

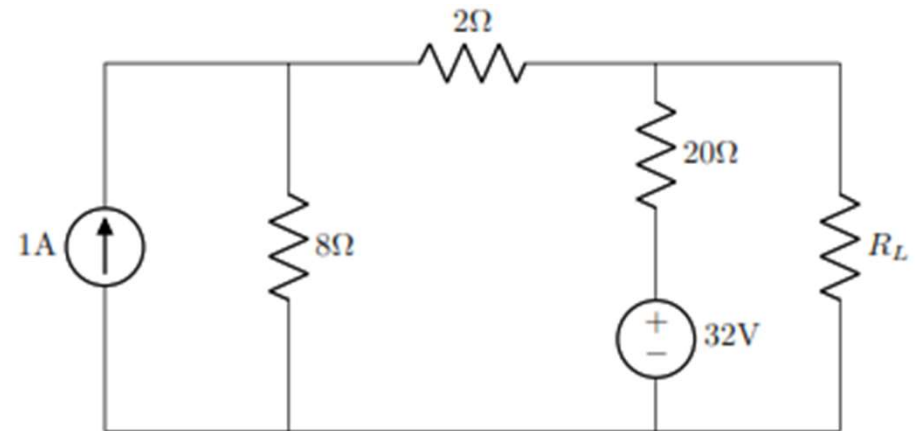

THEVENIN'S THEOREM

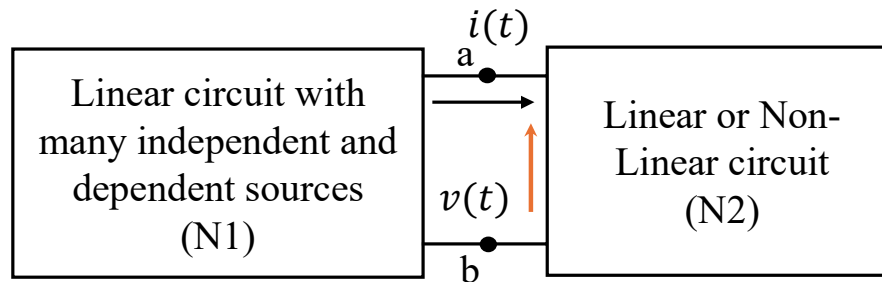

Any linear bilateral network (N1) can be represented by a voltage source (V_{TH}) in series with a resistance (R_{TH}), where

- ❖ The value of the voltage source is equal to the voltage that would appear across a-b terminal when a and b terminals are opened.
- ❖ The series resistance of the network N1 is measured between a-b terminal with N2 removed and the source emfs replaced by their internal resistances.

NB:

Ideal voltage sources are replaced by short circuit and the ideal current sources are replaced with open circuit.

THEVENIN'S THEOREM (INDEPENDENT SOURCES)


Problem-17:

Determine the Thevenin equivalent circuit of the given network across the load resistance R_L .

Ans:

$$V_{TH} = 16 \text{ V}$$

$$R_N = 6.6667 \Omega$$

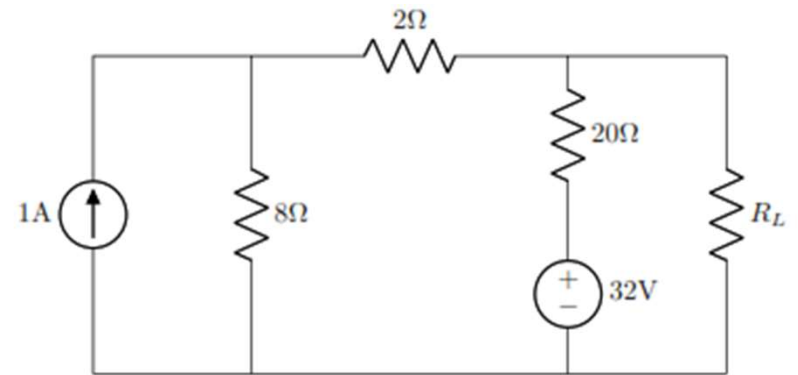

EXTRA PROBLEM

Problem:

Determine the galvanometer current in the wheastone bridge using the Thevenin's and Norton's Theorem.


Ans:

$$R_N = 16.0714 \, \Omega$$

$$I_N = 0.04 \, A$$



$$V_{TH} = 0.6428 \, V$$

$$I_{gal} = 11.4649 \, mA$$

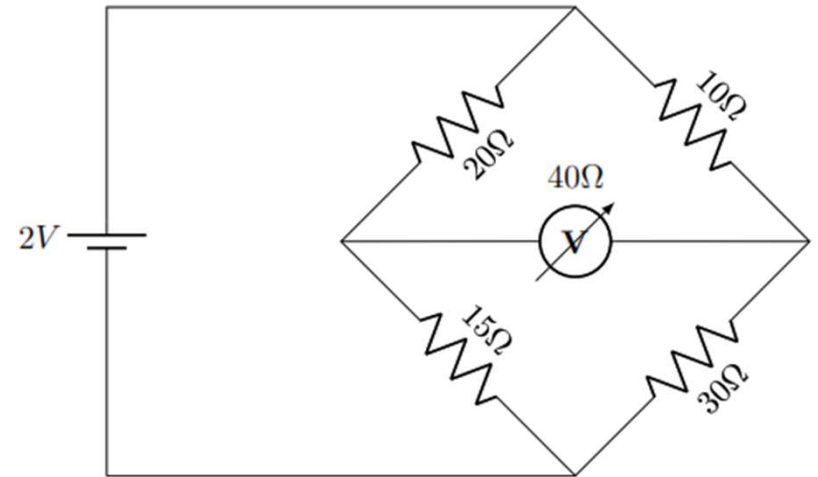


EQUIVALENT RESISTANCE

(DEPENDENT SOURCES)

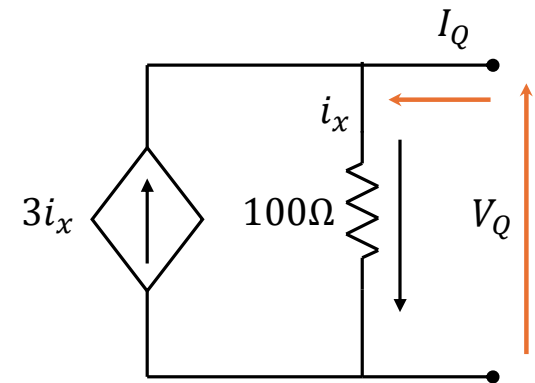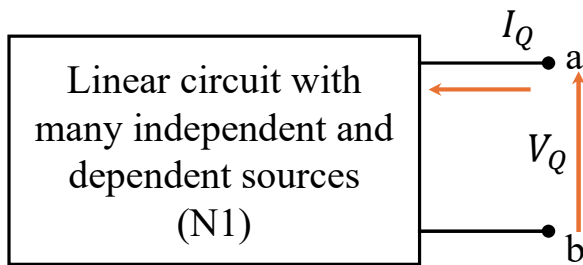

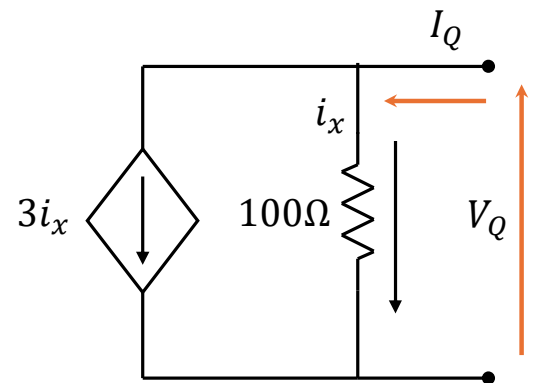- ❖ Determine the equivalent impedances for both circuits.
- ❖ With the change in the direction in the current sources, the ratio of $\frac{V_Q}{I_Q}$ is also changed which is the equivalent resistance observed by the V_Q source.



EQUIVALENT RESISTANCE

(DEPENDENT SOURCES)

- ❖ Set all independent sources equal to zero.
- ❖ Find the equivalent resistance.
 - a) When there are no dependent sources, find this equivalent resistance using the equivalent resistance rules (series combinations, parallel combinations, star-delta transformation) .
 - b) When there are dependent sources present, **apply a known test source to the two terminals of interest**. It can be either a voltage source or a current source.
 - 1) In case of **voltage source, measure the current** coming out of the voltage source.
 - 2) In case of **current source, measure the voltage** appeared across that current source.
 - 3) Find the ratio of the voltage to the current, which will be the equivalent resistance.
- ❖ Find out the Open circuit voltage (V_{oc}) and the short circuit current (I_{sc}) and find out the ratio which is supposed to be the equivalent resistance of the given circuit.

$$R_{eq} = \frac{V_{oc}}{I_{sc}} = R_{TH} = R_N$$

NORTON'S THEOREM EXAMPLE

(DEPENDENT SOURCES)


Problem-18:

For the given circuit determine the Norton's current and the Norton's equivalent resistance.

Ans:

$$I_N = -0.09434 \text{ A}$$

$$R_N = 2.21 \text{ k}\Omega$$

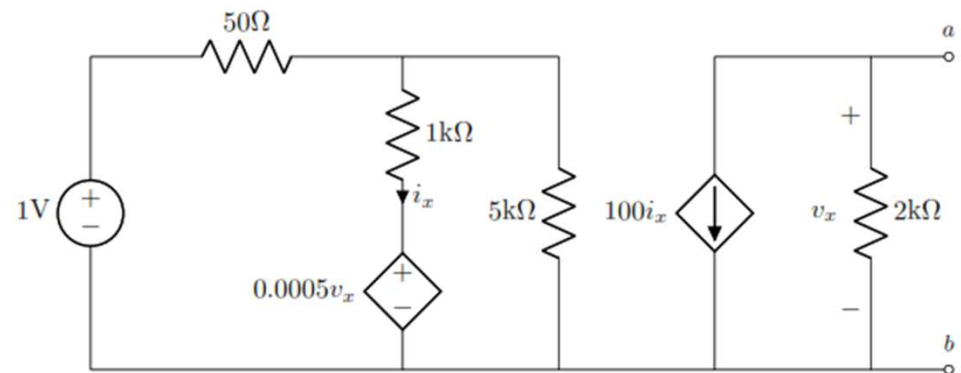

THEVENIN'S THEOREM EXAMPLE

(DEPENDENT SOURCES)


Problem-19:

For the given circuit determine the Thevenin's voltage and the Thevenin's equivalent resistance.

Ans:

$$V_{TH} = -208.5 \text{ V}$$

$$R_N = 2.21 \text{ k}\Omega$$

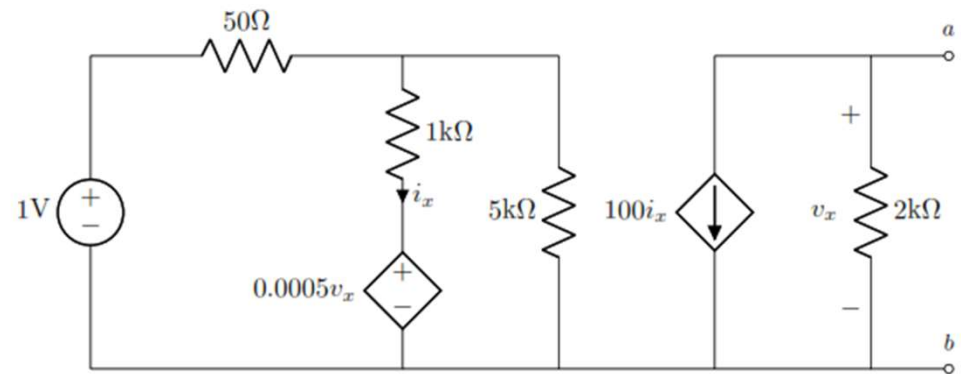

NETWORK THEOREM EXAMPLE

Problem-20:

For the given circuit determine the Thevenin's voltage, Norton's current and the equivalent resistance across the $22\text{ k}\Omega$ resistance terminal.

Ans:

$$\begin{aligned} I_N &= -102\text{ mA} \\ V_{th} &= 125.256\text{ V} \\ R_{eq} &= -1.228\text{ k}\Omega \end{aligned}$$

