

According to Amperes circuital law

$$\oint \vec{H} \cdot d\vec{l} = Ni \quad \mathcal{R} = \text{Reluctance}$$

$$\Rightarrow N_1 i_1 - N_2 i_2 = H \cdot l$$

$$\Rightarrow N_1 i_1 - N_2 i_2 = \Phi \mathcal{R}$$

$$\Rightarrow N_1 i_1 - N_2 i_2 = \Phi \frac{l}{\mu_0 \mu_r}$$

Now for practical T/F μ_r is finite, therefore


$$N_1 i_1 - N_2 i_2 = N_1 i_\psi$$

$$\Rightarrow N_1 i_1 = N_2 i_2 + N_1 i_\psi$$

$$\Rightarrow i_1 = \frac{N_2}{N_1} i_2 + i_\psi$$

$$\Rightarrow \bar{I}_1 = \frac{N_2}{N_1} \bar{I}_2 + \bar{I}_\psi \quad [\text{Phasor Representation}]$$
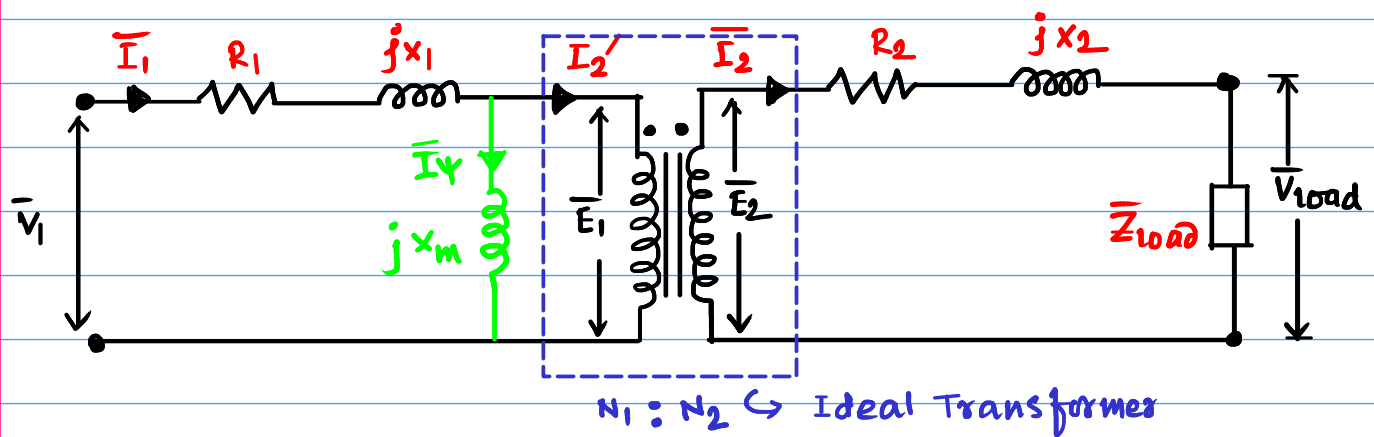
$$\Rightarrow \boxed{\bar{I}_1 = \bar{I}_2' + \bar{I}_\psi} \quad \bar{I}_\psi = \text{Magnetizing current.}$$




$$\bar{I}_\psi = \frac{\bar{E}_1}{jX_m}$$

X_m = Inductive Reactance that represents the mutual flux


\bar{I}_ψ creates the mutual flux Φ_m . So we can say Φ_m and \bar{I}_ψ are at same phase.

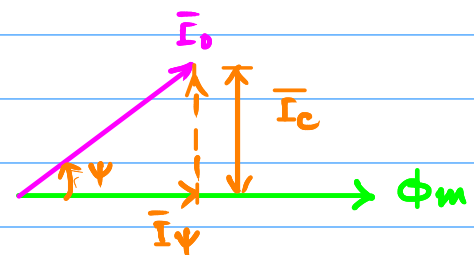However according to hysteresis curve the current leads the flux




The component of \bar{I}_0 which is along Φ_m creates the flux. The component of \bar{I}_0 perpendicular to Φ_m represents the core loss component.

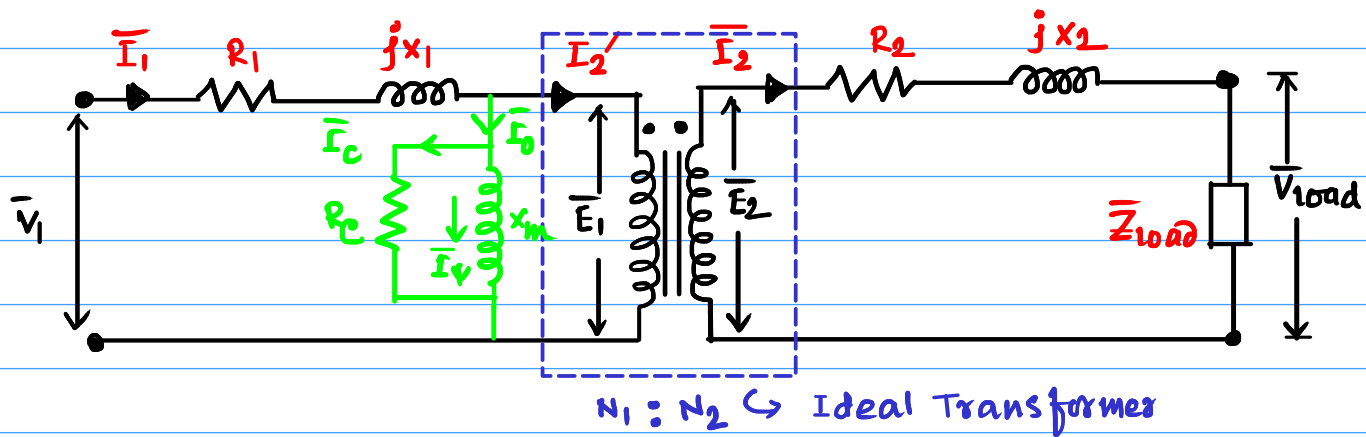● complete equivalent ckt diagram of t/f:-



$$\text{The core loss} = \frac{|\bar{E}_1|^2}{R_c} = P_{\text{core}}$$

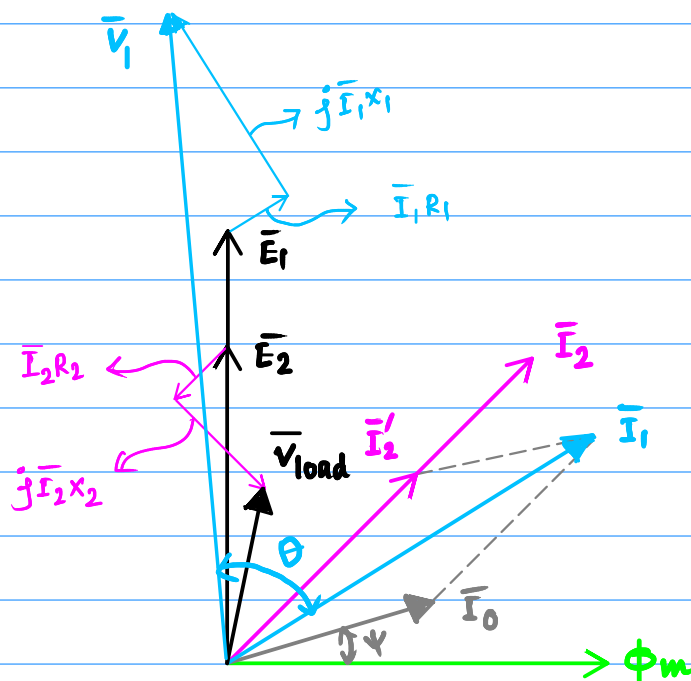

$$\begin{aligned} \bar{V}_1 &= \bar{I}_1 R_1 + j \bar{I}_1 X_1 + \bar{E}_1 \\ \bar{E}_2 &= \bar{I}_2 R_2 + j \bar{I}_2 X_2 + \bar{V}_{\text{load}} \\ N_1 \bar{I}_2' &= N_2 \bar{I}_2 \\ \bar{I}_1 &= \bar{I}_0 + \bar{I}_1' \end{aligned}$$

⊙ The equivalent circuit of a real T/F accounts for \Rightarrow

i) ohmic losses and voltage drops.

[Primary (coil-1) and Secondary (coil-2) resistances]

ii) Leakage flux [weak coupling]

[Primary (coil-1) and Secondary (coil-2) reactances]

iii) Finite permeability


[\bar{I}_m is introduced and so the jx_m]

iv) Core losses

[$R_c \rightarrow I_c$]

R_c is the resistance that represents the core loss.

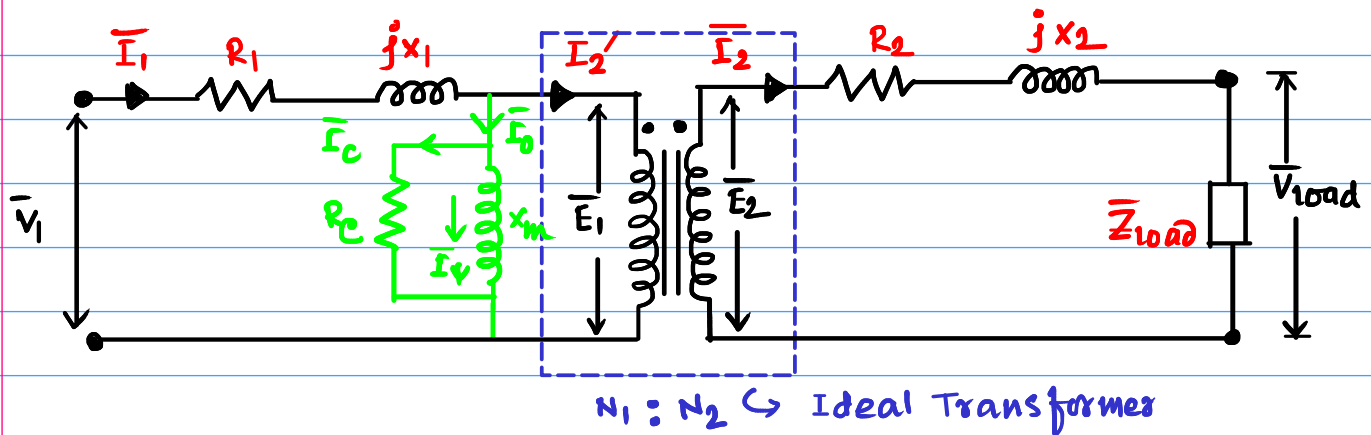⊙ T/F equivalent ckt referred to primary side:-



Secondary equations of the T/F is as follows

$$\bar{E}_2 = \bar{V}_{load} + \bar{I}_2 (R_2 + jx_2)$$

$$\frac{\bar{E}_1}{N_1} = \frac{\bar{E}_2}{N_2}$$

$$\Rightarrow \frac{N_2}{N_1} \bar{E}_1 = \bar{V}_{load} + \bar{I}_2 (R_2 + jx_2)$$

$$\bar{E}_1 = \frac{N_1}{N_2} \bar{E}_2$$

$$\Rightarrow \bar{E}_1 = \frac{N_1}{N_2} \bar{V}_{load} + \frac{N_1}{N_2} (R_2 + jx_2) \bar{I}_2$$

$$\begin{aligned} \bar{I}_2' N_1 &= \bar{I}_2 N_2 \\ \Rightarrow \bar{I}_2 &= \left(\frac{N_1}{N_2} \right) \bar{I}_2' \end{aligned}$$

$$\Rightarrow \bar{E}_1 = \bar{V}_{load}' + \left(\frac{N_1}{N_2} \right)^2 \bar{I}_2' (R_2 + jx_2)$$

$$\Rightarrow \bar{E}_1 = \bar{V}_{load}' + \bar{I}_2' (R_2' + jx_2')$$

where

$$R_2' = R_2 \left(\frac{N_1}{N_2} \right)^2$$


$$x_2' = x_2 \left(\frac{N_1}{N_2} \right)^2$$

} Secondary impedance referred to primary.

and

$$\bar{V}_{load}' = \left(\frac{N_1}{N_2} \right) \bar{V}_{load}$$

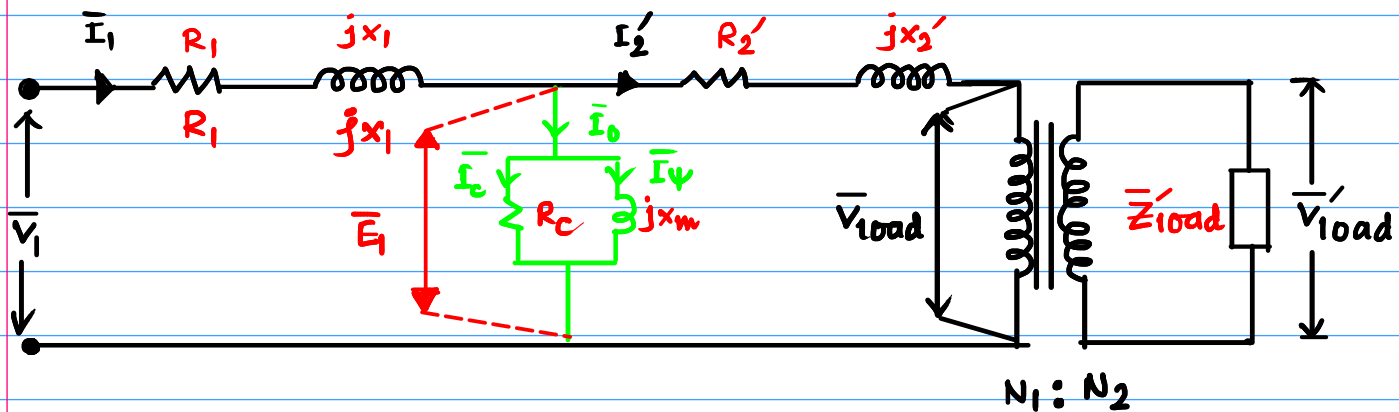} Secondary terminal voltage referred to primary.



we also can refer the load to the primary side.

$$\bar{V}_{load} = \bar{I}_2 \bar{Z}_{load}$$

$$\Rightarrow \left(\frac{N_2}{N_1} \right) \bar{V}'_{load} = \bar{I}_2 \bar{Z}_{load}$$

$$\Rightarrow \bar{V}'_{load} = \left(\frac{N_1}{N_2} \right) \bar{I}_2 \bar{Z}_{load}$$

$$\left[\bar{I}_2 = \left(\frac{N_1}{N_2} \right) \bar{I}_2' \right] \text{ as}$$

$$\Rightarrow \bar{V}'_{load} = \left(\frac{N_1}{N_2} \right)^2 \bar{I}_2' \bar{Z}_{load}$$




$$\Rightarrow \boxed{\bar{V}'_{load} = \bar{I}_2' \bar{Z}'_{load}}$$

$$\boxed{\bar{Z}'_{load} = \left(\frac{N_1}{N_2} \right)^2 \bar{Z}_{load}}$$

Now draw the equivalent ckt of t/f referred to the secondary




● Approximate equivalent circuit of T/F :-

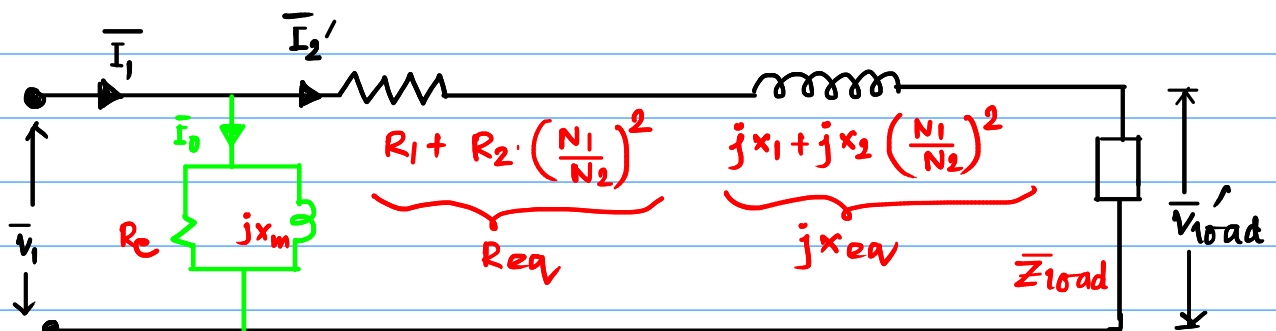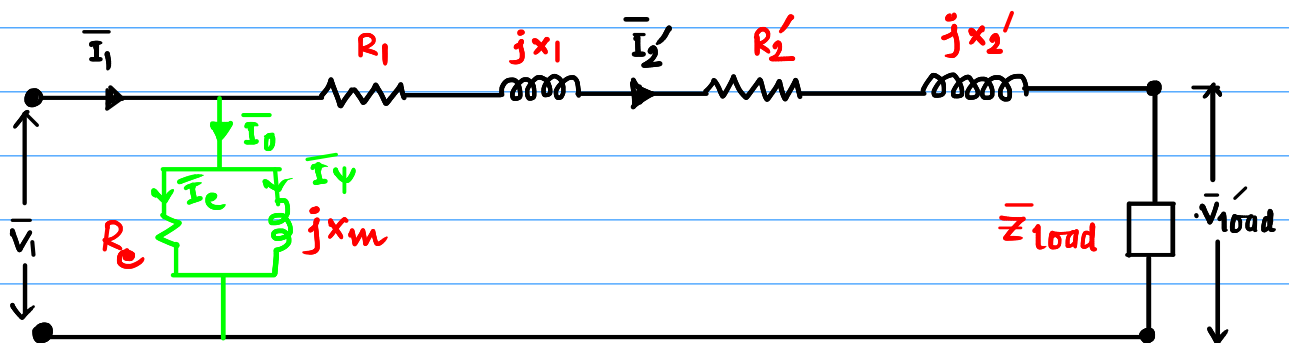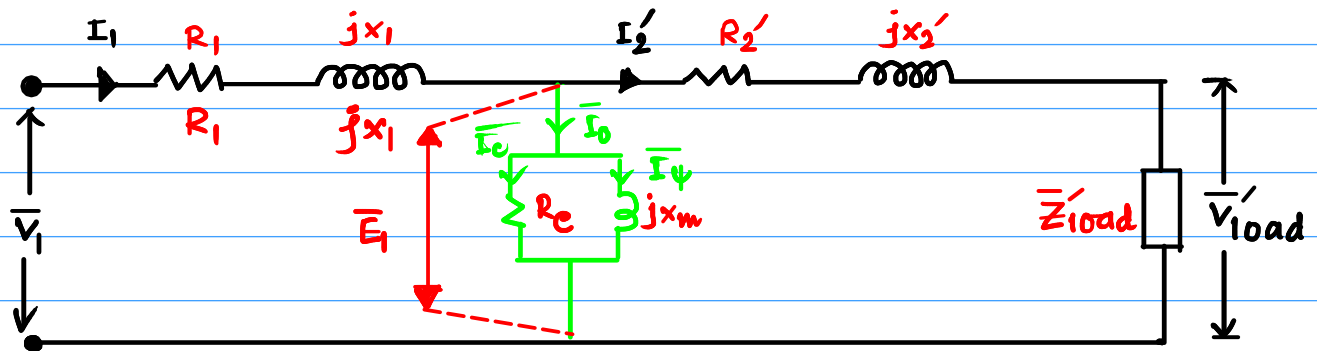The equivalent circuit of a Transformer referred to primary side is \Rightarrow



● Tests on T/F to find out circuit parameter:-

● Oc Test :-

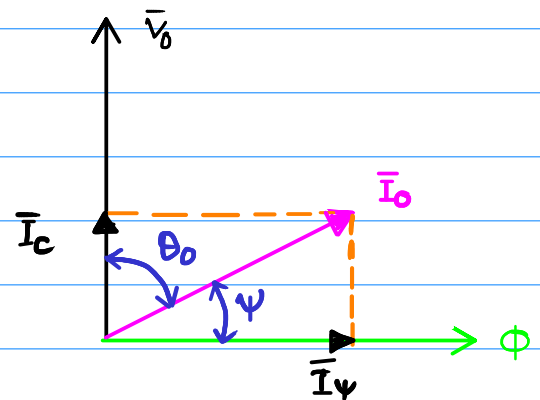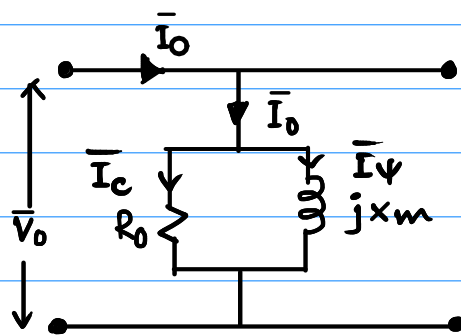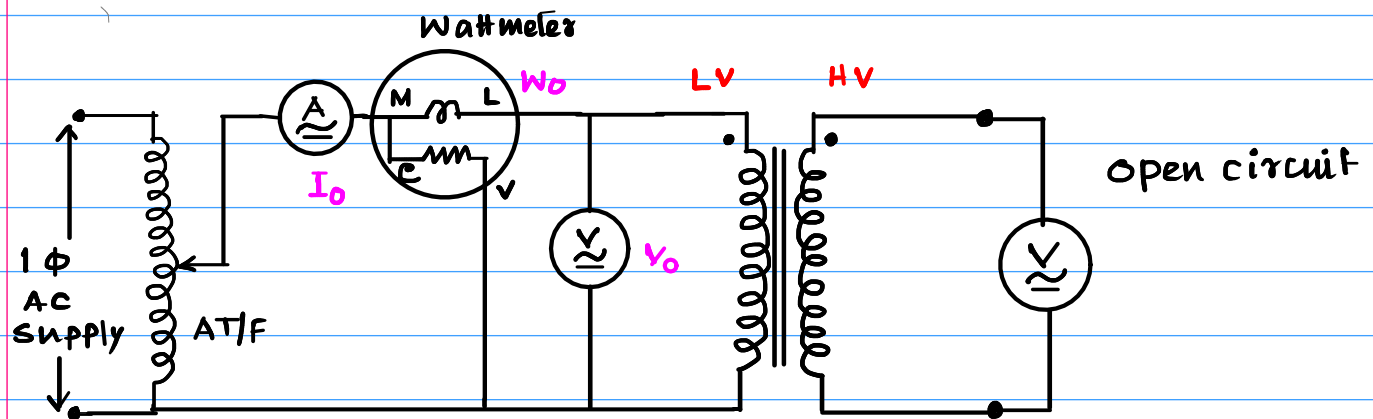

□ Calculation of oc test:-

We have the readings V_0, I_0, W_0

$$\cos \theta_0 = \frac{W_0}{V_0 I_0}$$

$$\theta_0 = \cos^{-1} \frac{W_0}{V_0 I_0}$$

$$I_c = I_0 \cos \theta_0 \quad \text{and} \quad I_\psi = I_0 \sin \theta_0$$


$$R_0 = \frac{V_0}{I_c} = \frac{V_0}{I_0 \cos \theta_0}$$

and



$$X_m = \frac{V_0}{I_\psi} = \frac{V_0}{I_0 \sin \theta_0}$$

These parameters are referred to (LV) side

SC Test:-

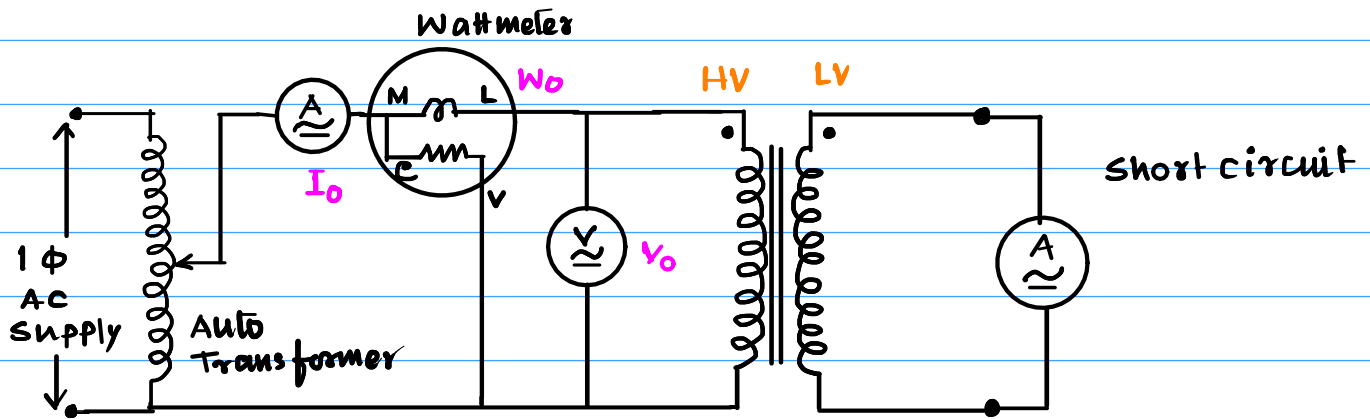

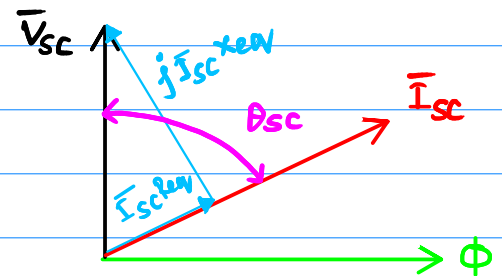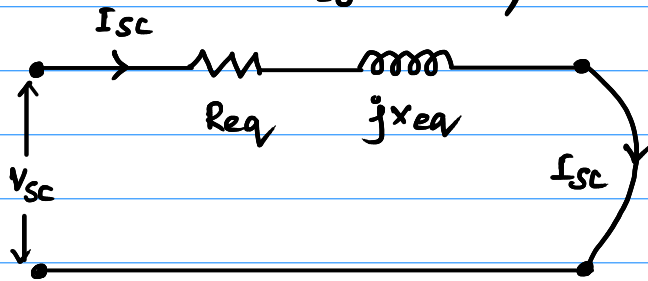I_0 is very small w.r.t I_{sc} and hence neglected



Calculation of SC test:-

We have the readings V_{sc} , I_{sc} , W_{sc}

$$\cos \theta_{sc} = \frac{W_{sc}}{V_{sc} I_{sc}}$$

$$\theta_{sc} = \cos^{-1} \frac{W_{sc}}{V_{sc} I_{sc}}$$

$$|Z| = \frac{V_{sc}}{I_{sc}}$$

$$R_{eq} = |Z| \cos \theta_{sc}$$

$$x_{eq} = |Z| \sin \theta_{sc}$$

These parameters are referred to (HV) side