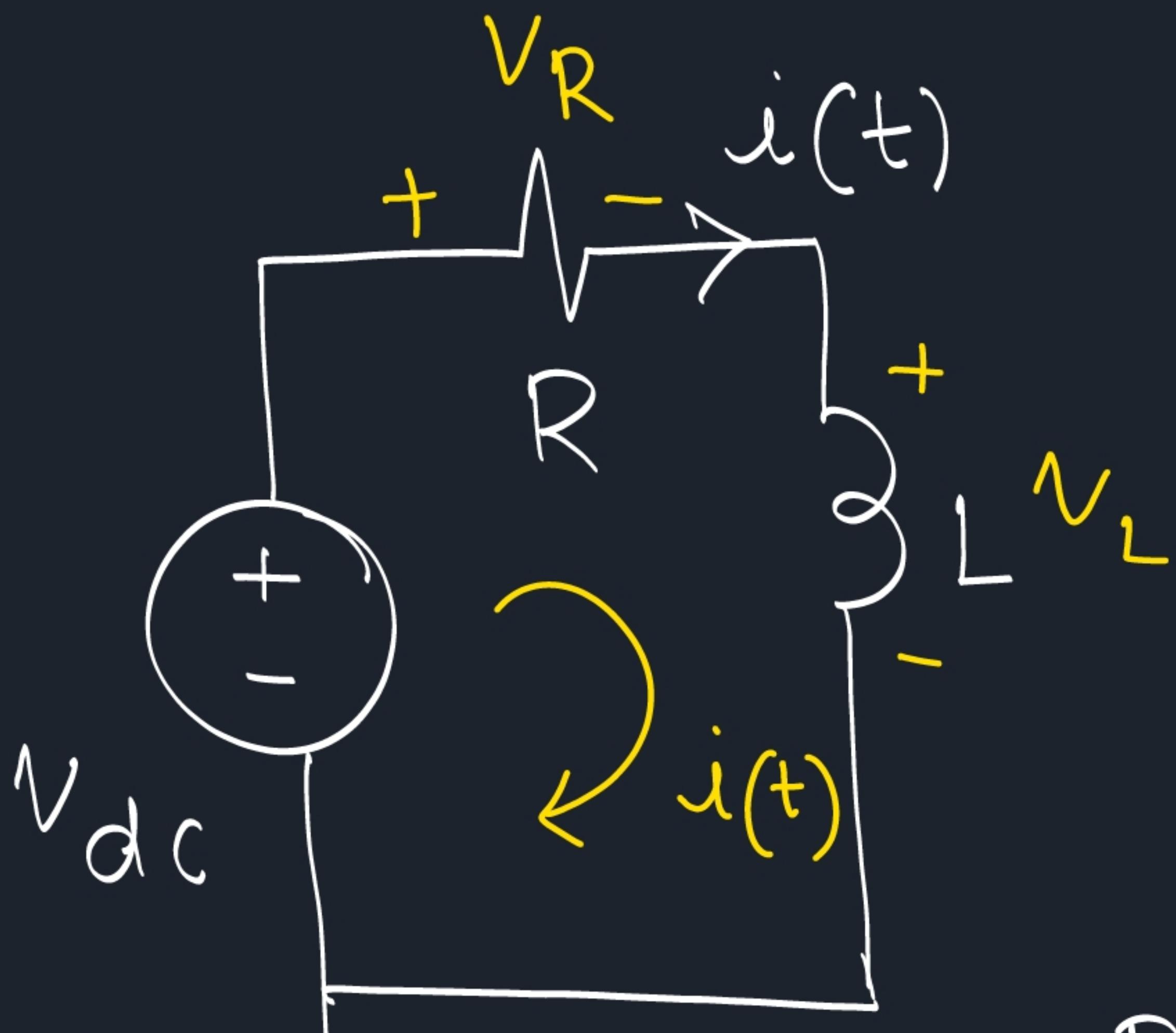


Basics :-



$$V_{dc} = V_R + V_L$$

$$\Rightarrow L \frac{di(t)}{dt} + R i(t) = V_{dc}$$

$$\Rightarrow \frac{di(t)}{dt} + \underbrace{\frac{R}{L} i(t)}_{P} = \underbrace{\frac{V_{dc}}{L}}_{Q}$$

$$e^{R/L t} \frac{di(t)}{dt} + e^{R/L t} \frac{R}{L} i(t) = e^{R/L t} \frac{V_{dc}}{L}$$

$$\Rightarrow \frac{d}{dt} \left(e^{R/L t} i(t) \right) = e^{R/L t} \cdot \frac{V_{dc}}{L}$$

$$e^{R/L t} i(t) = A + \frac{V_{dc}}{L} \int e^{R/L t} dt$$


$$i(t) = A e^{-R/L t} + \frac{V_{dc}}{L} \int e^{-R/L t} dt$$

$$i(t) = A e^{-R/L t} + \frac{V_{dc}}{R}$$

$$@ t=0 \quad i(t) = I_0$$

$$I_0 = A + \frac{V_{dc}}{R} \Rightarrow A = I_0 - \frac{V_{dc}}{R}$$

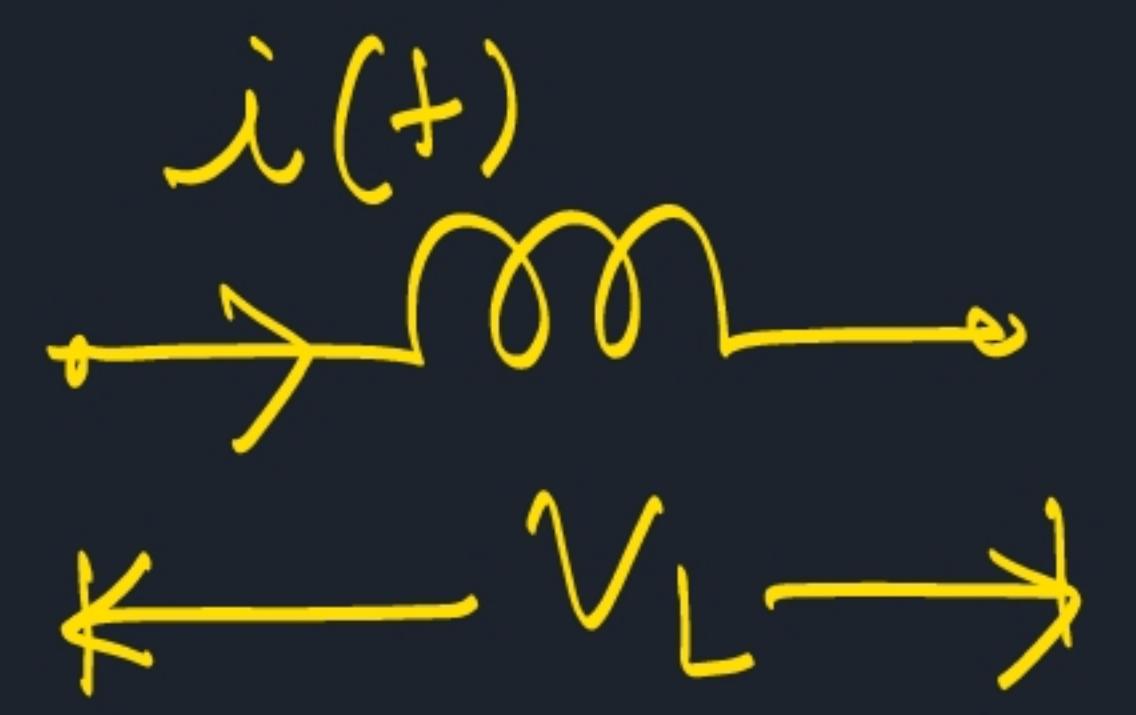
$$i(t) = \frac{V_{dc}}{R} \left(1 - e^{-R/L t} \right) + I_0 e^{-R/L t}$$



$$V_L(t) = L \frac{di^{(+)}}{dt}$$

$i(t) = e^{\pm \alpha t}$ α is integer.


$i(t) = \sin \omega t$

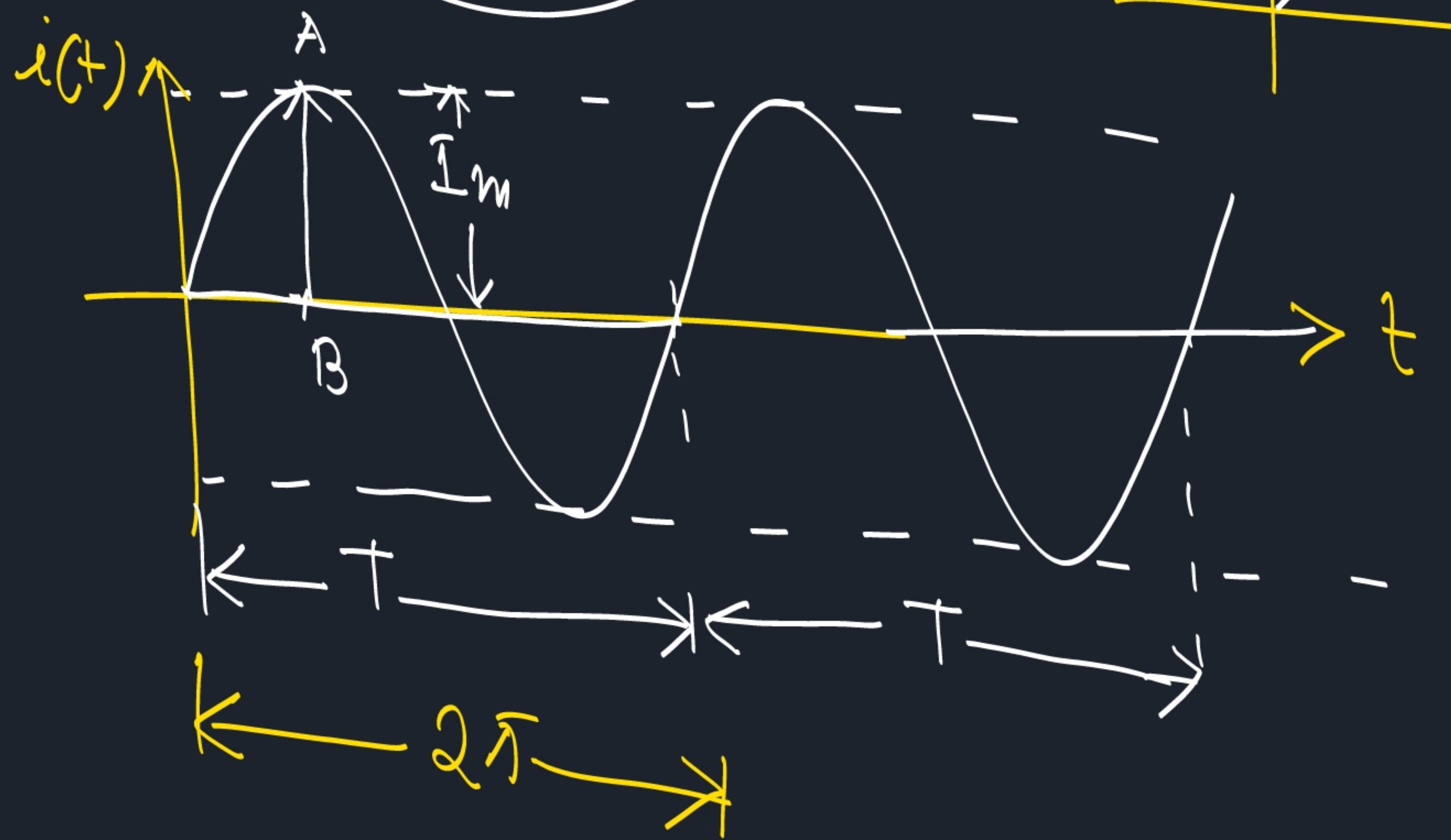

$$i_C(+) = C \frac{dV_C(+)}{dt}$$

$$V_C(+) = \frac{1}{C} \int i_C(+) dt$$

$f \propto \omega$

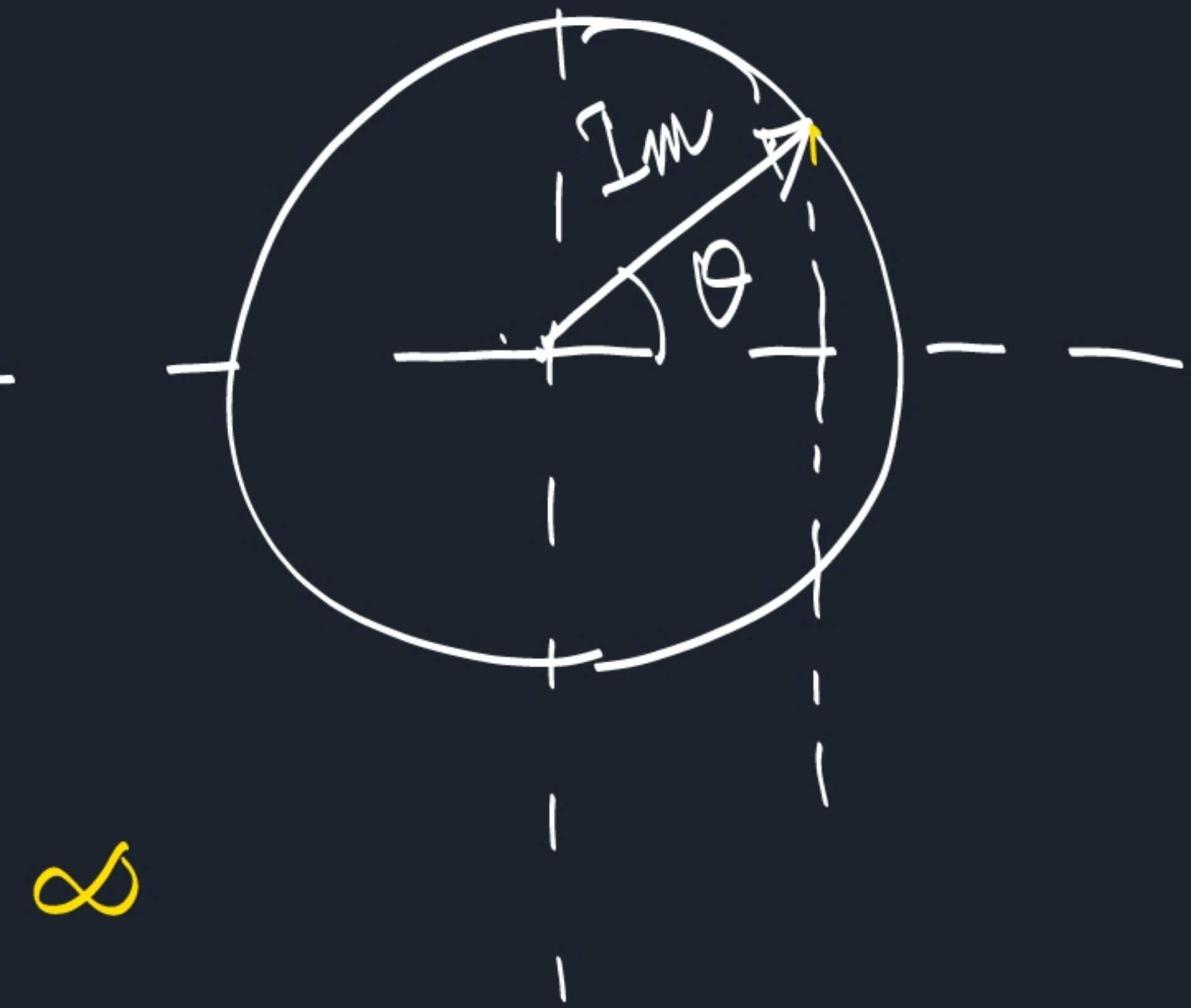

$m = 1, 2, \dots, \infty$

$f(t)$

$$f(t \pm \omega T) = f(t)$$

periodic waveform

$$\text{freq} = \frac{1}{T}$$


$$\omega t (t=+T) = 2\pi \frac{50 \text{ Hz}}{}$$

$I_m \sin \theta$

$I_m \sin \omega t$

Concept of Lagging


& Leadings :-

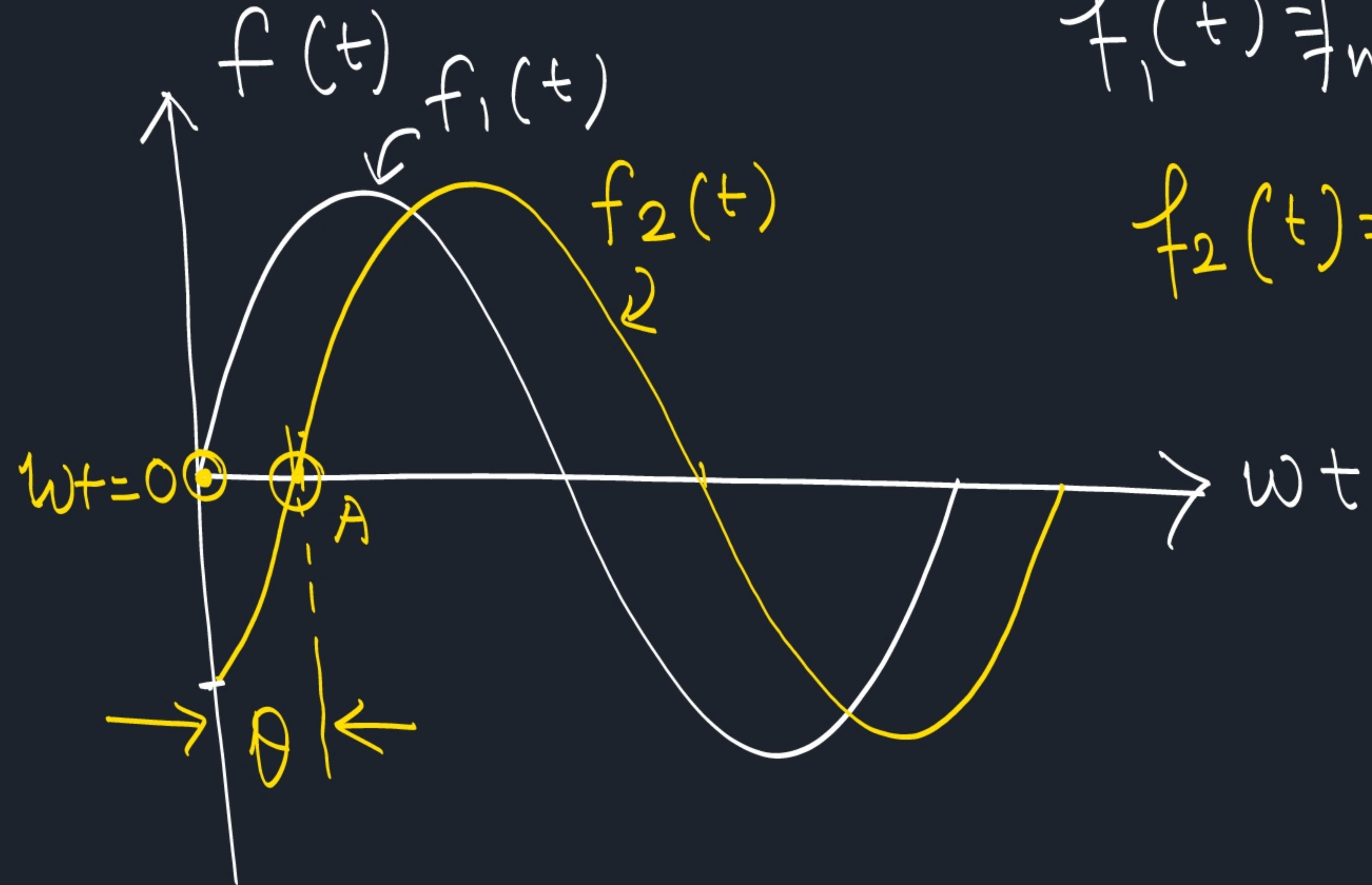

$$f_1(t) = f_m \sin(\omega t)$$

$$f_2(t) = f_m \sin(\omega t - \theta)$$

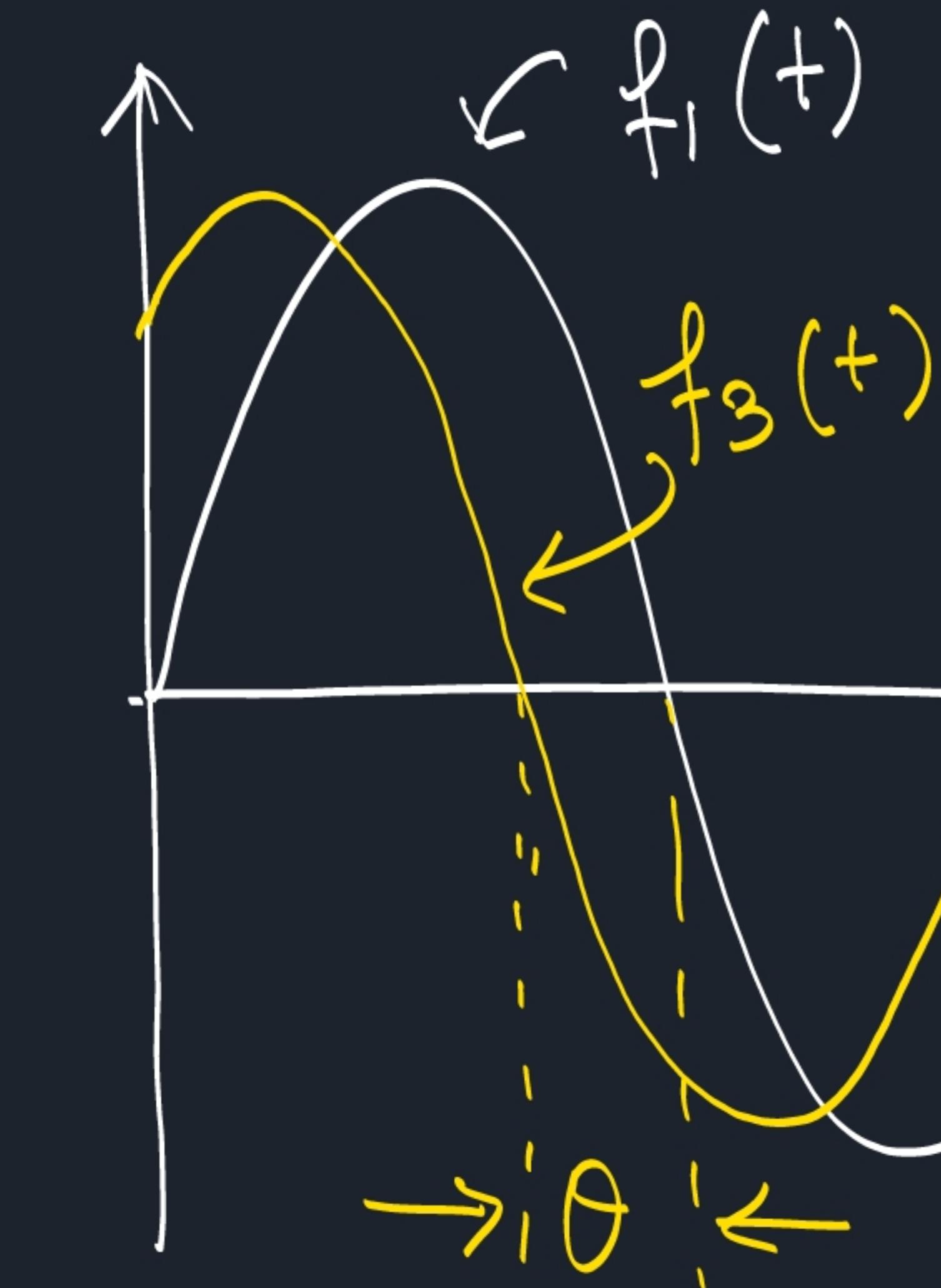
$f_2(t)$ is lagging behind $f_1(t)$ by an angle of θ .



$$f_3(t) = f_m \sin(\omega t + \theta)$$

$f_3(t)$ is leading $f_1(t)$ by an angle of θ .


RMS Value :-

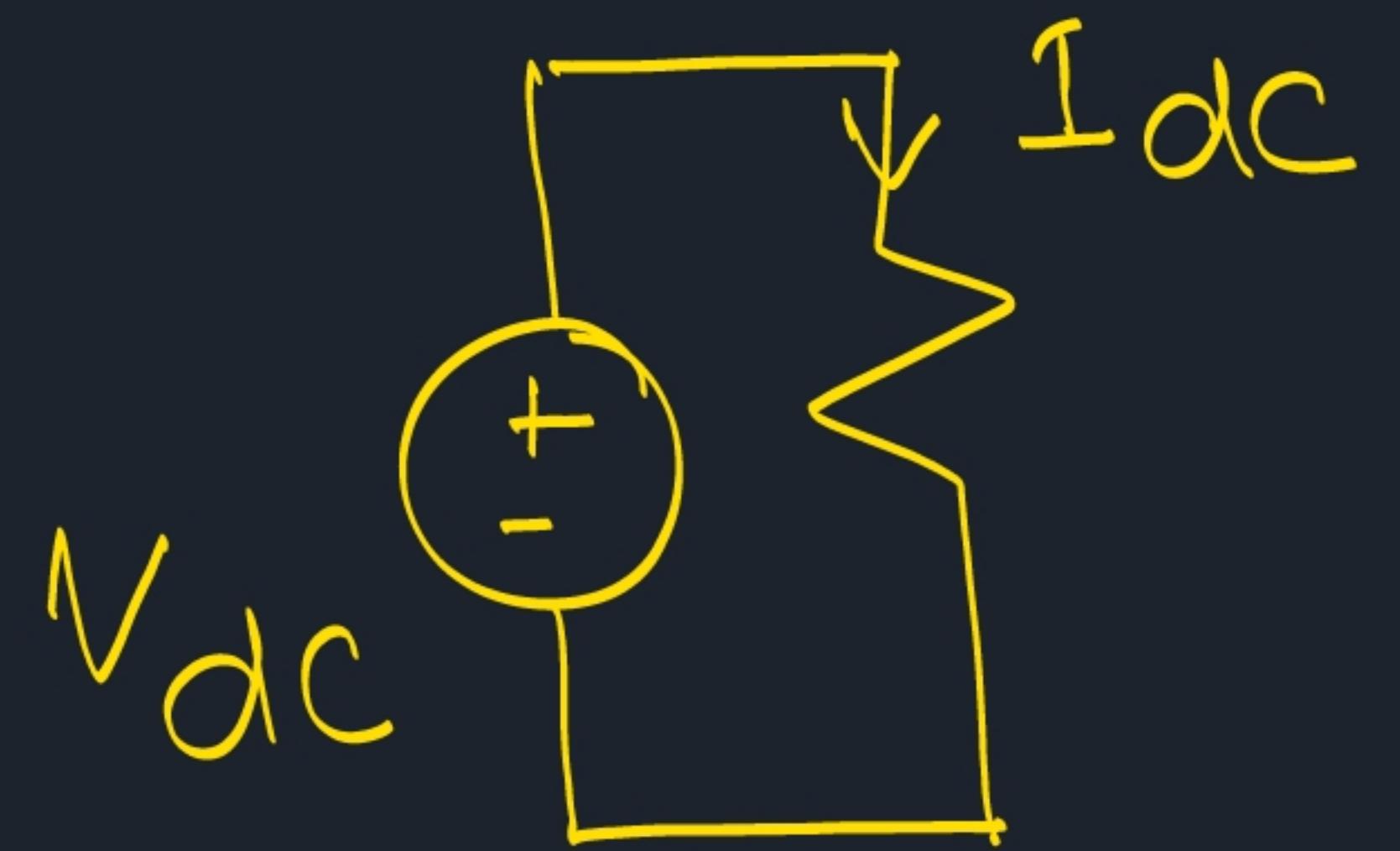

$$E_{dc} = I_{dc}^2 \cdot R \cdot T$$

$$I_{dc}^2 \cdot R \cdot T = \int_0^T i_{ac}^2(t) R dt$$
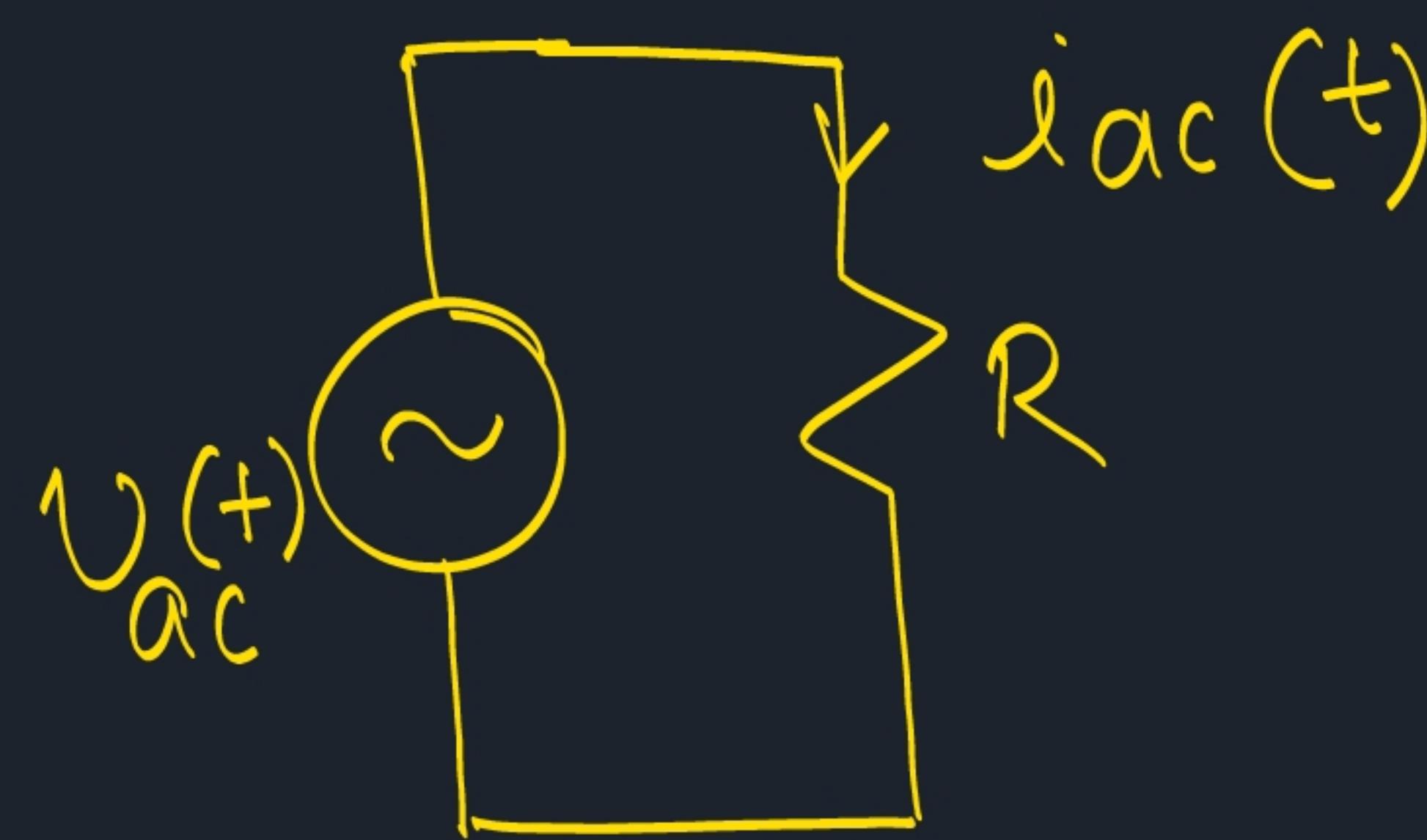
$$\boxed{I_{dc} = \left(\frac{1}{T} \int_0^T i_{ac}^2(t) dt \right)^{\frac{1}{2}}} = \underline{\underline{I_{ac}^{RMS}}}$$



$$E_{AC} = \int_0^T i_{ac}^2(t) R dt$$


$$I_{RMS} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

↳ Effective value

AVERAGE VALUE :-

$$I_{avg} = \frac{1}{T} \int_t^{t+T} i(t) dt$$

Sinusoidal Forced Response:-

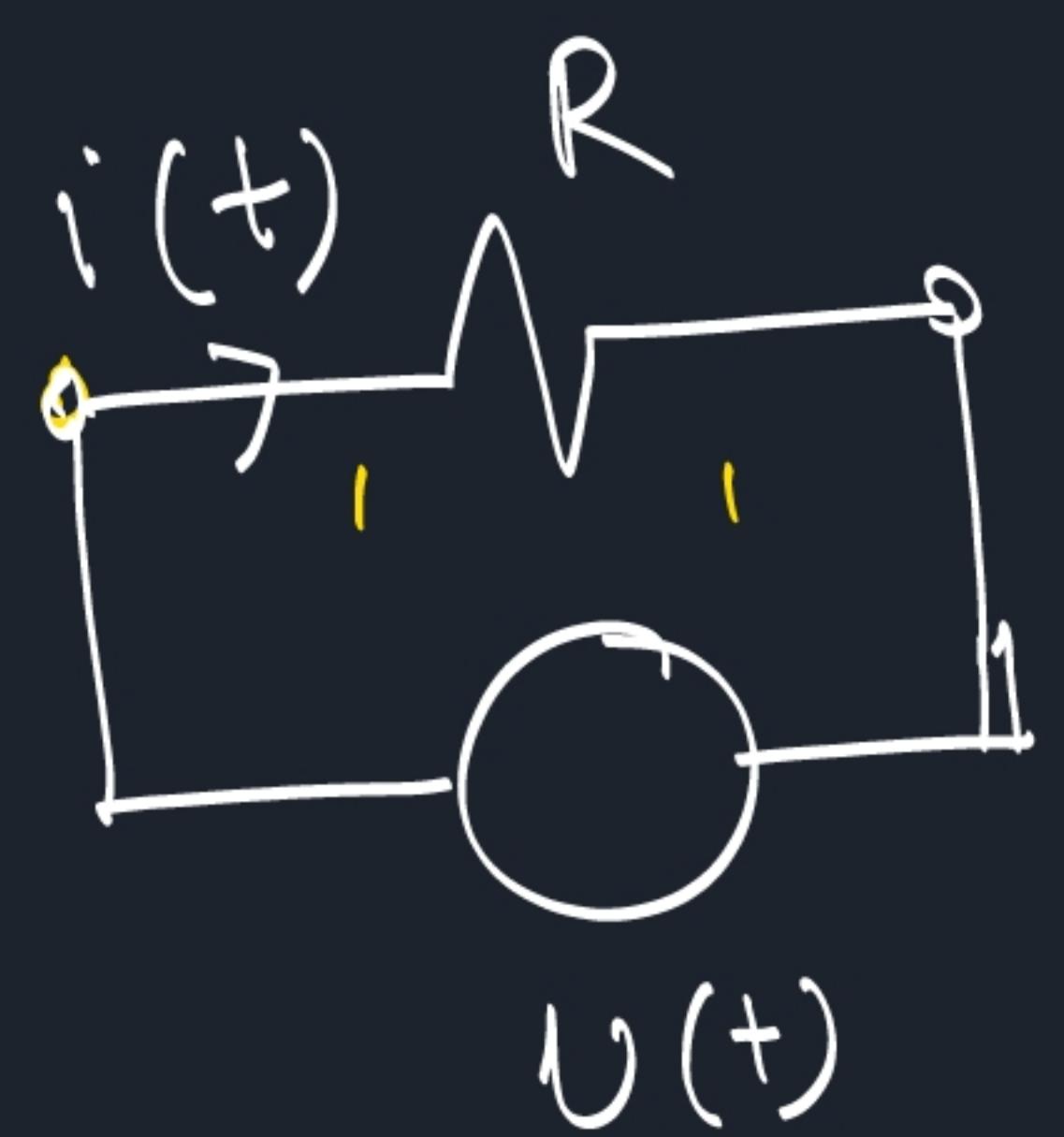

$$v(t) = V_m \cos \omega t$$

$$L \frac{di}{dt} + Ri = v(t)$$

$$= V_m \cos \omega t$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V_m}{L} \cos \omega t$$

$$e^{R/L t} \cdot \frac{di}{dt} + \frac{R}{L} e^{R/L t} \cdot i = \frac{V_m}{L} \cos \omega t \cdot e^{R/L t}$$

$$\Rightarrow \frac{d}{dt} (e^{R/L t} i(t)) = \frac{V_m}{L} e^{R/L t} \cos \omega t$$

$$e^{R/L t} i(t) = A + \int_0^t \frac{V_m}{L} e^{R/L t} \cos \omega t dt$$

$$i(t) = A e^{-R/L t} + e^{-R/L t} \int_0^t \frac{V_m}{L} e^{R/L t} \cos \omega t dt$$

$$\int \frac{V_m}{L} e^{R/L t} e^{j\omega t}$$

$$cos\omega t = \Re \{ e^{j\omega t} \}$$

$$e^{j\omega t} = cos\omega t + j sin\omega t$$

$$\frac{e^{j\omega t} + e^{-j\omega t}}{2}$$

$$\frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t - \theta)$$

$$\begin{aligned} &= \int \frac{V_m}{L} e^{(R/L + j\omega)t} \\ &= \frac{V_m}{L} \cdot \frac{e^{R/L t} \cdot e^{j\omega t}}{\frac{R}{L} + j\omega} \\ &= V_m \cdot \frac{e^{R/L t} \cdot e^{j\omega t}}{R + j\omega L} \\ &= \frac{V_m \cdot e^{j\omega t}}{|z| e^{j\theta}} \\ &= \frac{V_m}{|z|} e^{j(\omega t - \theta)} \end{aligned}$$

$$\begin{aligned} a + jb &= |z| \angle \theta \\ |z| &= \sqrt{a^2 + b^2} \\ \theta &= \tan^{-1}\left(\frac{b}{a}\right) \end{aligned}$$

$$a + jb = |z| e^{j\theta}$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$i(t) = A e^{-R/L t} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t - \theta)$$

Initial Condⁿ:

@ $t = 0$

$$0 = A + \frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos \theta$$

$$A = -\frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos \theta$$

$$i(t) = -\frac{V_m}{\sqrt{R^2 + (\omega L)^2}} e^{-R/L t} + \underbrace{\frac{V_m}{\sqrt{R^2 + (\omega L)^2}} \cos(\omega t - \theta)}_{\text{Steady State}}$$

Steady State



$$v_1(t) = V_m \cos \omega t$$

$$i_1(t) = I_m \cos(\omega t \pm \theta)$$



$$v_2(t) = V_m \sin \omega t$$

$$i_2(t) = I_m \sin(\omega t \pm \theta)$$



$$v_1(t) + jv_2(t)$$


$$\begin{aligned} &= V_m \cos \omega t + jV_m \sin \omega t \\ &= V_m e^{j\omega t}. \end{aligned}$$





$$v(t) = V_m e^{j\omega t}$$

$$i(t) = I_m e^{j(\omega t + \theta)}$$

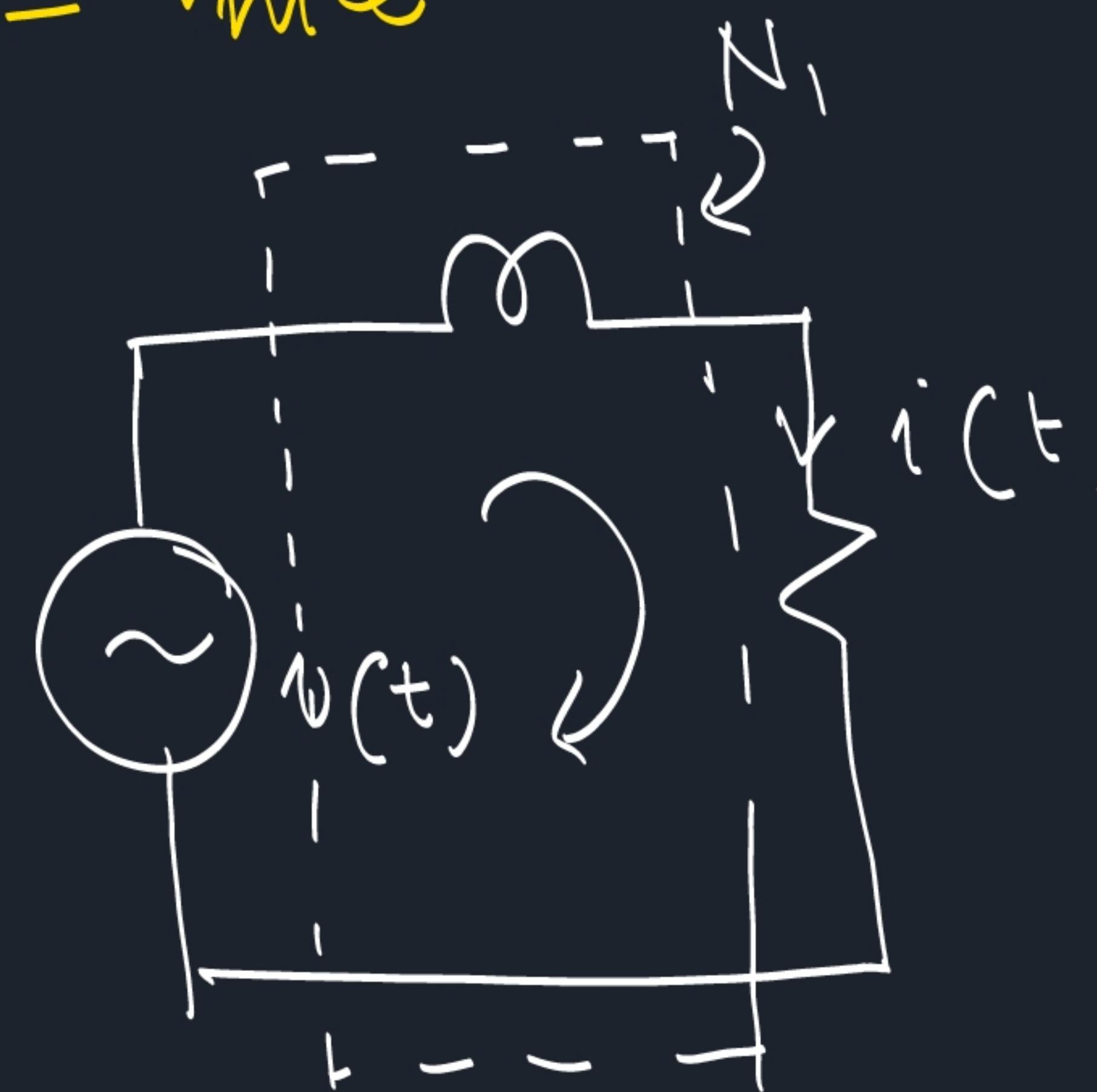

$$v(t) = R i(t) + L \frac{di(t)}{dt}$$

$$\Rightarrow j\omega L I_m e^{j(\omega t + \theta)} + R I_m e^{j(\omega t + \theta)} = V_m e^{j\omega t}$$

$$\Rightarrow j\omega L I_m e^{j\theta} + R I_m e^{j\theta} = V_m$$

$$\Rightarrow I_m e^{j\theta} (R + j\omega L) = V_m$$

$$I_m e^{j\theta} = \frac{V_m}{R + j\omega L}$$


$$I_m = |I_m e^{j\theta}| = \left| \frac{V_m}{R + j\omega L} \right|$$

$$= \frac{V_m}{\sqrt{R^2 + (\omega L)^2}}$$

$$\theta = \angle I_m e^{j\theta}$$


$$= \angle \frac{V_m}{R + j\omega L}$$

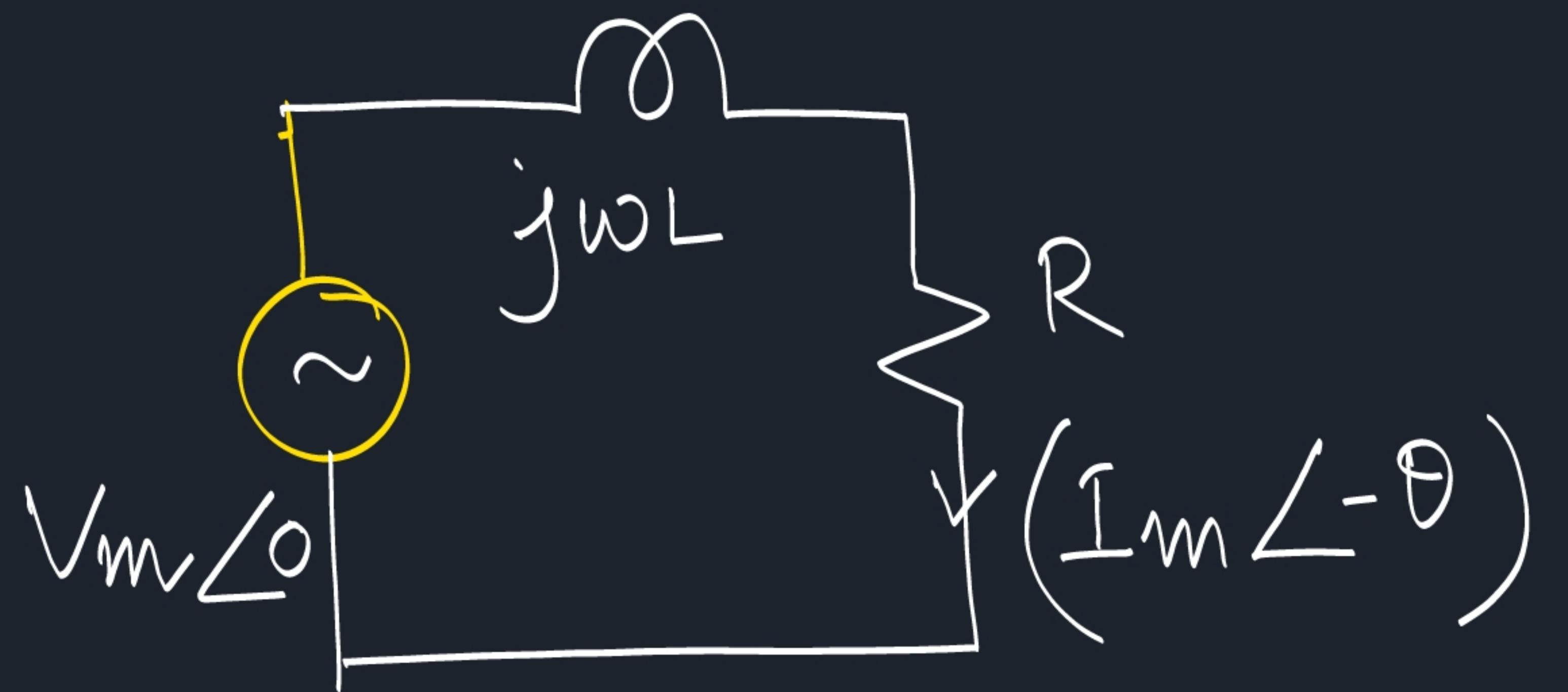
$$= -\tan^{-1} \left(\frac{\omega L}{R} \right)$$



$$\underline{I_m \angle -\theta} = \frac{V_m \angle 0}{R + j\omega L} \quad \left(\theta = \tan^{-1} \frac{\omega L}{R} \right)$$
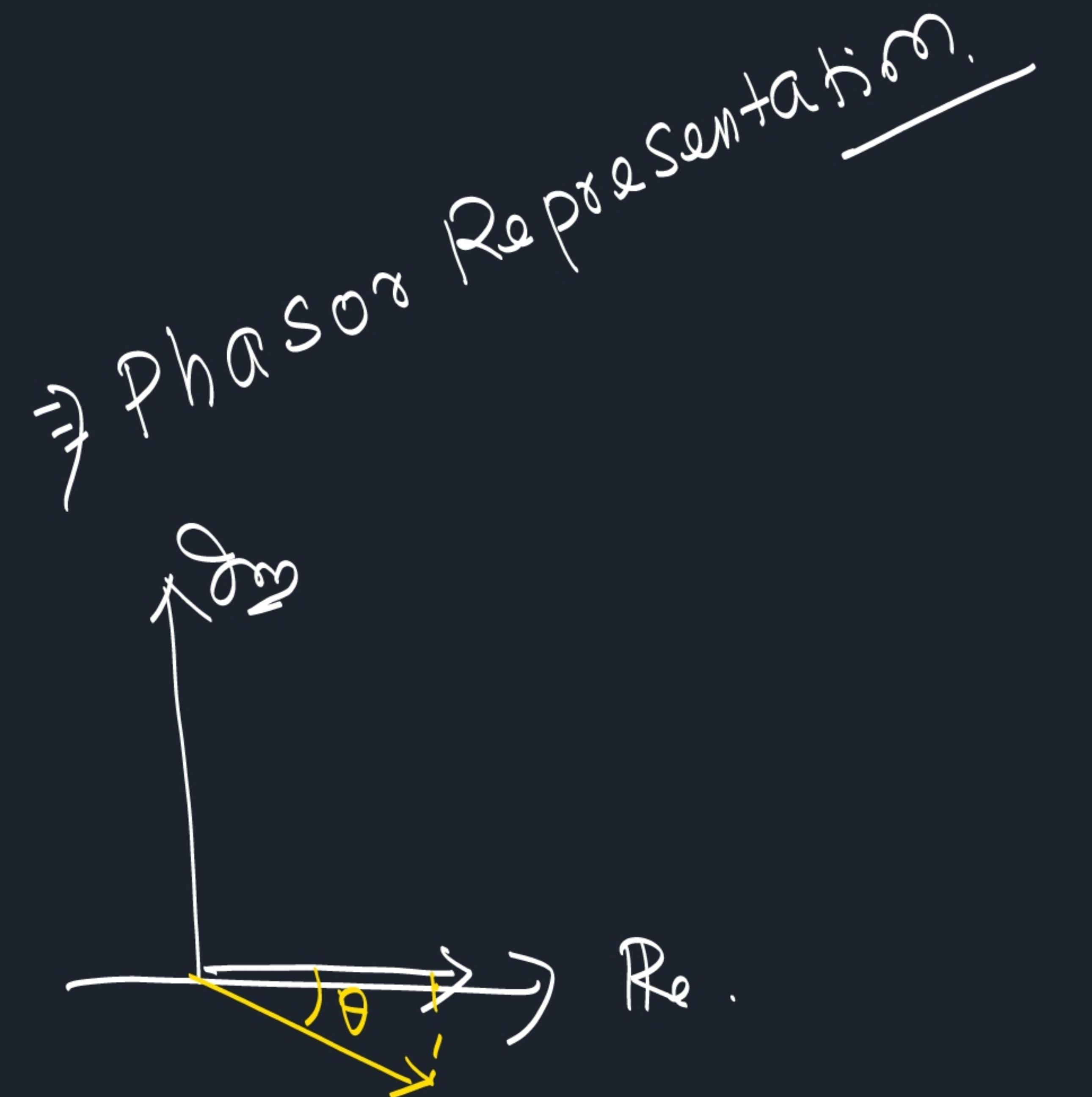
$$\begin{matrix} \vec{V} \\ \vec{I} \end{matrix} \rightarrow \begin{matrix} V_m \sin \omega t \\ I_m \sin(\omega t - \theta) \end{matrix}$$



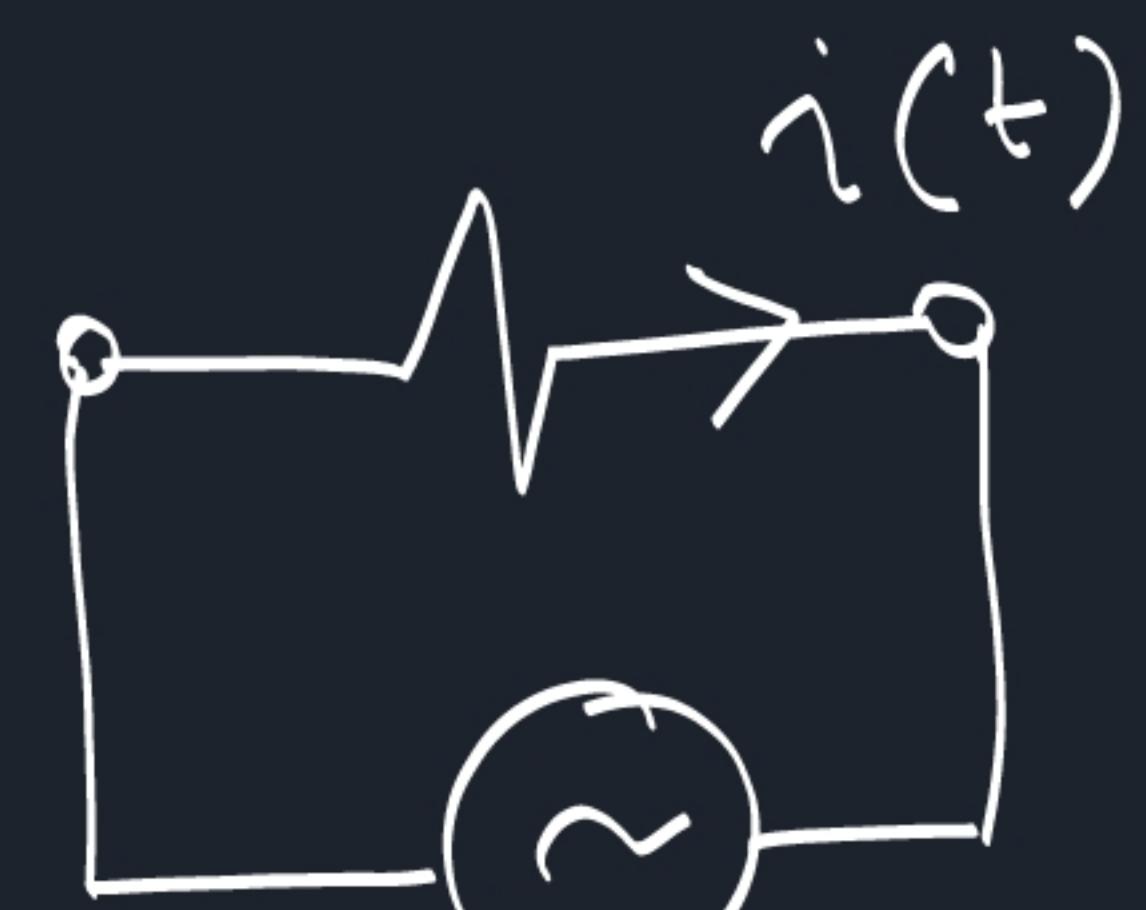

$$v(t) = V_m \cos(\omega t + \phi)$$

∴

$$v(t) = R i(t)$$

$$i(t) = \frac{V_m}{R} \cos(\omega t + \phi)$$

$$v(t) = V_m e^{j(\omega t + \phi)}$$

$$i(t) = I_m e^{j(\omega t + \phi)}$$




$$\tilde{v} = V_m \angle +\phi = V_m e^{j\phi}$$

$$\tilde{i} = I_m \angle +\phi = I_m e^{j\phi}$$

$(R > 1)$



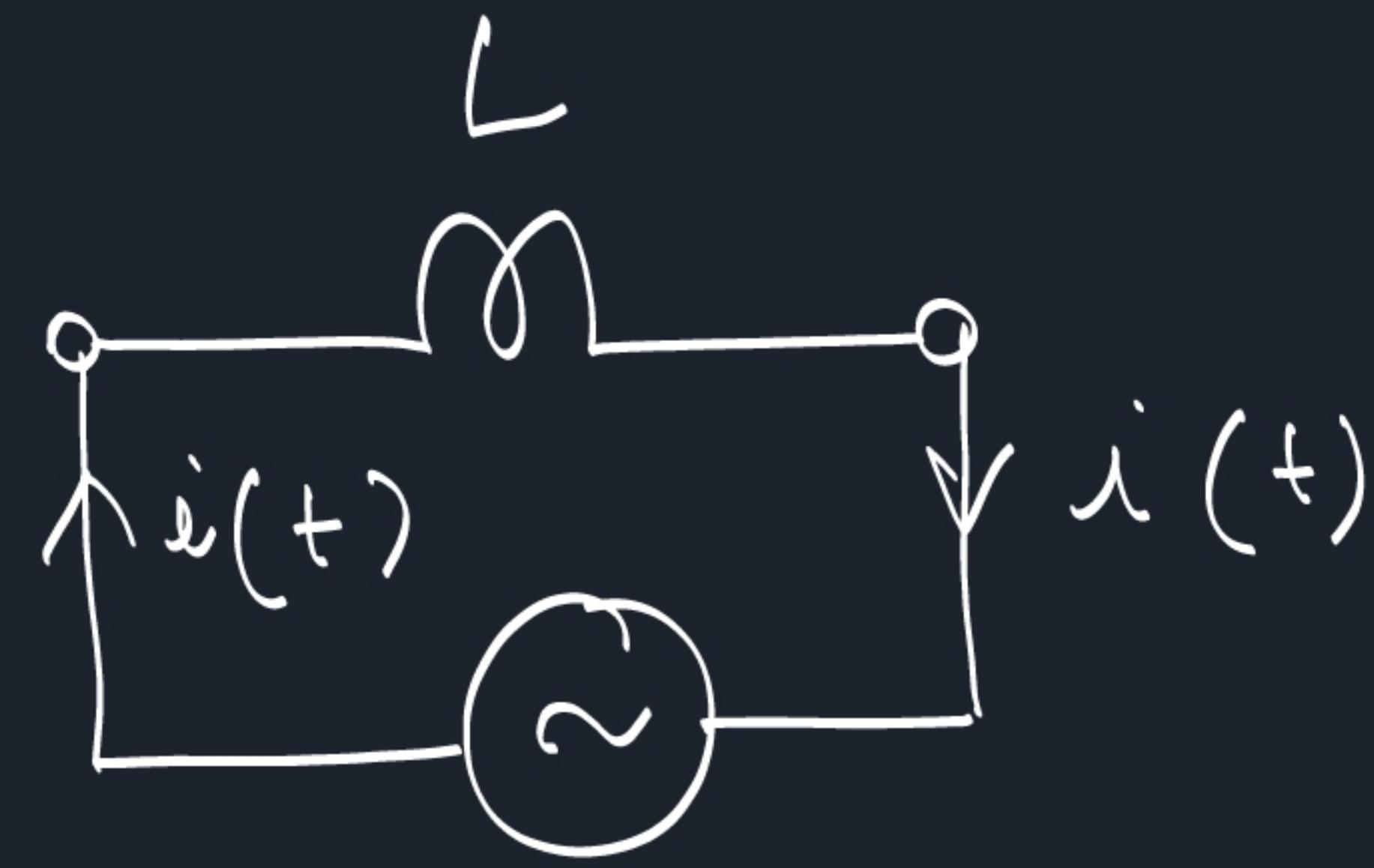

$$v(t) = V_m \cos(\omega t + \phi)$$

$$i(t) = \frac{1}{L} \int v(t) dt$$

$$= \frac{1}{L} \int V_m \cos(\omega t + \phi) dt$$

$$= \frac{1}{\omega L} V_m \sin(\omega t + \phi)$$

$$v(t) = L \frac{di(t)}{dt}$$

$$\tilde{V} = j\omega L \tilde{I}$$

$\frac{d}{dt}$ is replaced by
 $(j\omega)$




$$\tilde{V} = V_m \angle +\phi = V_m e^{j\phi}$$

$$\tilde{I} = \frac{V_m}{j\omega L} \cdot e^{j\phi} = \frac{V_m}{jX_L} e^{j\phi}$$

$X_L = \omega L$ = Inductive Resistance.

$$\tilde{V} = (j\omega L) \tilde{I}$$



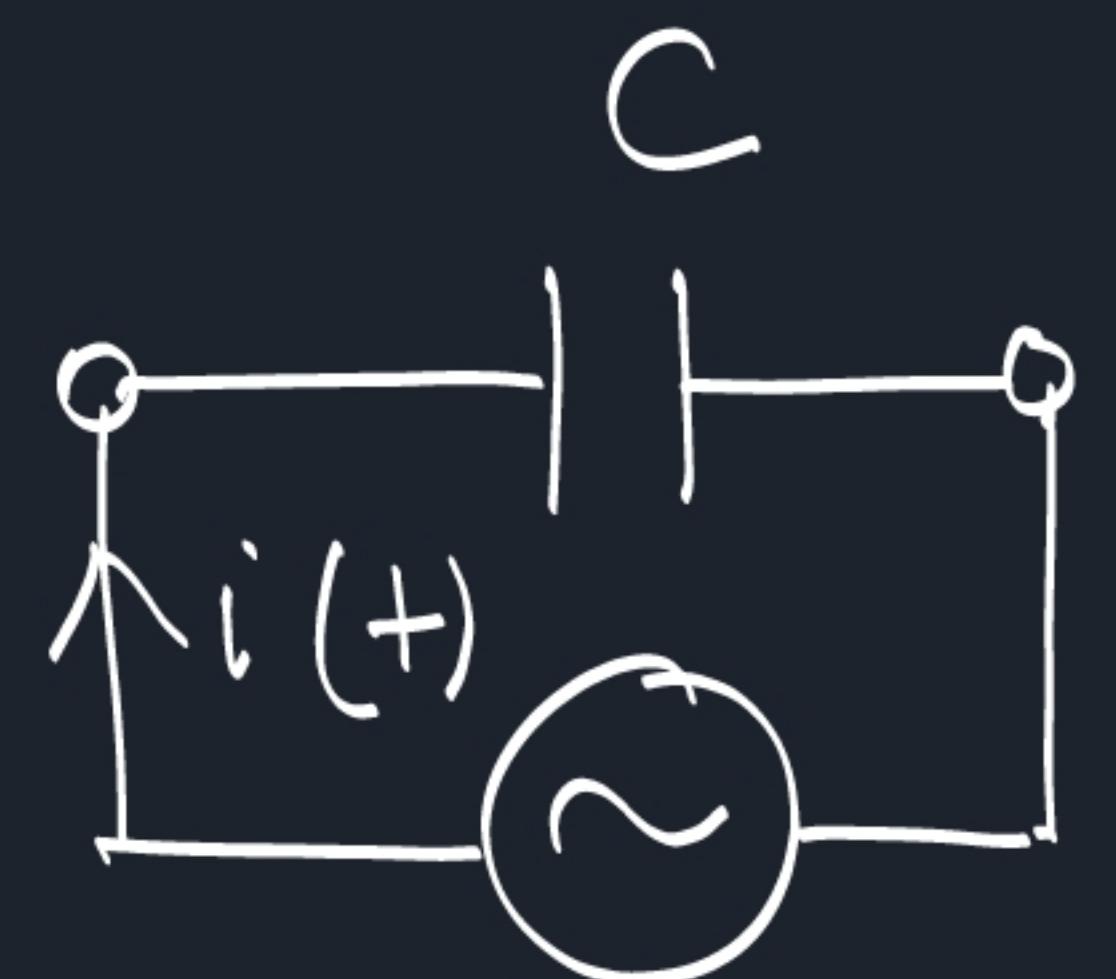

$$V(t) = V_m \cos(\omega t + \phi) \Leftrightarrow V_m e^{j(\omega t + \phi)}$$

$$i(t) = C \frac{dV(t)}{dt}$$


$$= -C\omega \sin(\omega t + \phi)$$



$$i(t) = j\omega C V_m e^{j(\omega t + \phi)}$$

$$\tilde{V} = \tilde{I} \cdot \left(\frac{1}{j\omega C} \right)$$

$$= -j I(X_C)$$

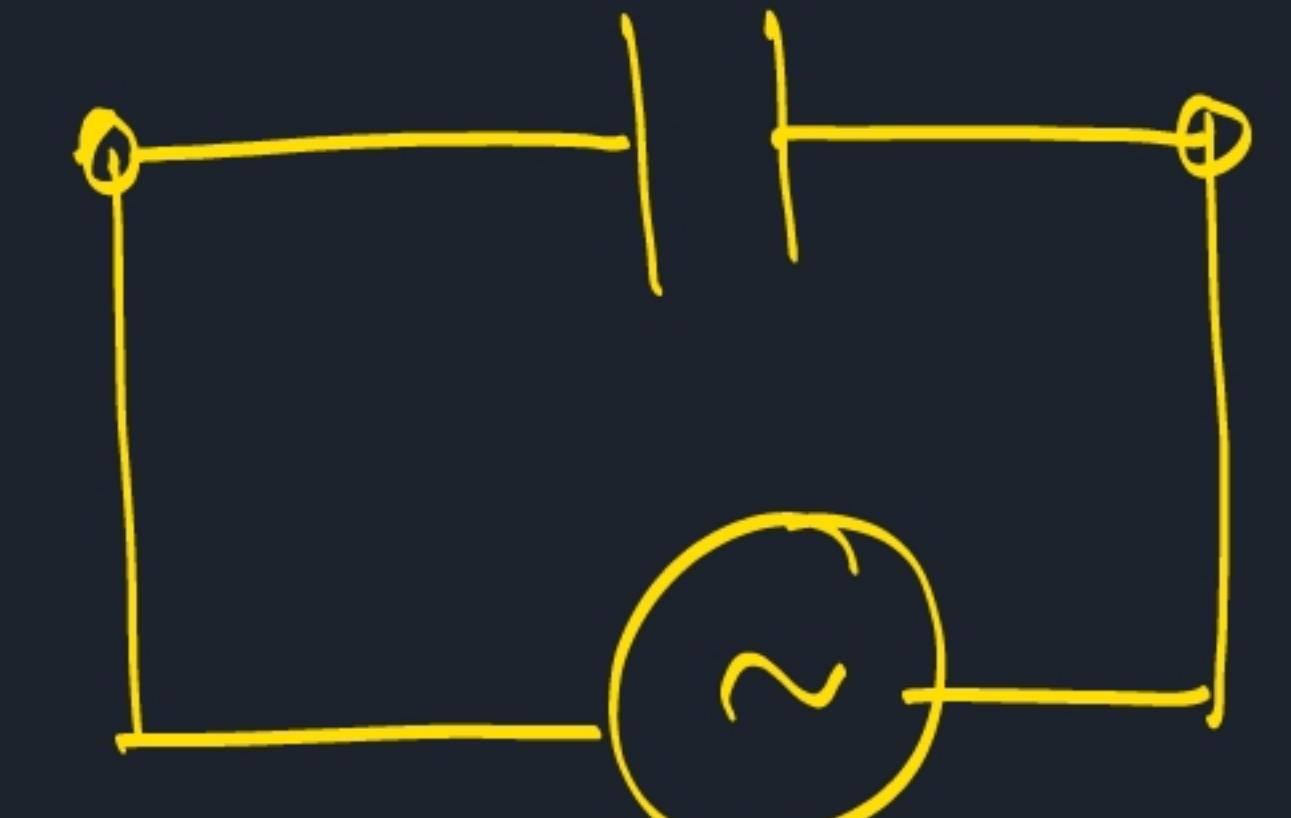

$$\tilde{V} = V_m e^{j(\omega t + \phi)}$$

$$\begin{aligned}\tilde{I} &= j\omega C V_m e^{j(\omega t + \phi)} \\ &= j\omega C \tilde{V}\end{aligned}$$

$$\begin{aligned}X_C &= \text{Capacitive Resistance} \\ &= \left(\frac{1}{\omega C} \right)\end{aligned}$$

$$a_2 \frac{d^2 i(t)}{dt^2} + a_1 \frac{di(t)}{dt} + b_1 \int i(t) dt + a_0 = C$$

$$a_2(j\omega)^2 \tilde{I} + a_1(j\omega) \tilde{I} + \frac{b_1}{j\omega} \cdot \tilde{I} = \tilde{C}$$

$$\tilde{I} = \frac{\tilde{C}}{a_2(j\omega)^2 + a_1(j\omega) + \frac{b_1}{j\omega} + a_0}$$