


We know $\Phi = \vec{B} \cdot \vec{A} = BA \cos \omega t = \Phi_m \cos \omega t$

$$e_1 = N_1 \frac{d\Phi}{dt} = -N_1 \omega \Phi_m \sin(\omega t) = (e_1)_m \cos(\omega t + \pi/2)$$

$$|\vec{E}_1| = (e_1)_{rms} = \frac{N_1 \omega \Phi_m}{\sqrt{2}} = \sqrt{2} \pi f N_1 \Phi_m$$

$$\Phi_m = \frac{E_1}{\sqrt{2} \pi f N_1} \approx \frac{V_1}{\sqrt{2} \pi f N_1}$$

as $R \approx 0$ Therefore, $|\vec{E}_1| \approx |\vec{V}_1|$

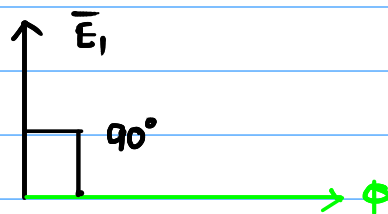


So from the phasor diagram E_1 leads Φ by 90°

⊙ Important Observations:-

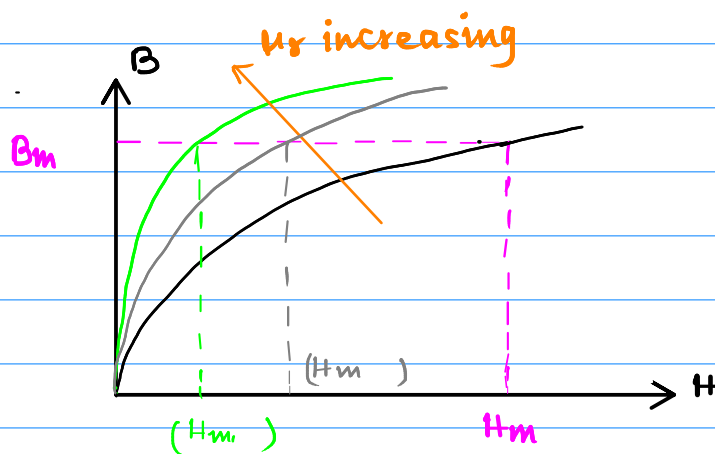- i) Φ_m only depends on N, f for a particular coil (N, f)
- ii) Φ_m does not depend on permeability μ which varies from core to core. That is for any core is N, f and N are fixed then Φ_m also will be fixed.

Now as Φ_m is decided then we are interested in finding out the value of the current that creates Φ_m .



$$B_m = \mu_0 \mu_r H_m$$


$$B_m = \frac{\Phi_m}{A}$$

$$H_m = \frac{N_1 i_m}{l}$$

$$I_m = \frac{i_m}{\sqrt{2}}$$

For a fixed value of B_m , H_m decreases as μ_r increases.

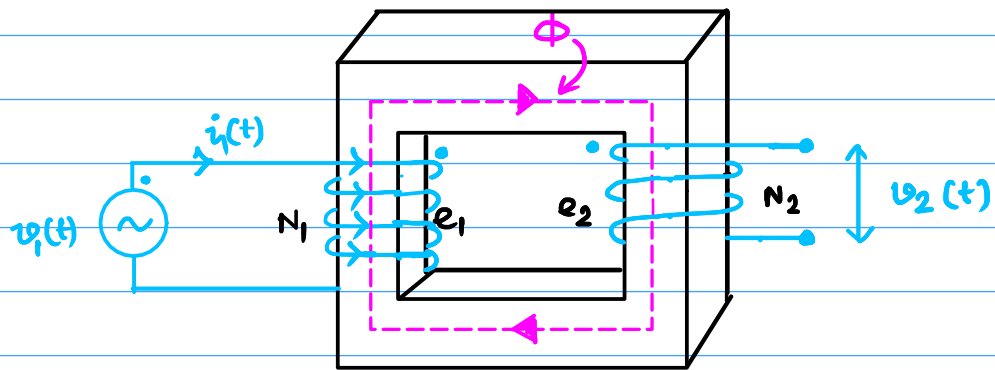8. Now we attach a second coil to the another limb



Flux linkage with coil-2 $\lambda_2 = N_2 \Phi$
 $= N_2 \phi_m \cos \omega t$

$$e_2 = \frac{d(\lambda_2)}{dt} = -N_2 \phi_m \omega \sin \omega t = N_2 \phi_m \omega \cos(\omega t + \pi/2)$$



$$|\bar{E}_2| = (e_2)_{\text{rms}} = \frac{N_2 \phi_m 2\pi f}{\sqrt{2}} = \sqrt{2} \pi f N_2 \phi_m$$

If $R_2 \approx 0$ then $|\bar{E}_2| \approx |\bar{V}_2|$

$$\frac{\bar{V}_1}{N_1} = \frac{\bar{V}_2}{N_2}$$

$$\underline{|\bar{E}_1| = 4.44 f \phi_m N_1 \qquad |\bar{E}_2| = 4.44 f \phi_m N_2}$$

□ Sense of winding:-

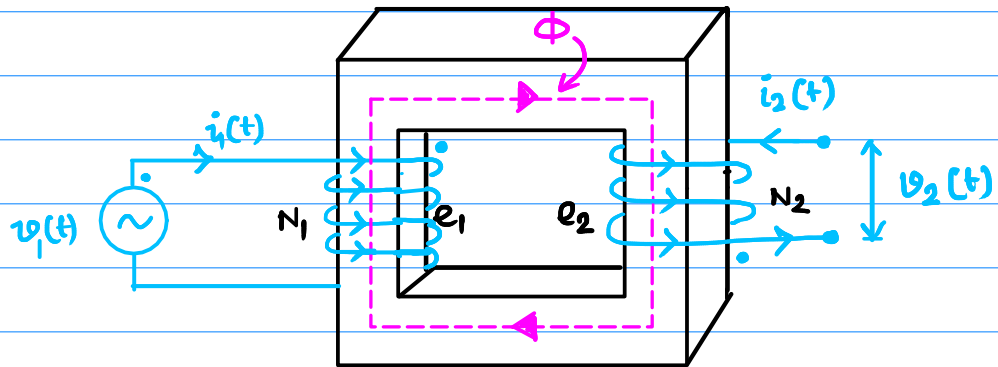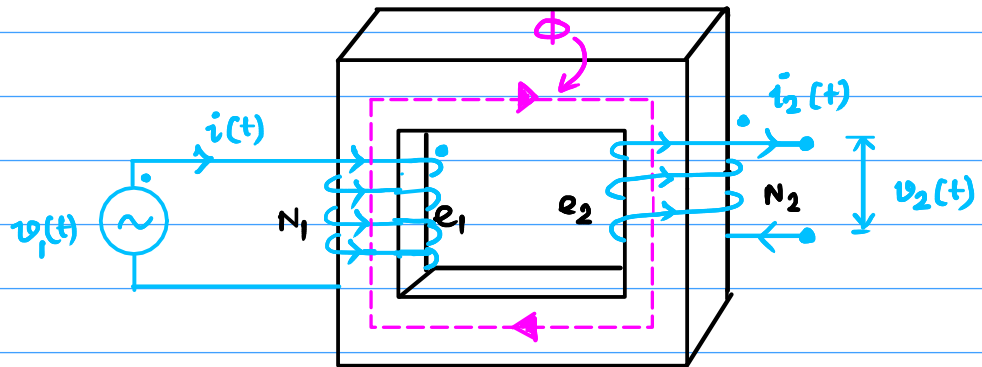


Ideal Transformer:-

1. winding resistances $R_1 = 0$; $R_2 = 0$
Voltage drop $= 0$; $I^2 (R_1 + R_2) = 0$

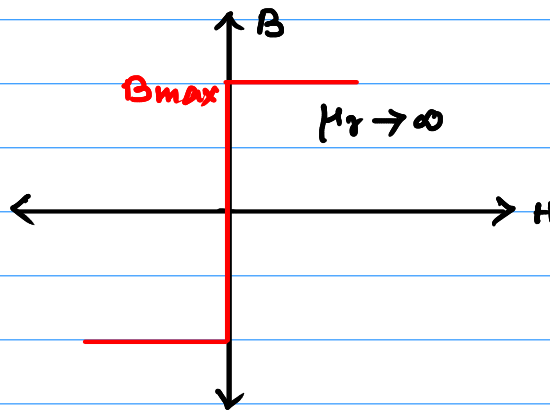2. $(\mu_r)_{\text{core}} \rightarrow \infty$ i.e magnetizing current $I_m = 0$

$$R = \frac{l}{A \mu_0 \mu_r} = 0$$


AS R is zero no mmf
is required to create
flux




3. Losses are zero, therefore efficiency $\eta = 100\%$.

4. leakage flux $= 0$; Flux linked to Coil-1 is equal to flux linked to coil-2

5.

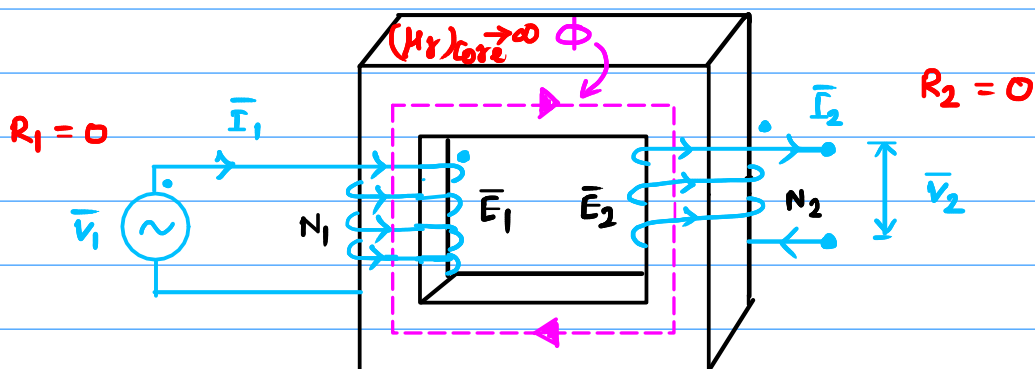

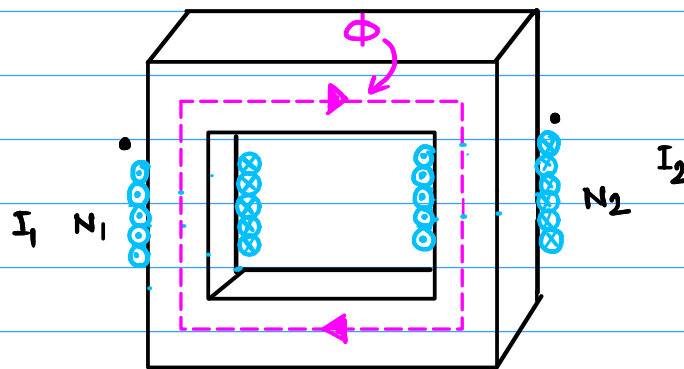

According to Amperes circuital law

$$\oint \vec{H} \cdot d\vec{l} = Ni \quad \mathcal{R} = \text{Reluctance}$$

$$\Rightarrow N_1 i_1 - N_2 i_2 = H \cdot l$$

$$\Rightarrow N_1 i_1 - N_2 i_2 = \Phi \mathcal{R}$$

$$\Rightarrow N_1 i_1 - N_2 i_2 = \Phi \frac{l}{\mu_0 \mu_r A}$$

Now $\mu_r \rightarrow \infty$

Therefore $N_1 i_1 - N_2 i_2 = 0$

$$N_1 \bar{I}_1 = N_2 \bar{I}_2$$

$$\frac{\bar{V}_1}{N_1} = \frac{\bar{V}_2}{N_2}$$

Together we have

$$\bar{V}_1 \bar{I}_1 = \bar{V}_2 \bar{I}_2$$

→ VA rating of T/F
(Capacity)

① Nameplate of a 1ϕ T/F :-



Example:-

For a 1-phase T/F $N_1 = 250$ and $N_2 = 500$. The net cross sectional area of the core = 60 cm^2 .

If the primary is connected to a 50 Hz supply at 230V then calculate

- a) The peak value of the flux density in the core.
- b) The voltage induced in the secondary.

Example:-

A 1-phase T/F has a core with cross sectional area is 150 cm^2 .

It operates at a max. flux density of 1.1 wb/m^2 when connected to a 50 Hz supply.

The secondary winding has 66 turns.

Determine the o/p in kVA if a load of 4Ω impedance is connected to its secondary.



[Assume all internal voltage drops are negligible]

Solution:-

● Phasor Diagram of an ideal T/F:-

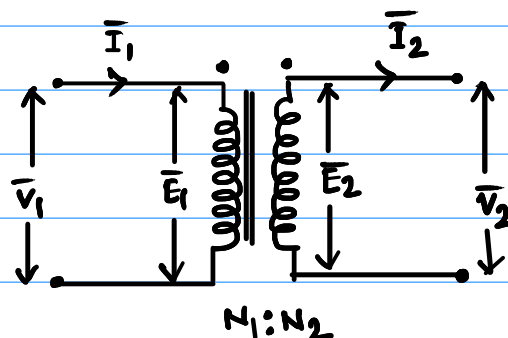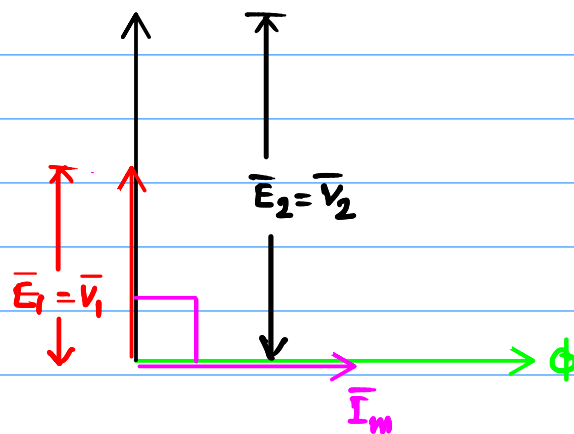- i) ϕ and i_m are in same phase
- ii) \bar{E}_1 leads ϕ by 90°
- iii) \bar{E}_1 and \bar{E}_2 are in phase.
- iv) $\bar{V}_1 = \bar{E}_1$ and $\bar{V}_2 = \bar{E}_2$

$$\frac{\bar{V}_1}{\bar{V}_2} = \frac{N_1}{N_2} = \frac{\bar{E}_1}{\bar{E}_2}$$



Real Transformer :-

Ideal T/F

Real T/F

i) Winding Resistance
 $R_1 = R_2 = 0$

i) $R_1, R_2 > 0$

- a) voltage drop
- b) cu loss (ohmic)
- c) efficiency $\eta \neq 100\%$

ii) $(\mu_r)_{\text{core}} \rightarrow \infty$; $R \rightarrow 0$
 $I_m = 0$

ii) $(\mu_r)_{\text{core}} \Rightarrow \text{finite value}$; $R \neq 0$
 $I_m \neq 0$

iii) Leakage flux = 0
Tight coupling

iii) Leakage flux exists
Induced emf due to ϕ_e

iv) Core loss = 0
 $\eta = 100\%$


iv) Core loss = $P_H + P_E$
 $P_H \propto B_{\text{max}}^n f$
 $P_E \propto B_{\text{max}}^2 f^2$

$P_{\text{core}} = E_1^2$

⊙ Real Transformer:-

In practical T/F μ_r is high but finite
Therefore a finite amount of current I_μ (say) is required to establish the flux ϕ_{max} .
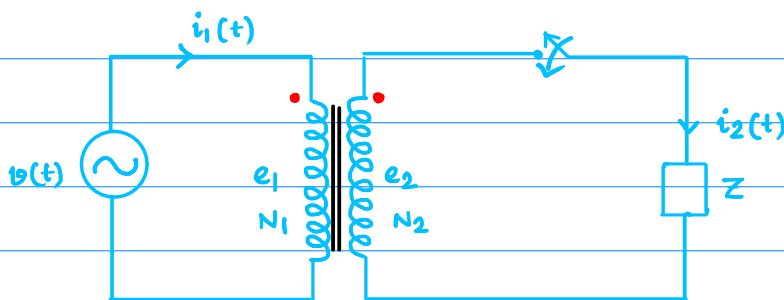
$$\phi_m = \frac{N_1 I_\mu}{\mathcal{R}} \quad I_\mu = \text{magnetizing current}$$



After the switch is closed a current I_2 flows through coil-2 which produces a flux that according to the Lenz's law try to oppose the main flux ϕ_m in the core.


$$\phi_m' = \frac{N_1 I_\mu - N_2 I_2}{\mathcal{R}}$$

As $\phi \downarrow$ $E_1 \downarrow$ So the coil-1 draws more current.
Let this extra current is I_2'

$$\phi_m'' = \frac{N_1 I_\mu - N_2 I_2 + N_1 I_2'}{\mathcal{R}}$$

This transient part exist until and unless

$$N_1 I_2' = N_2 I_2$$

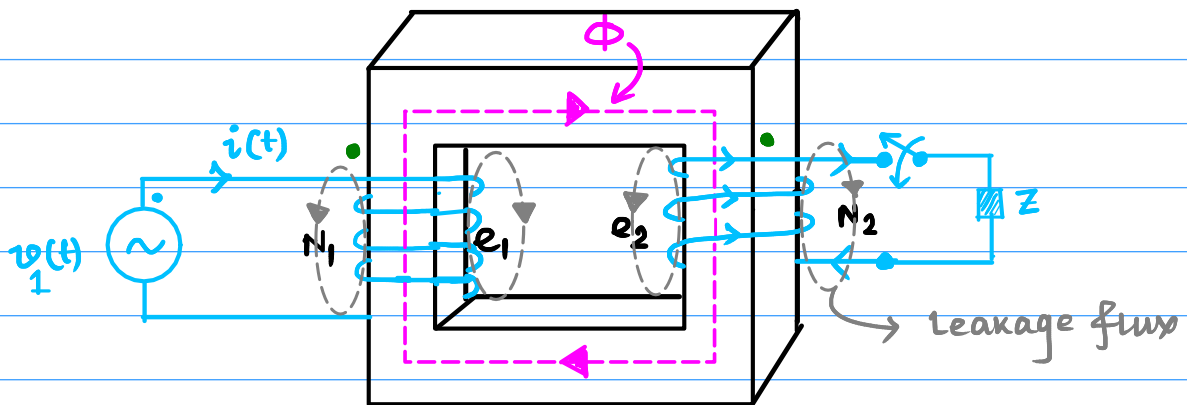

For coil-1 we can write $\phi_1 = \phi_m + \phi_{l1}$
 For coil-2 we can write $\phi_2 = \phi_m - \phi_{l2}$

For coil-1

$$\bar{V}_1 = \bar{I}_1 R_1 + \bar{E}_1'$$

$$\begin{aligned} \text{We know } E_1' &= \sqrt{2} \pi f \phi_1 N_1 \\ &= \sqrt{2} \pi f (\phi_m + \phi_{l1}) N_1 \\ &= \sqrt{2} \pi f \phi_m N_1 + \sqrt{2} \pi f \phi_{l1} N_1 \\ &= E_1 + E_{l1} \end{aligned}$$

voltage induced
due to mutual flux

voltage induced
due to leakage flux

$$\bar{V}_1 = \bar{I}_1 R_1 + \bar{E}_1 + \bar{E}_{l1}$$

The leakage flux is the flux that does not link the other coil. Therefore this flux has nothing to do with energy transfer b/w the coils. Therefore it is represented by a small leakage inductance.

Similarly for coil-2

$$\bar{E}_2' = \bar{V}_{load} + \bar{I}_2 R_2$$

$$E_2' = \sqrt{2} \pi f (\Phi_m - \Phi_{l2}) N_2$$

$$= \sqrt{2} \pi f \Phi_m N_2 - \sqrt{2} \pi f \Phi_{l2} N_2$$

$$= E_2 - E_{l2}$$

$$\bar{E}_2 - \bar{E}_{l2} = \bar{V}_{load} + \bar{I}_2 R_2$$

\bar{E}_{l1} and \bar{E}_{l2} are the voltages induced due to leakage flux. \bar{E}_{l1} and \bar{E}_{l2} can be represented by the corresponding reactances x_1 and x_2 which is basically the leakage reactances of coil-1 and coil-2.

$$\bar{V}_1 = \bar{I}_1 R_1 + j \bar{I}_1 x_1 + \bar{E}_1$$

$$\bar{E}_2 = \bar{I}_2 R_2 + j \bar{I}_2 x_2 + \bar{V}_{load}$$

$$N_1 \bar{I}_2' = N_2 \bar{I}_2 \longrightarrow \text{Transformer Action}$$

