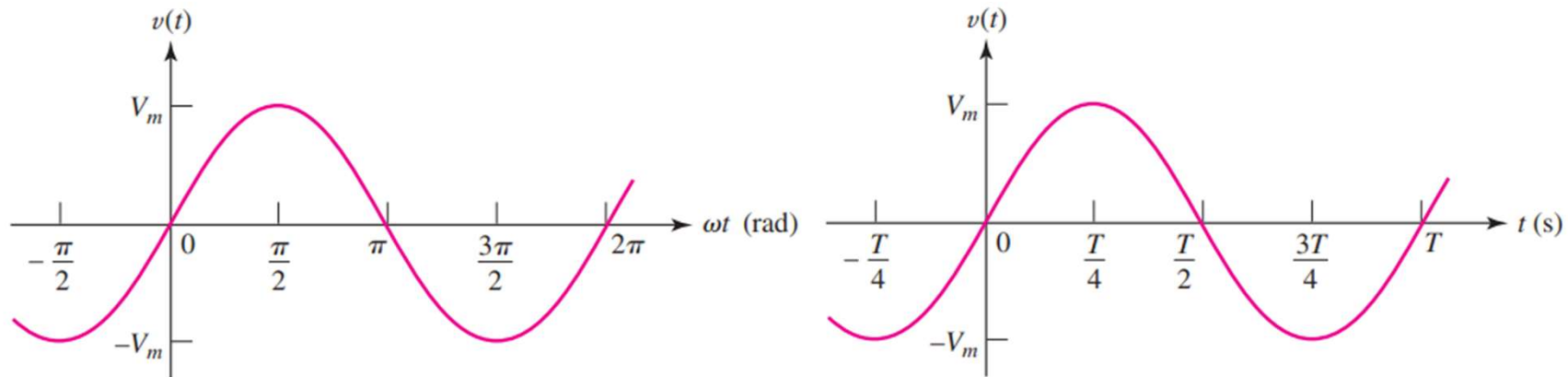



CHARACTERISTICS OF SINUSOIDS



- ❖ A sinusoidally varying voltage function can be represented by $v(t) = V_m \sin(\omega t)$
- ❖ The function repeats itself in every 2π radians. Therefore, period is 2π radians.
- ❖ Frequency $f = 1/T$
- ❖ We know $\omega T = 2\pi$

CONCEPTS OF LAGGING & LEADING

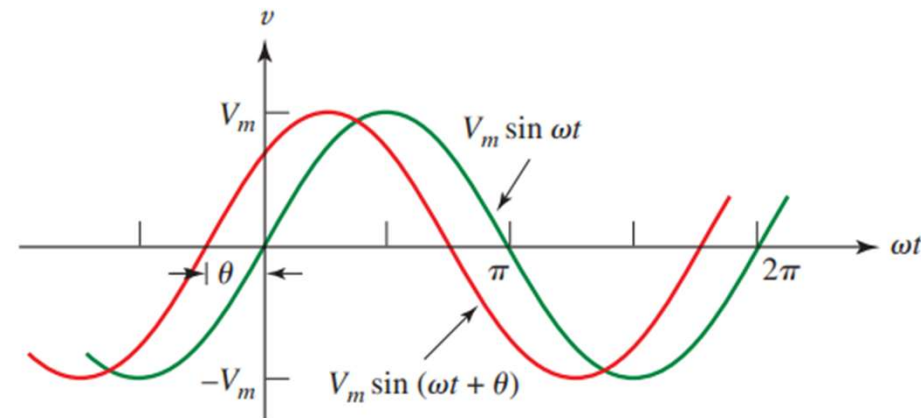- ❖ More general form of sinusoids is $v(t) = V_m \sin(\omega t + \theta)$
- ❖ Here θ is the phase angle measured in radian. However, for representation purpose sometimes we use to express θ in degree.
- ❖ At $t = 0$, $v(t = 0) = V_m \sin \theta$
- ❖ Therefore, $V_m \sin(\omega t + \theta)$ sinusoid leads $V_m \sin(\omega t)$ sinusoid.



COMMON TERMS IN AC CIRCUITS

RMS and the average value of a signal.

Ref. William H. Hayt Jr, Jack E. Kemmerly and Steven M. Durbin, “Engineering Circuits Analysis”, McGraw Hill publishers

SINUSOIDAL FORCED RESPONSE

❖ A series R-L circuit is excited by a sinusoidal voltage waveform.

❖ The corresponding differential equation is

$$Ri(t) + L \frac{di(t)}{dt} = V_m \cos \omega t$$

❖ The response $i(t)$ = Natural Response + Forced Response

❖ Natural Response


$$i_{nat}(t) = ke^{-\frac{R}{L}t}$$

❖ The forced Response is

$$i_{for}(t) = C_1 \cos \omega t + C_2 \sin \omega t$$



❖ Apply $i_{for}(t)$ in the differential equation and determine the values of C_1, C_2

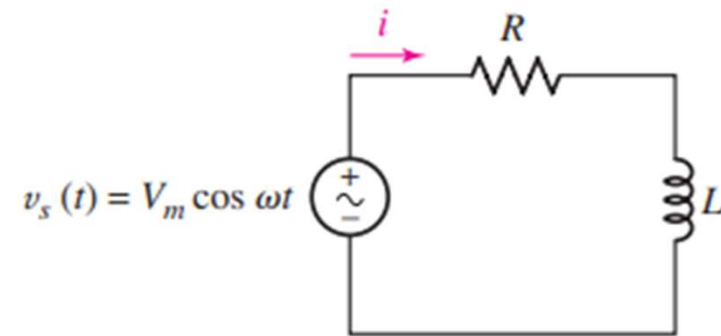❖ The overall response $i(t) = i_{for}(t) + ke^{-\frac{R}{L}t}$



COMPLEX FORCING FUNCTION

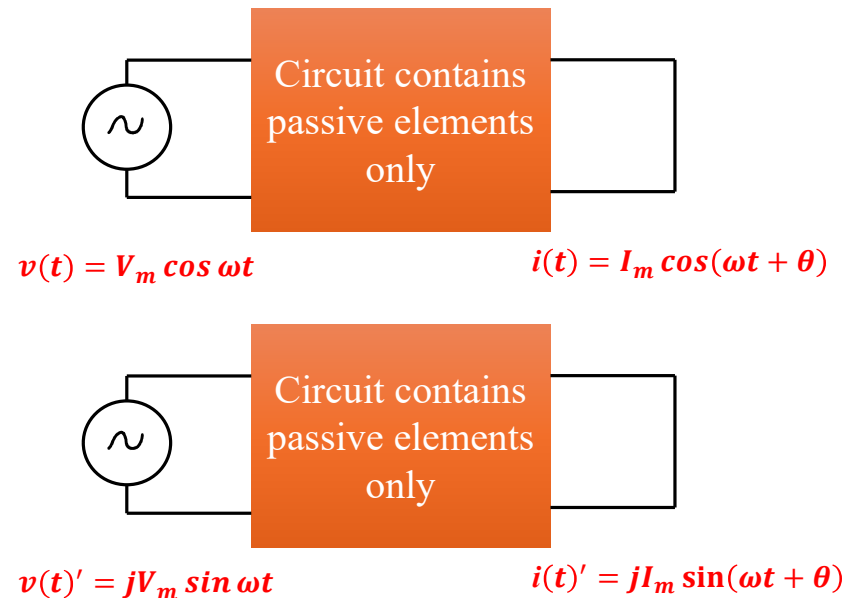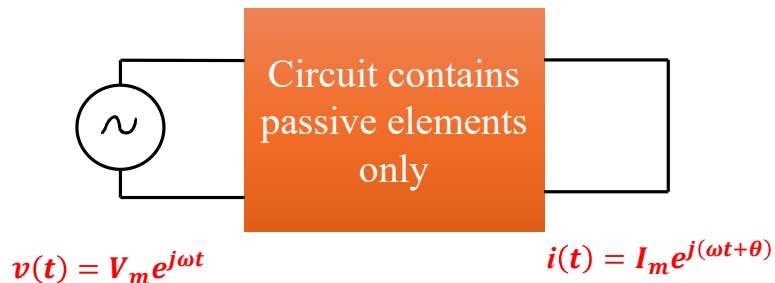- ❖ In this module we will focus only on the sinusoidal steady state response of the circuit.
- ❖ Using Mesh analysis/Nodal analysis we can solve the problem, however, the approach will be cumbersome.
- ❖ We use an alternative approach, where, $v - i$ relationship will be a simple algebraic expression.
- ❖ We start with Euler's identity $e^{j\theta} = \cos \theta + j \sin \theta$.



COMPLEX FORCING FUNCTION

❖ Put $v(t) = V_m e^{j\omega t}$, $i(t) = I_m e^{j(\omega t + \theta)}$ in the differential equation of R-L circuit.

$$L \frac{d}{dt} (I_m e^{j(\omega t + \theta)}) + R I_m e^{j(\omega t + \theta)} = V_m e^{j\omega t}$$


$$I_m e^{j\theta} = \frac{V_m}{R + j\omega L}$$

$$I_m \angle \theta = \frac{V_m \angle 0}{R + j\omega L}$$

❖ Find out I_m, θ in terms of R, L, ω, V_m .

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$
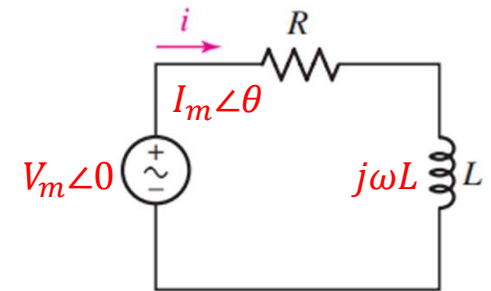
$$\theta = -\tan^{-1} \frac{\omega L}{R}$$





❖ This abbreviated complex representation is also known as phasor.

THE RESISTOR (PHASOR DIAG.)

- ❖ For the resistance $v(t) = Ri(t)$
- ❖ Let us apply a voltage $v(t) = V_m e^{j(\omega t + \phi)}$
- ❖ The current flowing through the resistance

$$i(t) = \frac{V_m}{R} e^{j(\omega t + \phi)} = I_m e^{j(\omega t + \phi)}$$

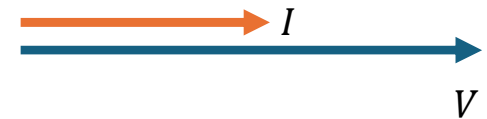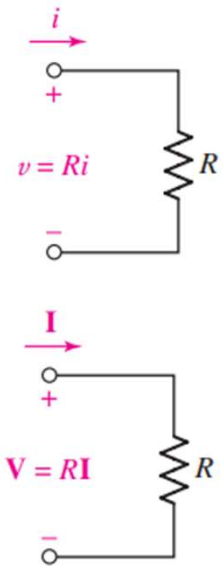- ❖ Which says that the voltage phasor and the current phasor are in the same direction and phase lag/lead is zero.
- ❖ For resistive load $V = RI$, where V, I are the phasor representation of voltage and current, respectively.



THE INDUCTOR (PHASOR DIAG.)


- ❖ For the inductor $v(t) = L \frac{di(t)}{dt}$
- ❖ Let us apply a voltage $i(t) = I_m e^{j(\omega t + \phi)}$
- ❖ The current flowing through the resistance

$$v(t) = j\omega L I_m e^{j(\omega t + \phi)} = j\omega L i(t)$$

- ❖ Which says that the voltage phasor leads the current phasor by an angle of 90° .
- ❖ For sinusoidal input, the effective impedance of an inductor is

$$X_L = \omega L$$

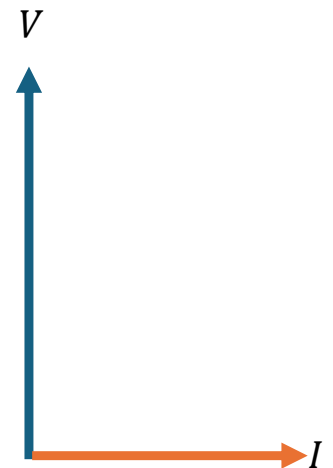- ❖ For inductive load $V = jX_L I$, where V, I are the phasor representation of voltage and current, respectively.



THE CAPACITOR (PHASOR DIAG.)

❖ For the capacitor $i(t) = C \frac{dv(t)}{dt}$

❖ Let us apply a voltage $v(t) = V_m e^{j(\omega t + \phi)}$

❖ The current flowing through the resistance



$$i(t) = j\omega C V_m e^{j(\omega t + \phi)} = j\omega C v(t)$$

❖ Which says that the voltage phasor lags the current phasor by an angle of 90° .




❖ For sinusoidal input, the effective impedance of a capacitor is

$$X_C = \frac{1}{\omega C}$$

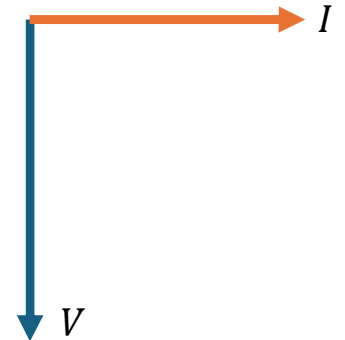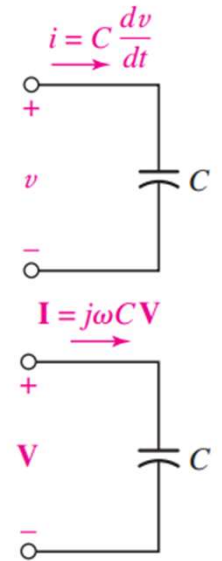❖ For capacitive load $V = -jX_C I$, where V, I are the phasor representation of voltage and current, respectively.



SERIES R-L CIRCUIT

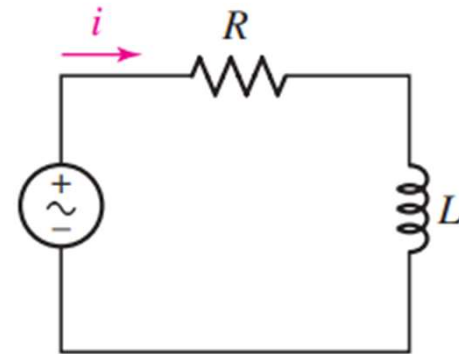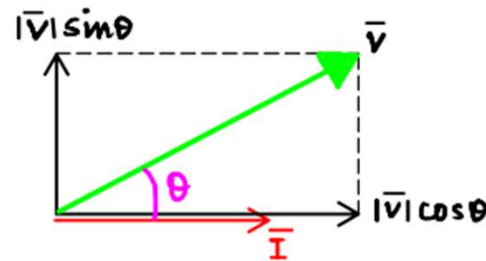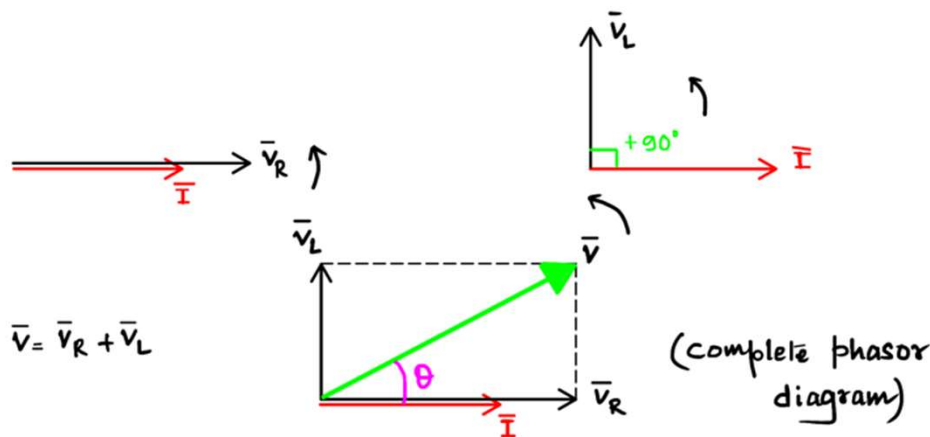


❖ Instantaneous power

$$p(t) = v(t)i(t)$$

$$= V_r I_r \cos \theta (1 - \cos 2\omega t) - V_r I_r \sin \theta \sin 2\omega t$$

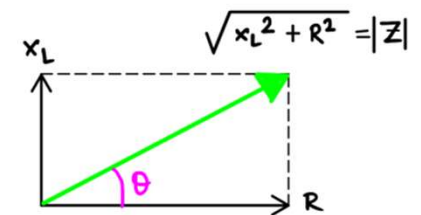As the current is a common phasor, subdivide each voltage phasor by current phasor



❖ Average Power

$$P_{avg} = V_r I_r \cos \theta$$

$$|Z| = \sqrt{X_L^2 + R^2} = \sqrt{(\omega L)^2 + R^2}$$





(Impedance Triangle)

$$R = |Z| \cos \theta \quad X_L = |Z| \sin \theta$$


$$\bar{Z} = R + jX_L = |Z| e^{j\theta} = |Z| \angle \theta$$

❖ Draw the power triangle from the phasor diagram.

SERIES R-L-C CIRCUIT

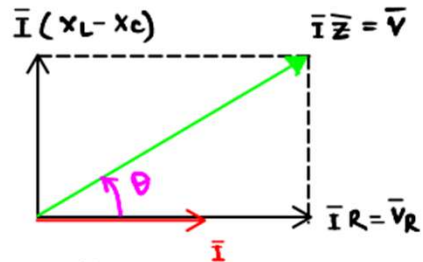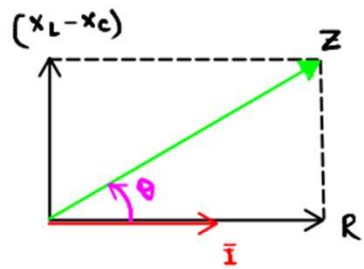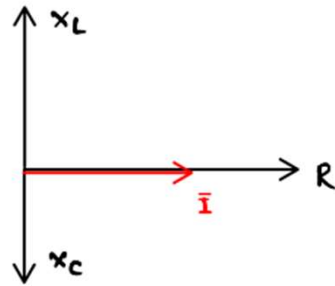
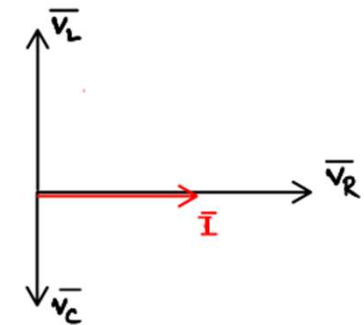


Resistive Inductive



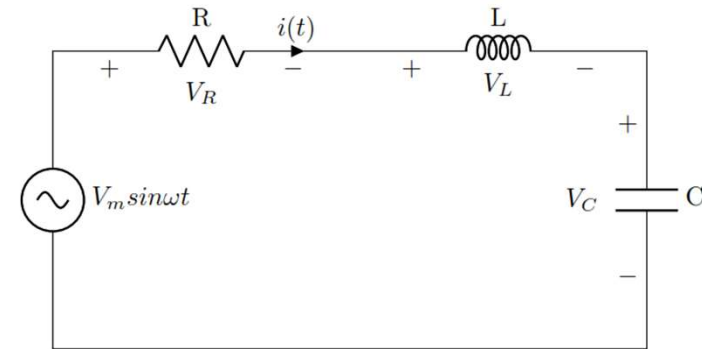


- ❖ For series R-L-C circuit assume $X_L > X_C$.
- ❖ The impedance $Z = R + j(X_L - X_C)$
- ❖ The power factor is $pf = \cos \theta = \frac{R}{|Z|}$

PARALLEL R-L-C CIRCUIT

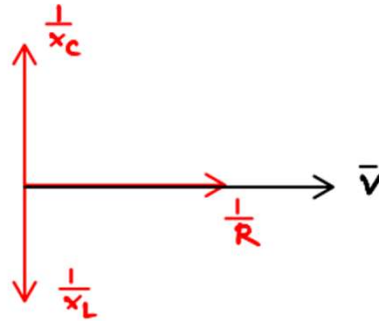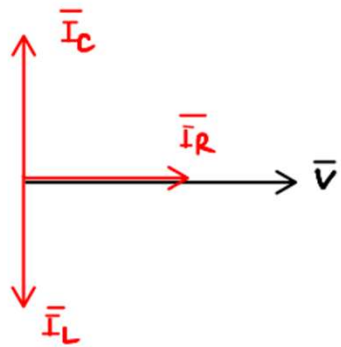

$$X_L > X_C$$

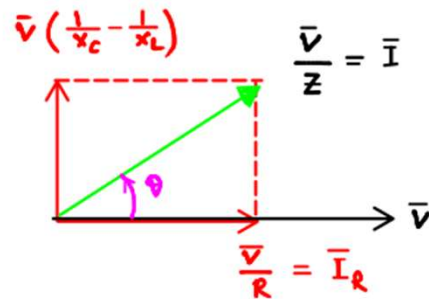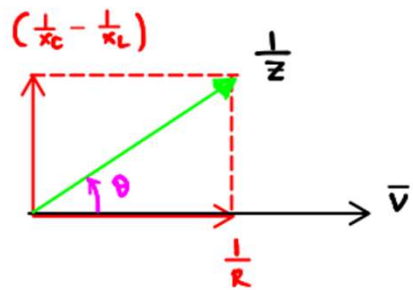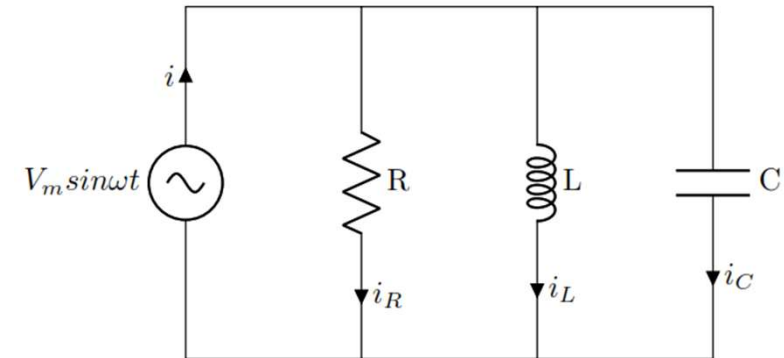

Resistive - Capacitive

❖ For series R-L-C circuit assume $X_L > X_C$.

❖ The admittance $\frac{1}{Z} = \frac{1}{R} + j\left(\frac{1}{X_C} - \frac{1}{X_L}\right)$

❖ The power factor is $pf = \cos \theta = \frac{|Z|}{R}$


PROBLEMS

Problem-2:

Consider the following circuit is at steady state. Determine the expression $i(t)$

Ans:

$$i(t) = 16 \cos(3000t - 126.9^\circ)$$

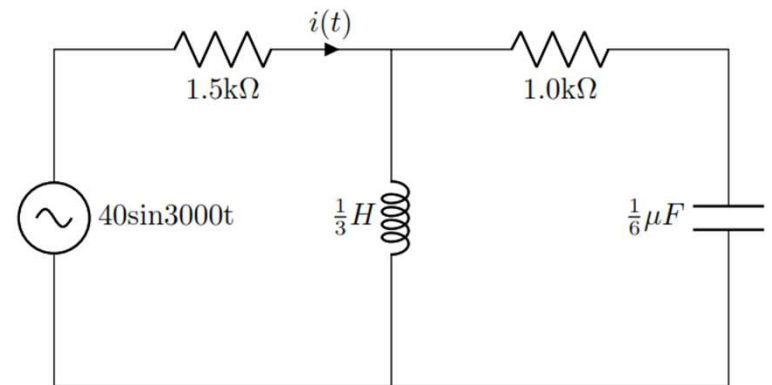

PROBLEMS


Problem-3:

Using the Nodal Analysis, determine the node voltages in phasor form.

Ans:

$$V_1 = 1.062 \angle 23.3^\circ \text{ V}$$
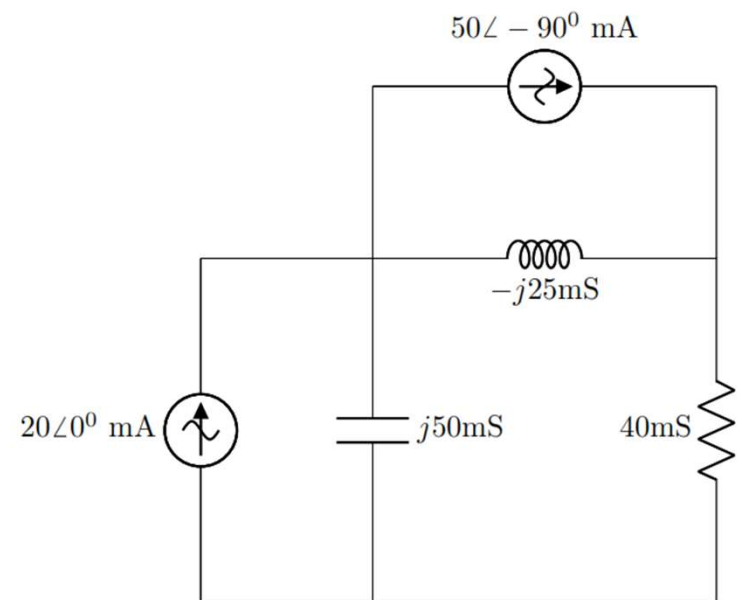
$$V_2 = 1.593 \angle -50^\circ \text{ V}$$



PROBLEMS

Problem-4:


Determine the Thevenin's and Norton's equivalent circuits of the given network.

Ans:

$$V_{th} = 16.77 \angle -33.4^\circ \text{ V}$$

$$I_N = 2.6 + j1.5 \text{ A}$$

$$R_{th} = R_N = 2.5 - j5 \, \Omega$$

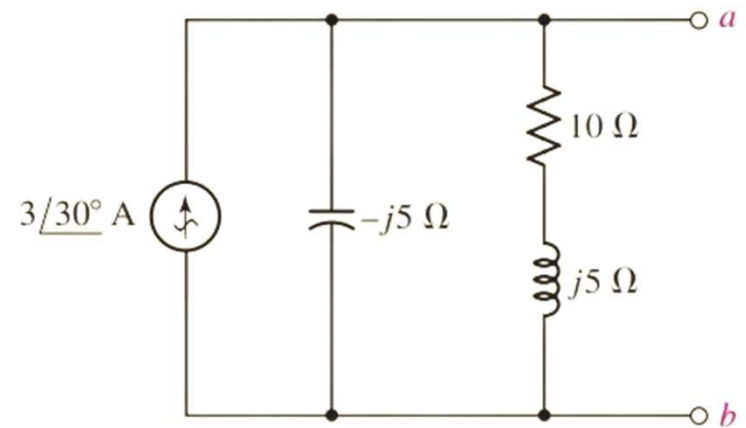


PROBLEMS

Problem-5:

Determine the rms and average of the given voltage waveform.

Ans:

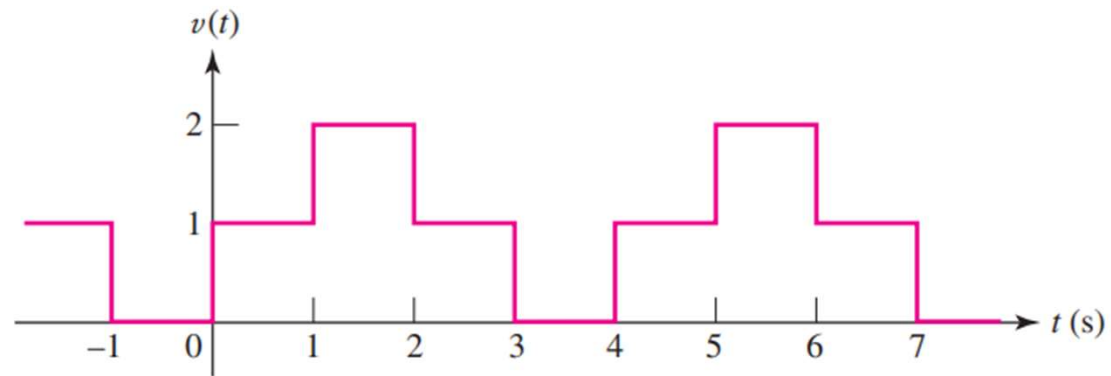

Ref. William H. Hayt Jr, Jack E. Kemmerly and Steven M. Durbin, "Engineering Circuits Analysis", McGraw Hill publishers

PROBLEMS

Problem-6:

Calculate the complex power delivered to each passive components of the given circuit. The voltage magnitude is given in rms.

Ans:

