

Digital Electronics (NECE 102)

(Digital Counter)

Nirupama Mandal

Email: nirupama@iitism.ac.in

Counters in Digital Logic

- ✓ Digital Counters are a specific type of sequential logic circuit.
- ✓ Used to count and store the number of occurrences of events or processes.
- ✓ Used for the frequency divider
- ✓ Counters are made using flip-flops to store count values and respond to clock signals

Digital Counters - Key Characteristics

- **Maximum Count:** Determined by the number of flip-flops (2^n states for n flip-flops)
- **Up/Down Counting:** Ability to count in ascending or descending order
- **Synchronous/Asynchronous Operation:** Timing of state changes
- **Free-Running/Self-Stopping:** Continuous or limited counting
- **Positive or Negative edge triggered:** depending on the connection provided at the clock input of the flip-flops.

The behavior of a counter can be explained in terms of timing diagram (waveforms), truth table and/or state diagrams.

Types of Counters

- Asynchronous (Ripple) Counters
- Synchronous Counters
- Up/Down Counters

Advanced Counter Concepts

- **Decade Counters:** Count from 0 to 9 in decimal
 - **Ring Counters:** Circular shift register-based counters
 - **Johnson Counters:** Twisted ring counters
 - **Gray-Code Counters:** Output Gray code sequences
-



Counter Design Considerations

- ❑ Modulus:
 - The *modulus* of a counter is the number of states in its count sequence.
 - A counter that has modulus value n is commonly referred to as a *modulo- n* or *MOD- n* counter. For example, a counter that counts up from 0 to 5 and then overflows is a MOD-6 counter because it has six states.
 - The maximum possible modulus of a counter is determined by the number of flip-flops
- ❑ Number of Flip-Flops: Determined by desired maximum count (2^n)
- ❑ Edge Triggering: Positive or negative edge-triggered designs

Asynchronous (Ripple) Counters



- Clock pulses "ripple" through flip-flops sequentially
- Simpler design but slower operation due to propagation delays

Asynchronous (Ripple) Counters

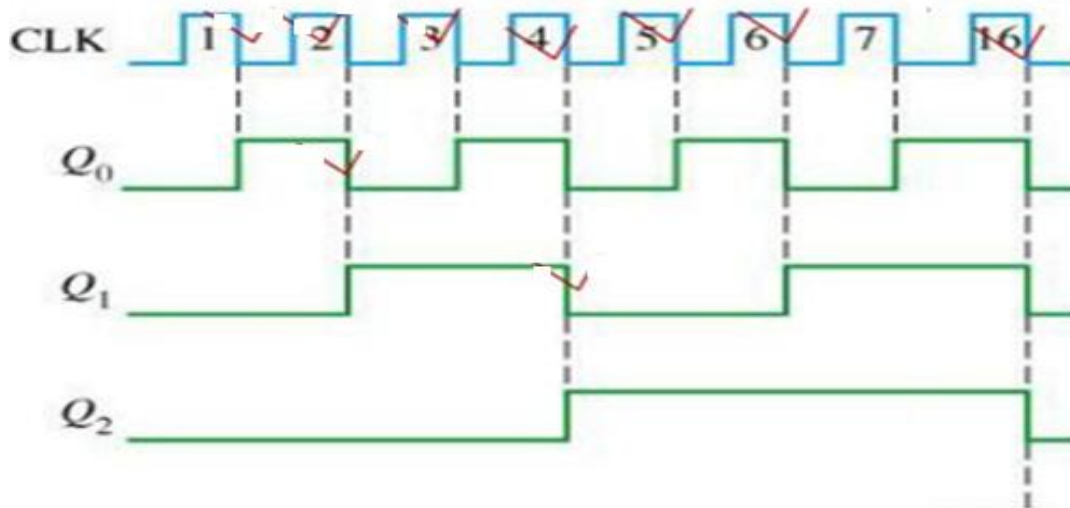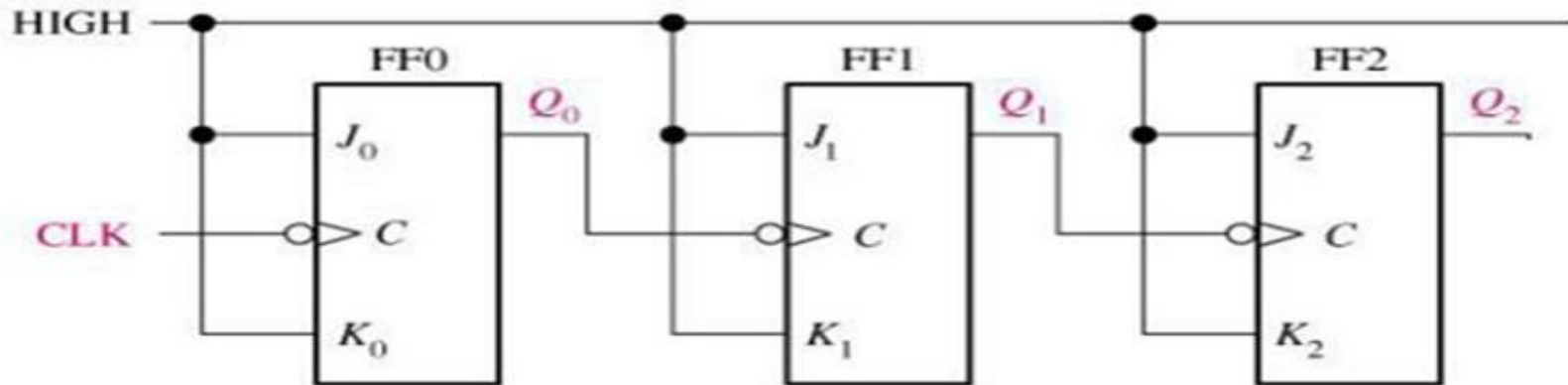




CLK PLUSE	Q2	Q1	Q0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
REPEAT	0	0	0

4-bit Asynchronous (Ripple) Counters

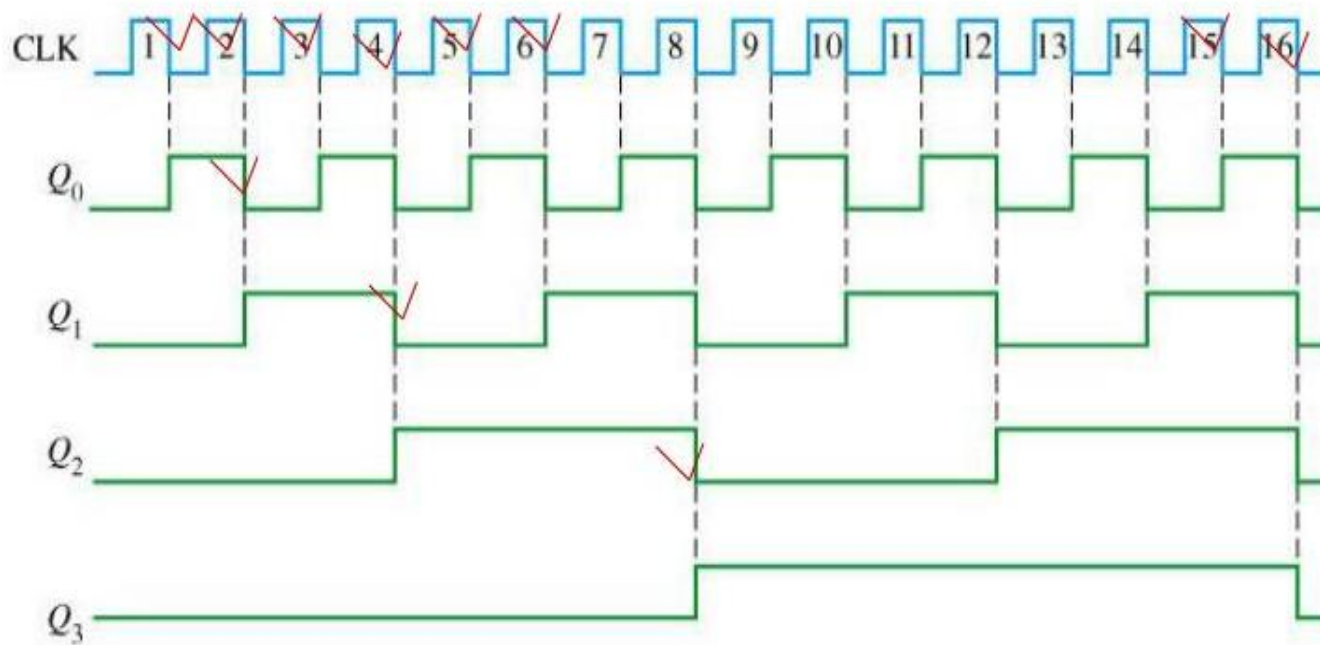
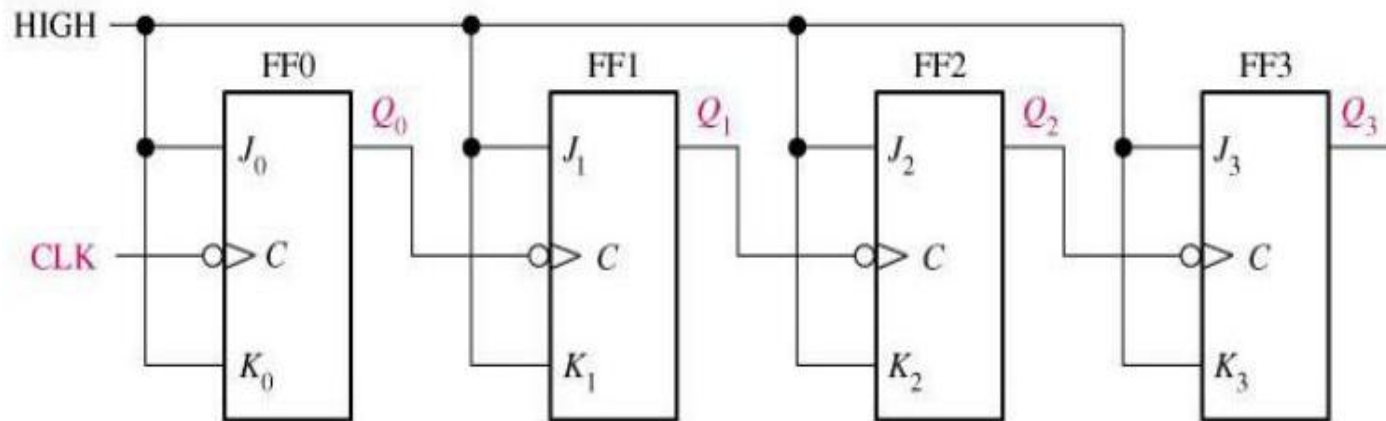


CLK PLUSE	Q3	Q2	Q1	Q0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1
16 REPEAT	0	0	0	0

MOD 6 Counter (Asynchronous)

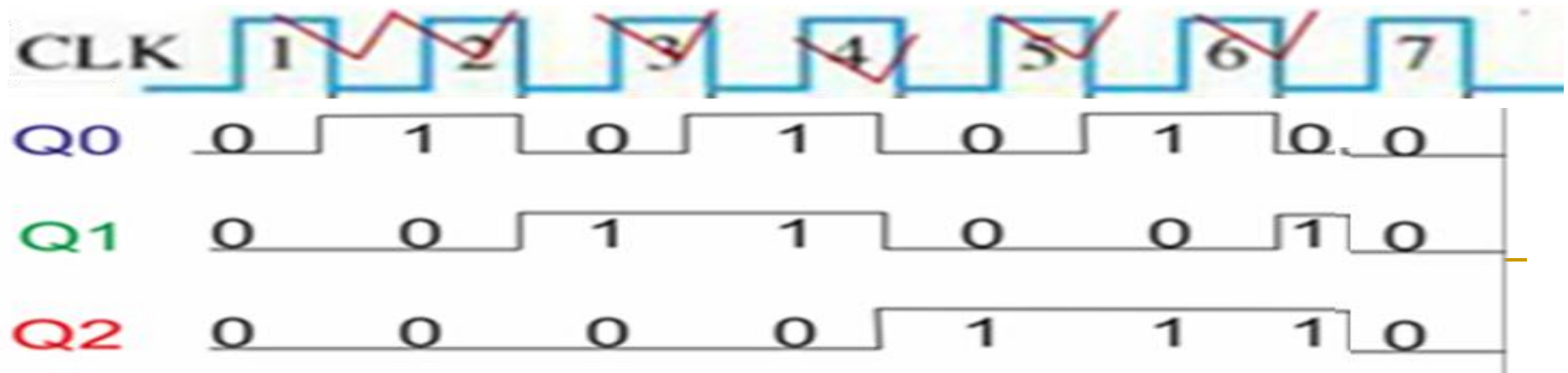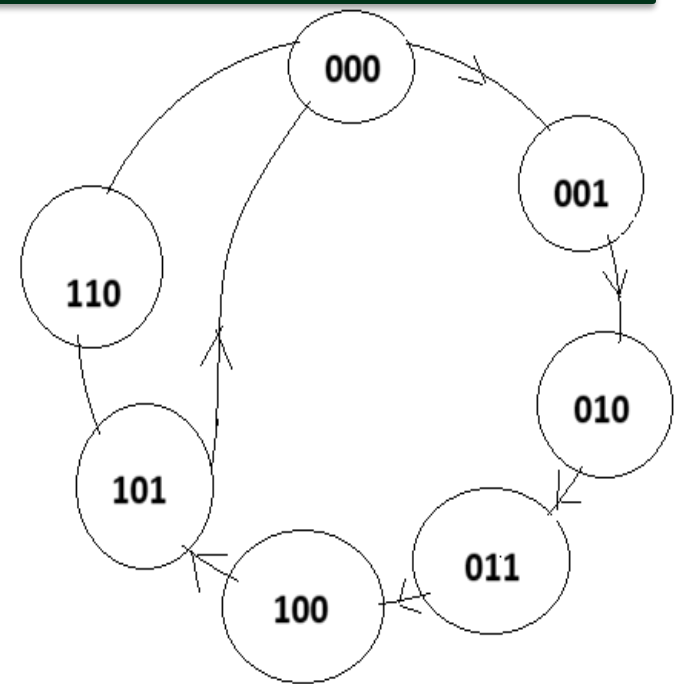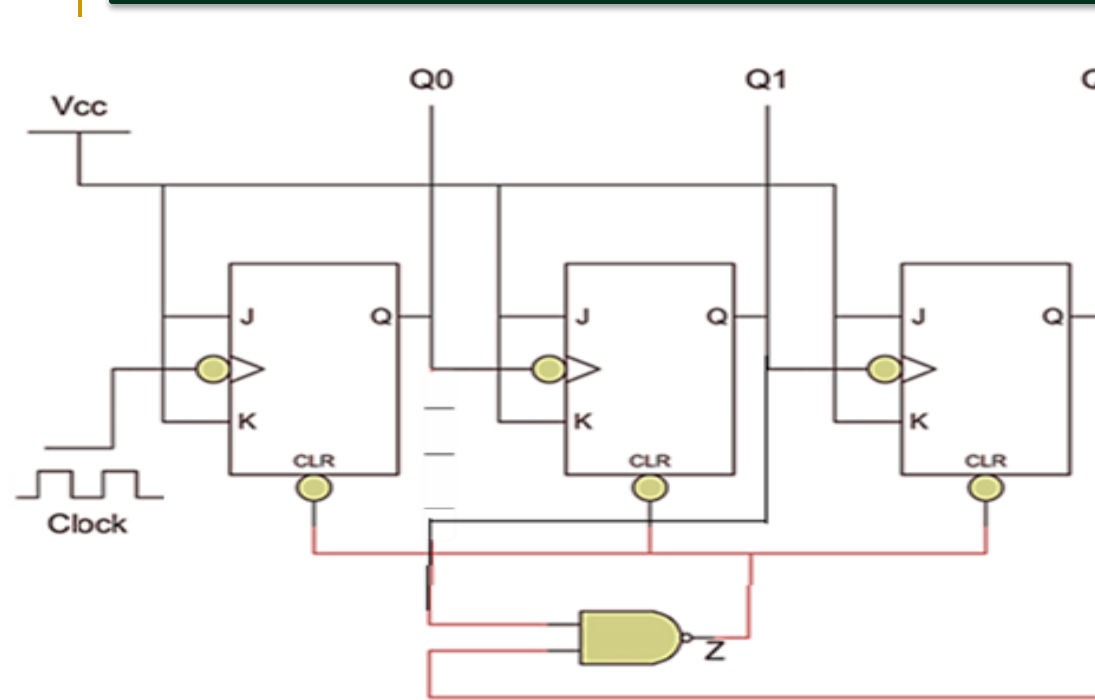

3 bit synchronous counter

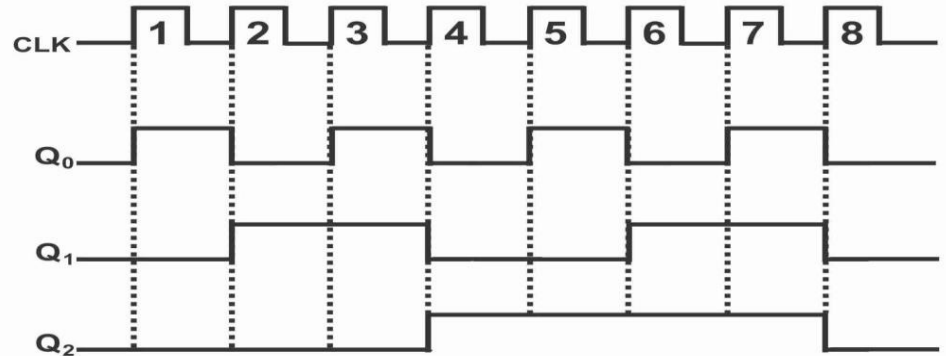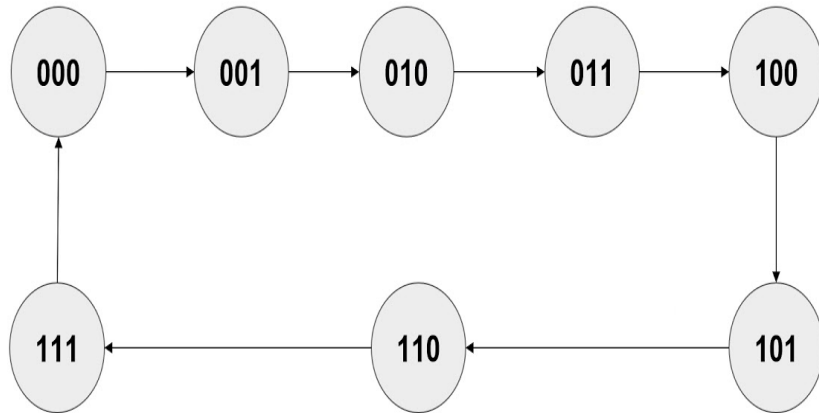

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	1	0
1	0	1

Q_2	Q_1	Q_0	Q_2^*	Q_1^*	Q_0^*	T_2	T_1	T_0
0	0	0	0	0	1			
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			

3 bit synchronous counter

Q_2	Q_1	Q_0	Q_2^*	Q_1^*	Q_0^*	T_2	T_1	T_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

$T_2 = Q_1 Q_0$


$Q_1 Q_0$	00	01	11	10
$\bar{Q}_2$ 0	0	0	1	0
1	0	0	1	0

$T_1 = Q_0$


$Q_1 Q_0$	00	01	11	10
$\bar{Q}_2$ 0	0	1	1	0
1	0	1	1	0

$T_0 = 1$


$Q_1 Q_0$	00	01	11	10
$\bar{Q}_2$ 0	1	1	1	1
1	1	1	1	1

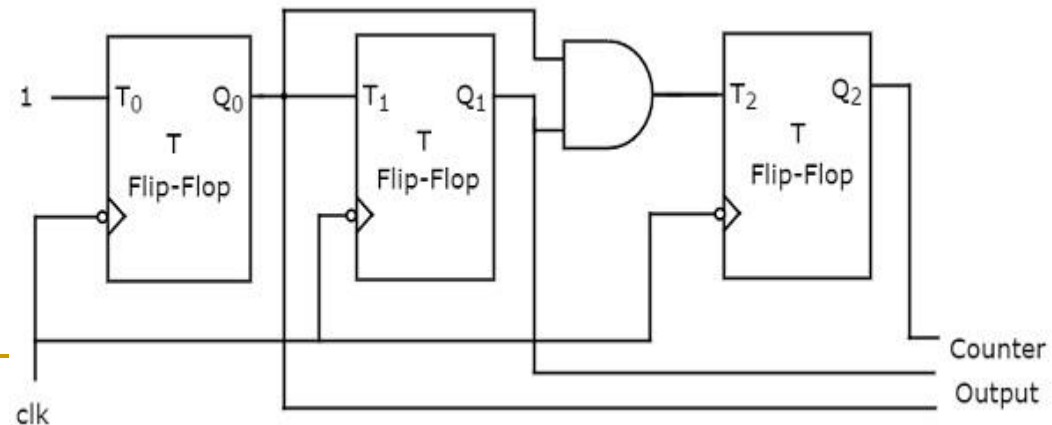

3 bit synchronous up/Down Counter

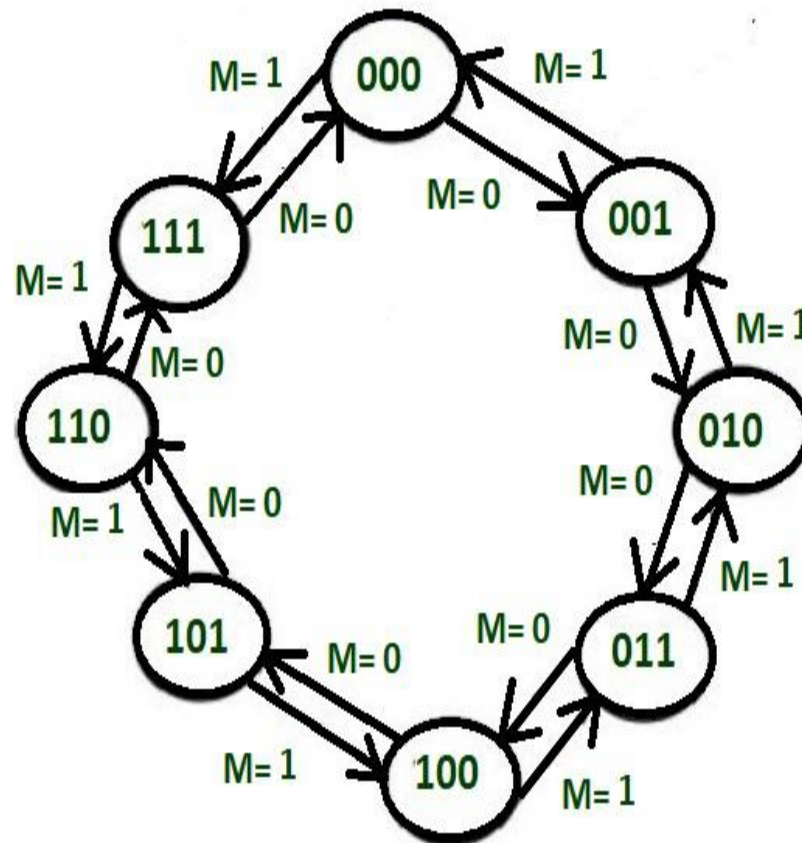

3 bit synchronous up/Down Counter

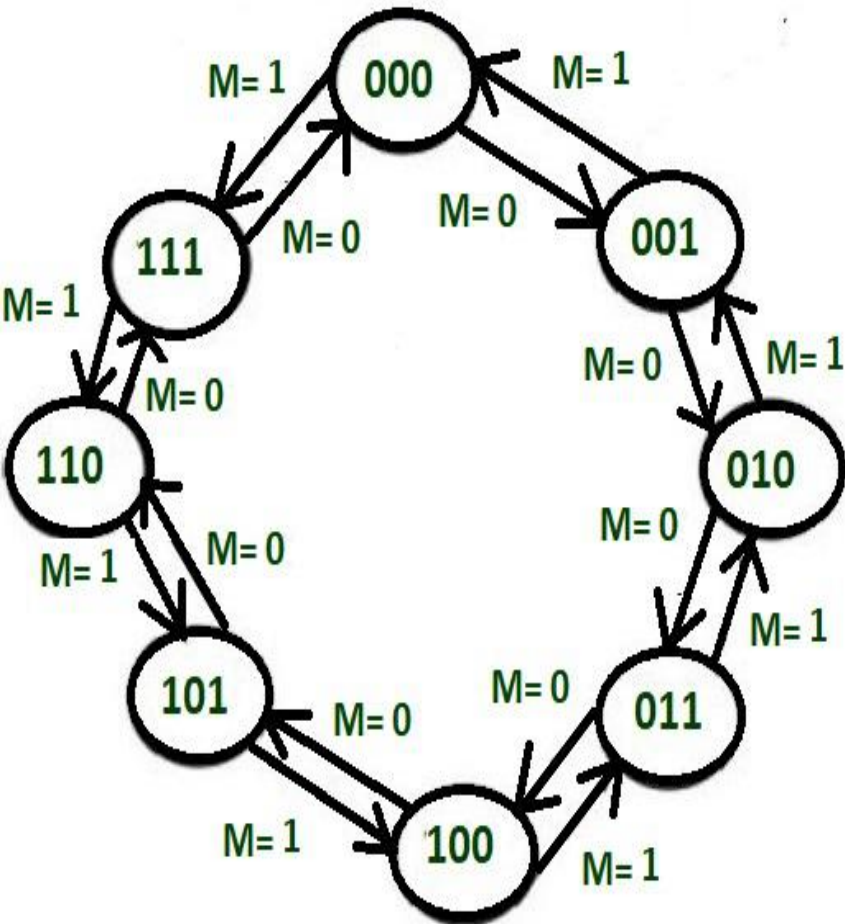

M	Q_3	Q_2	Q_1	Q_3^*	Q_2^*	Q_1^*	T_3	T_2	T_1
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

3 bit synchronous up/Down Counter

M Q ₃	Q ₂ Q ₁			
	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	1	0	0	0
10	1	0	0	0

$$T_3 = M'Q_2Q_1 + MQ_2'Q_1'$$

M Q ₃	Q ₂ Q ₁			
	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	1

$$T_2 = M'Q_1 + MQ_1'$$

M Q ₃	Q ₂ Q ₁			
	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$T_1 = 1$$


M	Q ₃	Q ₂	Q ₁	Q ₃ *	Q ₂ *	Q ₁ *	T ₃	T ₂	T ₁
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

3 bit synchronous up/Down counter


$$T_3 = M'Q_2Q_1 + MQ_2'Q_1'$$

$$T_2 = M'Q_1 + MQ_1'$$

$$T_1 = 1$$

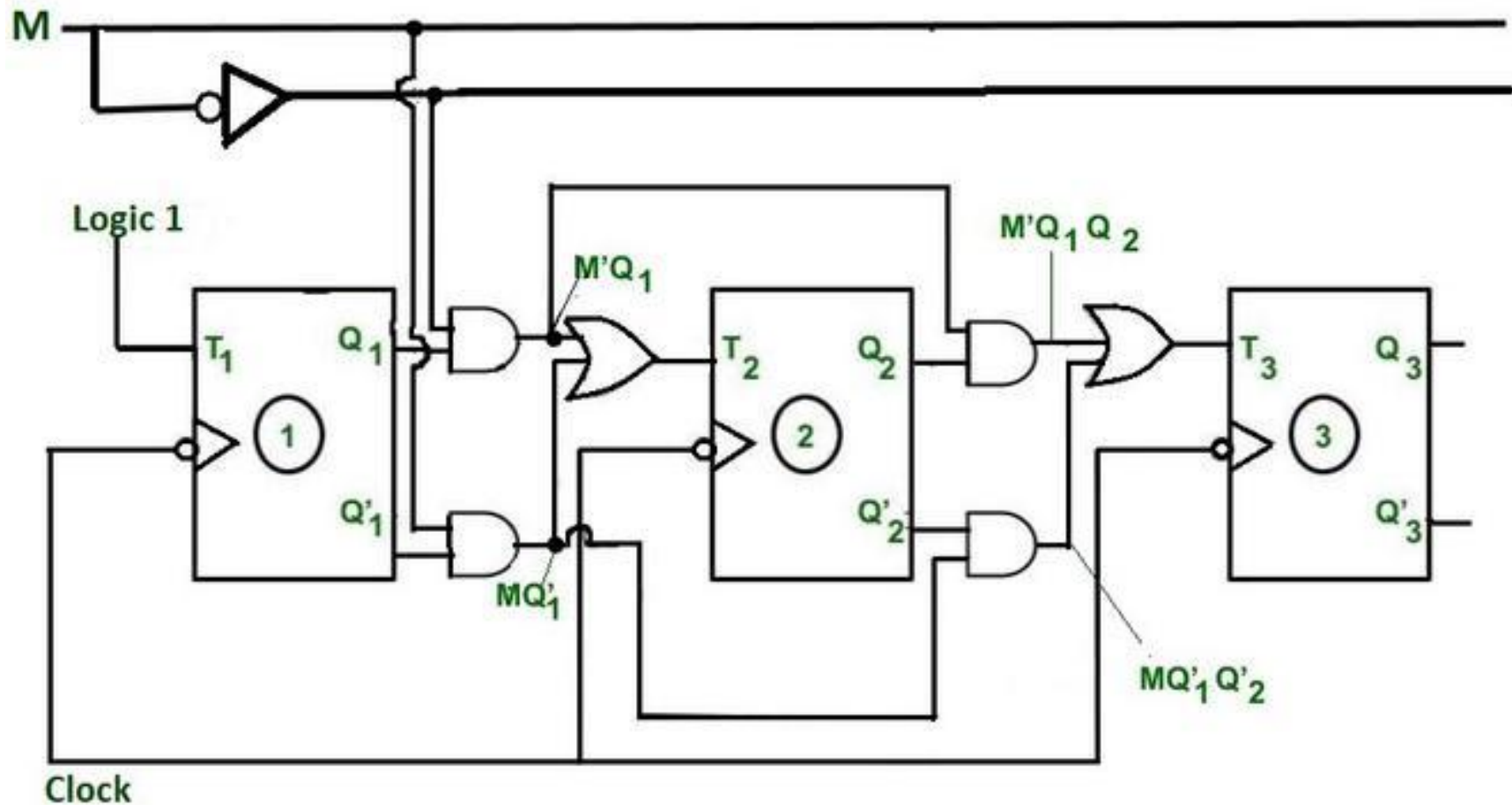


Ring counter

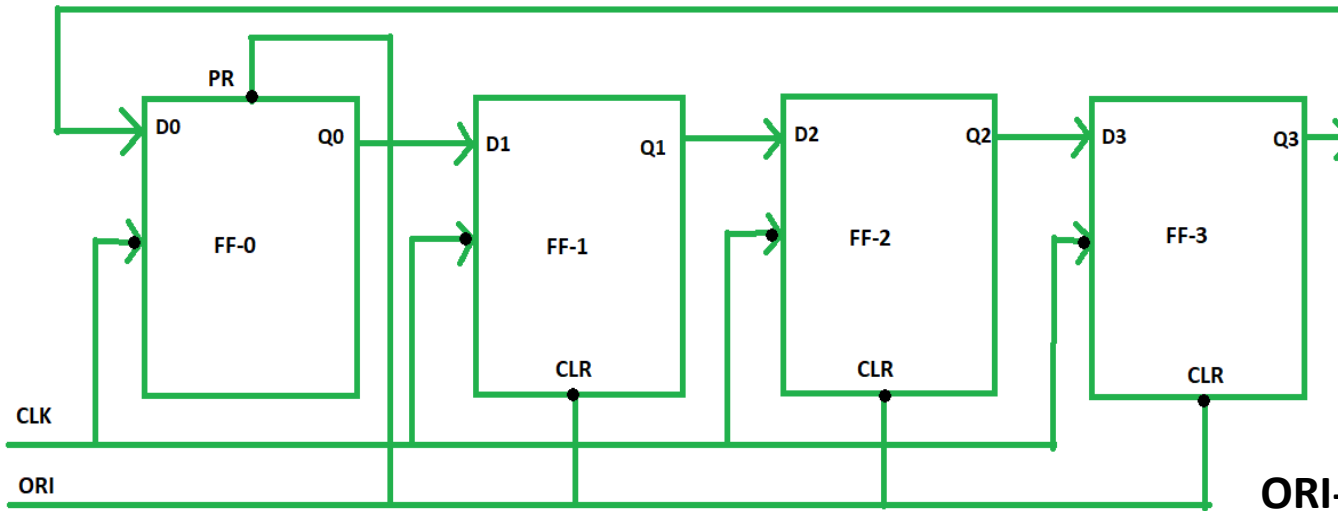


Ring Counter

ORI	clk	Q_0	Q_1	Q_2	Q_3
low	X	1	0	0	0
high	low	0	1	0	0
high	low	0	0	1	0
high	low	0	0	0	1
high	low	1	0	0	0

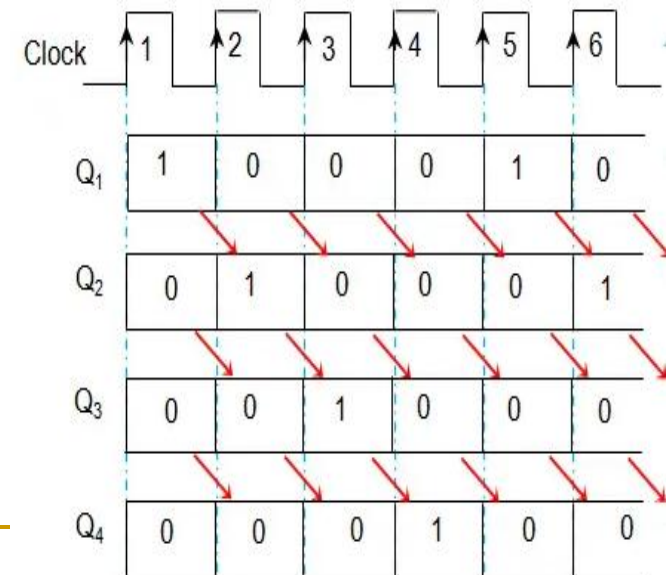

Output waveform of 4-bit ring counter

Ring counter

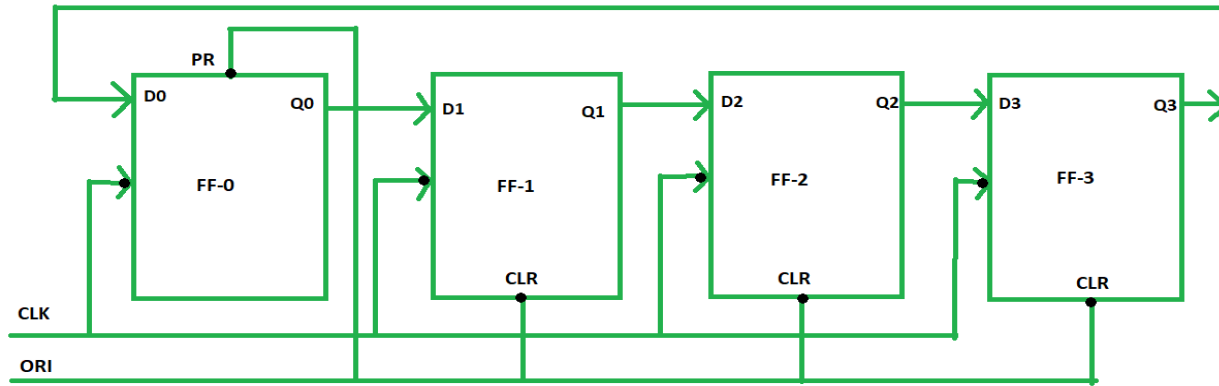


Ring Counter

ORI	clk	Q ₀	Q ₁	Q ₂	Q ₃
low	X	1	0	0	0
high	low	0	1	0	0
high	low	0	0	1	0
high	low	0	0	0	1
high	low	1	0	0	0




Johnson Counter

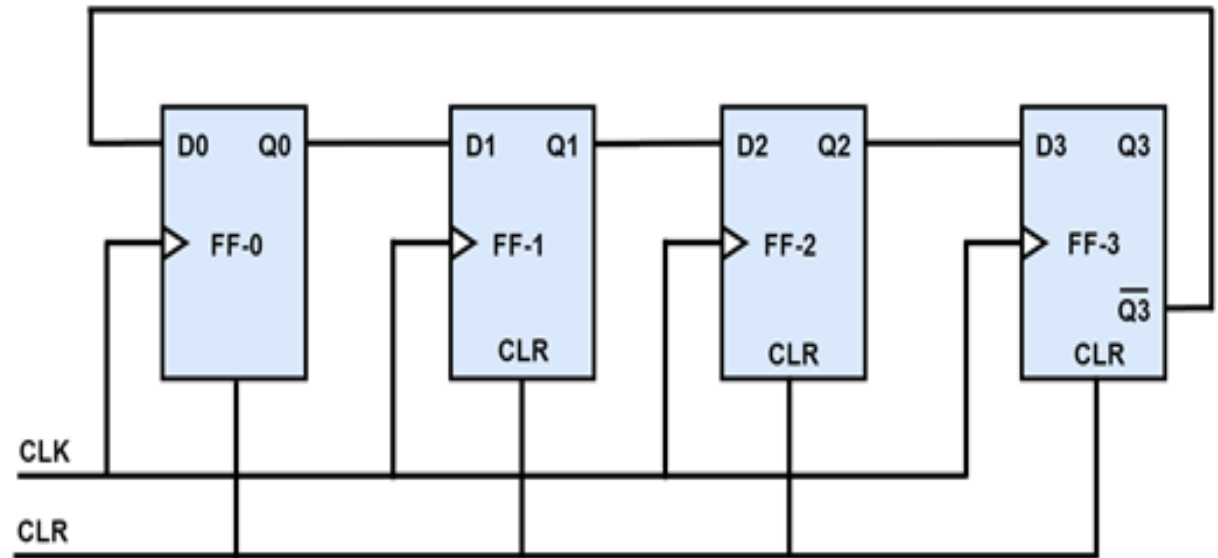


CP	Q1	Q2	Q3	Q4
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

Johnson Counter

CP	Q1	Q2	Q3	Q4
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

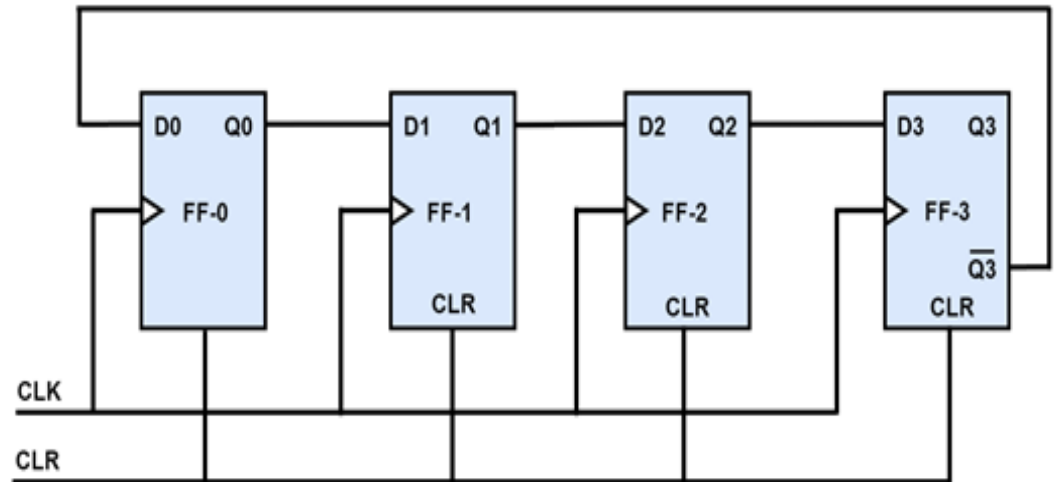


4 bit synchronous Decade Counters

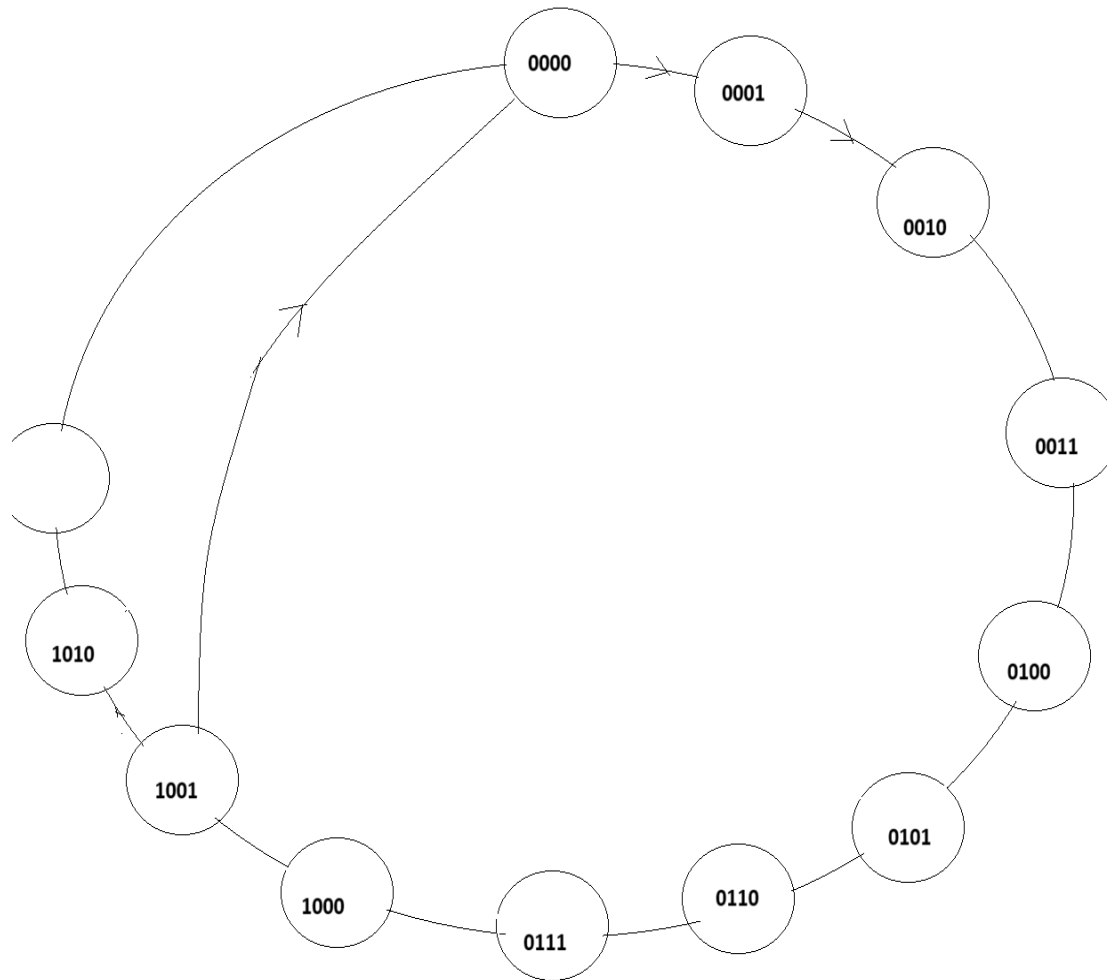

4 bit synchronous Decade Counters

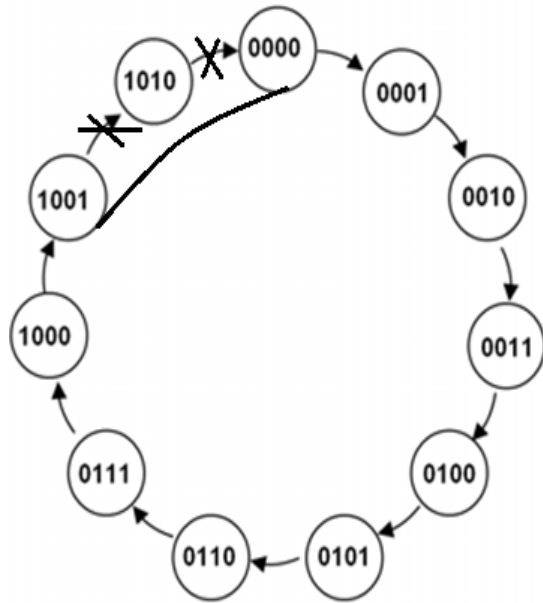State diagram and State table of decade counter



Present State				Next state							
Q ₃	Q ₂	Q ₁	Q ₀	Q ₃ '	Q ₂ '	Q ₁ '	Q ₀ '	T ₃	T ₂	T ₁	T ₀
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1

Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	1	0
1	0	1

4 bit synchronous Decade Counters – Input output relationship (using K Map)

Present State				Flip Flop Input			
Q_3	Q_2	Q_1	Q_0	T_3	T_2	T_1	T_0
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	0	0	0	0	1
0	0	1	1	0	1	1	1
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	1
0	1	1	0	0	0	0	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1
1	0	0	1	1	0	0	1

Q_3Q_2		Q_1Q_0			
		00	01	11	10
00	0	0	0	0	0
01	0	0	1	0	
11	X	X	X		X
10	0	1	X		X

$$T_3 = Q_3Q_0 + Q_2Q_1Q_0$$

Q_3Q_2		Q_1Q_0			
		00	01	11	10
00	0	0	1	0	
01	0	0	1	0	
11	X	X	X		X
10	0	0	X		X

$$T_2 = Q_1Q_0$$

Q_3Q_2		Q_1Q_0			
		00	01	11	10
00	0	1	1	0	
01	0	1	1	0	
11	X	X	X		X
10	0	0	X		X

$$T_1 = Q_3'Q_0$$

$M Q_3$	Q_2Q_1			
	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$T_0 = 1$$

4 bit synchronous Decade Counters

$$T_3 = Q_3Q_0 + Q_2Q_1Q_0$$

$$\tau_2 = Q_1 Q_0$$

$$T_1 = Q_3' Q_0$$

$$T_0 = 1$$

