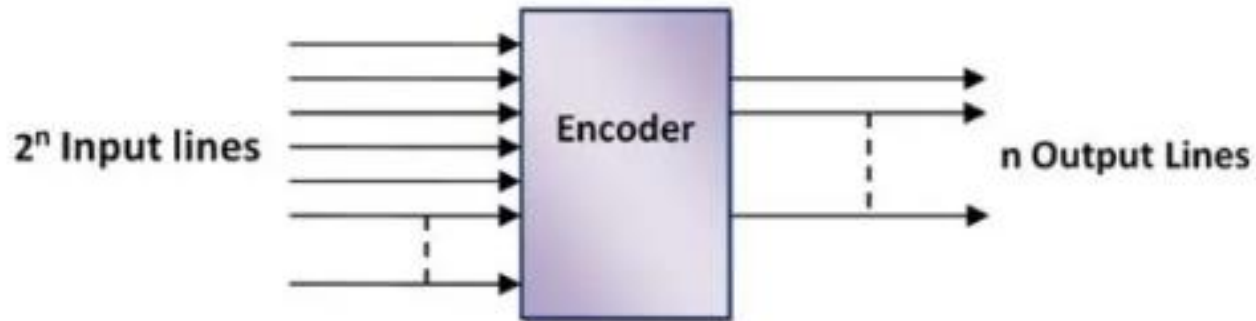
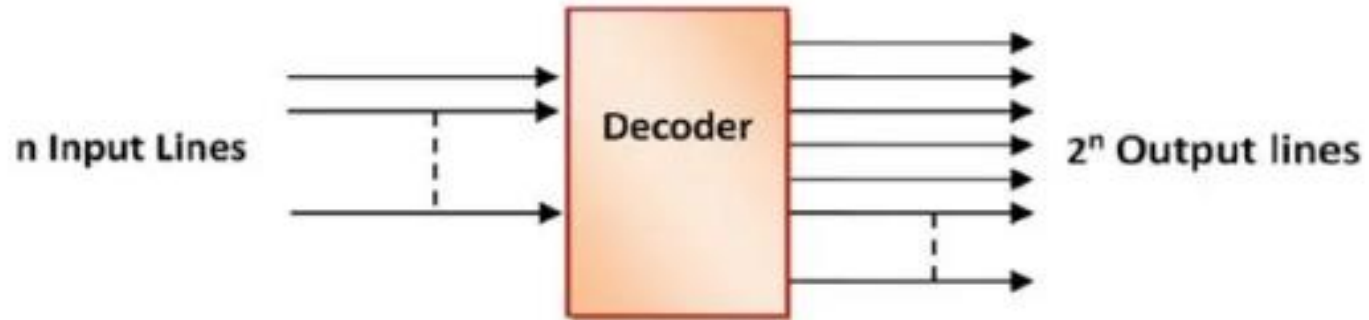

Digital Electronics (NECE102)

(Decoder and Encoder)

Nirupama Mandal

Email: nirupama@iitism.ac.in

Decoder and Encoder



Decoder

Decoder is a combinational logic circuit that converts an N-bit binary input code into M output channels in such a way that only one output channel is activated for each one of the possible combinations of inputs.

It is a multiple input and multiple output device.


It converts N input lines into a maximum of 2^N output lines.

Application: to convert binary to other codes


Binary to Octal

Binary to Hexadecimal


Binary to decimal

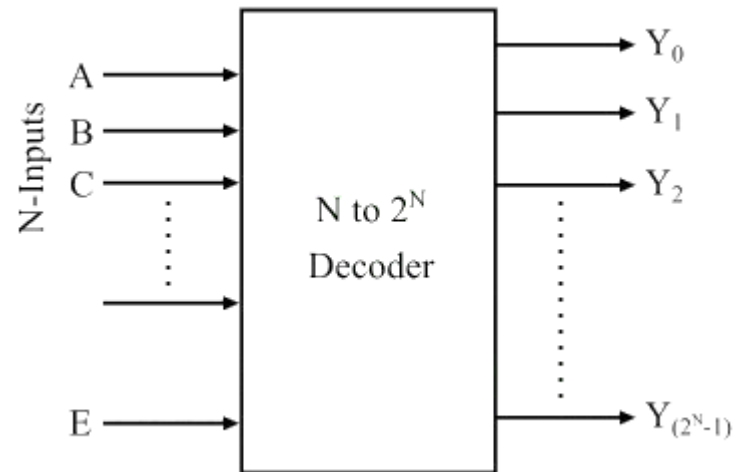


2 × 4 Decoder

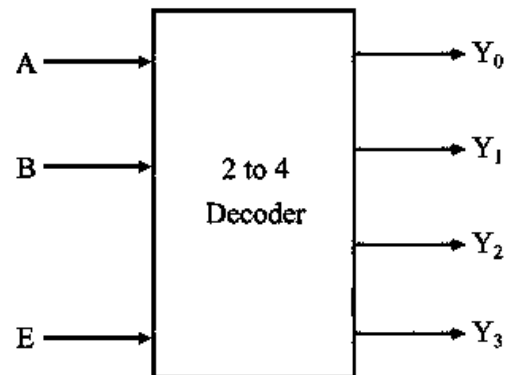


Inputs			Outputs			
EN	A	B	Y_3	Y_2	Y_1	Y_0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

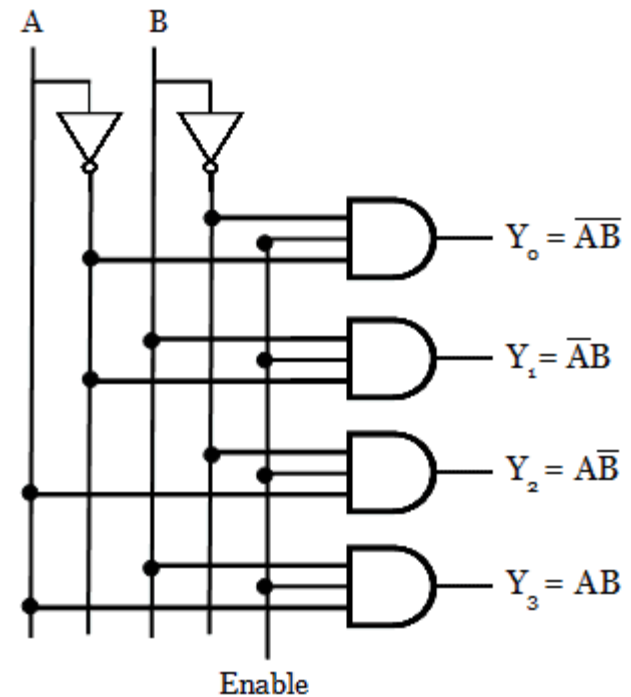


3 × 8 Decoder

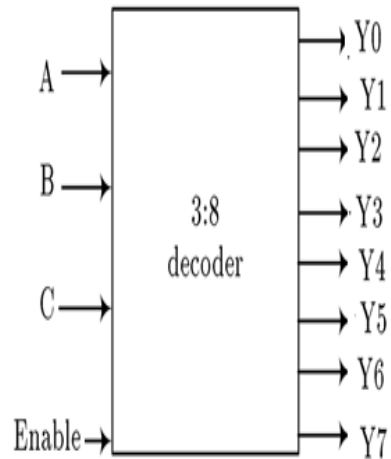


Inputs			Outputs							
A	B	C	Y ₇	Y ₆	Y ₅	Y ₄	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

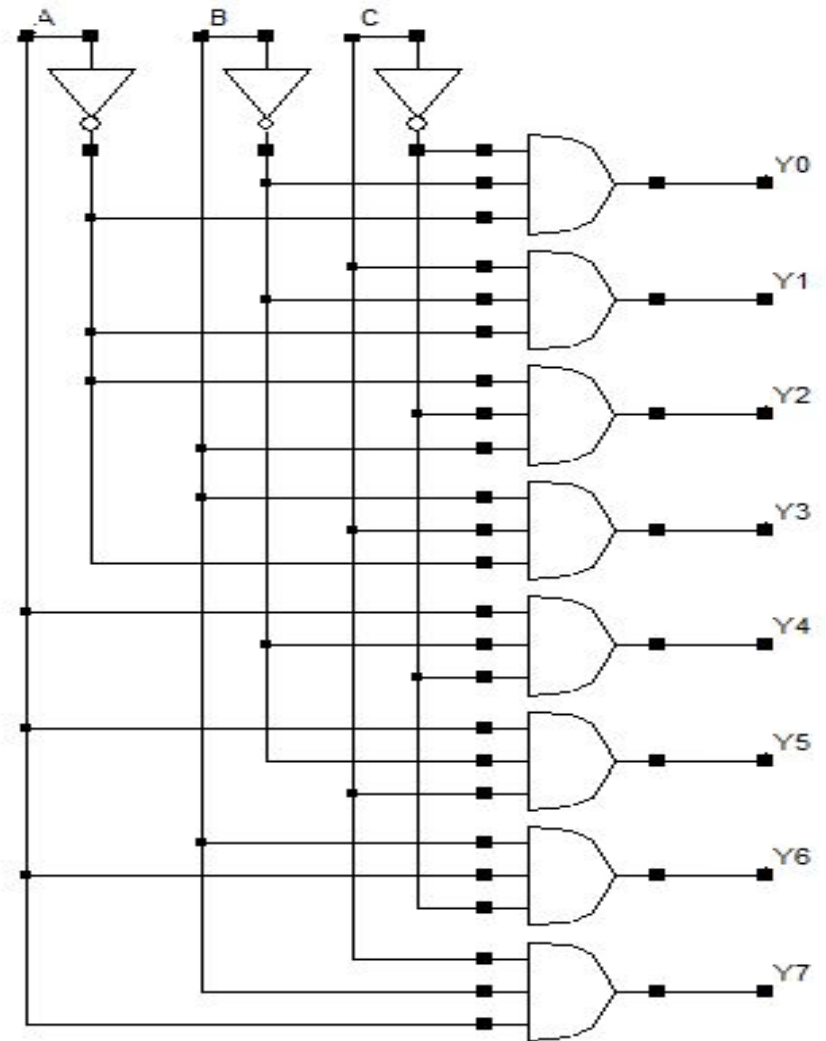


4 × 16 Decoder

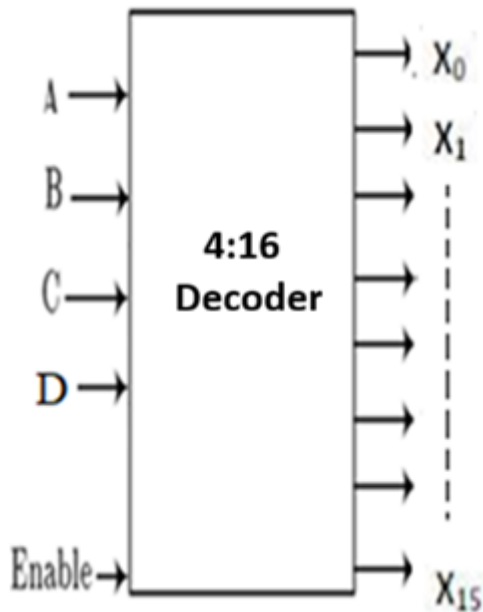[illegible]


4 × 16 Decoder

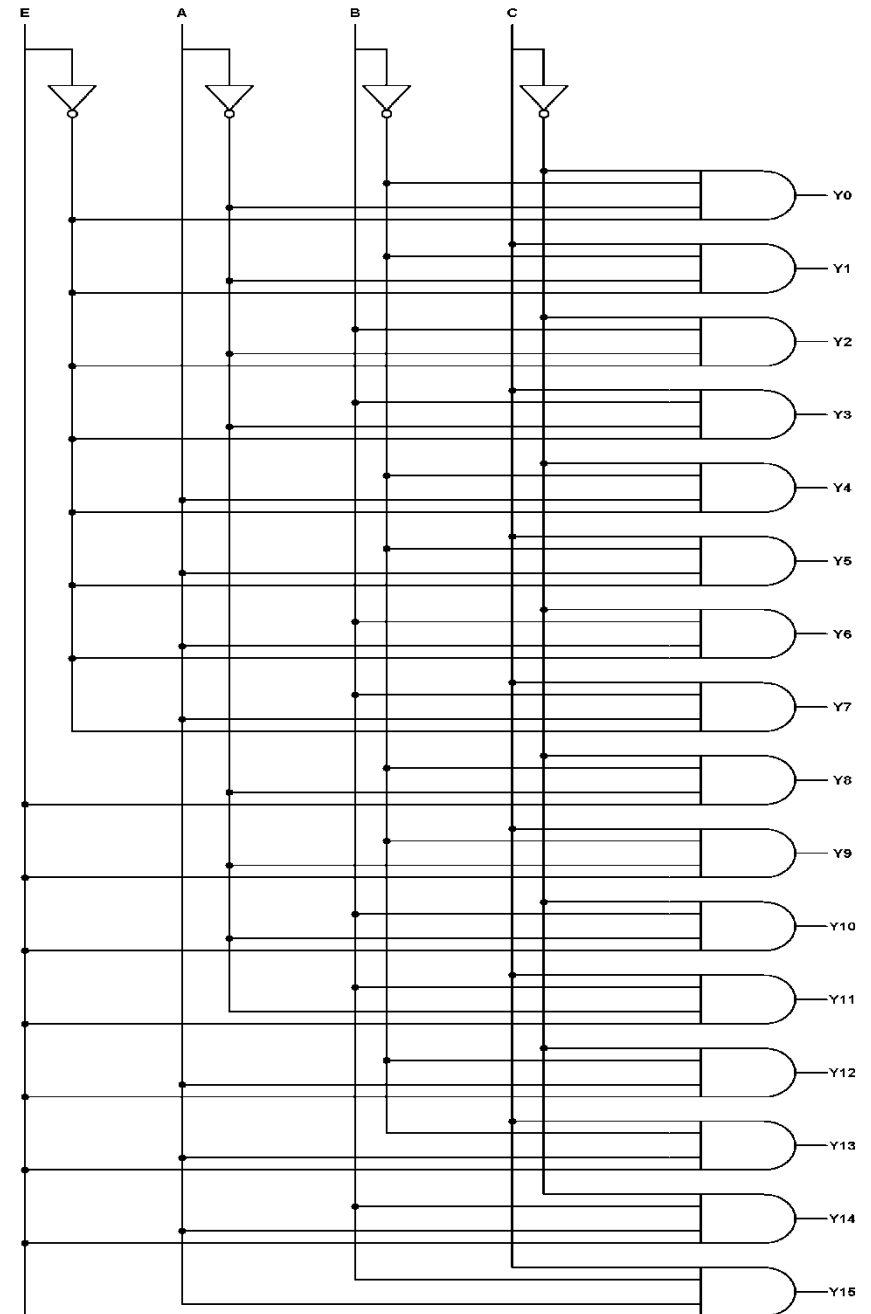

4×16 Decoder using 3×8 Decoder

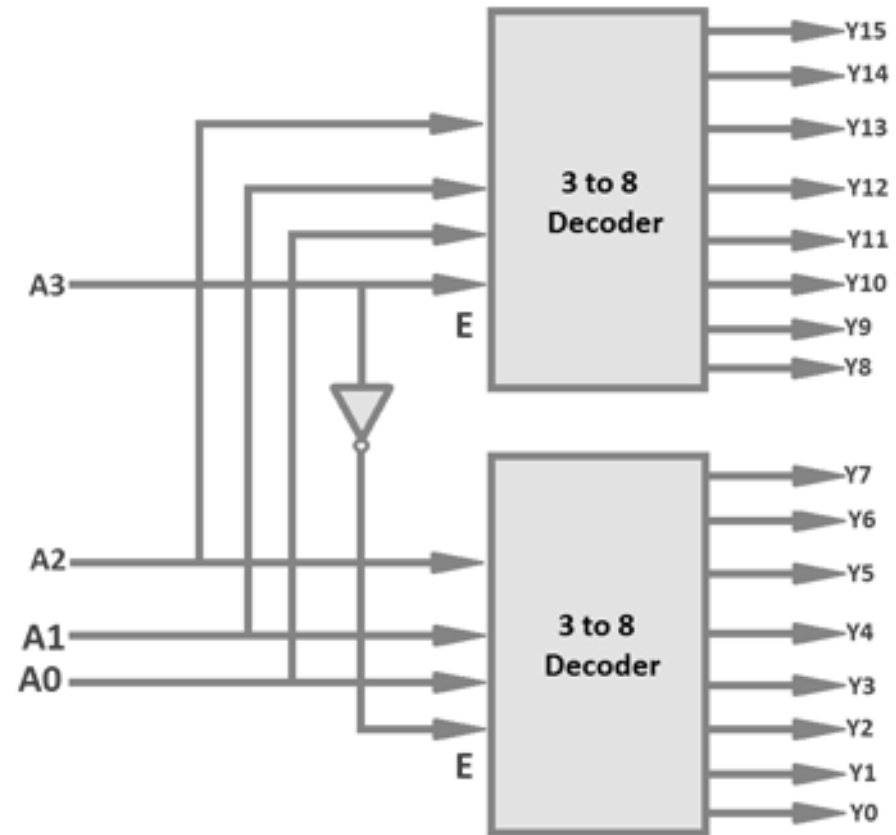


BCD to Decimal Decoder (4:10 decoder)

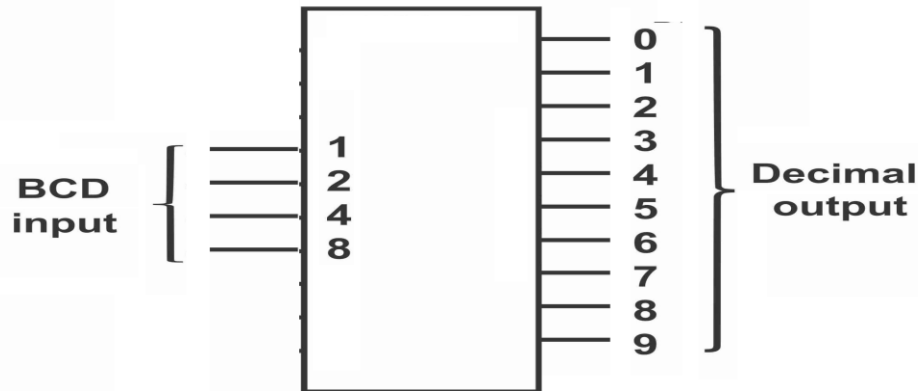

Truth Table:

B3	B2	B1	B0	D0	D1	D2	D3	D4	D5	D6	D7	D8	D9
0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1

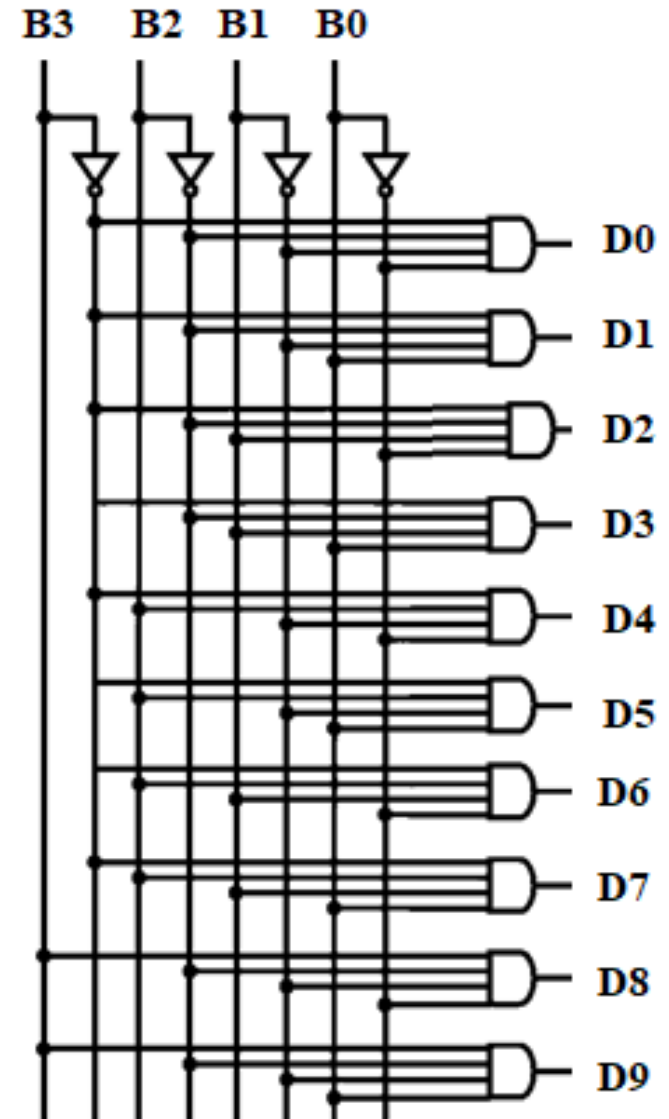

BCD to Decimal Decoder

		B1 B0			
		00	01	11	10
B3 B2	00	D_0	D_1	D_3	D_2
	01	D_4	D_5	D_7	D_6
	11	X	X	X	X
	10	D_8	D_9	X	X

$$D_0 = B_3' B_2' B_1' B_0'$$

$$D_1 = B_3' B_2' B_1' B_0$$

$$D_2 = B_2' B_1 B_0'$$

$$D_3 = B_2' B_1 B_0$$

$$D_4 = B_2 B_1' B_0'$$


$$D_5 = B_2 B_1' B_0$$

$$D_6 = B_2' B_1 B_0'$$

$$D_7 = B_2 B_1 B_0$$

$$D_8 = B_3 B_0'$$

$$D_9 = B_3 B_0$$

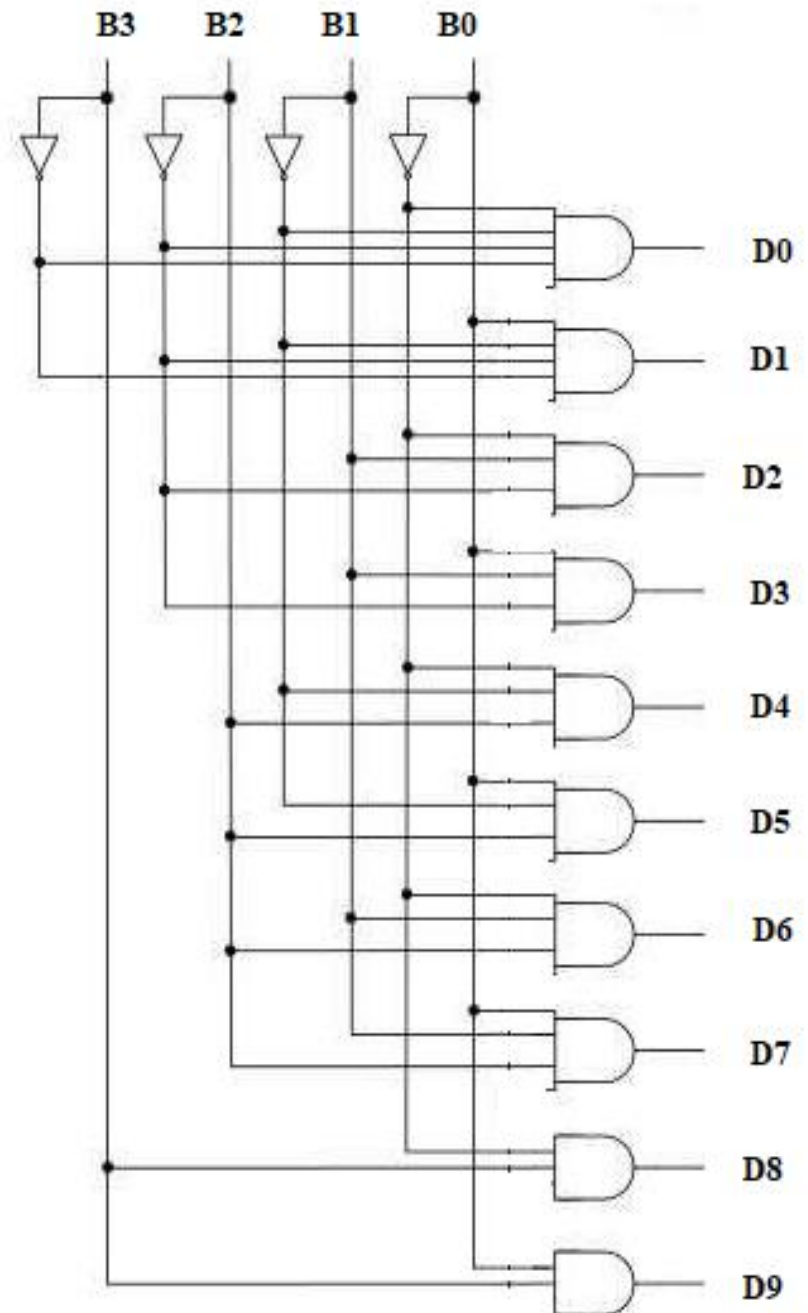

Encoder


Encoders – An encoder is a combinational circuit that converts binary information in the form of a 2^N input lines into N output lines, which represent N bit code for the input.

For simple encoders, it is assumed that only one input line is active at a time.


As an example, let's consider **Octal to Binary** encoder.

Encoders convert 2^N lines of input into a code of N bits and **Decoders** decode the N bits into 2^N lines


4 to 2 Encoder

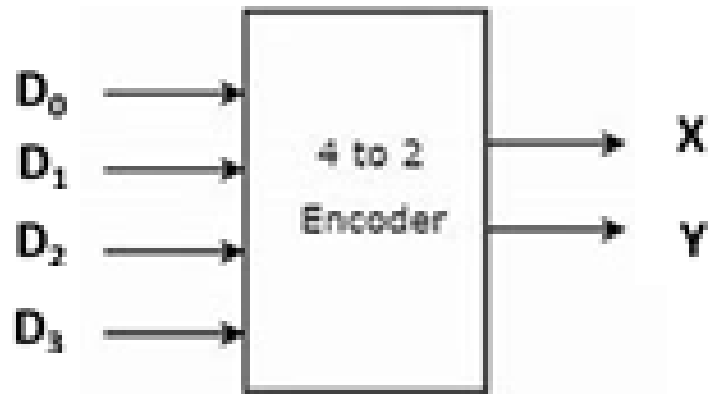


Input				Output	
D_0	D_1	D_2	D_3	X	Y
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

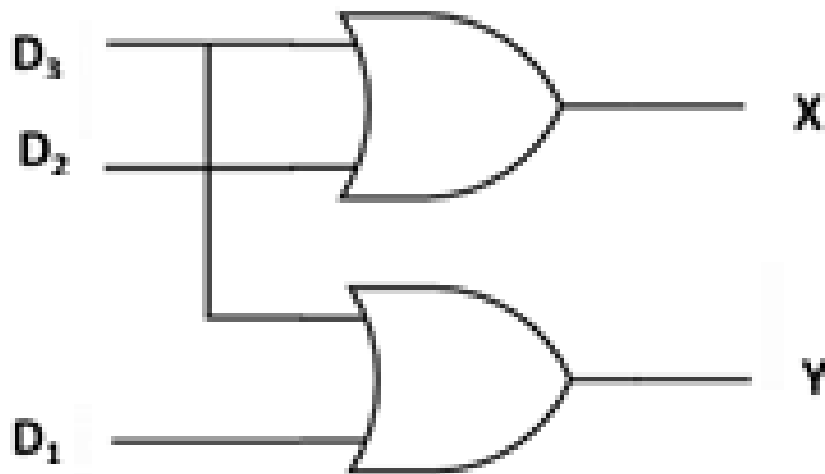

8 to 3 Encoder

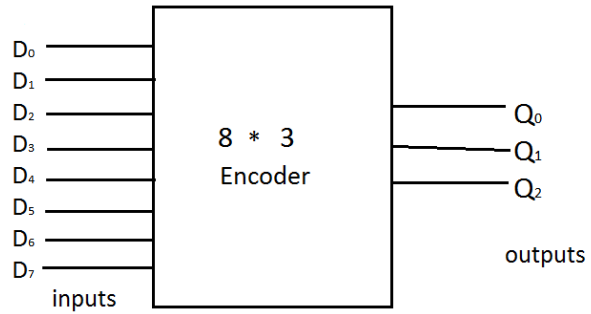

Input								Output		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

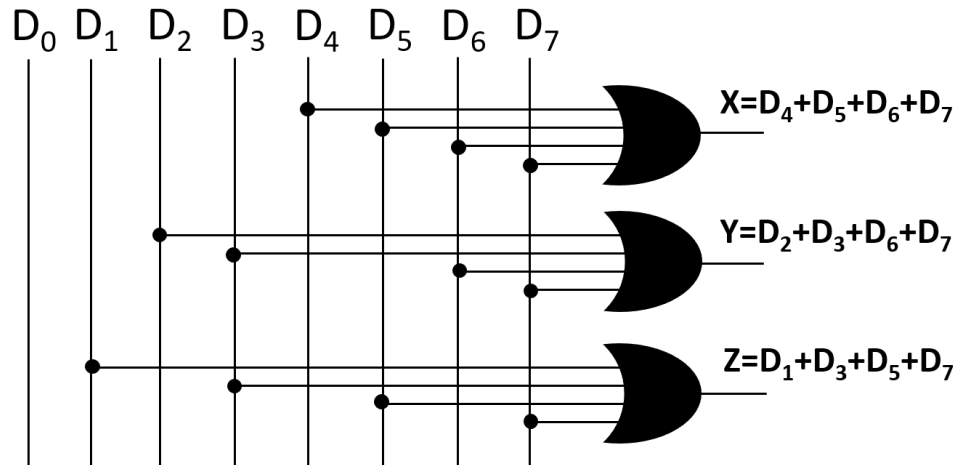

Decimal to BCD Encoder



D9	D8	D7	D6	D5	D4	D3	D2	D1	D0	B3	B2	B1	B0
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

$$B3 = D8 + D9$$

$$B2 = D4 + D5 + D6 + D7$$

$$B1 = D2 + D3 + D6 + D7$$

$$B0 = D1 + D3 + D5 + D7 + D9$$

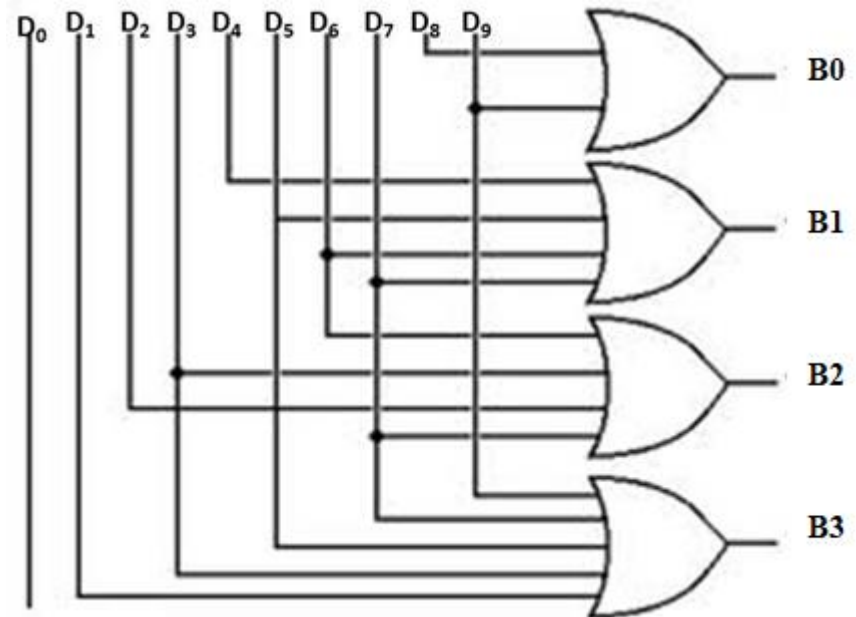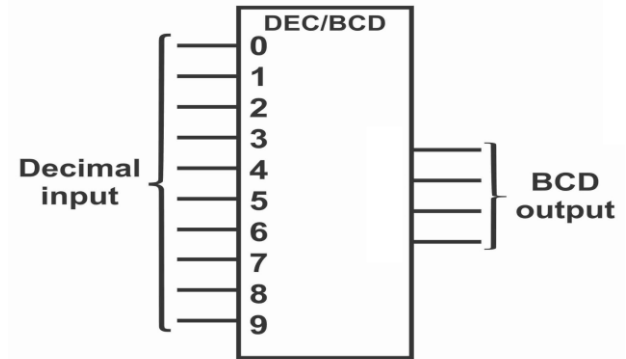

Digital Electronics (NECE102)

(Code Converter)

Binary to Gray Code Converter

Gray Code:

- It is un-weighted code
- It is referred as reflected binary code
- It is unit distance code
- It is cyclic code
- It changes in only one digit
- Switching time for gray code is less than any other code

1 bit
gray
code

0
1

2 bit
gray
code

0 0
0 1
1 1
1 0

3 bit
gray
code

0 0 0
0 0 1
0 1 1
0 1 0
1 1 0
1 1 1
1 0 1
1 0 0

4 bit
gray
code

0 0 0 0
0 0 0 1
0 0 1 1
0 0 1 0
0 1 1 0
0 1 1 1
0 1 0 1
0 1 0 0
1 1 0 0
1 1 0 1
1 1 1 1
1 1 1 0
1 0 1 0
1 0 1 1
1 0 0 1
1 0 0 0

Binary to Gray Code Converter (K-Map simplification)

Decimal Number 4 bit Binary Number

4 bit Gray Code

$B_3 B_2 B_1 B_0$

$G_3 G_2 G_1 G_0$

0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

$b_1 b_0$ $b_3 b_2$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$g_3 = b_3$$

$b_1 b_0$ $b_3 b_2$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$g_2 = \bar{b}_2 b_3 + b_2 \bar{b}_3 = b_2 \oplus b_3$$

Binary to Gray Code Converter (K-Map simplification)

Decimal Number	4 bit Binary Number	4 bit Gray Code
	$B_3 B_2 B_1 B_0$	$G_3 G_2 G_1 G_0$
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Binary to Gray Code Converter


Decimal Number	4 bit Binary Number $B_3 B_2 B_1 B_0$	4 bit Gray Code $G_3 G_2 G_1 G_0$
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

$b_1 b_0$	00	01	11	10
$b_3 b_2$ 00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1

$$g_1 = \bar{b}_2 b_1 + b_2 \bar{b}_1 = b_1 \oplus b_2$$

$b_1 b_0$	00	01	11	10
$b_3 b_2$ 00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1
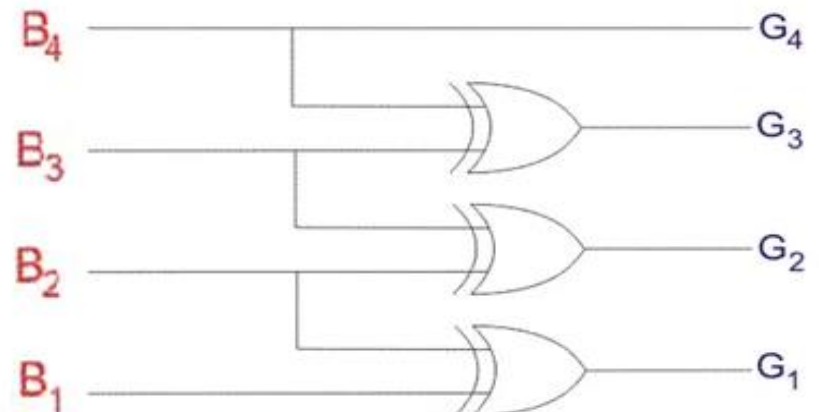
$$g_0 = \bar{b}_1 b_0 + b_1 \bar{b}_0 = b_1 \oplus b_0$$



Logic Circuit for Binary to Gray Code Converter

Gray to Binary Code Converter

4 bit
Gray Code

$G_3 G_2 G_1 G_0$

0	0000
1	0001
3	0011
2	0010
6	0110
7	0111
5	0101
4	0100
12	1100
13	1101
15	1111
14	1110
10	1010
11	1011
9	1001
8	1000

4 bit
Binary Code

$B_3 B_2 B_1 B_0$

0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

K-map for B3:

G1G0					
G3G2		00	01	11	10
		00	01	11	10
00		0	0	0	0
01		0	0	0	0
11		1	1	1	1
10		1	1	1	1

$$B_3 = G_3$$

K-map for B2:

G1G0					
G3G2		00	01	11	10
		00	01	11	10
00		0	0	0	0
01		1	1	1	1
11		0	0	0	0
10		1	1	1	1

$$B_2 = G_3 \oplus G_2$$

Gray to Binary Code Converter

4 bit
Gray Code

$G_3 G_2 G_1 G_0$

0	0000
1	0001
3	0011
2	0010
6	0110
7	0111
5	0101
4	0100
12	1100
13	1101
15	1111
14	1110
10	1010
11	1011
9	1001
8	1000

4 bit
Binary Code

$B_3 B_2 B_1 B_0$

0	0	0	0	0
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

Gray to Binary Code Converter

4 bit
Gray Code

$G_3 G_2 G_1 G_0$

4 bit
Binary Code

$B_3 B_2 B_1 B_0$

0	0000
1	0001
3	0011
2	0010
6	0110
7	0111
5	0101
4	0100
12	1100
13	1101
15	1111
14	1110
10	1010
11	1011
9	1001
8	1000

0	0	0	0	0
0	0	0	0	1
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

K-map for B1:

		G1G0			
		00	01	11	10
G3G2	00	0	0	1	1
	01	1	1	0	0
	11	0	0	1	1
	10	1	1	0	0

$$B1 = G3 \oplus G2 \oplus G1$$

K-map for B0:

		G1G0			
		00	01	11	10
G3G2	00	0	1	0	1
	01	1	0	1	0
	11	0	1	0	1
	10	1	0	1	0

$$B0 = G3 \oplus G2 \oplus G1 \oplus G0$$

BCD to Excess 3 Code Converter

Decimal Number	BCD code (Input)				Excess-3 code (Output)			
	D ₃	D ₂	D ₁	D ₀	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

$$E_3 = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

For E₃ output

D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	X	X	X	X
10	1	1	X	X

$$E_3 = D_3 + D_2 D_0 + D_2 D_1$$

$$E_2 = \sum m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

For E₂ output

D ₃ D ₂ \ D ₁ D ₀	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	X	X	X	X
10	0	1	X	X

$$E_2 = D_2 \bar{D}_1 \bar{D}_0 + \bar{D}_2 D_0 + \bar{D}_2 D_1$$

BCD to Excess 3 Code Converter

Decimal Number	BCD code (Input)				Excess-3 code (Output)			
	D ₃	D ₂	D ₁	D ₀	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

$$E_1 = \sum m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

For E₁ output

$\begin{matrix} D_1 D_0 \\ D_3 D_2 \end{matrix}$	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	X	X	X	X
10	1	0	X	X

$$E_1 = \overline{D_1} \overline{D_0} + D_1 D_0$$

$$E_0 = \sum m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

For E₀ output

$\begin{matrix} D_1 D_0 \\ D_3 D_2 \end{matrix}$	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	X	X

$$E_0 = \overline{D_0}$$

Decimal Number	BCD code (Input)				Excess-3 code (Output)			
	D ₃	D ₂	D ₁	D ₀	E ₃	E ₂	E ₁	E ₀
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

$$E_3 = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$E_2 = \sum m(1, 2, 3, 4, 9) + d(10, 11, 12, 13, 14, 15)$$

$$E_1 = \sum m(0, 3, 4, 7, 8) + d(10, 11, 12, 13, 14, 15)$$

$$E_0 = \sum m(0, 2, 4, 6, 8) + d(10, 11, 12, 13, 14, 15)$$

	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

BCD to Excess 3 Code Converter

$$\begin{aligned}E_3 &= D_3 + D_2 D_0 + D_2 D_1 \\E_2 &= D_2 \bar{D}_1 \bar{D}_0 + \bar{D}_2 D_0 + \bar{D}_2 D_1 \\E_1 &= \bar{D}_1 \bar{D}_0 + D_1 D_0 \\E_0 &= \bar{D}_0\end{aligned}$$

